

EE2020-Electrical Circuits Analysis



Dr. Ahmed Nassef

Tutorial



Key inductor relationships:

Primary v - i equation

$$v(t) = L \frac{di(t)}{dt}$$

Alternate v - i equation

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

Initial condition

$$i(t_0)$$

Behavior with a constant source

If $i(t) = I$, $v(t) = 0$ and the inductor behaves like a short circuit

Continuity requirement

$i(t)$ is continuous for all time so $v(t)$ is finite

Power equation

$$p(t) = v(t)i(t) = Li(t) \frac{di(t)}{dt}$$

Energy equation

$$w(t) = \frac{1}{2} Li(t)^2$$

Series-connected equivalent

$$L_{\text{eq}} = \sum_{j=1}^n L_j$$
$$i_{\text{eq}}(t_0) = i_j(t_0) \quad \text{for all } j$$

Parallel-connected equivalent

$$\frac{1}{L_{\text{eq}}} = \sum_{j=1}^n \frac{1}{L_j}$$
$$i_{\text{eq}}(t_0) = \sum_{j=1}^n i_j(t_0)$$

Problem #1


6.2 The triangular current pulse shown in Fig. P6.2 is applied to a 500 mH inductor.

PSpice
Multisim

- Write the expressions that describe $i(t)$ in the four intervals $t < 0$, $0 \leq t \leq 25 \text{ ms}$, $25 \text{ ms} \leq t \leq 50 \text{ ms}$, and $t > 50 \text{ ms}$.
- Derive the expressions for the inductor voltage, power, and energy. Use the passive sign convention.

calculus
①

Figure P6.2

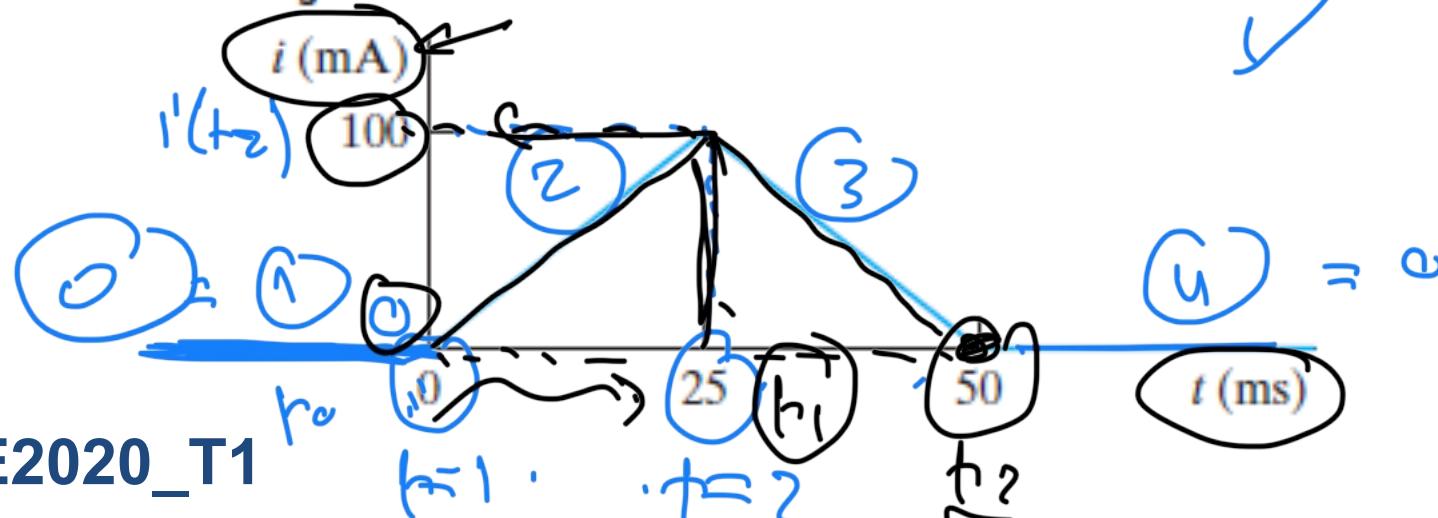

$$i(t) \rightarrow m(t - t_0) + \underline{i(t_0)} \xrightarrow{t \rightarrow \infty} \underline{i(t_0)}$$

Q2

$$m = \frac{i(t_2) - i(t_1)}{t_2 - t_1} = \frac{100 - 0}{55 - 0}$$

$$m \leftarrow y$$

$$i(t) = Ut + \phi \rightarrow \boxed{i(t) \rightarrow Ut} \quad A$$

β]

$$m = \frac{i(t_2) - i(t_1)}{t_2 - t_1} = \frac{0 - 100}{50 - 25}$$

$$m = \frac{-100}{25} = -4 \rightarrow$$


$$i(t) = -4(t - 25 \text{ ms}) + 100 \text{ mA}$$

$\underbrace{-4t + 100 \text{ ms}}_{-4t + 100 \text{ ms}}$

$$i(t) = -4t + 200 \text{ mA}$$

$\underbrace{-4t + 200 \text{ ms}}_{-4t + 200 \text{ ms}}$

$r(t) =$

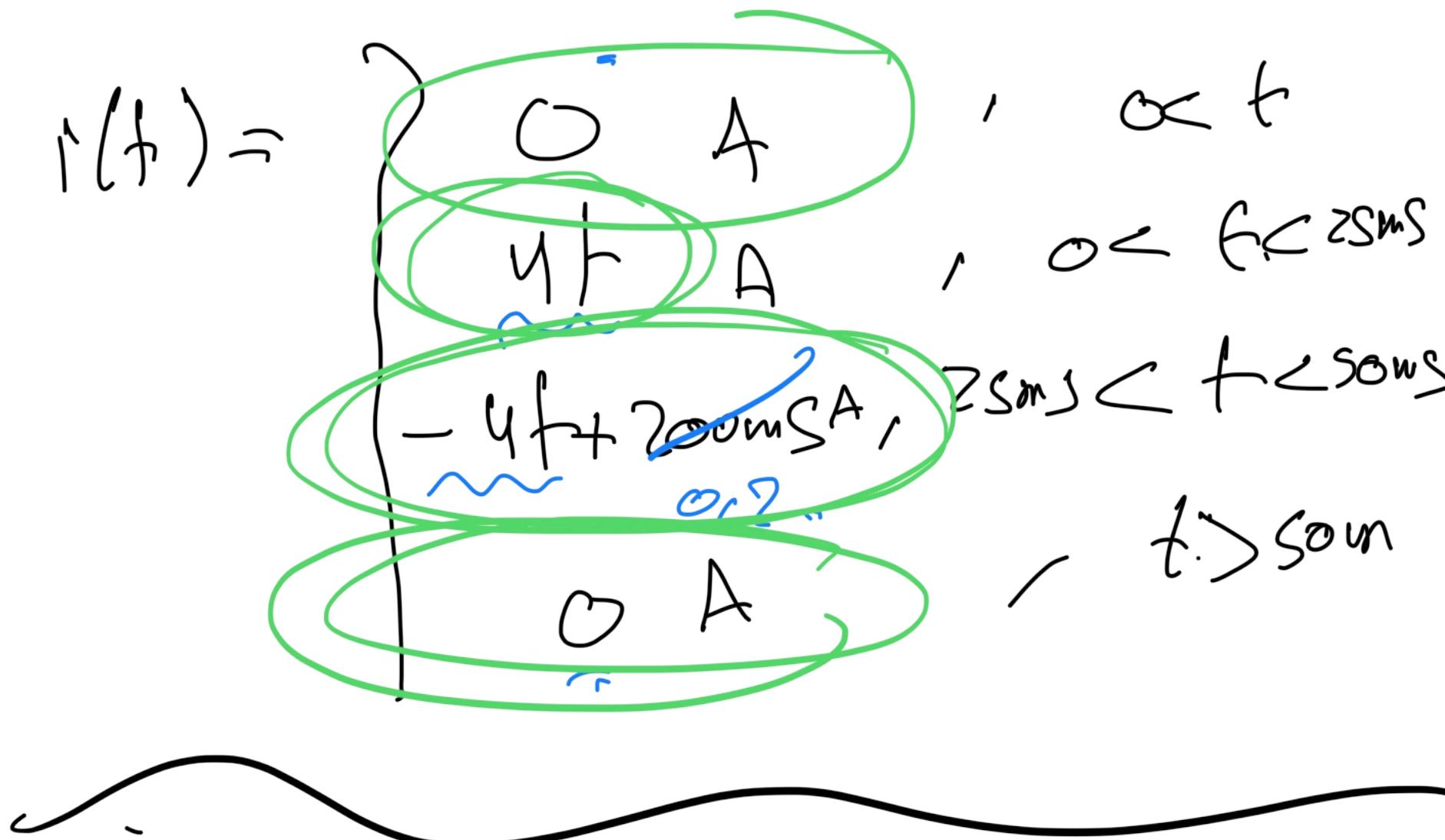



$$200 \times 10^{-3} = 0,2 + \uparrow$$

$$N = L$$

$$\frac{\partial C}{\partial t}$$

$$L = \text{some } H$$

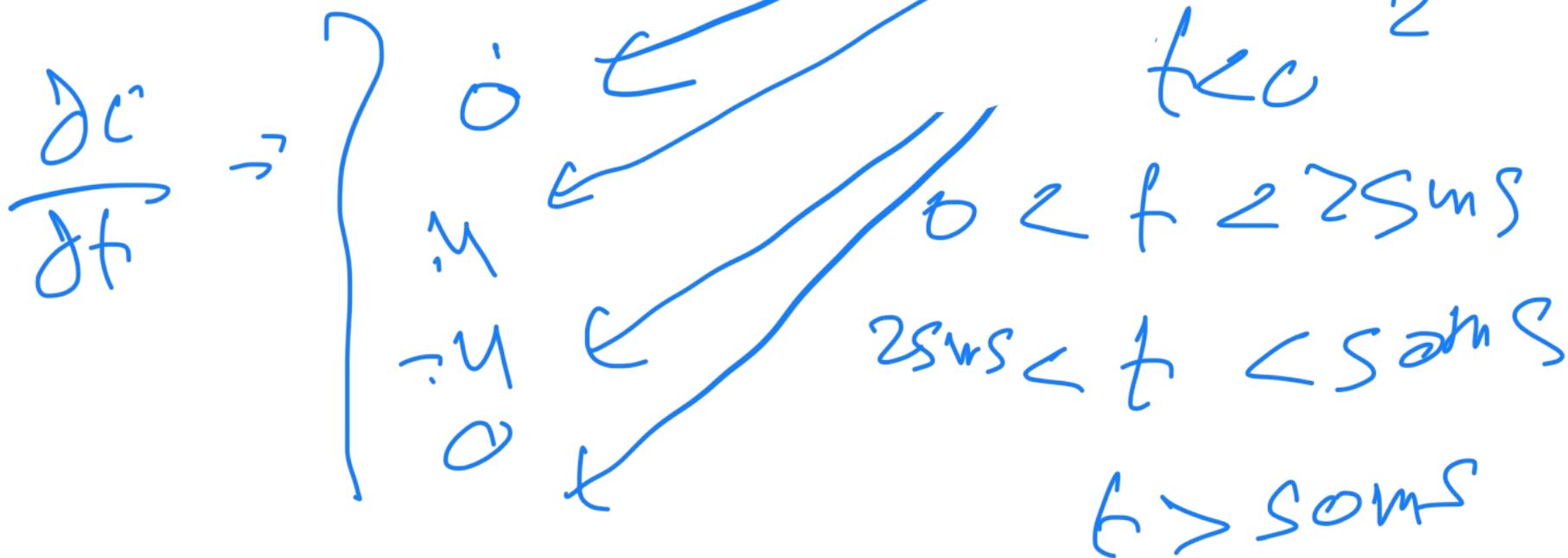

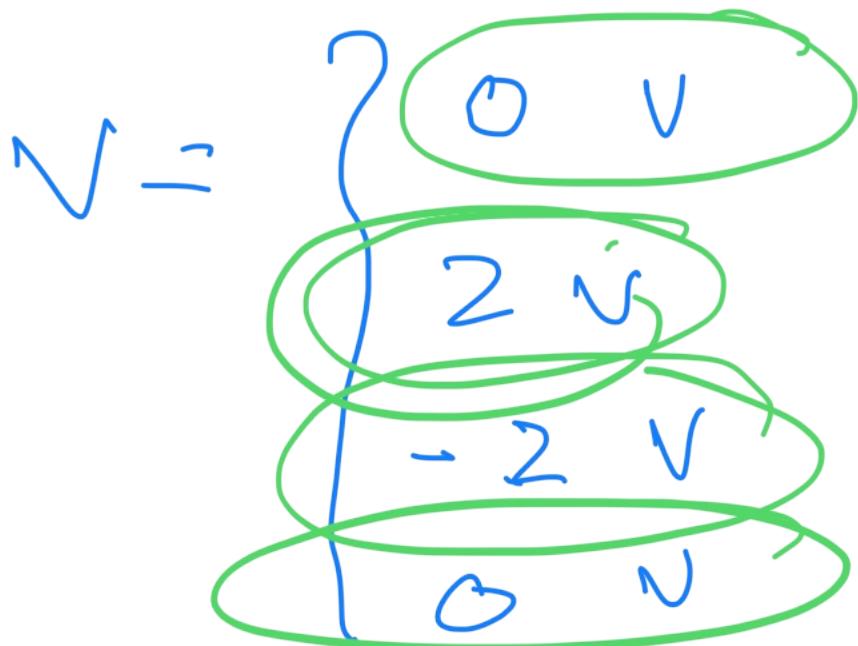

$$t < 0$$

$$0 < t < 2\text{ms}$$


$$2\text{ms} < t < 4\text{ms}$$

$$t > 4\text{ms}$$



$$P = V C$$

$$(-2)(-9t + \theta, 2)$$

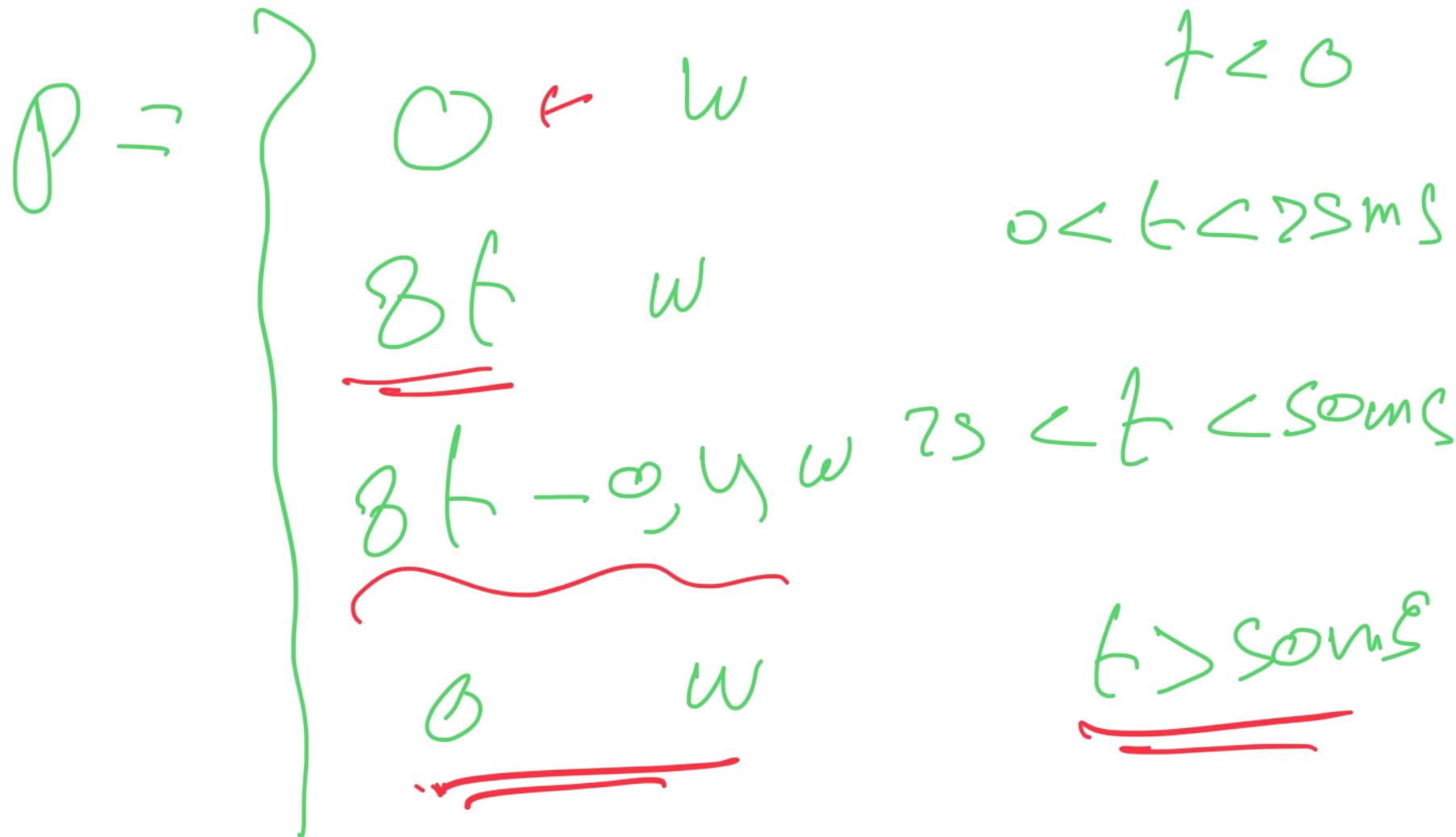

$$w = \frac{1}{2} L r^2 \cancel{X \rightarrow \epsilon}$$

$$W \leftarrow \int \underline{\underline{\rho(f)}}$$

$$W = \begin{cases} 0 < \bar{J} & t < 0 \\ ut^2 \bar{J} & 0 < t < \text{some} \\ ut^2 - 0.5ut + 0.1\bar{J}^2 \text{some} & t > \text{some} \\ 0, 0.9 \bar{J} & t > \underline{\underline{\text{some}}} \end{cases}$$

$$w = \int_0^t 8x' dx + w(t=0) = 0$$

انجذاب

①

$$= w \cancel{\frac{x^2}{x}} \int_0^t \cdot = u(t^2 - 0) = 4t^2$$

$$w = \int_{0,025}^t \underline{8x - 0,4} dx + w(t=0,025)$$

انجذاب

$2,8 \times 10^{-3}$

$0,025$

$u(0,025) = 2,8 \times 10^{-3}$

$0,0025$

$$w = u t^2 - 0,4x + 0,025 + 0,0025$$

$$(ut^2 - 0,4t) - \underbrace{(u(0,025)^2 - 0,4(0,025) + 0,0025)}_{+ 0,0025} + \cancel{+ 0,00975}$$

$$w = ut^2 - 0,4t + 0,1$$

$$w = f(t) + w(t = \text{some})$$

$\leftarrow \text{some}$
 θ

$$w(t = \text{some}) = u/(\theta \times 10^{-3})^2$$

$$- 0.1 (10^{-3}) \rightarrow 0.1$$

$$= 0.01$$

Solution for Problem #1

[a] $i = 0$

$$t < 0$$

$$i = 4t \text{ A}$$


$$0 \leq t \leq 25 \text{ ms}$$

$$i = 0.2 - 4t \text{ A}$$

$$25 \leq t \leq 50 \text{ ms}$$

$$i = 0$$

$$50 \text{ ms} < t$$

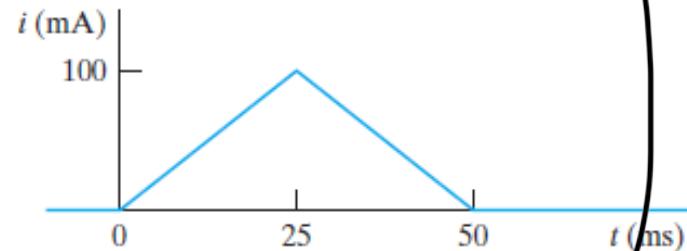

[b] $v = L \frac{di}{dt} = 500 \times 10^{-3} (4) = 2 \text{ V}$ $0 \leq t \leq 25 \text{ ms}$

$$v = 500 \times 10^{-3} (-4) = -2 \text{ V}$$
 $25 \leq t \leq 50 \text{ ms}$

$$v = 0$$

$$t < 0$$

$$v = 2 \text{ V}$$

$$0 < t < 25 \text{ ms}$$

$$v = -2 \text{ V}$$

$$25 < t < 50 \text{ ms}$$

$$v = 0$$

$$50 \text{ ms} < t$$

Cont. Solution for Problem #1

$$p = vi$$

$$p = 0$$

$$t < 0$$

$$p = (4t)(2) = 8t \text{ W}$$

$$0 < t < 25 \text{ ms}$$

$$p = (0.2 - 4t)(-2) = 8t - 0.4 \text{ W}$$

$$25 < t < 50 \text{ ms}$$

$$p = 0$$

$$50 \text{ ms} < t$$

$$w = 0$$

$$t < 0$$

$$w = \int_0^t (8x) dx = 8 \frac{x^2}{2} \Big|_0^t = 4t^2 \text{ J}$$

$$0 < t < 25 \text{ ms}$$

$$w = \int_{0.025}^t (8x - 0.4) dx + 2.5 \times 10^{-3}$$

$$= 4x^2 - 0.4x \Big|_{0.025}^t + 2.5 \times 10^{-3}$$

$$= 4t^2 - 0.4t + 10 \times 10^{-3} \text{ J}$$

$$25 < t < 50 \text{ ms}$$

$$w = 0, 109 \text{ J} \therefore$$

$$50 \text{ ms} < t$$



Problem #2


6.7 The voltage at the terminals of the $750 \mu\text{H}$ inductor in Fig. P6.7(a) is shown in Fig. P6.7(b). The inductor current i is known to be zero for $t \leq 0$.

PSPICE
MULTISIM

- Derive the expressions for i for $t \geq 0$.
- Sketch i versus t for $0 \leq t \leq \infty$.

Figure P6.7

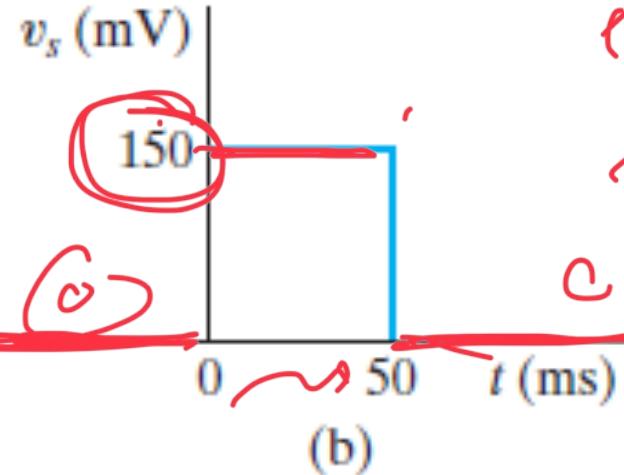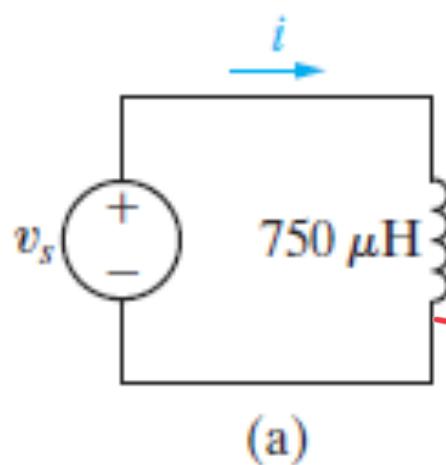

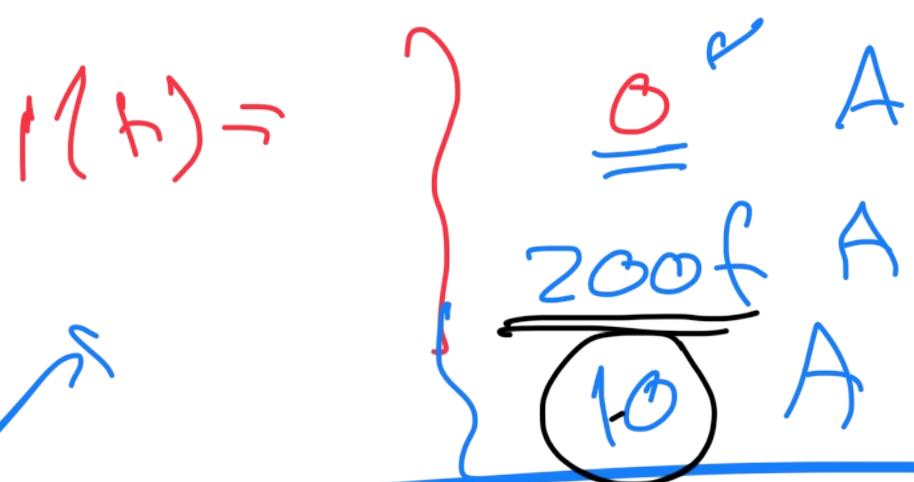

$t \leq 0$
 $0 < t < \text{some}$
 $t > \text{some}$




$$i_L(t) = \frac{1}{L} \int_{t_0}^t V_L(t') dt + \frac{i_L(t_0)}{L}$$

$t_0 = 0$


$$i_L(f) = \frac{750 \times 10^{-6}}{750 \times 10^{-6}} \int_0^t 1 \, dx + 0$$

$$\frac{150 \times 10^{-3}}{750 \times 10^{-6}} \int_0^t 1 \, dx = x \Big|_0^t = t$$

$$i_L(t) = 200t \leftarrow$$

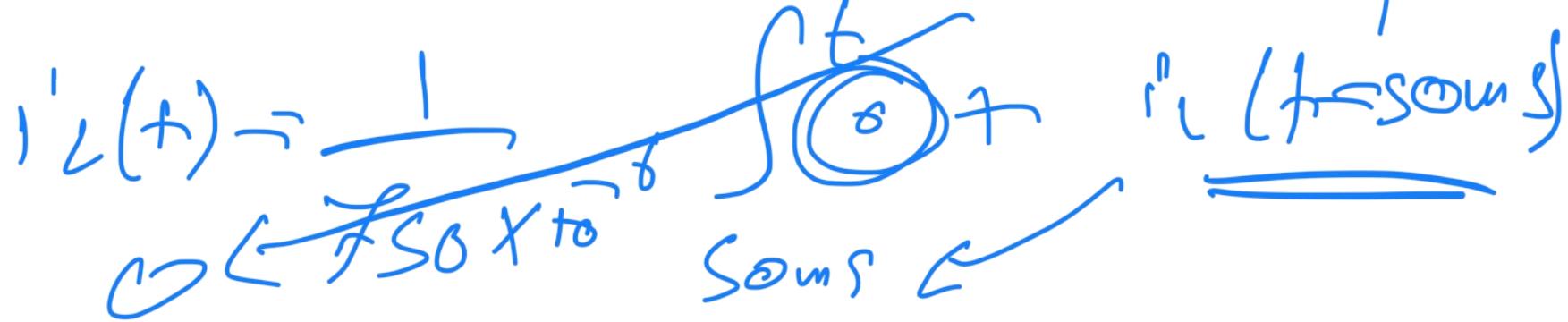
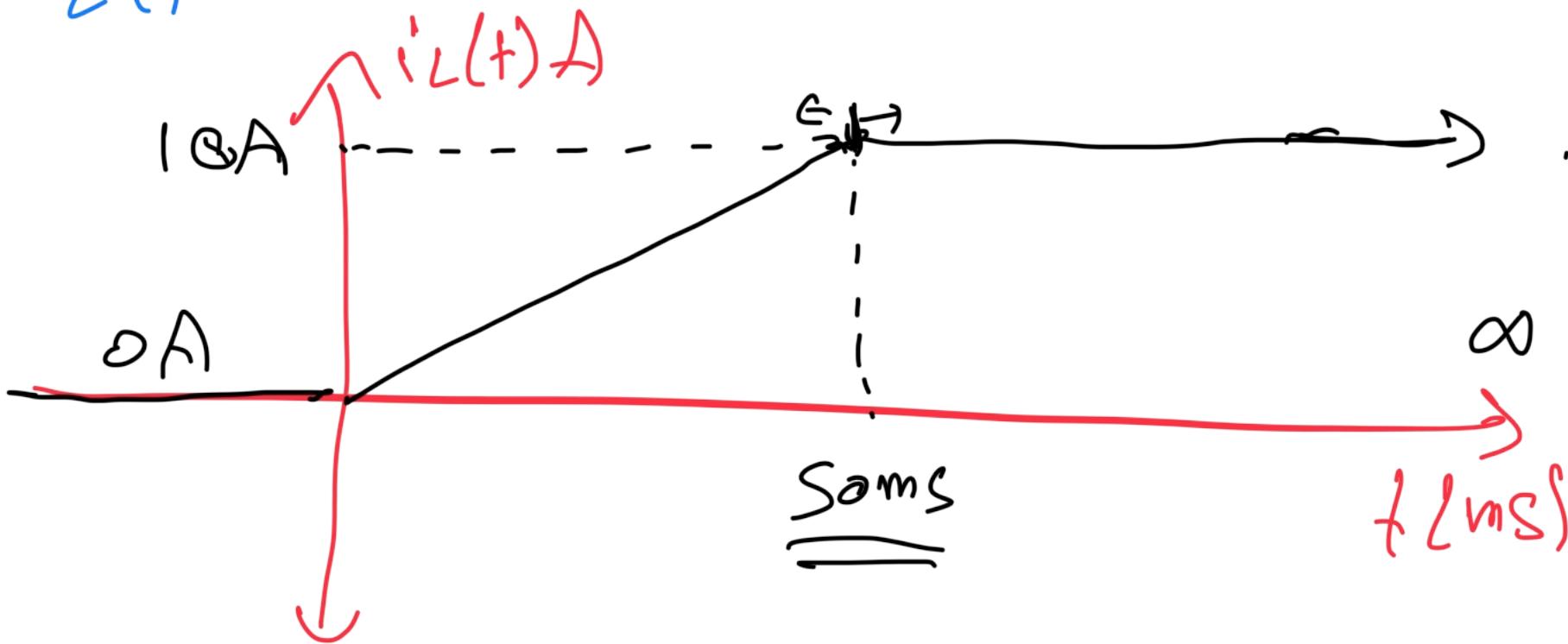
$$i_L(t=50ms) = 200 \times 50 \times 10^{-3} = 10A$$



Solution for Problem #2

[a] $0 \leq t \leq 50 \text{ ms}$:

$$i = \frac{1}{L} \int_0^t v_s dx + i(0) = \frac{10^6}{750} \int_0^t 0.15 dx + 0$$


$$= 200x \Big|_0^t = 200t \text{ A}$$

$$i(0.05) = 200(0.05) = 10 \text{ A}$$

$$t \geq 50 \text{ ms} : \quad i = \frac{10^6}{750} \int_{50 \times 10^{-3}}^t (0) dx + 10 = 10 \text{ A}$$

Cont. Solution for Problem #2

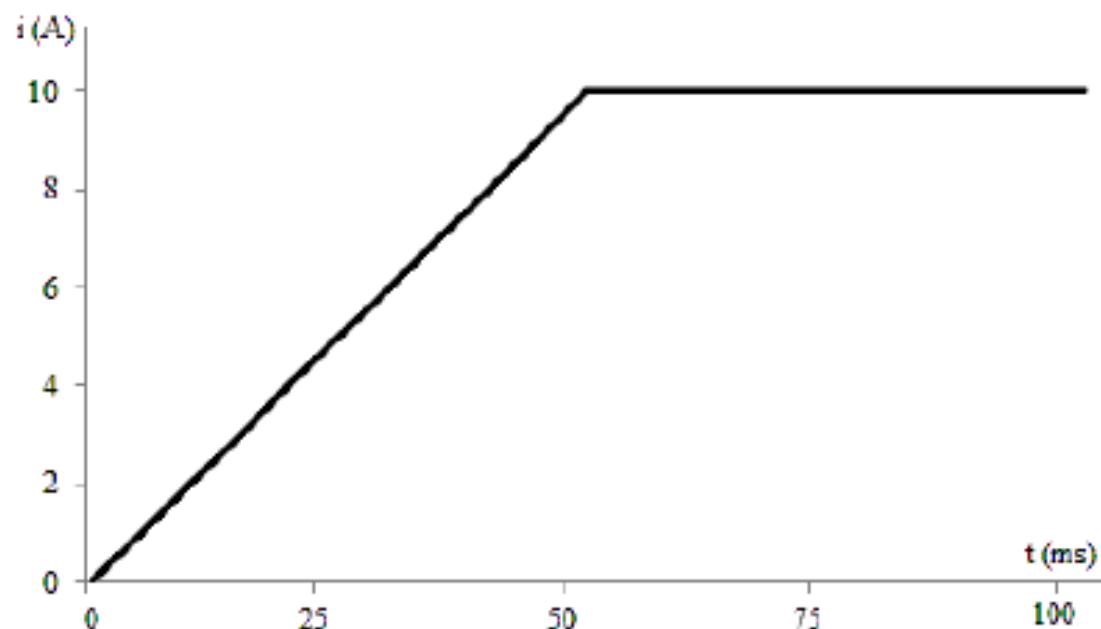
[b] $i = 200t \text{ A}, \quad 0 \leq t \leq 50 \text{ ms}; \quad i = 10 \text{ A}, \quad t \geq 50 \text{ ms}$




Problem #3

6.12 Initially there was no energy stored in the 5 H inductor in the circuit in Fig. P6.12 when it was placed across the terminals of the voltmeter. At $t = 0$ the inductor was switched instantaneously to position b where it remained for 1.6 s before returning instantaneously to position a. The d'Arsonval voltmeter has a full-scale reading of 20 V and a sensitivity of $1000 \Omega/\text{V}$. What will the reading of the voltmeter be at the instant the switch returns to position a if the inertia of the d'Arsonval movement is negligible?

Figure P6.12

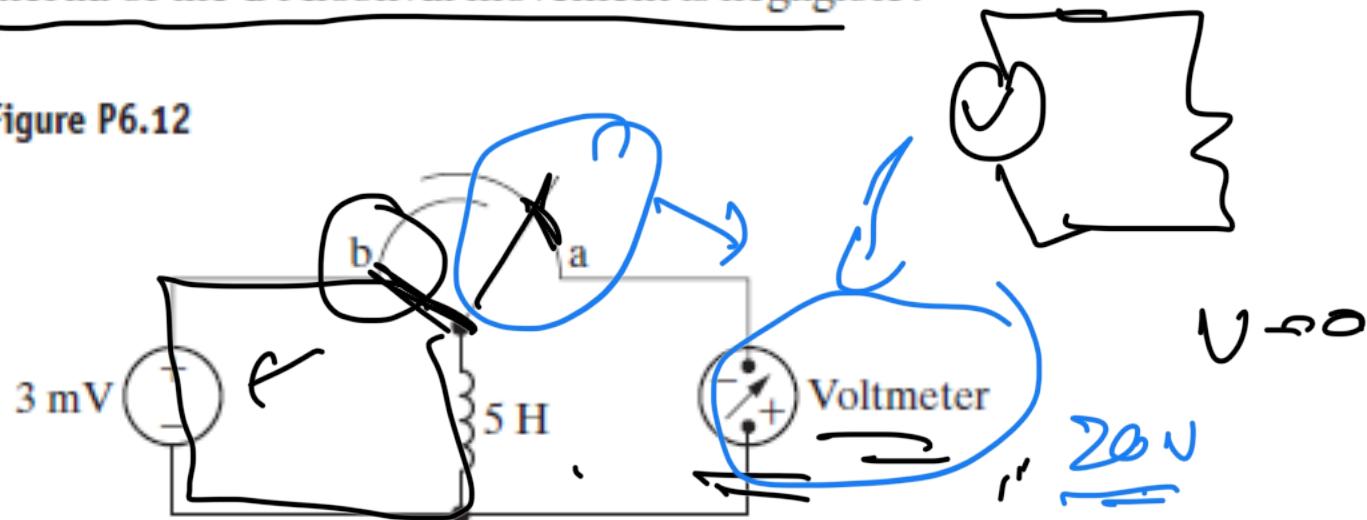

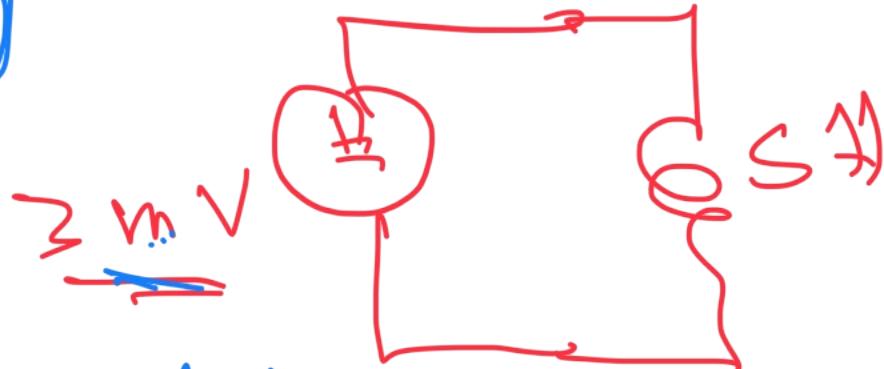$\text{O} \subset \mathbb{R}^3 \leftarrow \mathbb{R}, f, S$




$$i_{V(f)} = \frac{1}{L} \quad \left. \begin{array}{l} f \\ \vdash \\ V \delta x_1 \end{array} \right\} i_c(0) = 0$$

$$i \rightarrow \left. \begin{array}{l} f \\ \vdash \\ 3 \times 10 \end{array} \right\} \delta J_x =$$

$$\left. \begin{array}{l} f \\ \vdash \\ \frac{3 \times 10}{S} \end{array} \right\} = x \left. \begin{array}{l} f \\ \vdash \\ 1 \end{array} \right\} = \left. \begin{array}{l} f \\ \vdash \\ 0, f, t, m, A \end{array} \right\}$$

$$i_L(t) = 0,6 t \text{ mA} \quad \rightarrow$$

$$t \geq 1,6 \text{ ms}$$

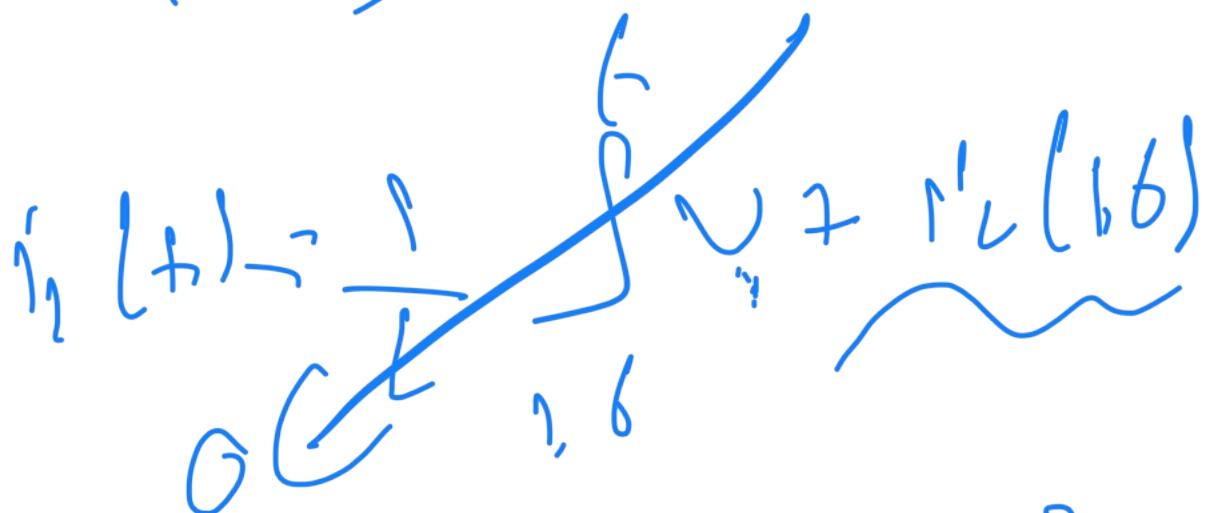


$$i_L(t) = 0,6 \times 1,6 \times 10^3 \times 10^{-3} = \underline{\underline{0,96 \text{ mA}}}$$

$$i_L(f) = \begin{cases} 0 \text{ A} & f < 0 \\ 0,6 \text{ mA} & 0 < f < 1,6 \text{ mHz} \\ \underline{\underline{0,96 \text{ mA}}} & f > 1,6 \text{ mHz} \end{cases}$$

$$\underline{\underline{1000 \text{ Ohm}}} \times 20 \text{ N} = 20 \text{ X}$$
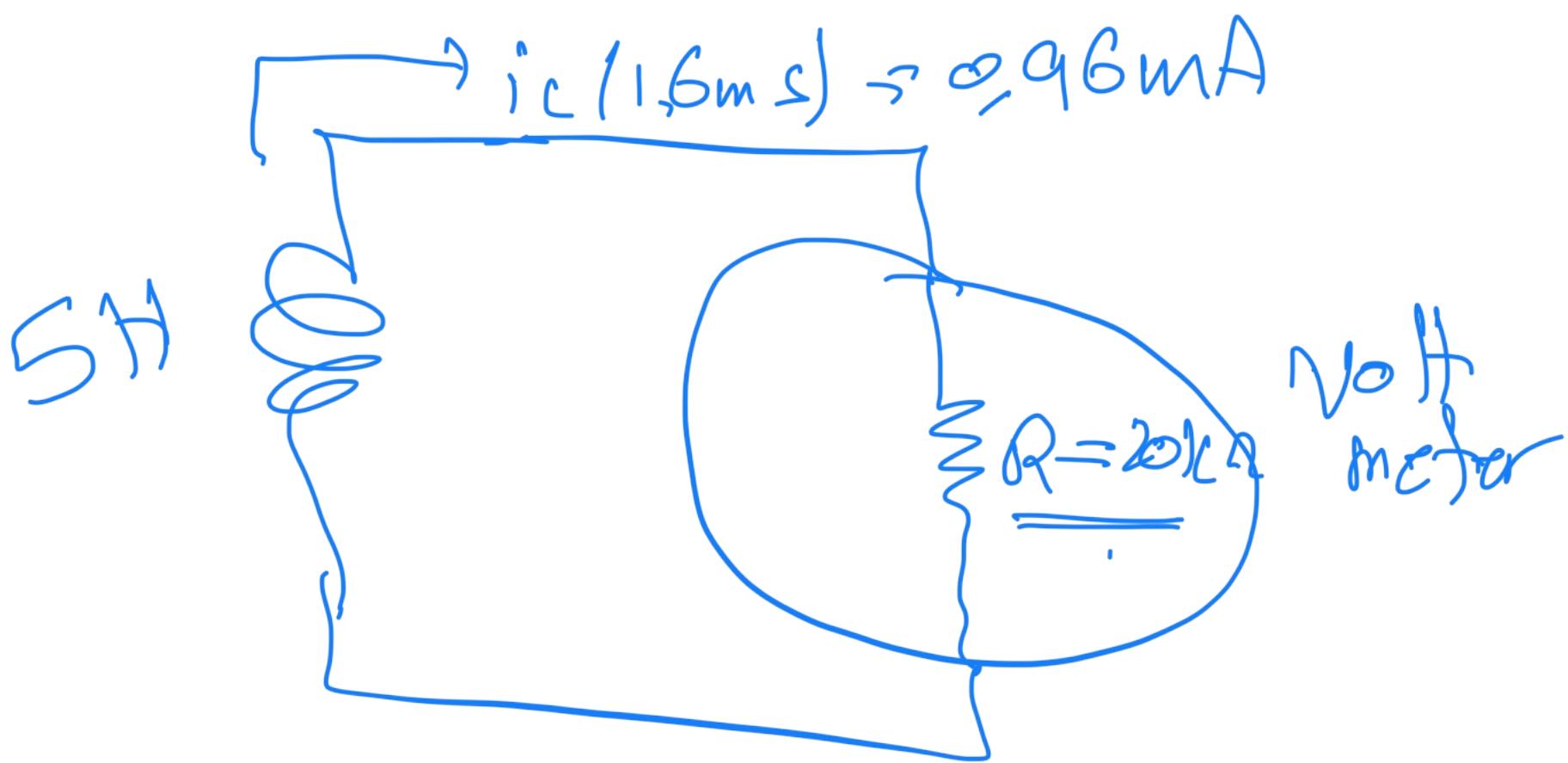
$$R = \underline{\underline{1000 \frac{\text{Ohm}}{\text{V}}}} \times 20 \text{ N} \Rightarrow \boxed{20 \text{ kN}}$$



$$N_m (t = 1,6\text{ms}) = I R$$

$$0,96\text{mA} \times 20\text{k}\Omega \Rightarrow 19,2\text{V}$$

Solution for Problem #3

For $0 \leq t \leq 1.6$ s:

$$i_L = \frac{1}{5} \int_0^t 3 \times 10^{-3} dx + 0 = 0.6 \times 10^{-3}t$$

$$i_L(1.6 \text{ s}) = (0.6 \times 10^{-3})(1.6) = 0.96 \text{ mA}$$

$$R_m = (20)(1000) = 20 \text{ k}\Omega$$

$$v_m(1.6 \text{ s}) = (0.96 \times 10^{-3})(20 \times 10^3) = 19.2 \text{ V}$$

Problem #4

The voltage pulse applied to the 100 mH inductor shown in Fig. 6.5 is 0 for $t < 0$ and is given by the expression

$$v(t) = 20te^{-10t} \text{ V}$$

for $t > 0$. Also assume $i = 0$ for $t \leq 0$.

- a) Sketch the voltage as a function of time.
- b) Find the inductor current as a function of time.
- c) Sketch the current as a function of time.


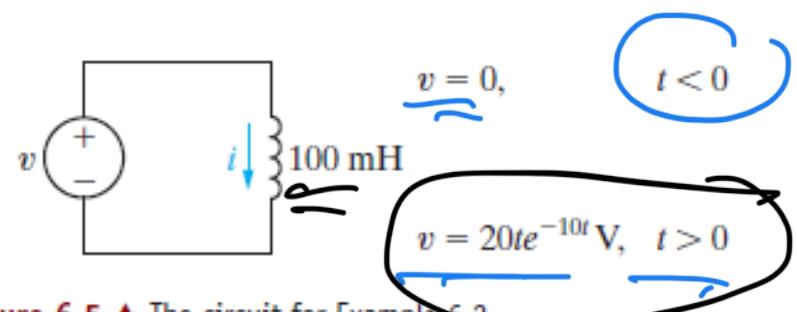


Figure 6.5 ▲ The circuit for Example 6.2

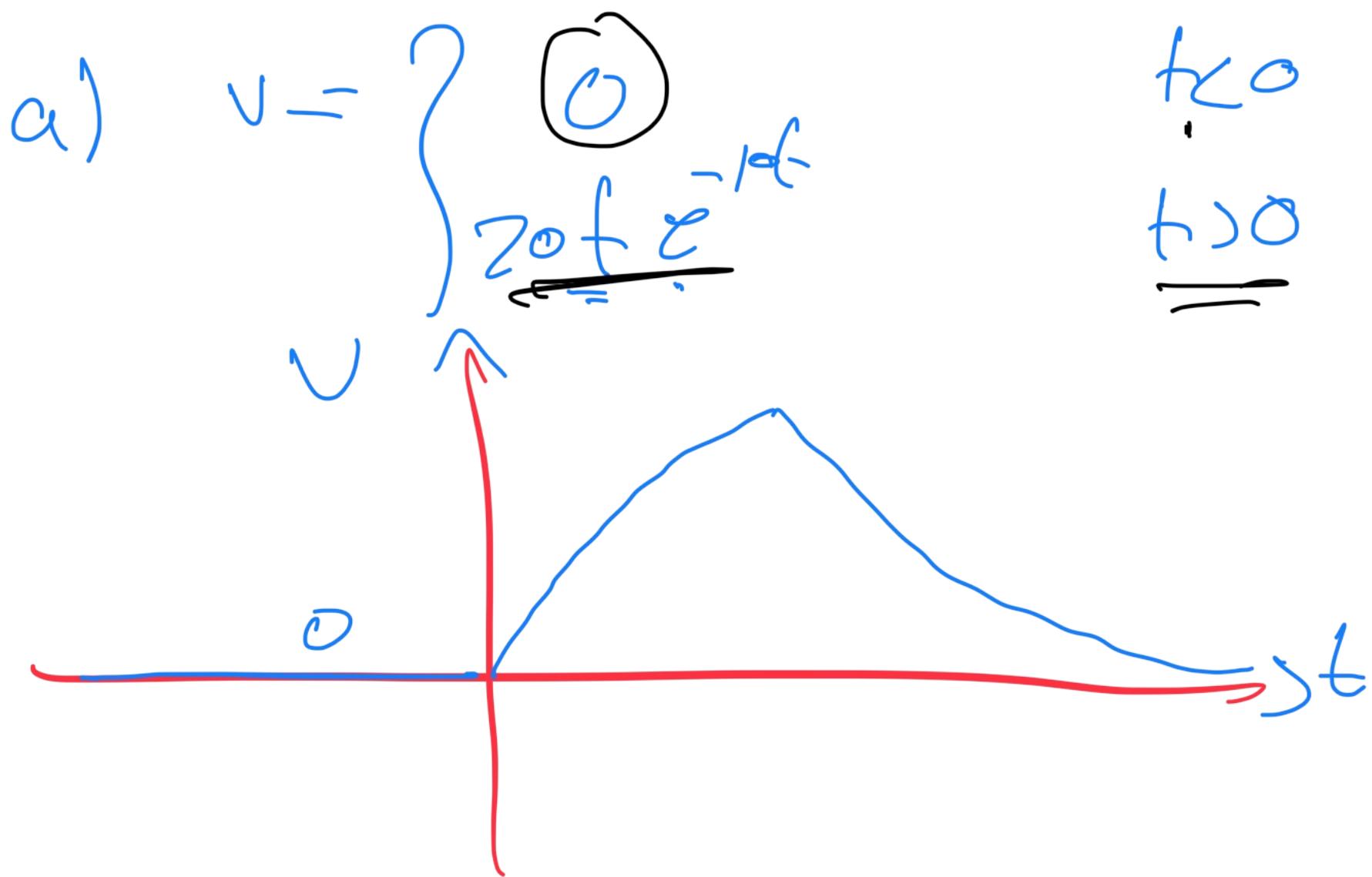

$$b) i = \frac{1}{L} \int^t v_r (t) + \overset{i(t) \rightarrow 0}{\cancel{i(t)}}$$

$$i(t) = \frac{\frac{R_C x}{100 \times 10^3}}{t} e^{-10x} dx + 0$$

$$\int x e^{-10x} \quad \downarrow \quad \text{by parts}$$

$$\begin{aligned} & \cdot \quad \partial u \\ & + x \quad \cdot \\ & - 1 \quad \cdot \\ & \rightarrow 0 \end{aligned}$$

$$\begin{aligned} & \partial v \\ & e^{-10x} \\ & e^{-10x} \int -10 \\ & e^{-10x} \int 100 \end{aligned}$$

$$200 \left[\frac{-i e^{-10t}}{10} - \frac{e^{-10t}}{100} \right]_0^{\infty} e^0 = 1$$

$$200 \left[\left(\frac{-t e^{-10t}}{10} - \frac{e^{-10t}}{100} \right) \Big|_0^{\infty} \right]$$

$$200 \left[\frac{-t e^{-10t}}{10} - \frac{e^{-10t}}{100} \Big|_0^{\infty} + \frac{1}{100} \right]$$

$$i_1(t) = ? - 20t e^{-10t} - ? e^{-10t} A$$

$$i_2(t) = \begin{cases} 0 & , t < 0 \\ 2 - 20 \bar{t}e^{-10t} - 2\bar{e}^{-10t}, & t \geq 0 \end{cases}$$



Solution for Problem #4

a) The voltage as a function of time is shown in Fig. 6.6.

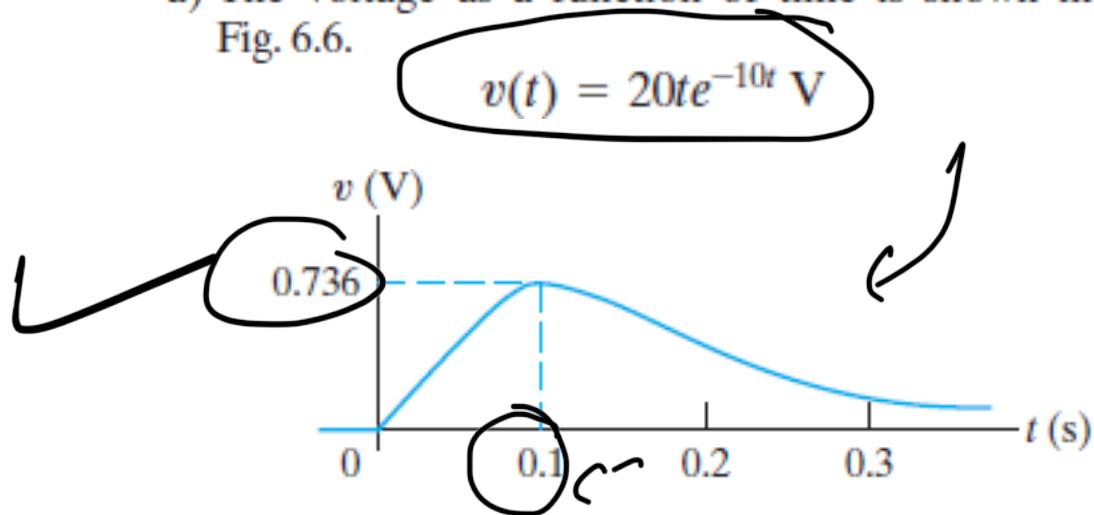


Figure 6.6 ▲ The voltage waveform for Example 6.2.

$$20 \frac{t}{e^{-10t}}$$

$$\frac{\partial V}{\partial t} \approx 20 \left[1 - e^{-10t} + t e^{-10t} \cdot \frac{1}{10} \right] \approx$$

$$20 \frac{e^{-10t}}{10} \left[1 - \cancel{10t} \right] \approx 0.$$

~~10t~~ ~~10t~~

$$1 - 10t = 0$$

$$\frac{1 - 10t}{10} \rightarrow t = \frac{1}{10} = 0,1s$$

$$V(0,1) = 20(0,1) e^{-10(0,1)} = 0,736$$

Cont. Solution for Problem #4

b) The current in the inductor is 0 at $t = 0$.
Therefore, the current for $t > 0$ is


$$i = \frac{1}{0.1} \int_0^t 20\tau e^{-10\tau} d\tau + 0$$

Use integration by parts: $\int_0^t u \, dv = uv|_0^t - \int_0^t v \, du$

$$= \cancel{2}(1 - 10te^{-10t} - e^{-10t}) \text{ A}, \quad t > 0.$$

$t(s)$	0	0.1	0.2	0.3	0.4	0.5
$v(t)$	0	0.53	1.2	1.6	1.8	1.9

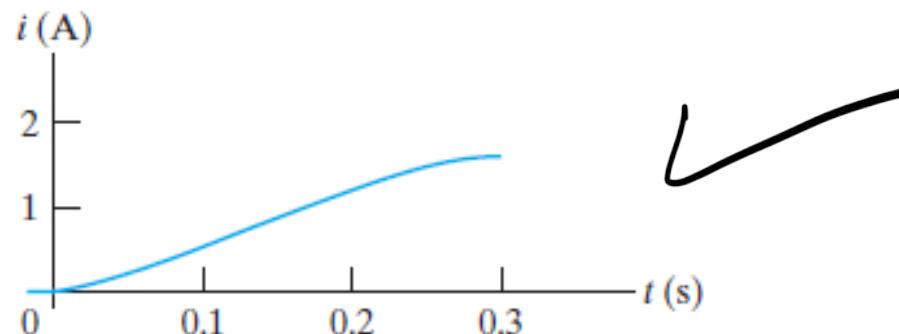c) Figure 6.7 shows the current as a function of time.



Homework

6.1 The current in a $150 \mu\text{H}$ inductor is known to be

PSPICE
MULTISIM

$$i_L = 25te^{-500t} \text{ A} \quad \text{for } t \geq 0.$$

- a) Find the voltage across the inductor for $t > 0$.
(Assume the passive sign convention.)
- b) Find the power (in microwatts) at the terminals of the inductor when $t = 5 \text{ ms}$.
- c) Is the inductor absorbing or delivering power at 5 ms ?
- d) Find the energy (in microjoules) stored in the inductor at 5 ms .
- e) Find the maximum energy (in microjoules) stored in the inductor and the time (in milliseconds) when it occurs.