



## **ELECTRICAL ENGINEERING DEPARTMENT**

**EE242: Electric Circuits II**

**Lecture 1-3**

**COURSE SYLLABUS**  
**&**  
**Review on DC Circuit Analysis Methods**

**Dr.Nawel AFSI**

[nafsi@kfu.edu.sa](mailto:nafsi@kfu.edu.sa)

**Instructor:**

**Dr. Nawel AFSI**

Email: [nafsi@kfu.edu.sa](mailto:nafsi@kfu.edu.sa)

Room: Building 59 – Room 3113

**Office hours:**

Monday/ Thursday : 11:00-12:00 AM

Other appointments can be scheduled by email.

# Course Description:

- A continuation of Electric Circuits I
- AC sinusoidal analysis and power calculations
- Balanced three phase circuits
- Laplace Transform and Circuit analysis using Laplace Transform
- Passive filters analysis and design and Bode diagram
- Two port Circuits
- Three hours lectures per week and 5 to 6 labs per semester

# Course Learning Outcomes:

---



1. An ability to analyze AC sinusoidal circuits (1).
2. An ability to perform power calculations and analyze balanced three phase circuits (1).
3. An ability to perform circuit analysis for magnetically coupled circuits
4. An ability to perform Circuit analysis using Laplace Transform (1).
5. An ability to analyze and design passive filters (1, 3, 7).
6. An ability to plot Bode diagram (1).
7. An ability to solve two port Circuits (1).
8. A familiarity with basic electric equipment like AC power sources signal generators and measuring instruments (3, 5, 6).

# Major Topics to be Covered and Schedule in Weeks:

No	List of Topics	Contact Hours
1	Review of DC Circuit Analysis Methods	3
2	Principals of Waveforms and Power Calculations	3
3	AC sinusoidal analysis	6
4	Balanced three phase circuits;	4.5
5	Magnetically Coupled Circuits	4.5
6	Passive Filters Analysis and design	6
7	S-Domain and Frequency Domain applications	3
8	Bode Plot and Electric circuits design and analysis using software	4.5
9	Two port Circuits	3
10	Lab experiments	7.5
Total		45

# Marking Scheme:



(1)	Quizzes and HWKs	15%
(2)	Project (Research Assignments)	10%
(3)	Labs Experiments	15%
(4)	Midterm Exam	20%
(5)	Final Exam	40%
Total		100%

# Textbook and References

---

Essential References	Fundamentals of Electric Circuit, 5th edition, Mathew and Alexander, McGraw-Hill, 2012, ISBN-10: 0077263197
Supportive References	Electric circuits, 9 <sup>th</sup> Edition, Nilsson/Riedel, Pearson Publishing Company, 2011, ISBN-10: 0137050518. Engineering circuit analysis, 9th edition, Hayt, Kemmerly and Durbin, McGraw-Hill Science/Engineering/Math, 2011), ISBN-10: 0073529575-ISBN-13: 978-0073529578
Electronic Materials	Blackboard
Other Learning Materials	Power point slides

# Review on DC Circuit Analysis Methods

## 1- Basic Concepts



- Basics of Electric Circuits (Units, Quantities, Components, and Network Connections (series and Parallel))
- Basic Electric Lows (Ohm's law, KCL, KVL)
- Series Resistors and Voltage Division
- Parallel Resistors and Current Division
- Resistor Combination and Wye-Delta transformation

# Kirchhoff's Current Law (KCL)

$$\sum I_{in} = \sum I_{out}$$

single node




Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0$$

$N \triangleq$  number of branches connected to node

$i_n \triangleq n^{th}$  current entering (or leaving) the node

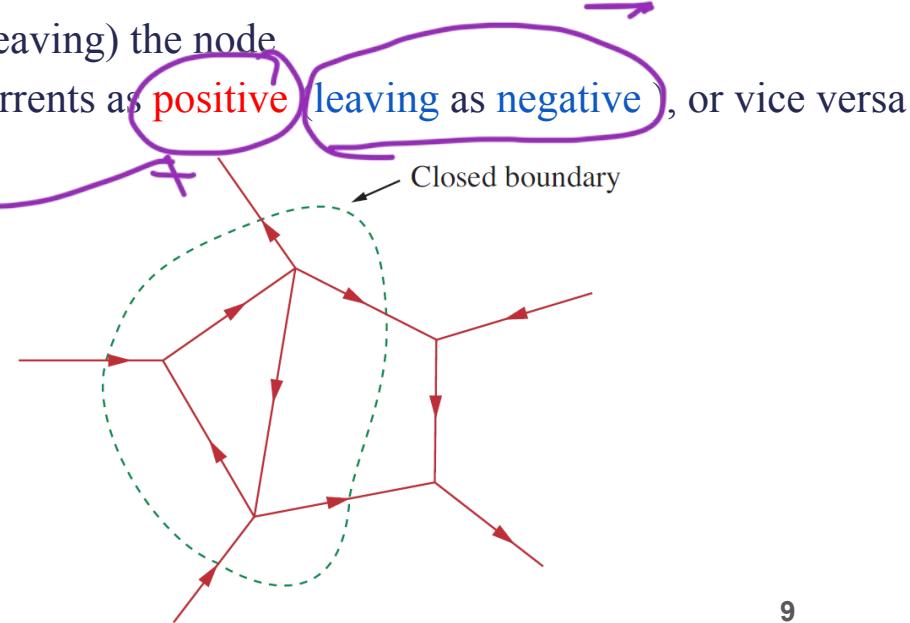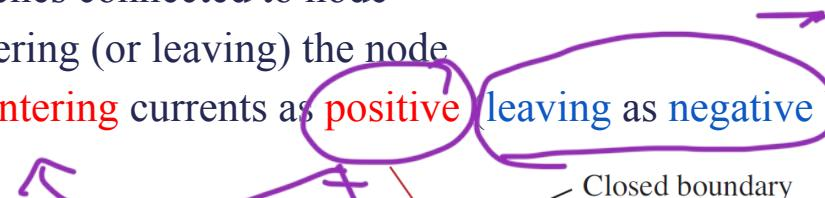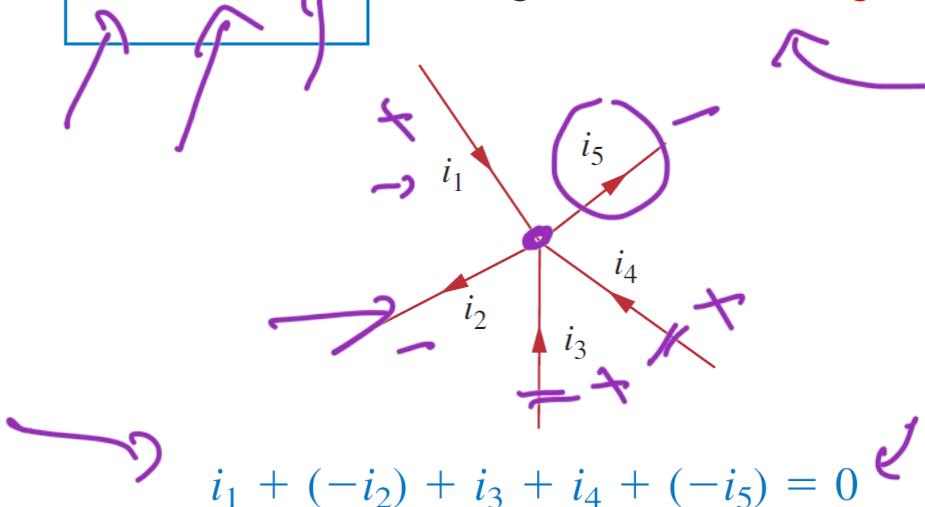We might consider **entering** currents as **positive** **leaving** as **negative**, or vice versa



$$\sum I_{in} = \sum I_{out}$$
$$I_1 + I_3 + I_4 = + \underbrace{I_2 + I_5}_{-}$$
$$\boxed{I_1 - I_2 + I_3 + I_4 - I_5 = 0} *$$

# Kirchhoff's Voltage Law - KVL



$$\sum V = 0$$

Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

loop

$$\sum_{m=1}^M v_m = 0$$


$M \triangleq$  number of branches in a loop

$v_m \triangleq m^{\text{th}}$  voltage (across  $m^{\text{th}}$  element) in the loop

KVL can be applied clockwise or counter-clockwise around the loop. Either way, the algebraic sum is zero

"series"

series

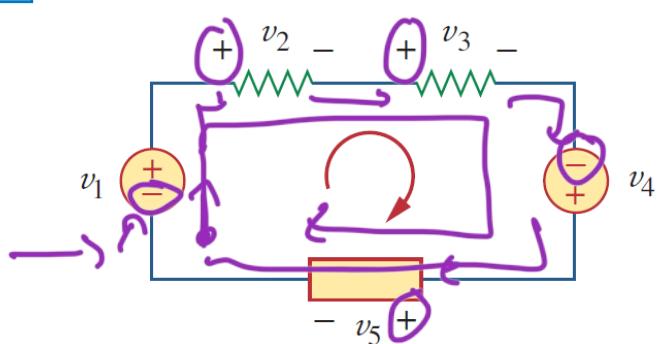


$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

$$v_2 + v_3 + v_5 = v_1 + v_4$$

Alternative Form

Sum of voltage drops = Sum of voltage rises

$$v_2 + v_3 + v_5 = v_1 + v_4$$

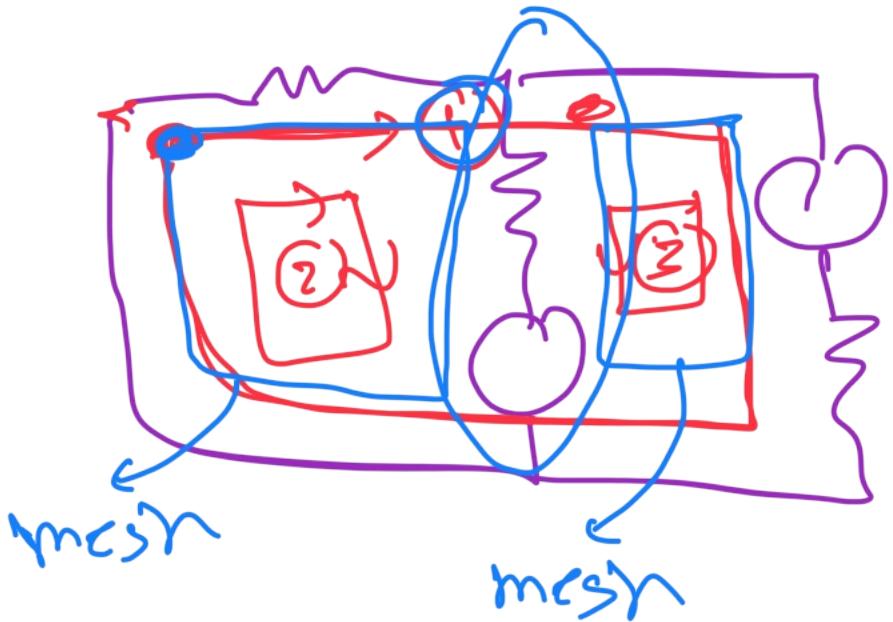


loop  → 3

mesh  → 2  
grid mesh

زوجي غير صحيح لكنه loop of mesh ok

# Voltage Divider Rule

→ Series

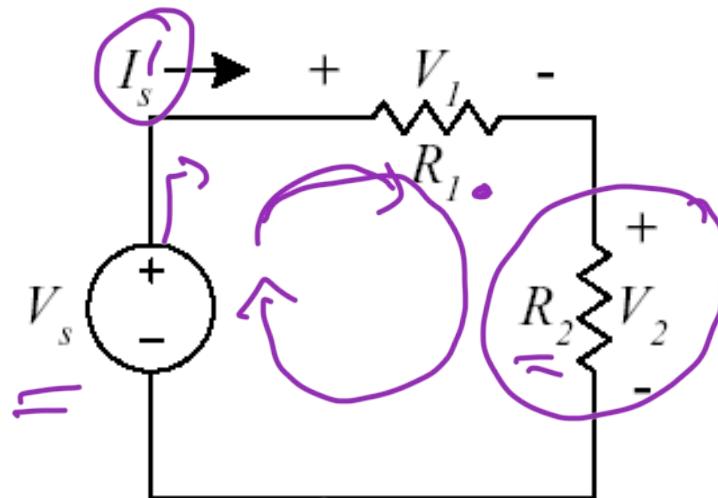

$$\text{Series } I_s \Rightarrow I_1 = I_2$$

Voltage is divided by same ratio of resistors

$$V = IR$$

$$R_{eq} = R_1 + R_2$$

$$I_s = \frac{V_s}{R_{eq}}$$


$$= \frac{V_s}{R_1 + R_2}$$

$$V_2 = I_s R_2$$

$$= V_s \frac{R_2}{R_1 + R_2}$$

$$V_1 = I_s R_1$$

$$= V_s \frac{R_1}{R_1 + R_2}$$

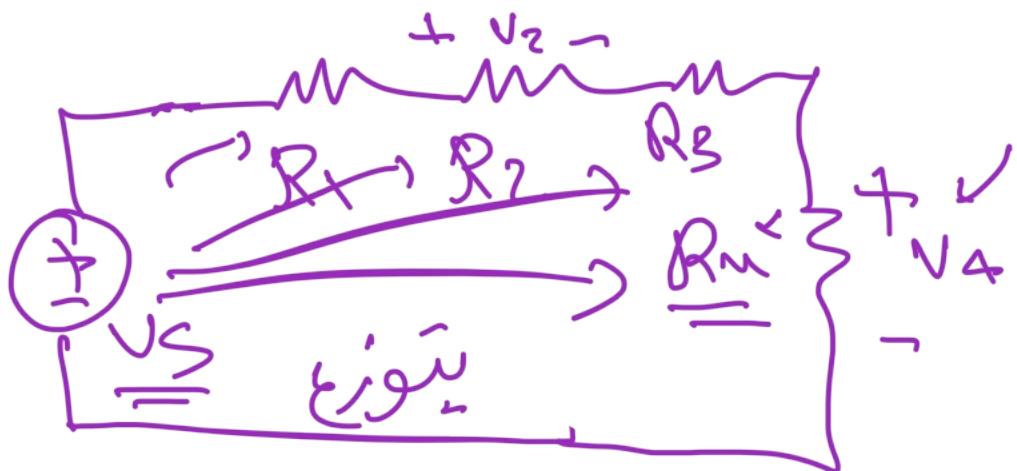

$\Rightarrow$  series

Voltage divider

الحال  $\Rightarrow$  ~~حال~~


$$V_2 = \frac{R_u}{R_1 + R_2 + R_3 + R_u} \times V_s$$

$$V_2 = \frac{R_2}{R_1 + R_2 + R_3 + R_u} \times V_s$$

Voltage divider  $\rightarrow$  "series only"

$$N_N = \frac{R_N}{R_{\text{eq}}} \times N_S$$

$$R_1 + R_2 + R_3 + \dots$$

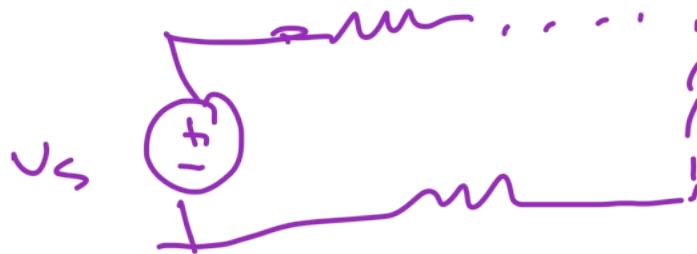


Series  
N, R

# Current Divider Rule

"Parallel"

$\mathcal{L}, R$

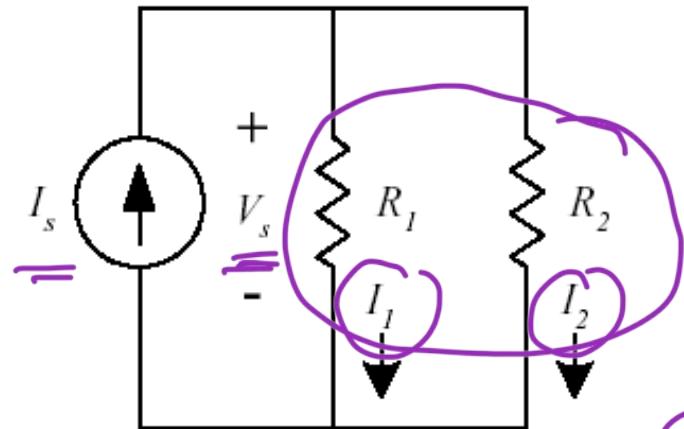

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \dots \textcircled{1}$$

$$V_s = I_s \frac{R_1 R_2}{R_1 + R_2}$$

$$I_2 = \frac{V_s}{R_2}$$


$$= I_s \frac{R_1}{R_1 + R_2}$$

$$I_1 = \frac{V_s}{R_1}$$

$$= I_s \frac{R_2}{R_1 + R_2}$$

Current is divided by opposite ratio of resistor

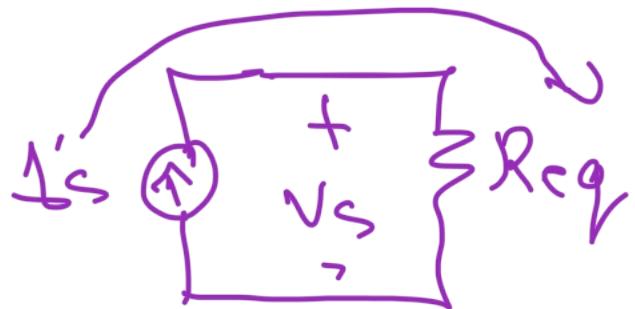نسبة  $\rightarrow$  Parallel  $\rightarrow V_s = V_1 = V_2$



$$\underline{V_s} = \underline{I_s} * \text{Req} \quad (2)$$

$$I_1 = \frac{V_s}{R_1}, \quad \text{and} \quad I_2 = \frac{V_s}{R_2} \dots \quad (3)$$

# Current divider

"Parallel"




$$I_2 = \frac{R_{\text{eq}}}{R_2} \times I_s$$

Parallel

$$R_{\text{eq}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Current divider

"Parallel"

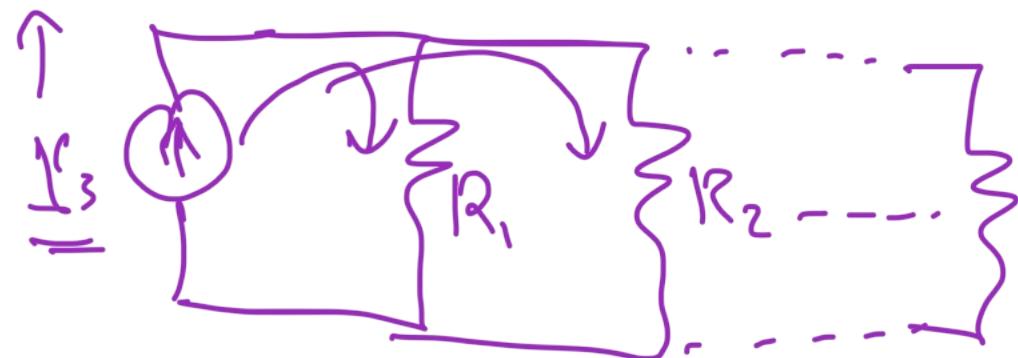

$$I_N = \frac{R_{eq}}{R_N} \times I_S$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \dots$$

gesamt



currents

$I_2 = \frac{R_2}{R_1 + R_2} * I_S$


currents


$I_1 = \frac{R_1}{R_1 + R_2} * I_S$


خواص دائرة سلسلة
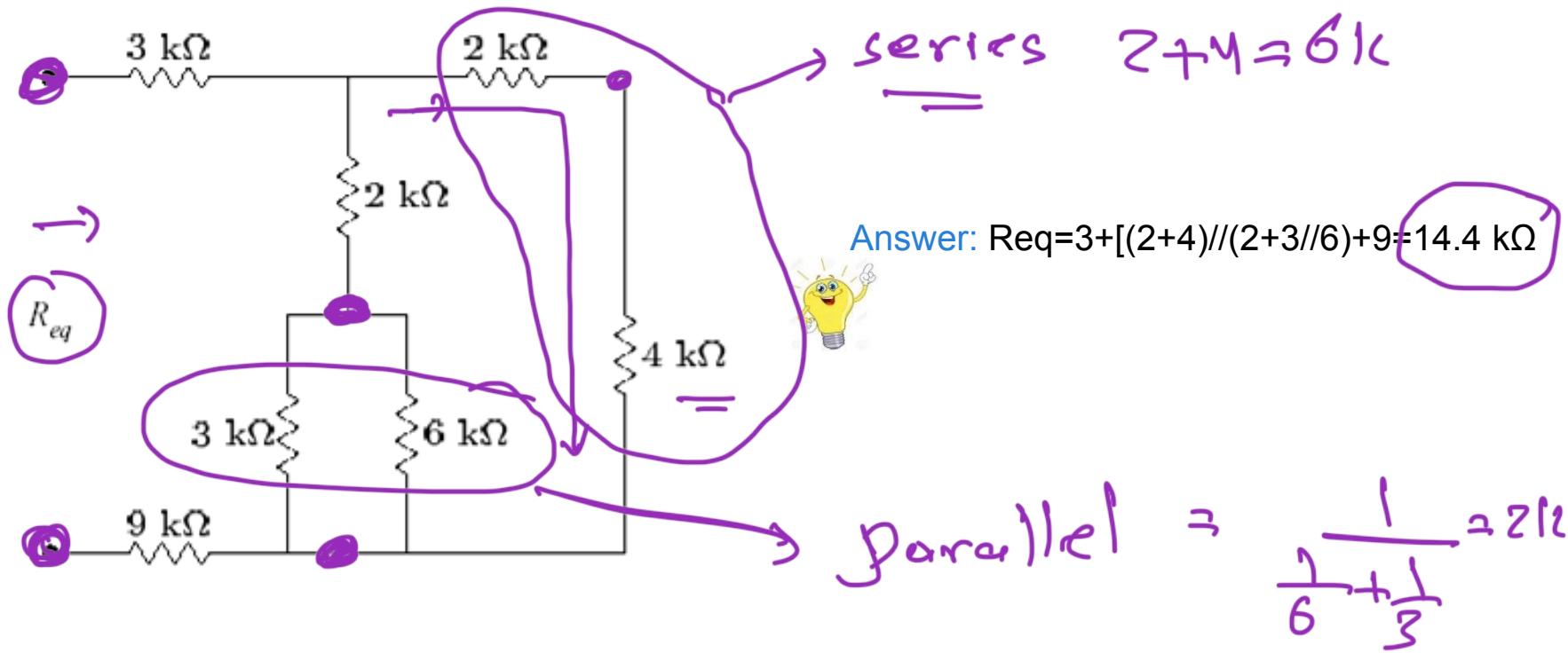
# Series and Parallel Resistors

- Find  $R_{eq}$  in the given circuit below:



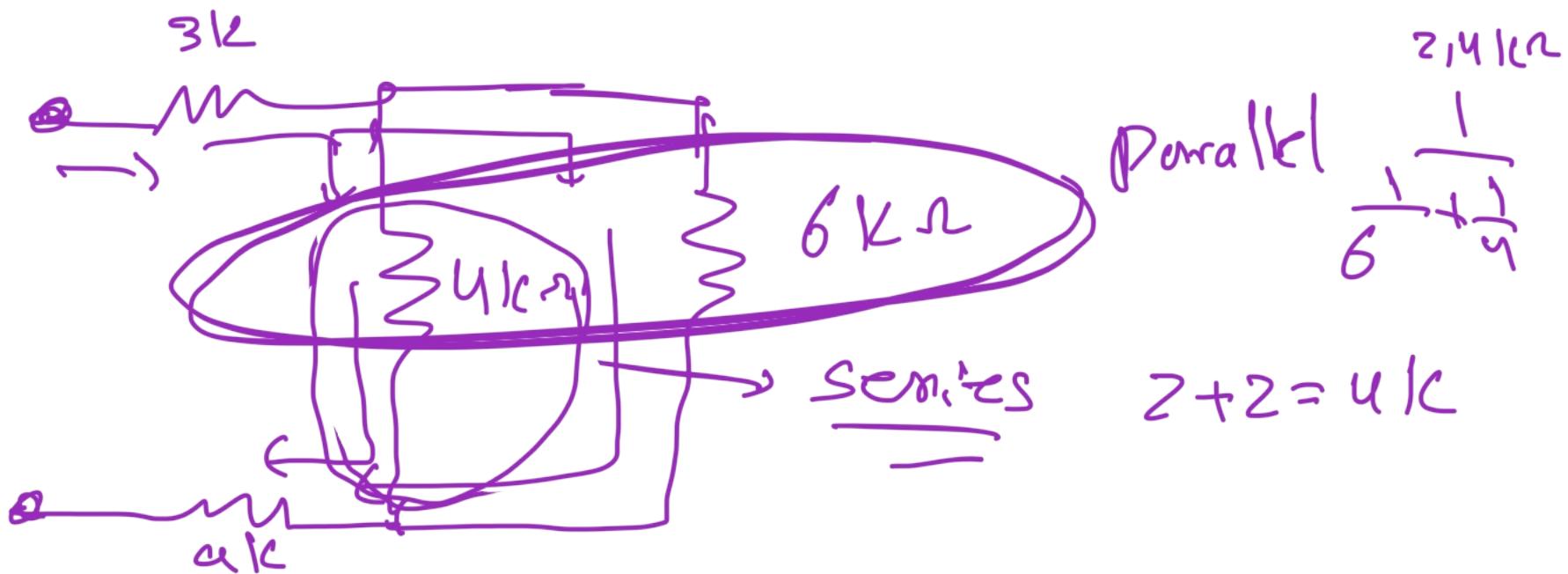

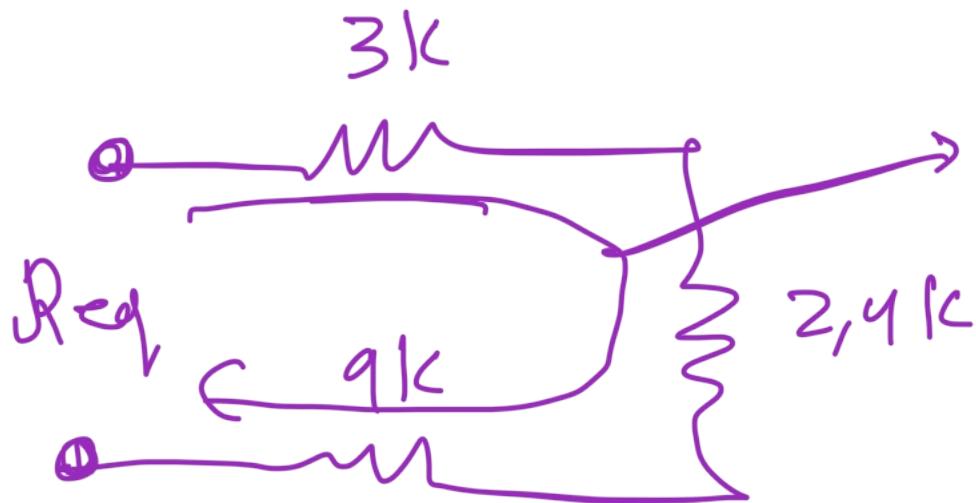

$$\text{series} = 3 + 9 + 2,4$$

$$R_{eq} = (4,4) \text{ k} \Omega$$



## 2- Circuits Methods of Analysis




- Nodal analysis
- Nodal analysis with voltage source
- Mesh analysis
- Mesh analysis with current source
- Nodal and mesh analyses by inspection
- Nodal versus mesh analysis

# Nodal Analysis

Nodal Analysis utilizes **KCL** to solve for **unknown node voltages**

Circuit Example

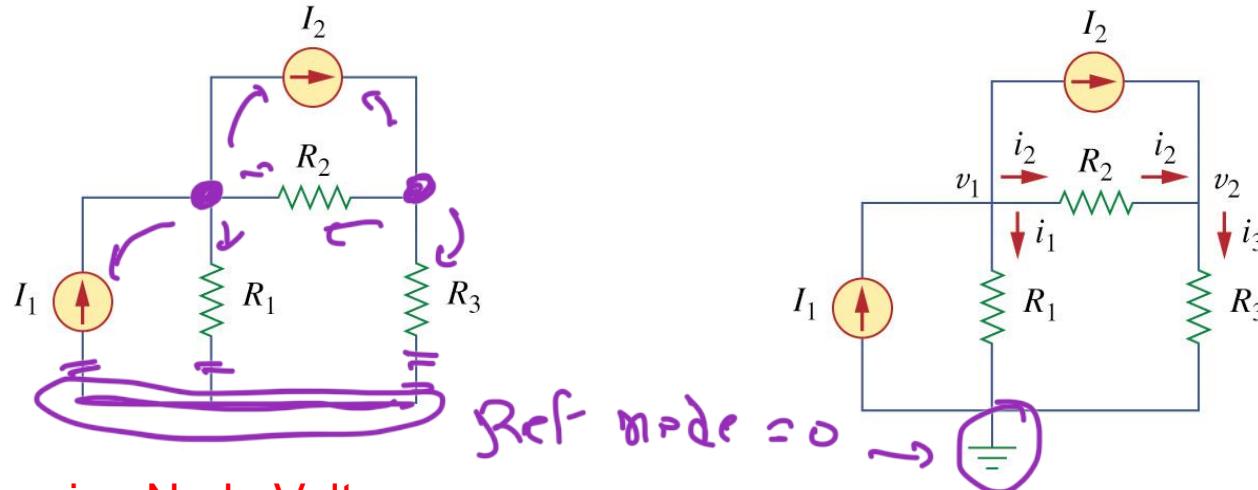



Steps to Determine Node Voltages:

1. Select a node as the **reference node**. Assign voltage  $v_1$ ,  $v_2$ , ...  $v_{n-1}$  to the remaining  $n-1$  nodes. The voltages are referenced with respect to the reference node.
2. Apply **KCL** to each of the  $n-1$  nonreference **nodes**. Use **Ohm's law** to express the branch currents in terms of node voltages.
3. Solve the resulting **simultaneous equations** to obtain the unknown node voltages.
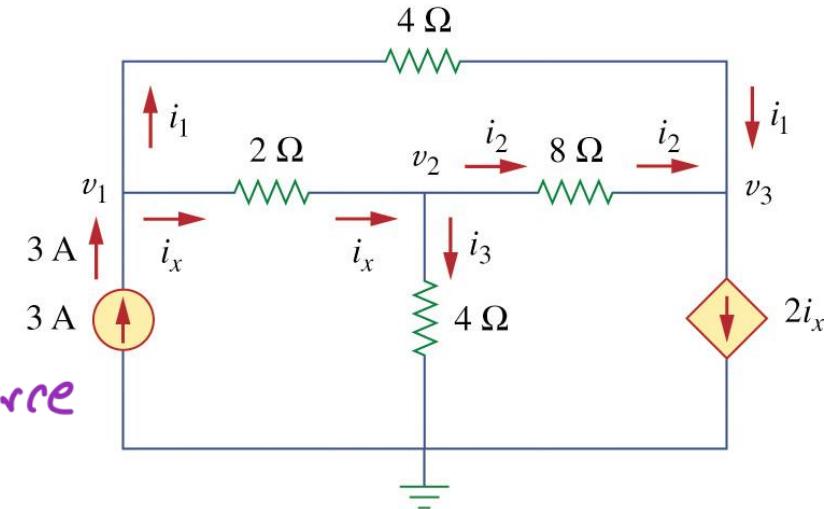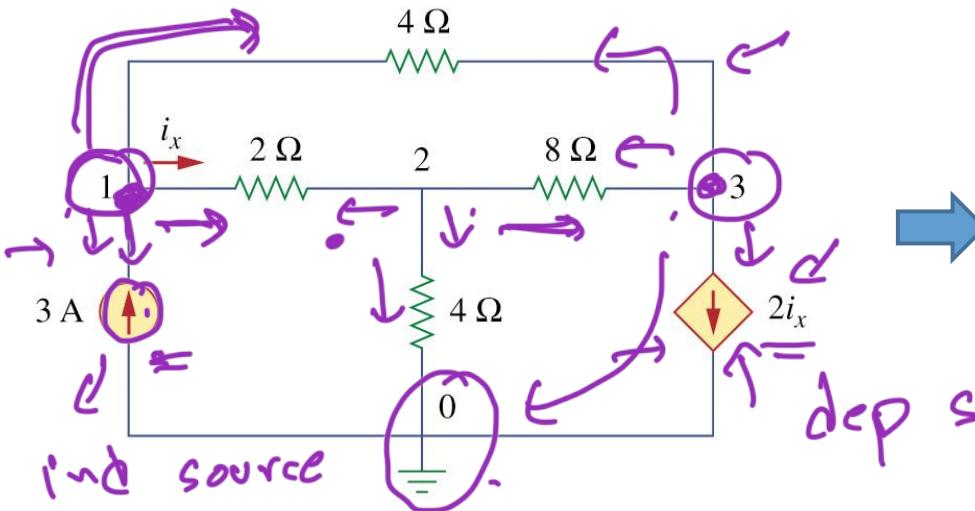
## Example 2

$$\text{Node } \frac{V}{R} = I_e$$

Determine the node voltages in the following circuit



$$i_x = \frac{v_1 - v_2}{2}$$

node ①

$$-3 + \frac{N_1 V_1}{N_2} + \frac{N_3 V_1}{N_1} = 0$$

node ②

$$N_1 V_2 + N_2 V_2 = 0$$

node ③

$$N_3 V_3 + N_2 V_3 + [N_1 V_3 - N_2 V_3] = 0$$

$$\frac{3}{5} \dot{V_1} - \frac{\dot{V_2}}{2} - \frac{\dot{V_3}}{5} = 3 \rightarrow \textcircled{1}$$

$$-\frac{1}{2} \dot{V_1} + \frac{7}{8} \dot{V_2} - \frac{\dot{V_3}}{8} = 0 \rightarrow \textcircled{2}$$

$$\frac{3}{5} \dot{V_1} - \frac{9}{8} \dot{V_2} + \frac{3}{8} \dot{V_3} = 0 \rightarrow \textcircled{3}$$

mode  $\rightarrow 5 \rightarrow 2$

$$\boxed{V_1 = 4,8 \text{ V}}, \boxed{V_2 = 2,4 \text{ V}}, \boxed{V_3 = -2,4 \text{ V}}$$

# Example 2

KCL at node 1:

$$3 = i_1 + i_x \Rightarrow 3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$

Multiplying by 4 and rearranging terms, we get

$$3v_1 - 2v_2 - v_3 = 12 \quad (1)$$

KCL at node 2:

$$i_x = i_2 + i_3 \Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

Multiplying by 8 and rearranging terms, we get


$$-4v_1 + 7v_2 - v_3 = 0 \quad (2)$$

KCL at node 3:

$$i_1 + i_2 = 2i_x \Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{2(v_1 - v_2)}{2}$$

Multiplying by 8, rearranging terms, and dividing by 3, we get

$$2v_1 - 3v_2 + v_3 = 0 \quad (3)$$

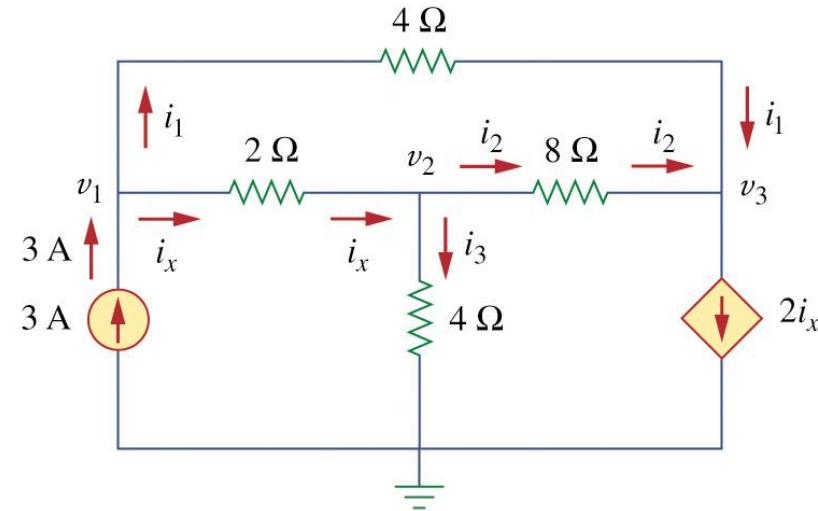

## Example 2



$$3v_1 - 2v_2 - v_3 = 12 \quad (1),$$

$$-4v_1 + 7v_2 - v_3 = 0 \quad (2),$$

$$2v_1 - 3v_2 + v_3 = 0 \quad (3)$$

**Solve using any technique**

(Elimination technique, Equations reduction, Cramer's rule, or calculator)

Thus:

$$v_1 = 4.8 \text{ V},$$

$$v_2 = 2.4 \text{ V},$$

$$v_3 = -2.4 \text{ V}$$

# Nodal Analysis with Voltage Sources

Case 1: The voltage source is connected between a nonreference node and the reference node:


- The nonreference node voltage is equal to the magnitude of voltage source

Example: in the circuit to the right:

$$v_1 = 10 \text{ V}$$


- The number of unknown nonreference nodes is reduced by one.

节点数，即  
0 8 5 6 0 2 0 =

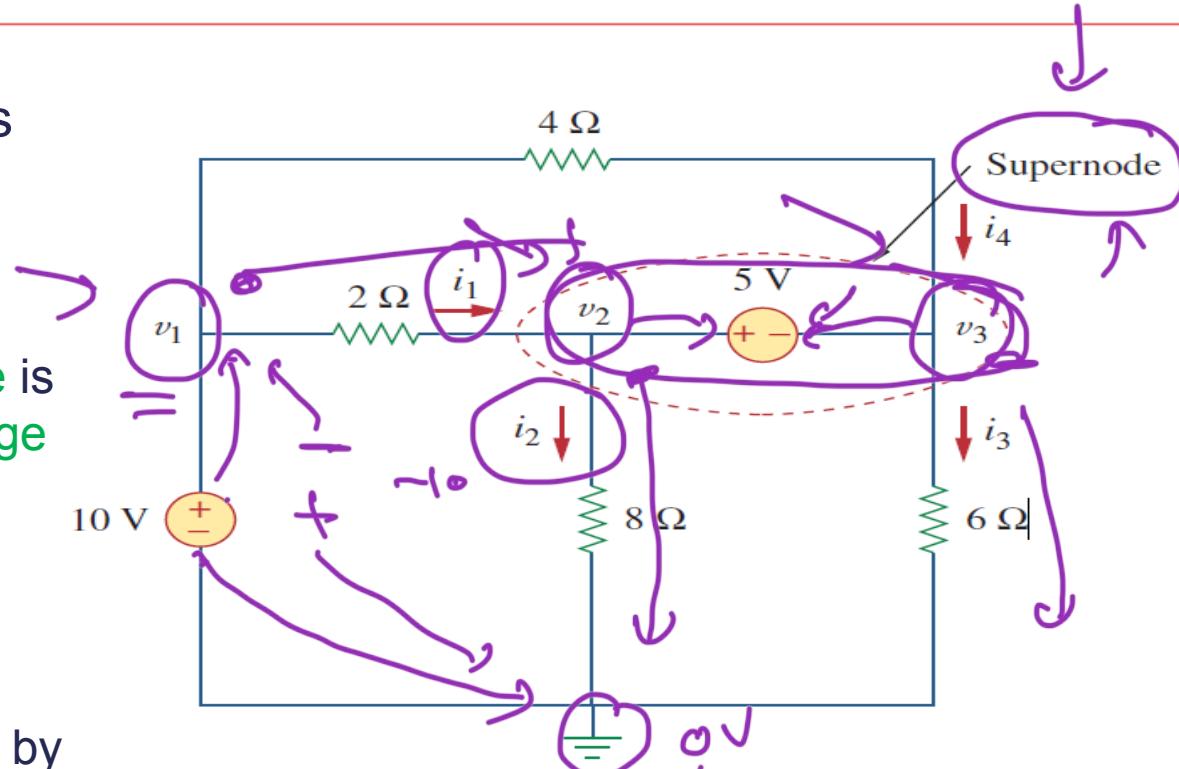

$$V_2 - V_3 = 5 \rightarrow ①$$


super node

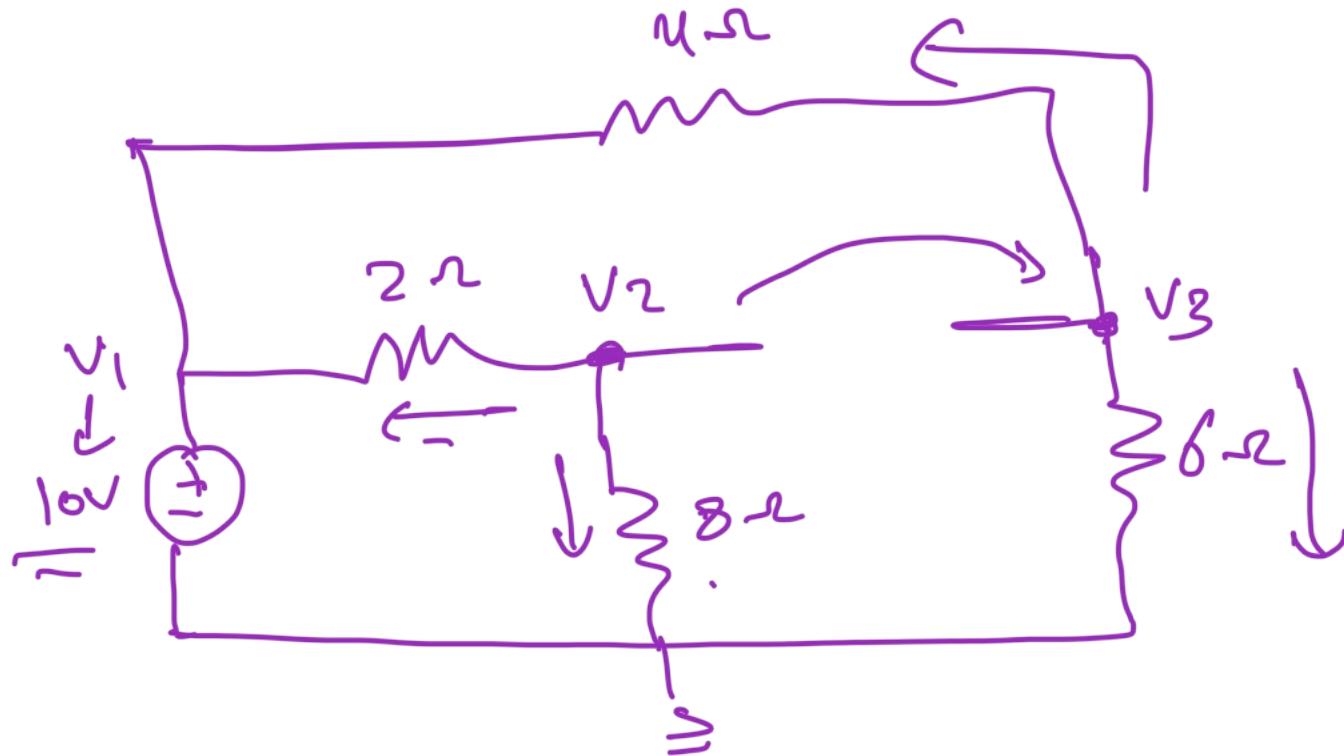

node 2 + 3

Fusion

" $\rightarrow$ "

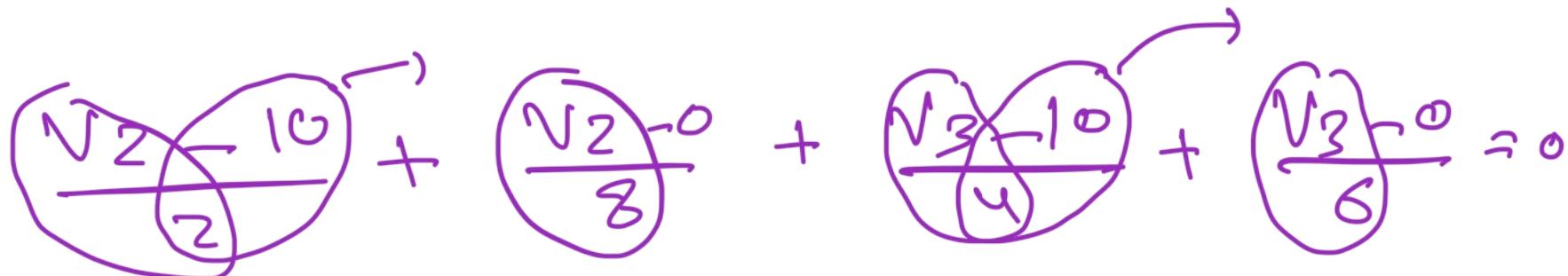

$$\frac{5}{8} \sqrt{2} + \frac{5}{12} \sqrt{3} = \frac{10}{9} + \frac{10}{2} = 7, 5 \rightarrow 2$$

$$\sqrt{2} - \sqrt{3} = 5 \rightarrow 1$$

mode  $\rightarrow$  5  $\rightarrow$  1

$$V_2 = 9,2V$$

$$V_3 = 4,2V$$

$$I_1 = \frac{N_1 - V_2}{2} = \frac{10 - 9,2}{2} = 0,4A$$

$$I_2 = \frac{N_2 - 0}{8} = \frac{9,2}{8} = 1,15A$$

$$I_3 = \frac{N_3 - 0}{6} = \frac{4,2}{6} = 0,7A$$

$$I_4 = \frac{V_1 - V_3}{4} = \frac{10 - 4,2}{4} = 1,45A$$

# Nodal Analysis with Voltage Sources

Case 2: The voltage source is connected between two nonreferenced nodes:


- a generalized node (supernode) is formed.
- Write KCL of the supernode (combining node 2 and 3) as a closed surface

Example: in the circuit to the right:

$$i_1 + i_4 = i_2 + i_3$$

- Use supernode KVL as one equation


Example: in the circuit to the right:

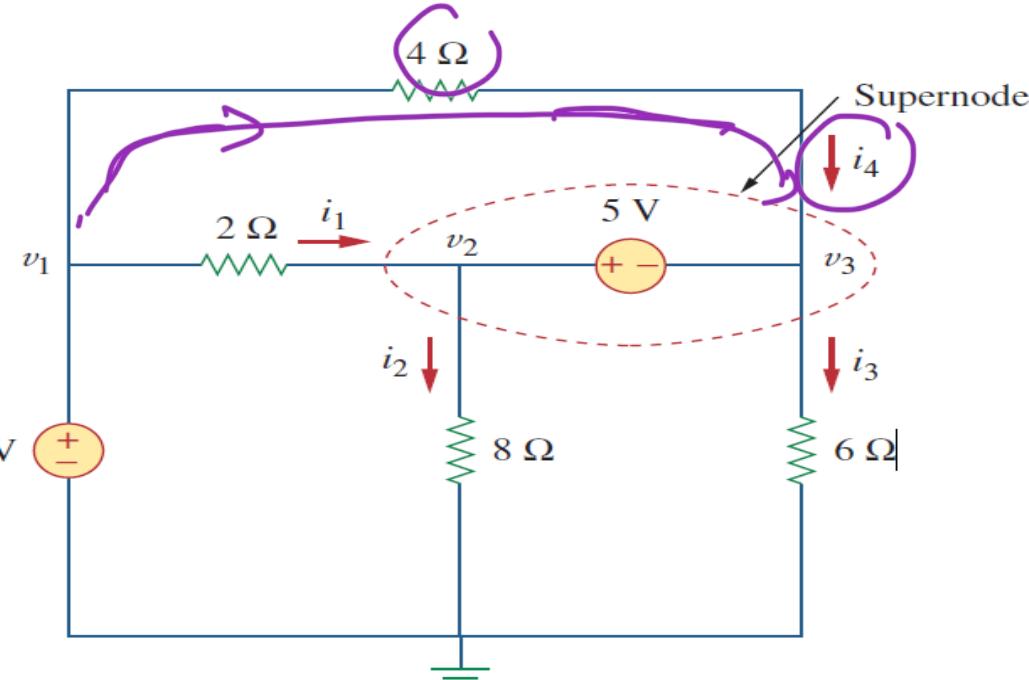

$$v_2 - v_3 = 5$$
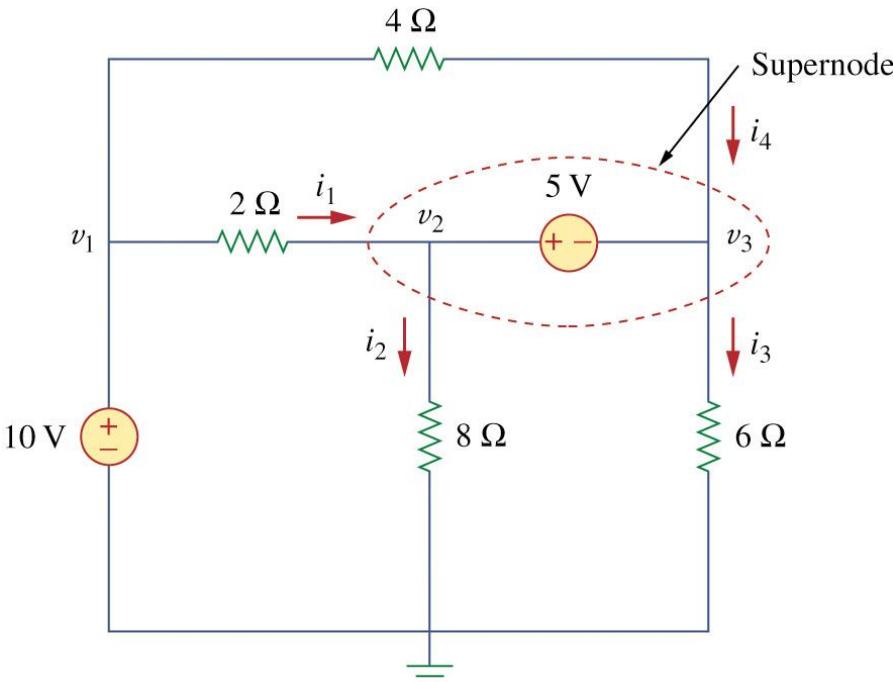
# Example 3

Find the node voltages in the following circuit



## Solution:

The voltage at node 1 is already known

$$v_1 = 10 \text{ V} \quad (1)$$

We have only two unknown node voltages ( $v_2$  and  $v_3$ )

We need two equations

KCL at the supernode  $i_1 + i_4 = i_2 + i_3$

$$\frac{10 - v_2}{2} + \frac{10 - v_3}{4} = \frac{v_2}{8} + \frac{v_3}{6}$$

$$120 - 12v_2 + 60 - 6v_3 = 3v_2 + 4v_3$$


$$180 = 15v_2 + 10v_3 \quad (2)$$

$$v_2 - v_3 = 5 \quad (3)$$

KVL at the supernode
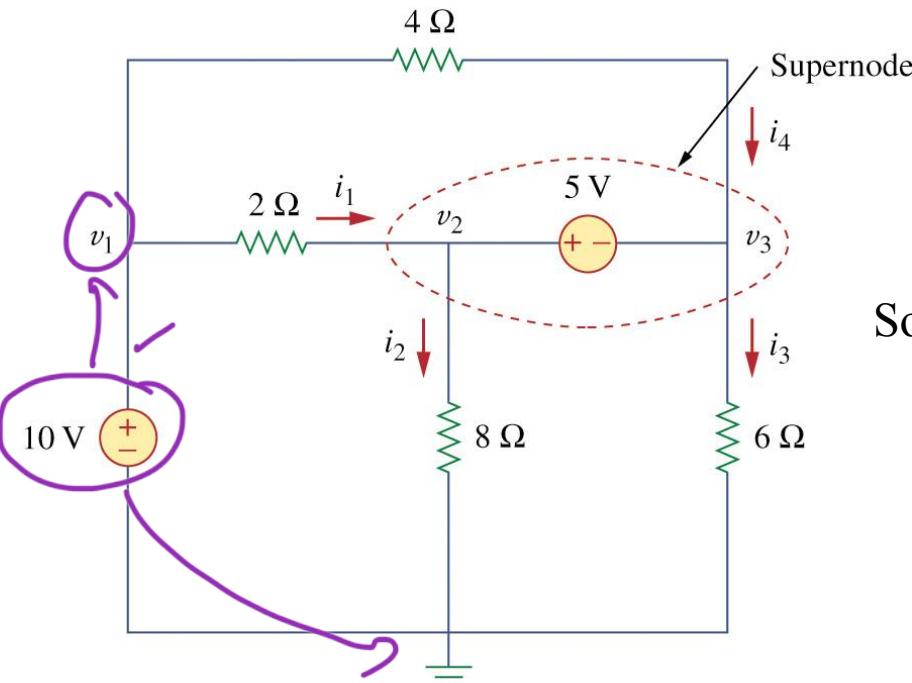
# Example 3

Find the node voltages in the following circuit



**Solution:**

$$180 = 15v_2 + 10v_3 \quad (2)$$

$$v_2 - v_3 = 5 \quad (3)$$

Solving equations (2) and (3) simultaneously:

$$v_2 = 9.2V$$

$$v_3 = 4.2V$$



## 2- Methods of Analysis 2




- Nodal analysis
- Nodal analysis with voltage source
- Mesh analysis
- Mesh analysis with current source
- Nodal and mesh analyses by inspection
- Nodal versus mesh analysis
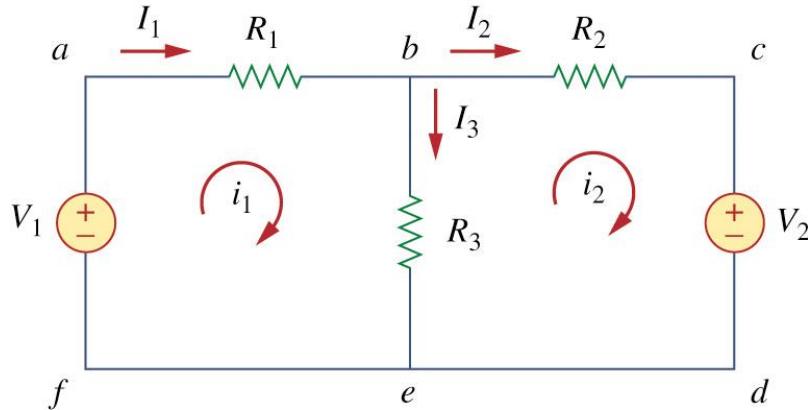
# Mesh Analysis

A **mesh** is a loop which does not contain any other loops within it.

Mesh Analysis utilizes **KVL** to solve for **unknown mesh currents**




$$\text{I} = \text{I}\Delta R$$

Steps to Determine mesh currents:

1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
2. Apply **KVL** to each of the  $n$  meshes. Use **Ohm's law** to express the voltages in terms of the mesh currents.
3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.
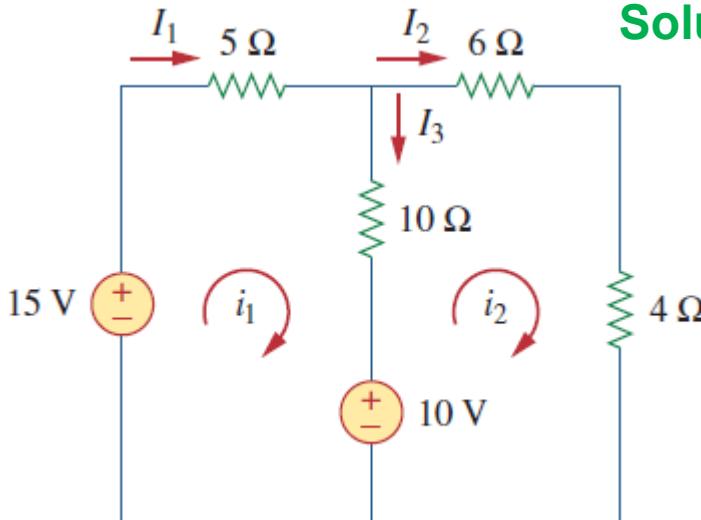
# Example 4

For the following circuit, use mesh analysis to find the branch currents  $I_1$ ,  $I_2$  and  $I_3$



$$I_1 = i_1,$$

$$I_2 = i_2,$$

$$I_3 = i_1 - i_2$$

**Solution:** Step#1: Assign mesh currents

Step#2: Write KVL for each mesh

□ KVL at mesh1:  $-15 + 5I_1 + 10I_3 + 10 = 0$

$$5i_1 + 10(i_1 - i_2) = 5$$

Divide both sides by 5 and collect common terms:


$$3i_1 - 2i_2 = 1 \quad (1)$$

□ KVL at mesh 2:  $-10 - 10I_3 + 10I_2 = 0$

$$-10(i_1 - i_2) + 10i_2 = 10$$

Divide both sides by 10 and collect common terms:

$$-i_1 + 2i_2 = 1 \quad (2)$$

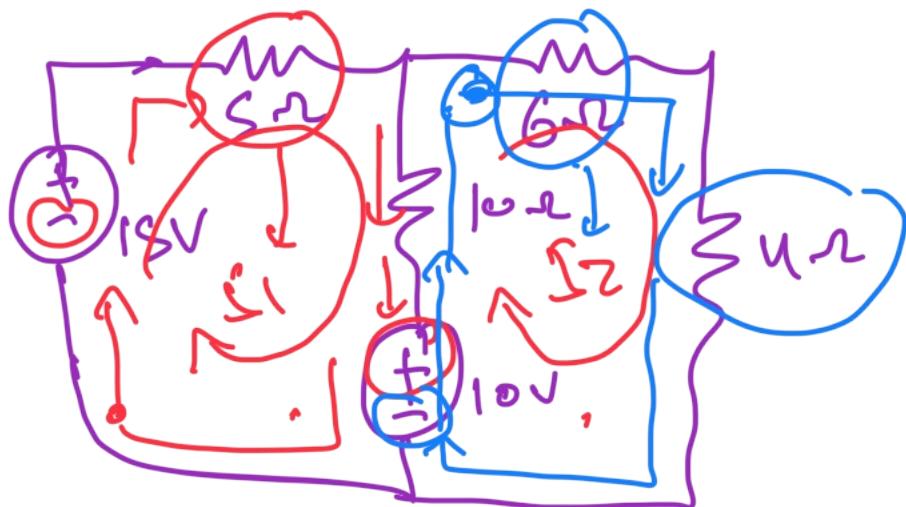

mesh  $\rightarrow I$   
 یک چند گانه  
 $\sum V = 0$

mesh ①  $\leftarrow$

$$\underline{-15} + \underline{5I_1} + \underline{10(I_1 - I_2)} + \underline{10} = 0$$

$15I_1 - 10I_2 = 5 \rightarrow ①$

mesh ②

$$6 \underline{I_2} + 4 \underline{I_2} + (-10) + \underline{10(I_2 - I_1)} = 0$$

$$-10I_1 + 20I_2 = 10 \rightarrow ②$$

mode  $\rightarrow S \rightarrow ①$

$$I_1 = 1A$$

$$I_2 = 1A$$

# Example 5

Use mesh analysis to find the current  $I_o$  in the following circuit

**Solution:**

□ KVL at mesh1:  $-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$

$$22i_1 - 10i_2 - 12i_3 = 24 \quad (1)$$


□ KVL at mesh2:  $-10(i_1 - i_2) + 24i_2 + 4(i_2 - i_3) = 0$

$$-10i_1 + 38i_2 - 4i_3 = 0 \quad (2)$$

□ KVL at mesh3:  $-12(i_1 - i_3) + 4(i_3 - i_2) + 4I_o = 0$

$$-12(i_1 - i_3) + 4(i_3 - i_2) + 4(i_1 - i_2) = 0$$

$$-8i_1 - 8i_2 + 16i_3 = 0 \quad (3)$$

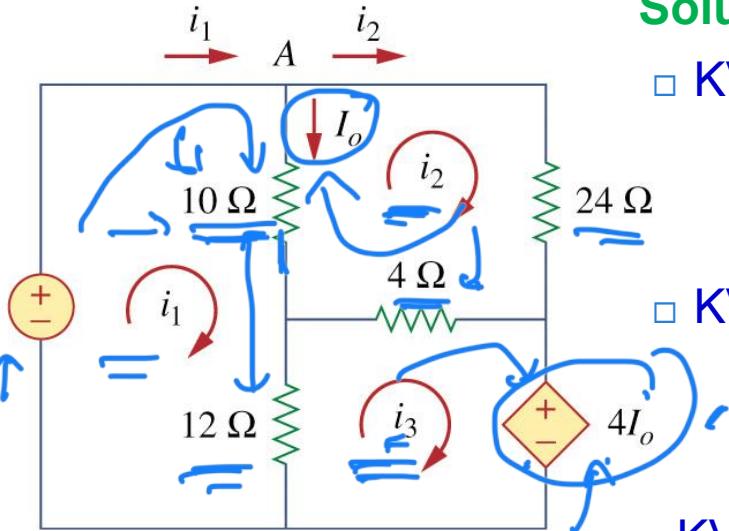

$$I_o = (i_1 - i_2)$$

$$I_o = I_1 - I_2$$

mesh ①

$$22f_1 - 10f_2 - 12f_3 = 24 \rightarrow ①$$

$$\begin{cases} f_1 = 2,25 \text{ A} \\ f_2 = 0,75 \text{ A} \\ f_3 = 1,5 \text{ A} \end{cases}$$

mesh ②

$$-10f_1 + 38f_2 - 4f_3 = 0 \rightarrow ②$$

$$\underline{-12f_1 - 4f_2 + 16f_3 + 4f_1 - 4f_2 = 0}$$

$$\underline{-8f_1 - 8f_2 + 16f_3 = 0} \rightarrow ③$$

mode  $\rightarrow S \rightarrow 2$

## Example 5

Solve using any technique

(Elimination technique, Equations reduction, Cramer's rule, or calculator)

$$i_1 = 2.25 A,$$

$$i_2 = 0.75 A,$$

$$i_3 = 1.5 A$$

$$\rightarrow I_o = (i_1 - i_2)$$

$$\text{Thus, } I_o = i_1 - i_2 = 1.5 A.$$

11

# Mesh Analysis with Current Sources


## Case 1: Current source exist only in one mesh

- The mesh current is equal to the current source

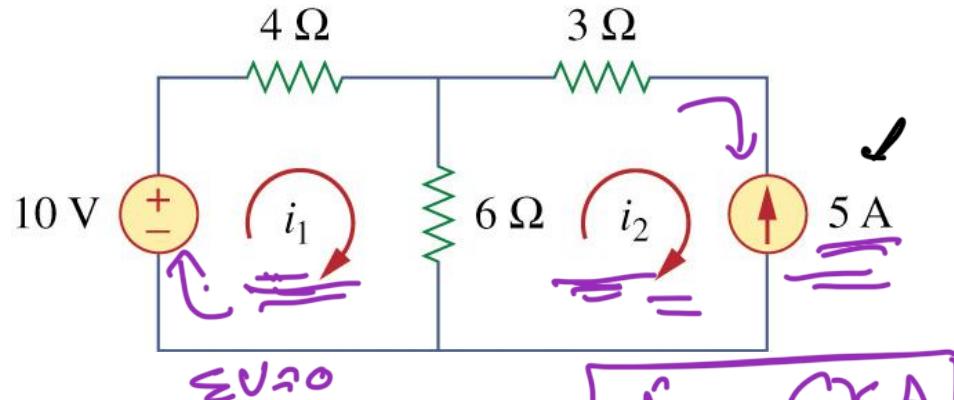Example: in the circuit to the right:

$$i_2 = -5 \text{ A}$$

- The number of unknown currents is reduced by one.



$$i_2 = -5 \text{ A}$$

الخطوة الخامسة

$$-10 + 4i_1 + 6(i_1 - 5) = 0$$
$$-10 + 4i_1 + 6i_1 - 30 = 0$$
$$\frac{10}{5}i_1 = 10 - 30 = -20$$
$$i_1 = -2 \text{ A}$$

# Mesh Analysis with Current Sources

□ **Case 2:** Current source exists between two meshes, a **super-mesh** is obtained.:

- a **supermesh** results when two meshes have a (dependent , independent) current source in common.
- A supermesh has no current of its own.
- ❖ Write **KVL** of the supermesh (combining Loop1 and 2) as one equation


Example: in the circuit to the right:

$$-20 + 6i_1 + 14i_2 = 0$$

- ❖ Use supermesh KCL as second equation

Example: in the circuit to the right:


$$i_2 - i_1 = 6$$

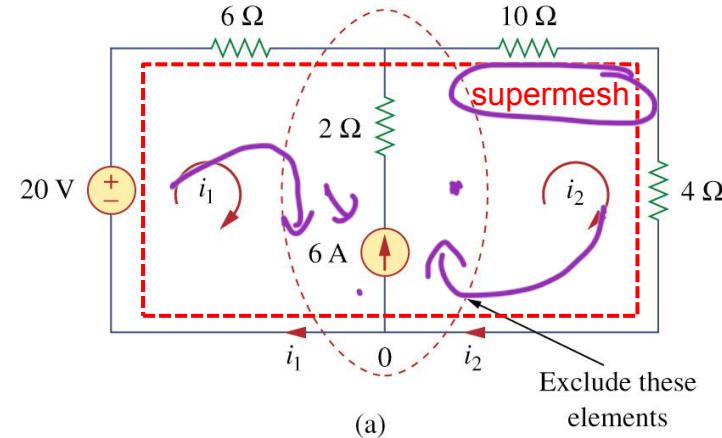

(a)

Super mesh

$$i_2 - i_1 = 6$$

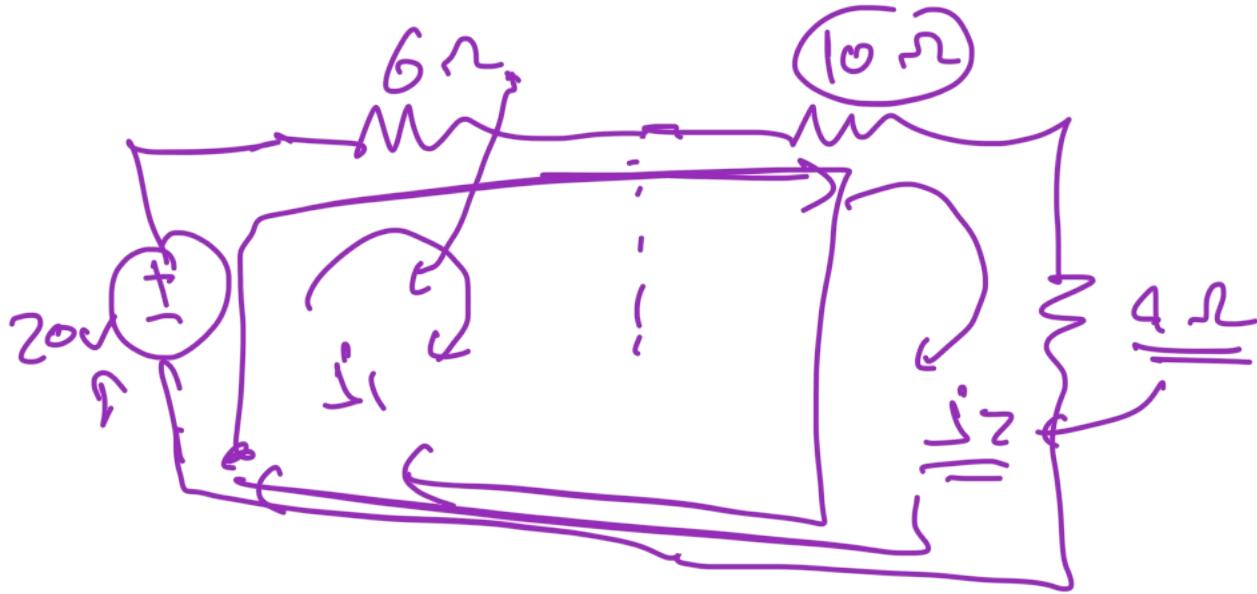

mesh 1 + 2  $\Sigma \text{v}$

$$\begin{aligned}
 & \text{(-20)} + 6f_1 + \underline{10f_2} + \underline{4f_2} = 0 \\
 \Rightarrow & \boxed{6f_1 + 14f_2 = 20}
 \end{aligned}$$

$$\Rightarrow \boxed{I_1 + I_2 = 6} \rightarrow ①$$

$$\boxed{6I_1 + 14I_2 = 20} \rightarrow ②$$


mode  $\rightarrow S \rightarrow 1$

$$\boxed{I_1 = -3,2 \text{ A}}$$

$$\boxed{I_2 = 2,8 \text{ A}}$$
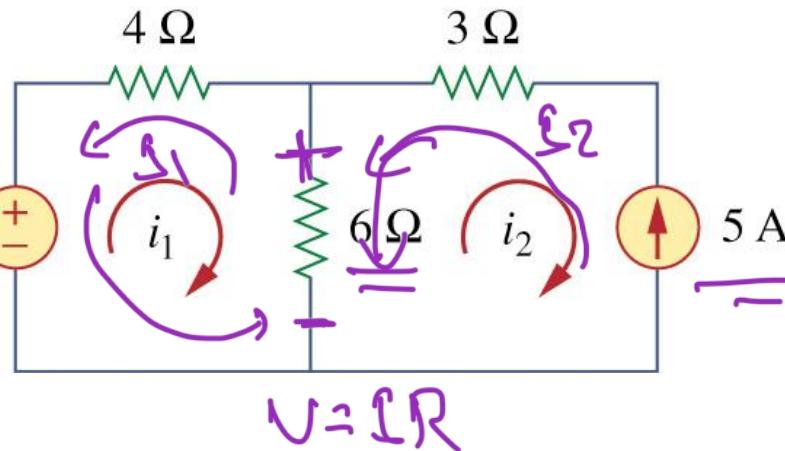
## Example 6

Use mesh analysis to find the voltage across the  $6\Omega$  resistor



For mesh 2:  $i_2 = -5A$

KVL at mesh 1:  $-10 + 4i_1 + 6(i_1 - i_2) = 0$   
 $-10 + 10i_1 - 6(-5) = 0$   
 $10i_1 = -20$

$i_1 = -2A$  ✓

The voltage across the  $6\Omega$  resistor =  $6(i_1 - i_2) = 6(-2 + 5) = 18V$

$V_{6\Omega} = 6(i_2 - i_1) = 5 - 2 = 3 \times 6 = 18V$

just like  
mesh 1

# Example 7

Find the mesh currents  $i_1$  and  $i_2$


**Solution:**

- Supermesh consists of two meshes, two equations are needed;
  - one equation is obtained using **KVL** and Ohm's law to the **supermesh**, and

$$-20 + 6i_1 + 14i_2 = 0$$

$$6i_1 + 14i_2 = 20 \quad (1)$$

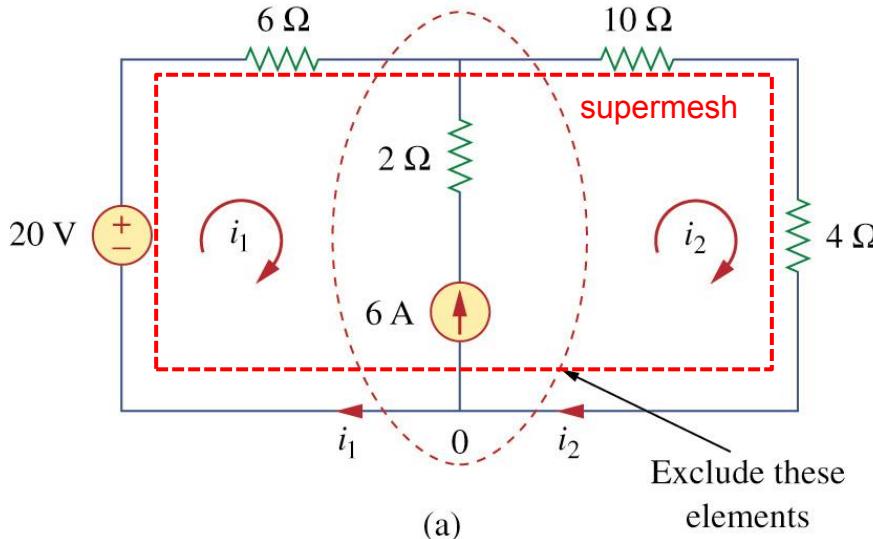- the other equation is obtained by **KCL** at the **current source**.



$$i_1 - i_2 = -6 \quad (2)$$

**form (2) in (1)**

$$6(i_2 - 6) + 14i_2 = 20$$

$$i_2 = 2.8A$$



**in (2)**

$$i_1 = -3.2A$$





## 2- Methods of Analysis- 3

---

- Nodal analysis
- Nodal analysis with voltage source
- Mesh analysis
- Mesh analysis with current source
- Nodal and mesh analyses by inspection
- Nodal versus mesh analysis


# Nodal and Mesh Analysis by Inspection

conductance

The analysis equations can be obtained by direct inspection

(a) For circuits with only resistors and independent current sources

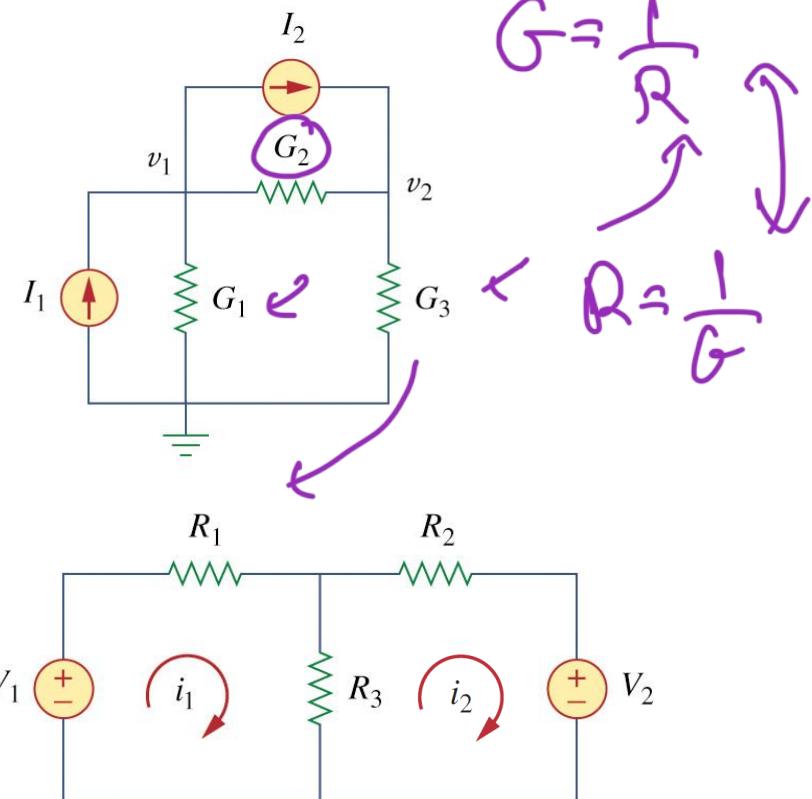(b) For planar circuits with only resistors and independent voltage sources



# Nodal by Inspection

$$\frac{V_1 - V_2}{S}$$

For circuits with **only resistors and independent current sources**

NOTE: For consistency, while writing each node equation, use KCL form of:

$$\sum \text{currents exiting the node} = 0 \quad \sum i_{\text{out}} = 0$$

Example: Write the nodal equations for the following circuit.

KCL at node 1:  $-I_1 + I_2 + G_1 v_1 + G_2(v_1 - v_2) = 0$

$$(G_1 + G_2)v_1 - G_2 v_2 = I_1 - I_2$$

KCL at node 2:  $-I_2 + G_3 v_1 + G_2(v_2 - v_1) = 0$

$$-G_2 v_1 + (G_2 + G_3)v_2 = I_2$$

Other nodes X - sum of Common G


Same nodes X sum of connected G

Matrix form:

$$\begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$



- 1) FIND A REFERENCE NODE WITH KNOWN VOLTAGE
- 2) ASSIGN VOLTAGES TO OTHER NODES
- 3) ASSIGN CONDUCTANCE TO EACH RESISTOR
- 4) FIND THE ELEMENTS OF THE CONDUCTANCE MATRIX
  - a) FOR EACH NODE  $G_{ii}$
  - b) BETWEEN EACH 2 NODES  $G_{ij} = G_{ji}$
- 5) SET UP THE NODE EQUATIONS IN MATRIX FORM
- 6) SOLVE THE NODE-VOLTAGE EQUATIONS
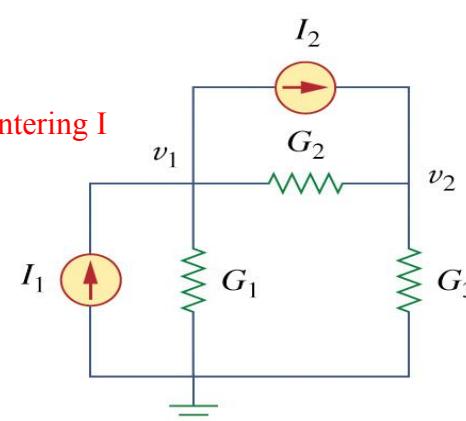
$$G = \frac{1}{R}$$


$$V = I R$$
$$I = V G$$

# Mesh by Inspection

For circuits with **only resistors and independent voltage sources**

**NOTE:** For consistency, while writing each mesh equation, use **same mesh current** to provide **reference for voltage polarity**

**Example:** Write the mesh equations for the following circuit.

KVL at mesh1:  $-V_1 + R_1 i_1 + R_3(i_1 - i_2) = 0$

$$(R_1 + R_3) i_1 - R_3 i_2 = V_1$$


KVL at mesh2:  $R_3(i_1 - i_2) - R_2 i_2 - V_2 = 0$

$$-R_3 i_1 + (R_2 + R_3) i_2 = -V_2$$

Other mesh X – sum of Common R

Same mesh X sum of loop R

Sum of V supporting the mesh current

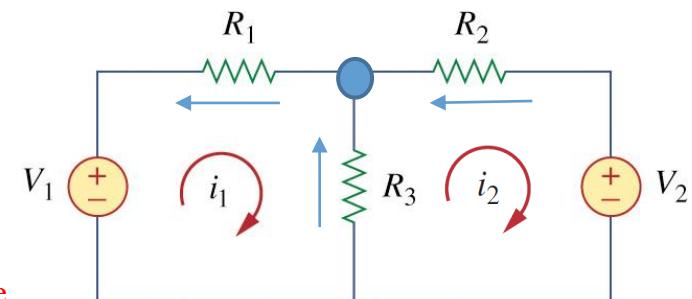

Matrix form:

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

$$i_c = i_1 - i_2$$

# Nodal Versus Mesh Analysis

- ❑ Both nodal and mesh analyses provide a systematic way of analyzing a complex network.
- ❑ The choice of the better method dictated by two factors.
  - ❑ First factor : nature of the particular network. The key is to select the method that results in the smaller number of equations.
  - ❑ Second factor : information required.

Diagram illustrating the relationship between Nodal and Mesh analysis:

Nodal       $\rightarrow$        $n$  node       $\rightarrow$  1 super node

mesh       $\rightarrow$        $z$  mesh

$\ddot{\text{C}}$

## 3- Circuit Theorems

Introduction and Linearity property

Superposition

Source transformations

**Thevenin's theorem**

Norton's theorem


Maximum power transfer



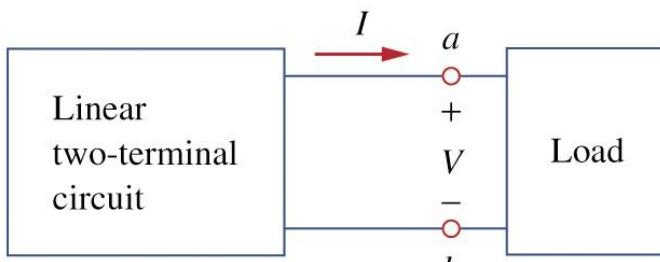
# Thevenin's Theorem

- Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$

Where;  $V_{Th}$  is the open circuit voltage at the terminals and  $R_{Th}$  is the input or equivalent resistance at the terminals when the independent source are turn off.



Original Circuit

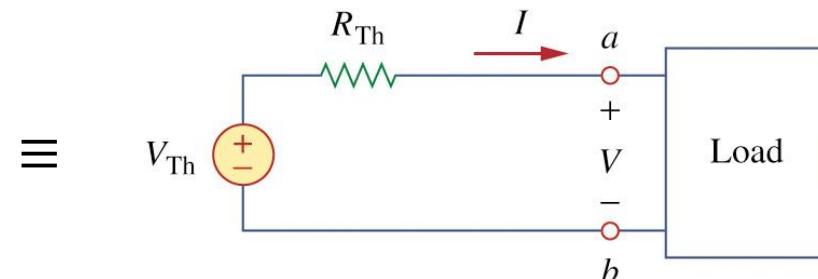


Thevenin equivalent circuit

# Thevenin's equivalent circuit


Simplified circuit

$$I_L = \frac{V_{\text{Th}}}{R_{\text{Th}} + R_L}$$
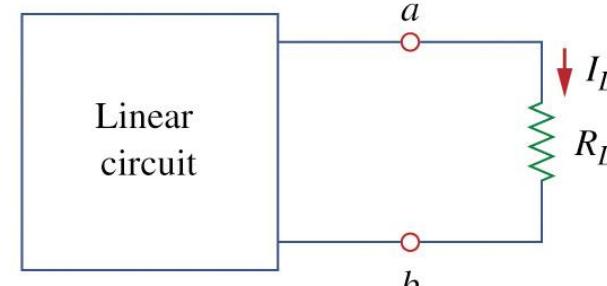
$$V_L = R_L I_L = \frac{R_L}{R_{\text{Th}} + R_L} V_{\text{Th}}$$



(a)

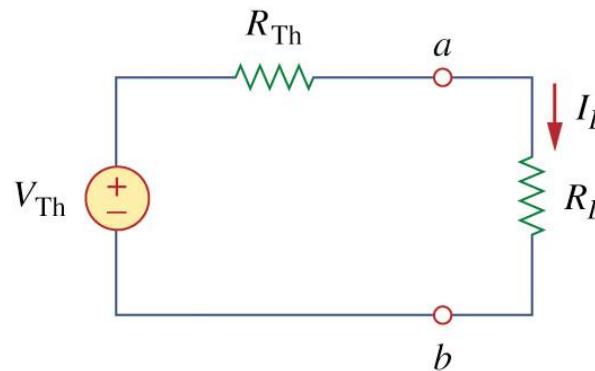


(b)

# How to Find Thevenin Equivalent Circuit


- First, **Open the circuit** (remove the load) at the **points** of interest **a-b**

1-  $V_{th}$ = Open circuit voltage (keep all sources intact)

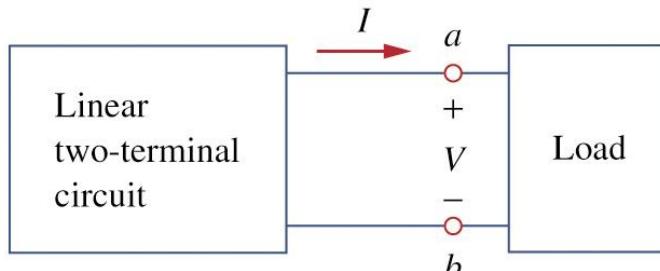2-  $R_{th}$ = Open circuit **equivalent resistance** appears at terminals **a-b** while all **independent sources=0** (voltage source=SC , current source=OC).



Original Circuit

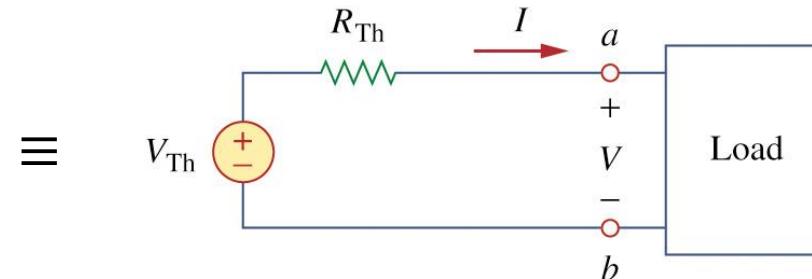


Thevenin equivalent circuit

# How to Find Thevenin Equivalent Circuit

- ❖ To find  $R_{th}$  we have to consider two cases

- 1- Case 1 (Circuit has No dependent sources): turn off all independent sources, then find the equivalent  $R_{th}$  using series/parallel combinations.
- 2- Case 2 (Circuit has dependent sources): turn off all independent sources and keep dependent sources intact (as superposition). In order to find equivalent  $R_{th}$ , apply  $v_o$  and find the produced current  $i_o$ . Then,  $R_{th} = \frac{v_o}{i_o}$

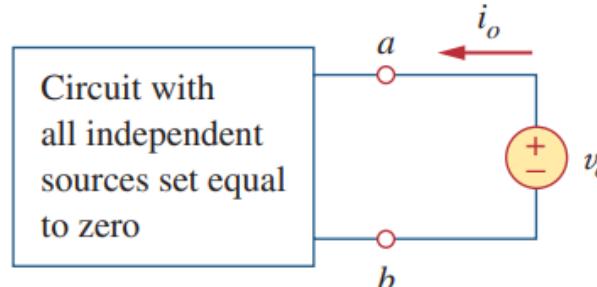For simplicity: put  $v_o = 1V$  and find the produced current  $i_o$ . Then,  $R_{th} = \frac{1}{i_o}$




$$R_{Th} = \frac{v_o}{i_o}$$
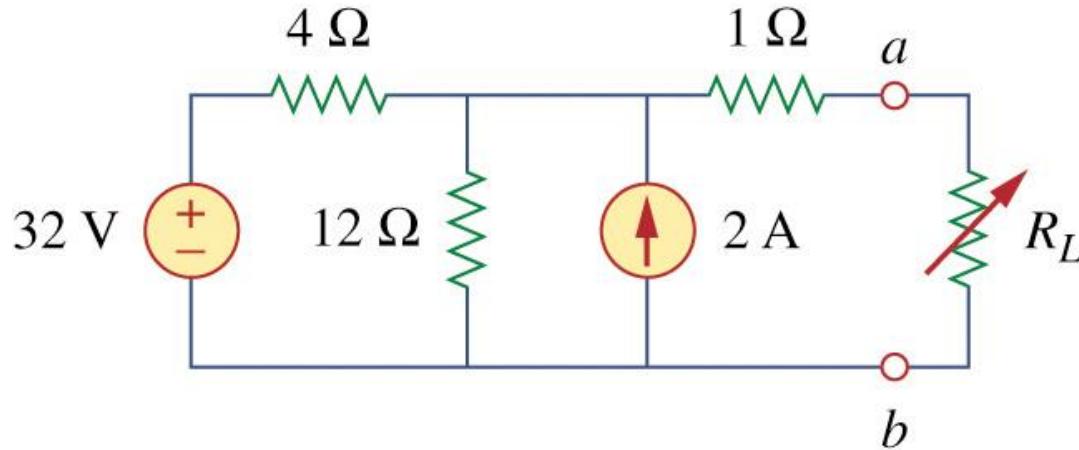
## Example 10

---

□ Find the Thevenin's equivalent of the circuit shown below, to the left of the terminals  $a-b$ . Then find the current through  $R_L = 6, 16, \text{ and } 36 \Omega$ .



# Example 10

Solution:

For  $R_{th}$ ,

Voltage source = SC,  
Current source = OC

$$R_{th} = 1 + 4//12 = 4\Omega$$

For  $V_{th}$ ,

Keep original circuit

$$V_{th} = V_{ac} \text{ (OC)}$$



$$V_{th} = 12(i_1 - i_2) = ?$$

Using mesh analysis


$$i_2 = -2A,$$

$$16i_1 - 12i_2 = 32,$$

$$i_1 = 0.5A,$$

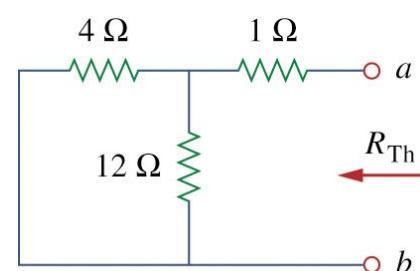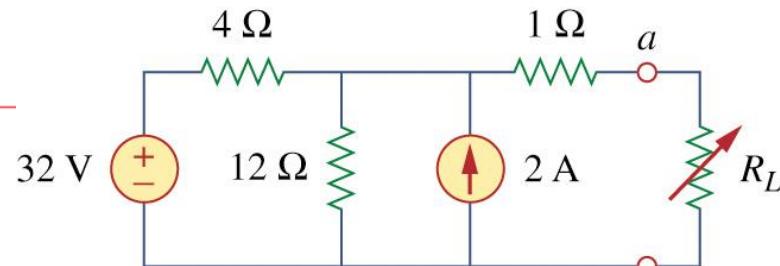

(a)

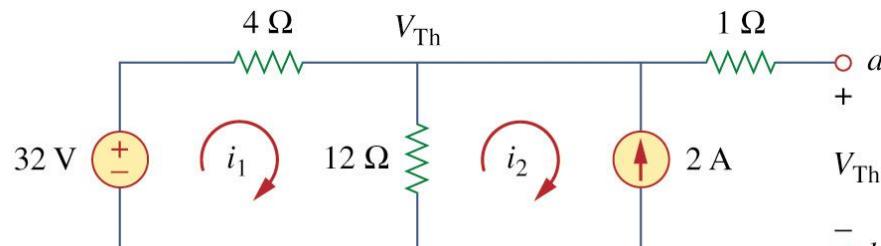

(b)

$$V_{th} = 12(i_1 - i_2) = 30V$$

## Example 10

Solution:


To get  $i_L$  :

$$i_L = \frac{V_{\text{Th}}}{R_{\text{Th}} + R_L} = \frac{30}{4 + R_L}$$

$$R_L = 6 \rightarrow I_L = 30/10 = 3\text{A}$$


$$R_L = 16 \rightarrow I_L = 30/20 = 1.5\text{A}$$
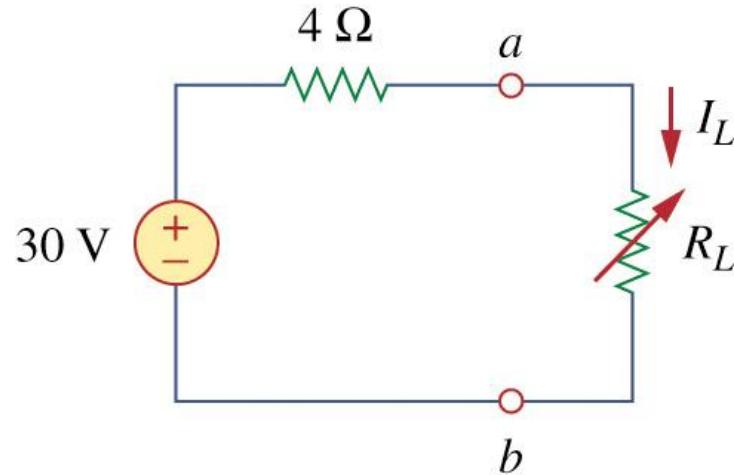
$$R_L = 36 \rightarrow I_L = 30/40 = 0.75\text{A}$$


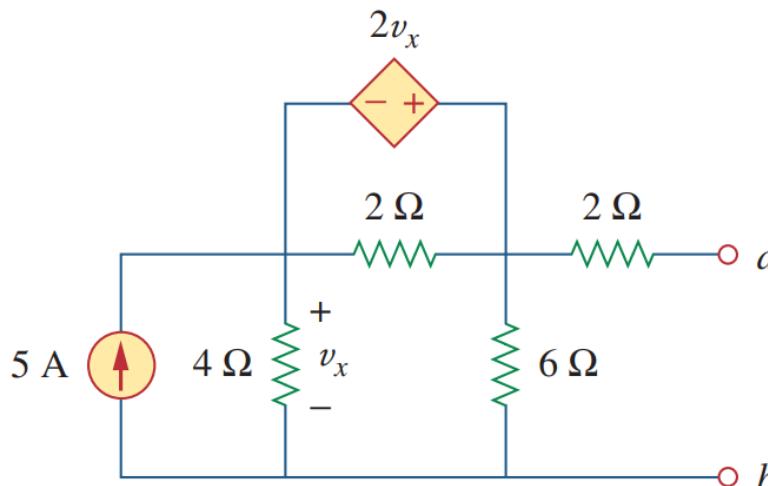
# Example 11


Find the Thevenin equivalent of the following circuit at terminals a-b.



Solution:



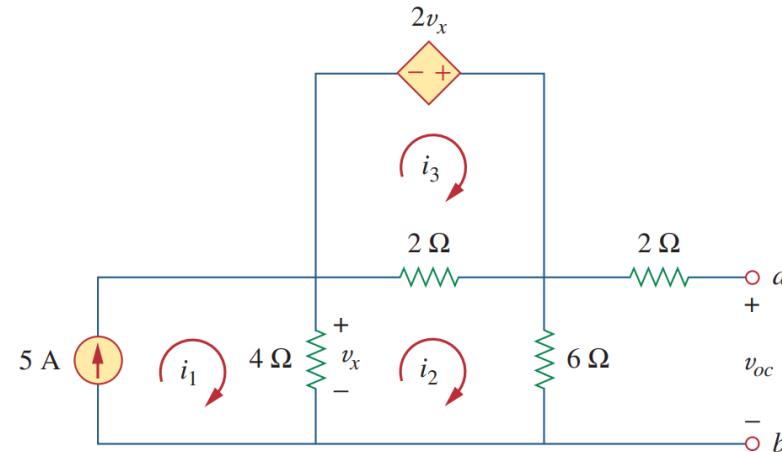1- For  $V_{th}$ , solve the following circuit to find  $v_{ab}$  ( $v_{oc}$ ).




(b)

# Example 11


Find the Thevenin equivalent of the following circuit at terminals a-b.

Solution:

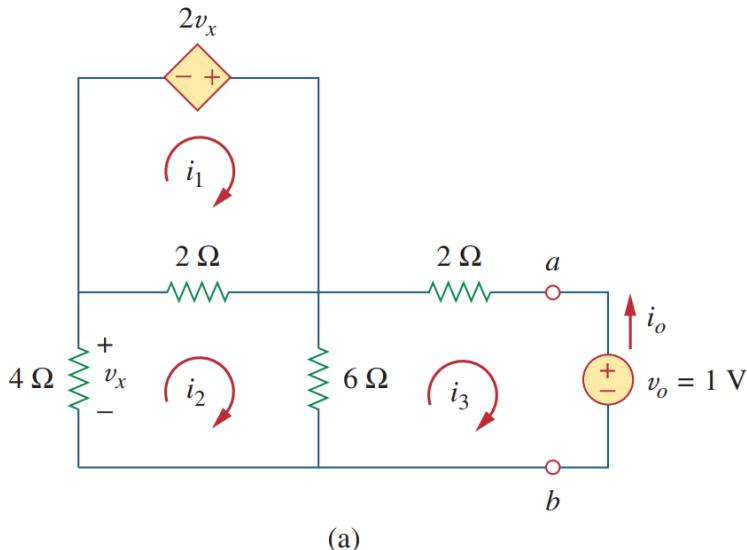2- For  $R_{th}$ , solve the following circuit to find  $i_o$ . Then,  $R_{th} = 1/i_o$



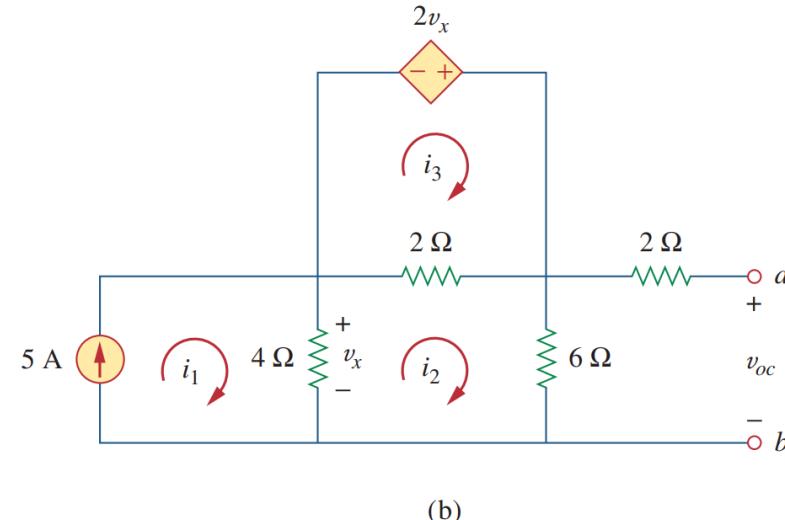1- For  $V_{th}$ , solve the following circuit to find  $v_{ab}$  ( $v_{oc}$ ).




# Example 11

Find the Thevenin equivalent of the following circuit at terminals a-b.

Solution:

1- For  $V_{th}$ ,

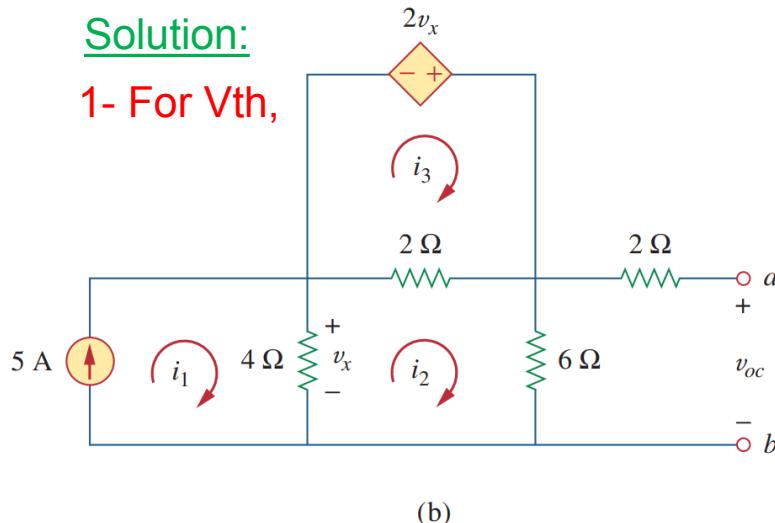

Applying mesh analysis:

$$\text{Mesh 1: } i_1 = 5$$

$$\text{Mesh 2: } 4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$$

$$\Rightarrow 12i_2 - 4i_1 - 2i_3 = 0$$

$$\text{Mesh 3: } -2v_x + 2(i_3 - i_2) = 0 \Rightarrow v_x = i_3 - i_2$$

$$\text{But, } 4(i_1 - i_2) = v_x \Rightarrow 4i_1 - 3i_2 - i_3 = 0$$

Solving these equations leads to  $i_2 = 10/3$ .

$$V_{th} = v_{oc} = 6i_2 = 20 \text{ V}$$


# Example 11

Find the Thevenin equivalent of the following circuit at terminals a-b.

Solution:

2- For  $R_{\text{th}}$ , Put  $v_o = 1V$

and kill any independent sources

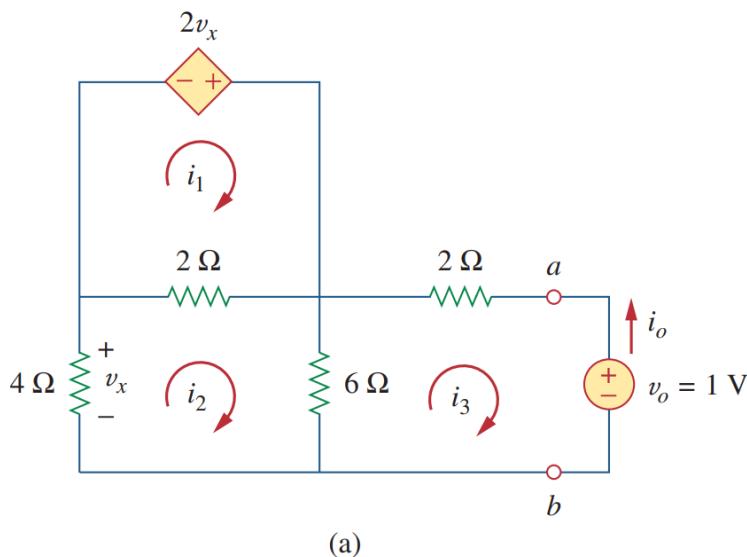

Applying mesh analysis:

$$\text{Mesh 1: } -2v_x + 2(i_1 - i_2) = 0 \quad \text{or} \quad v_x = i_1 - i_2$$

$$\text{But } -4i_2 = v_x = i_1 - i_2; \text{ hence, } \Rightarrow i_1 = -3i_2$$

$$\text{Mesh 2: } 4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$

$$\text{Mesh 3: } 6(i_3 - i_2) + 2i_3 + 1 = 0$$

Solving these equations gives


$$i_3 = -\frac{1}{6} \text{ A}$$

But  $i_o = -i_3 = 1/6 \text{ A}$ . Hence,

$$R_{\text{Th}} = \frac{1 \text{ V}}{i_o} = 6 \Omega$$
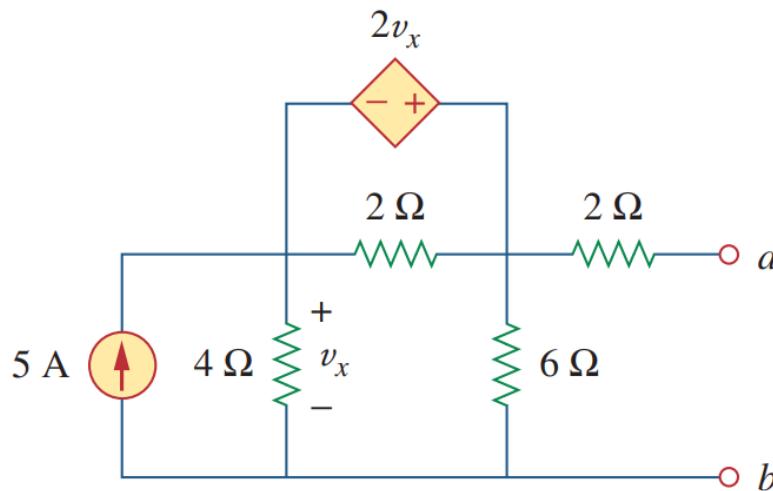
## Example 11


Find the Thevenin equivalent of the following circuit at terminals a-b.



Solution:



$\equiv$

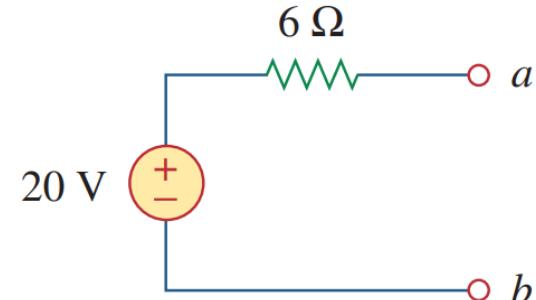

## 3- Circuit Theorems 2

Introduction and Linearity property

Superposition


Source transformations

Thevenin's theorem

Norton's theorem

Maximum power transfer

# Maximum Power Transfer

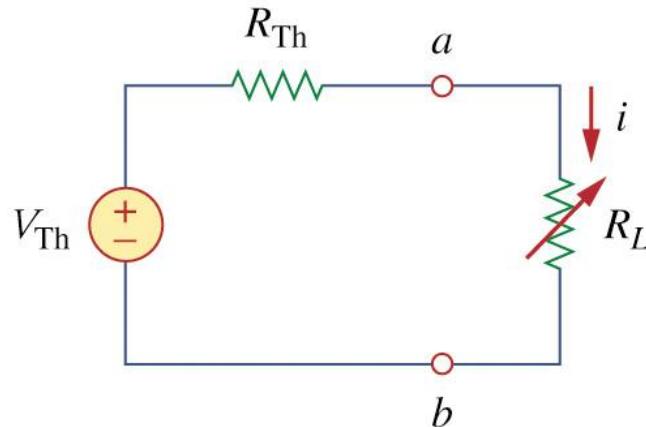


$$p = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

□ **Maximum power** is transferred to the **load** when the load resistance equals the Thevenin resistance as seen the load ( $R_L = R_{TH}$ ).

$$R_L = R_{TH}$$

$$p_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

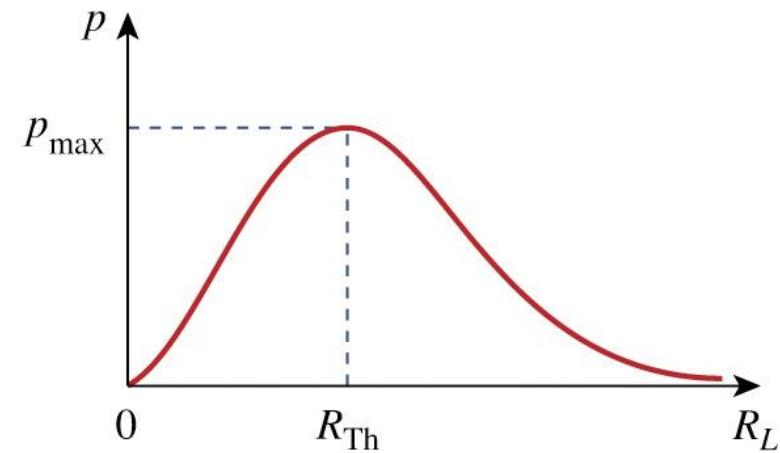

# Maximum Power Transfer: Mathematical Proof

$$\frac{dp}{dR_L} = V_{TH}^2 \left[ \frac{(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right]$$

$$= V_{TH}^2 \left[ \frac{(R_{TH} + R_L - 2R_L)}{(R_{TH} + R_L)^3} \right] = 0$$


$$0 = (R_{TH} + R_L - 2R_L) = (R_{TH} - R_L)$$

$$R_L = R_{TH}$$

$$p_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$
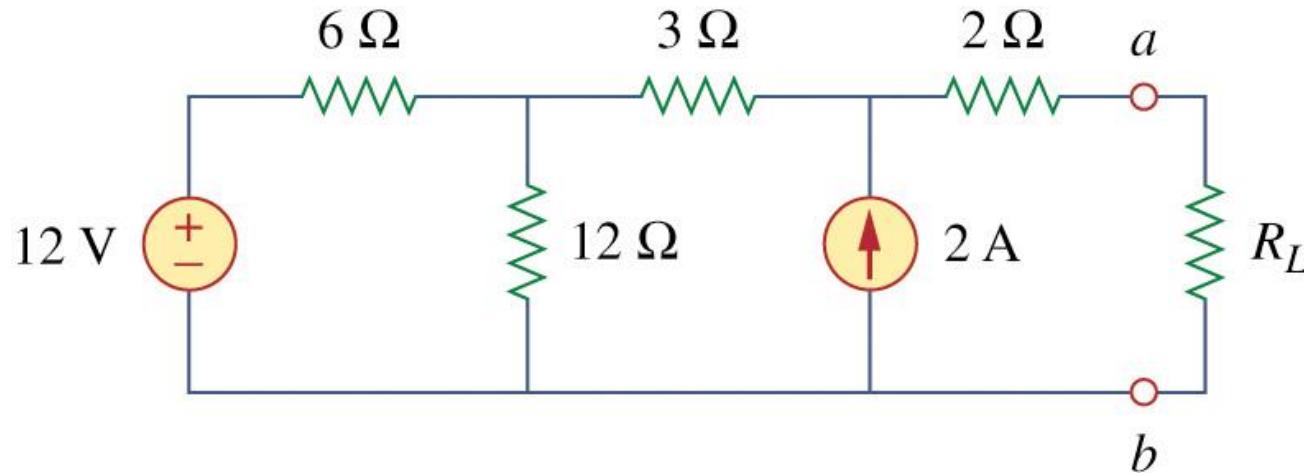
## Example 12

□ Find the value of  $R_L$  for maximum power transfer in the circuit of the following figure. Find the maximum power.




## Example 12

Solution:

1- To find  $R_{TH}$ ,
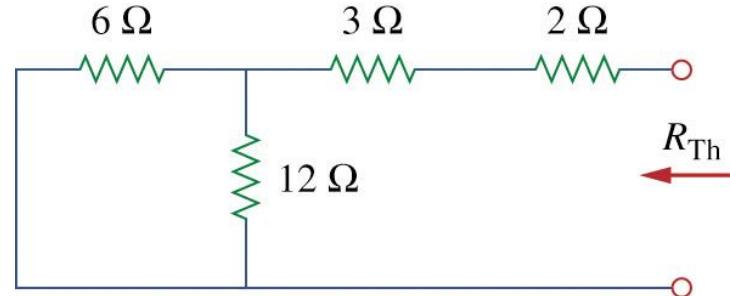
$$R_{TH} = 2 + 3 + 6\parallel 12 = 5 + \frac{6 \times 12}{18} = 9\Omega$$




2- To find  $V_{TH}$ ,

$$\text{Mesh: } -12 + 18i_1 - 12i_2, \quad i_2 = -2A$$

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{TH} = 0$$

$$\therefore V_{TH} = 22V$$

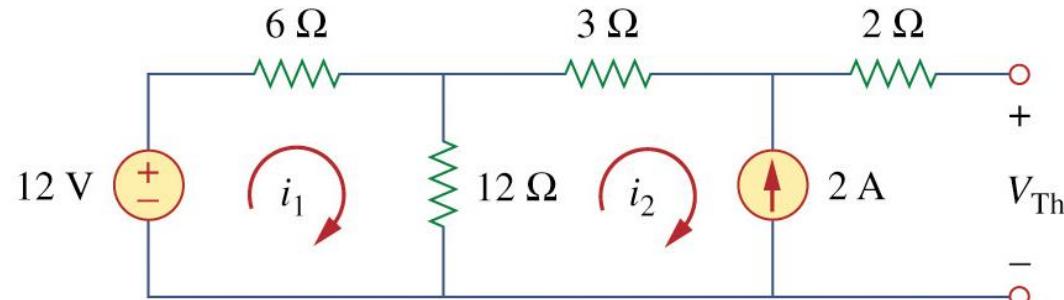

For maximum power:

$$R_L = R_{TH} = 9\Omega$$


$$P_{\max} = \frac{V_{TH}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44W$$



## 4- Capacitors and Inductors




# Summary of Capacitors

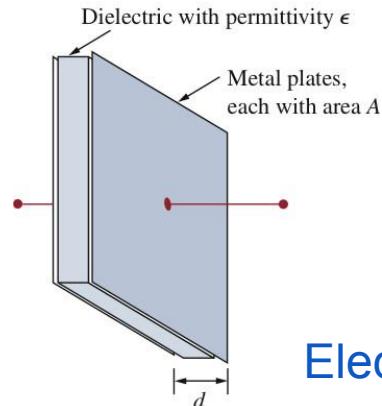

## Physical structure

$$C = \frac{\epsilon A}{d}$$

## Electrical Characteristics

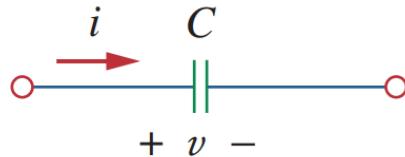


$$q = Cv$$

$$i = C \frac{dv}{dt}$$
 O.C. in DC

## Energy Stored


$$w = \frac{1}{2} C v^2$$

## Parallel Capacitors

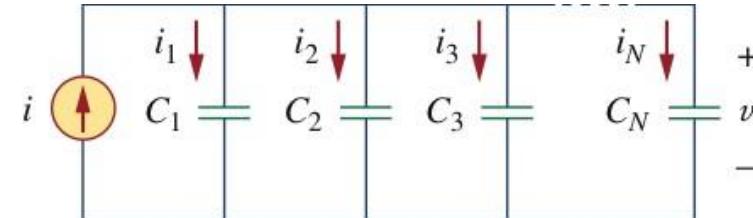


$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

## Series Capacitors

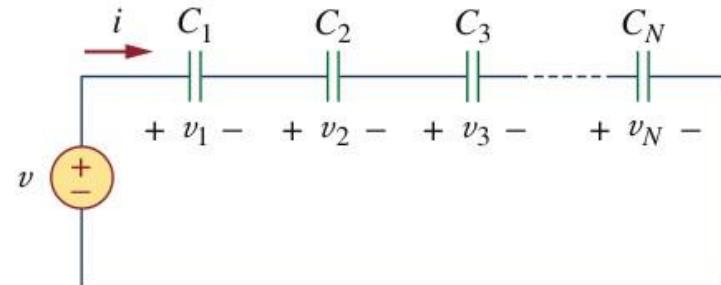


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

# Summary of Inductors

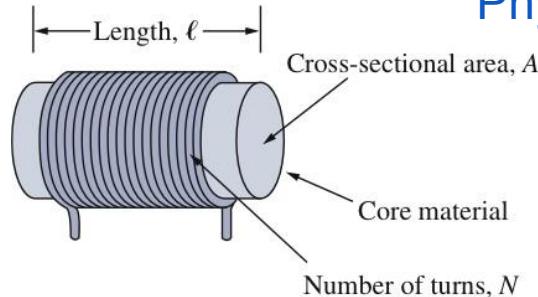

## Physical structure

$$L = \frac{N^2 \mu A}{l}$$

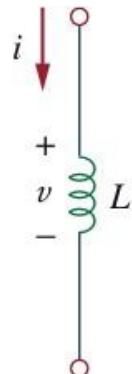


## Electrical Characteristics

$$v = L \frac{di}{dt}$$
 S.C. in DC

## Energy Stored


$$w(t) = \frac{1}{2} L i^2(t)$$

## Series Inductors

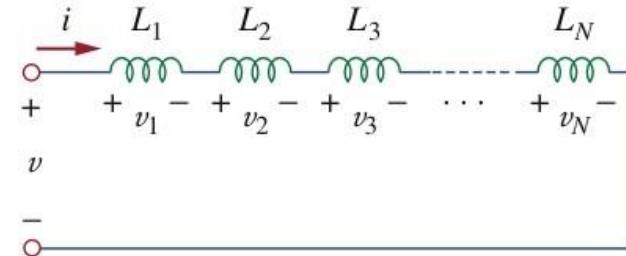

$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$

## Parallel Inductors

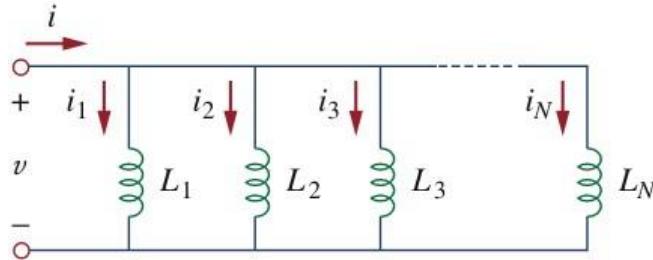


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

# Remember: Important characteristics of basic elements

Relation	Resistor ( $R$ )	Capacitor ( $C$ )	Inductor ( $L$ )
$v$ - $i$ :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
$i$ - $v$ :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
$p$ or $w$ :	$p = i^2R = \frac{v^2}{R}$	$w = \frac{1}{2} Cv^2$	$w = \frac{1}{2} Li^2$
Series:	$R_{\text{eq}} = R_1 + R_2$	$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{\text{eq}} = L_1 + L_2$
Parallel:	$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{\text{eq}} = C_1 + C_2$	$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	$v$	$i$


# Summary of Transient-Response for RC and RL circuits

## Step Response (Forced Response):

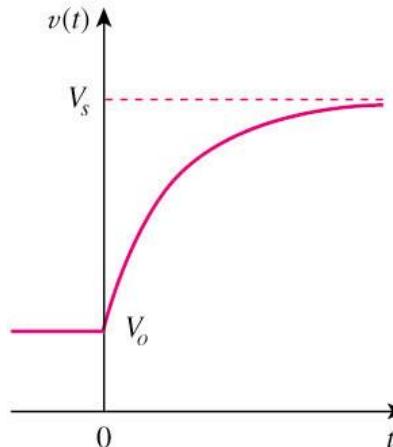

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$
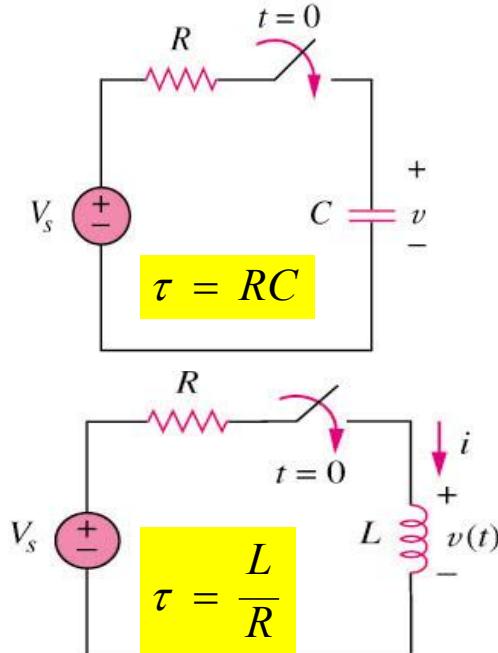
$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$



Three steps to solve any transient-response problem:

1. The initial Values.
2. The final value (after long time, C acts as OC and L acts as SC).
3. The time constant  $\tau$ .

Note: Natural Response (source free) is a special case where final value = 0



End of Lecture



Questions?