

Chapter 1

Basic components and electric
circuits

Objectives

To be familiarized with

- Basic electrical quantities and associated units
- Current direction and voltage polarity
- The passive sign convention for calculating power
- Ideal voltage and current sources
- Dependent sources
- Resistance and Ohm's law

Units and scales



Six basic units

Quantity	Basic unit	Symbol
طول Length	meter	m
الكتلة Mass	kilogram	Kg
الوقت Time	second	s
التيار Electric current	ampere	A
الحرارة Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

التيار
الحرارة

شدة الضوء

Units and scales

- The derived units commonly used in electric circuit theory

Quantity	Unit	Symbol
electric charge	coulomb	C
electric potential	volt	V
resistance	ohm	Ω
conductance	siemens	S
inductance	henry	H
capacitance	farad	F
frequency	hertz	Hz
force	newton	N
energy, work	joule	J
power	watt	W
magnetic flux	weber	Wb
magnetic flux density	tesla	T

Factor	Prefix	Symbol
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p

Decimal multiples and submultiples of SI units

3.6 Ω

3.6

2k $\Omega \Rightarrow 2 \times 10^3 \Omega$
7M Ω

X
R
ind
C
cap


}

الشحنات

Charges

- Charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C).
- The charge **e** on one electron is **negative** and equal in magnitude to $1.602 \times 10^{-19} \text{ C}$ which is called as electronic charge.
- Q for constant charge and q(t) if time variant.
- Coulomb is a large unit and in 1C of charge there are $1/(1.602 \times 10^{-19}) = 6.24 \times 10^{18}$ electrons.
- The charges that occur in nature are **integral multiples** of the electronic charge
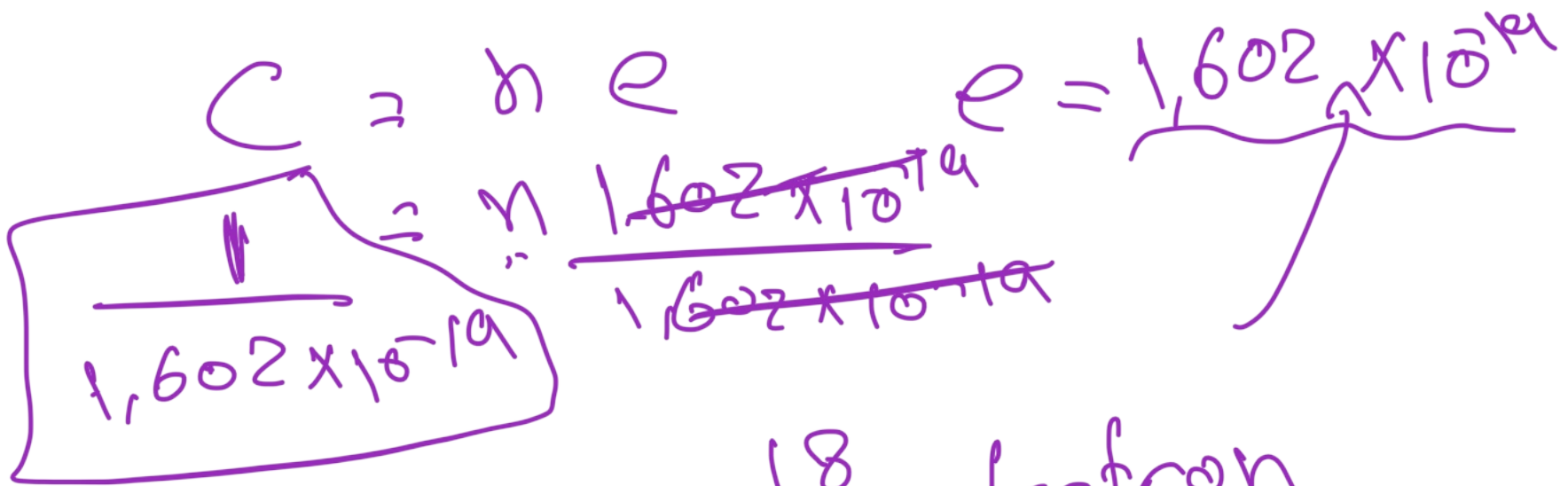
$$\text{Charge} = \text{Number of electron} \times \text{charge of electron}$$



$n = 6,24 \times 10^{18}$ electron

electron = $-1,602 \times 10^{-19}$
 proton = $+1,602 \times 10^{-19}$



example


- How much charge represented by 4600 electrons?
- **Solution:** each electron has -1.602×10^{-19} C. hence 4600 electrons will have -1.602×10^{-19} C/electron \times 4600 electrons =


$$-7.369 \times 10^{-16} \text{ C}$$

$$Q = ne \Rightarrow \underline{4600 \times 1.602 \times 10^{-19}}$$


Current

- Is the time rate of change of charge measured in ampere(A)
- Electric current $i = dq/dt$. The unit of ampere can be derived as $1 A = 1 C/s$.
- A direct current (dc) is a current that remains constant with time.
- An alternating current (ac) is a current that varies sinusoidally with time. (reverse direction)

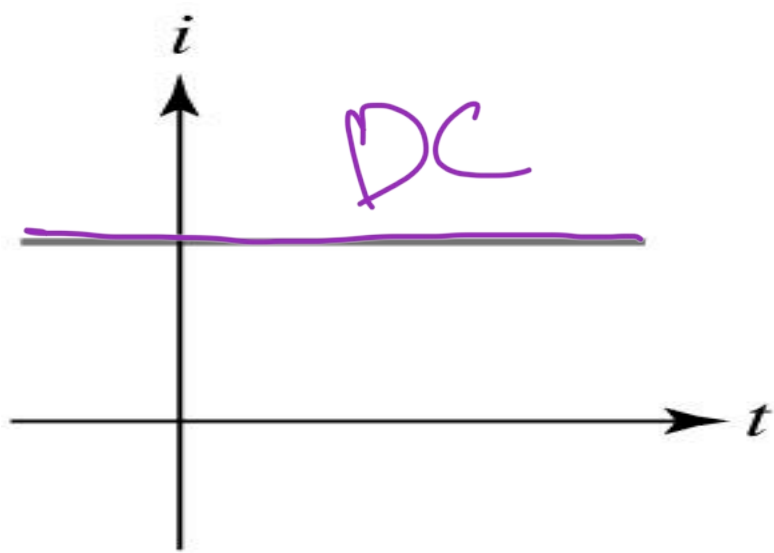

$$i = \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$




(a)

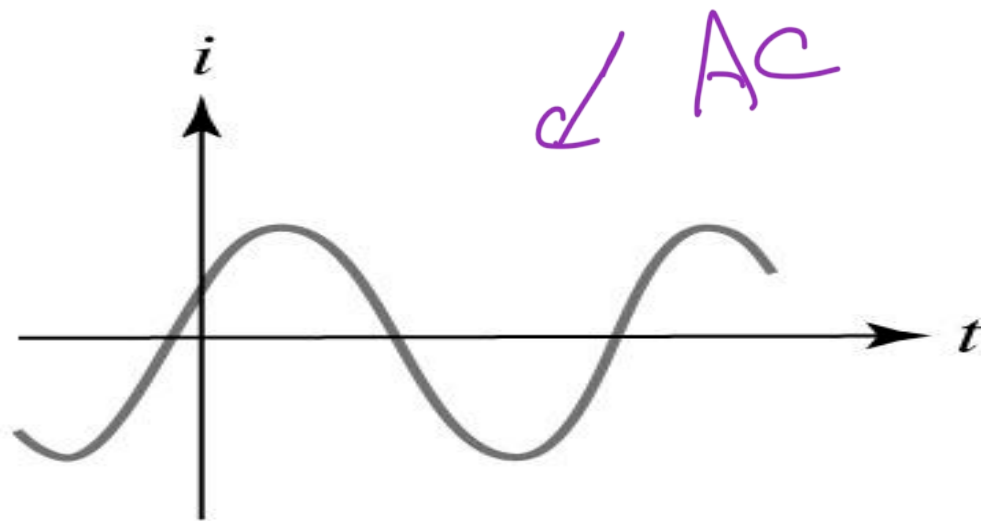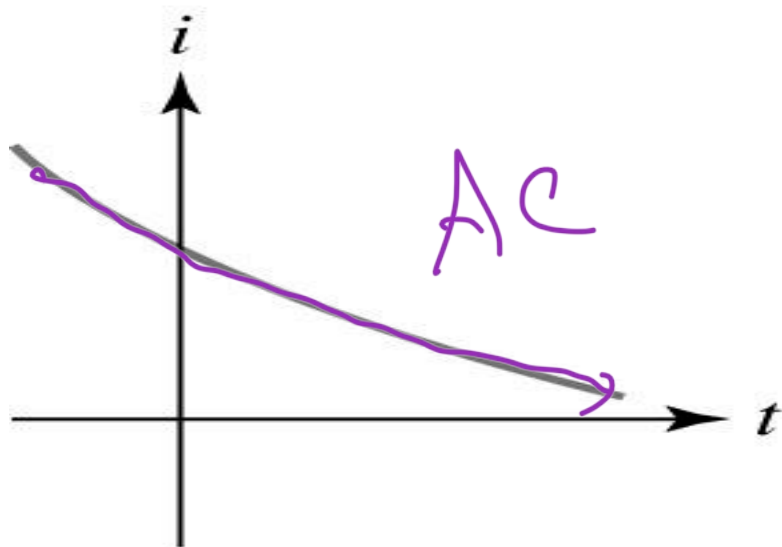

(b)




(c)

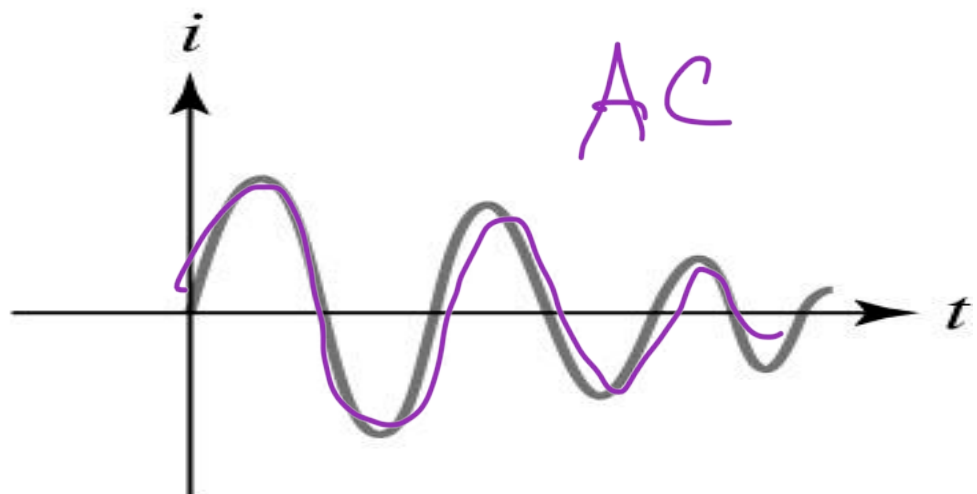

(d)

Current

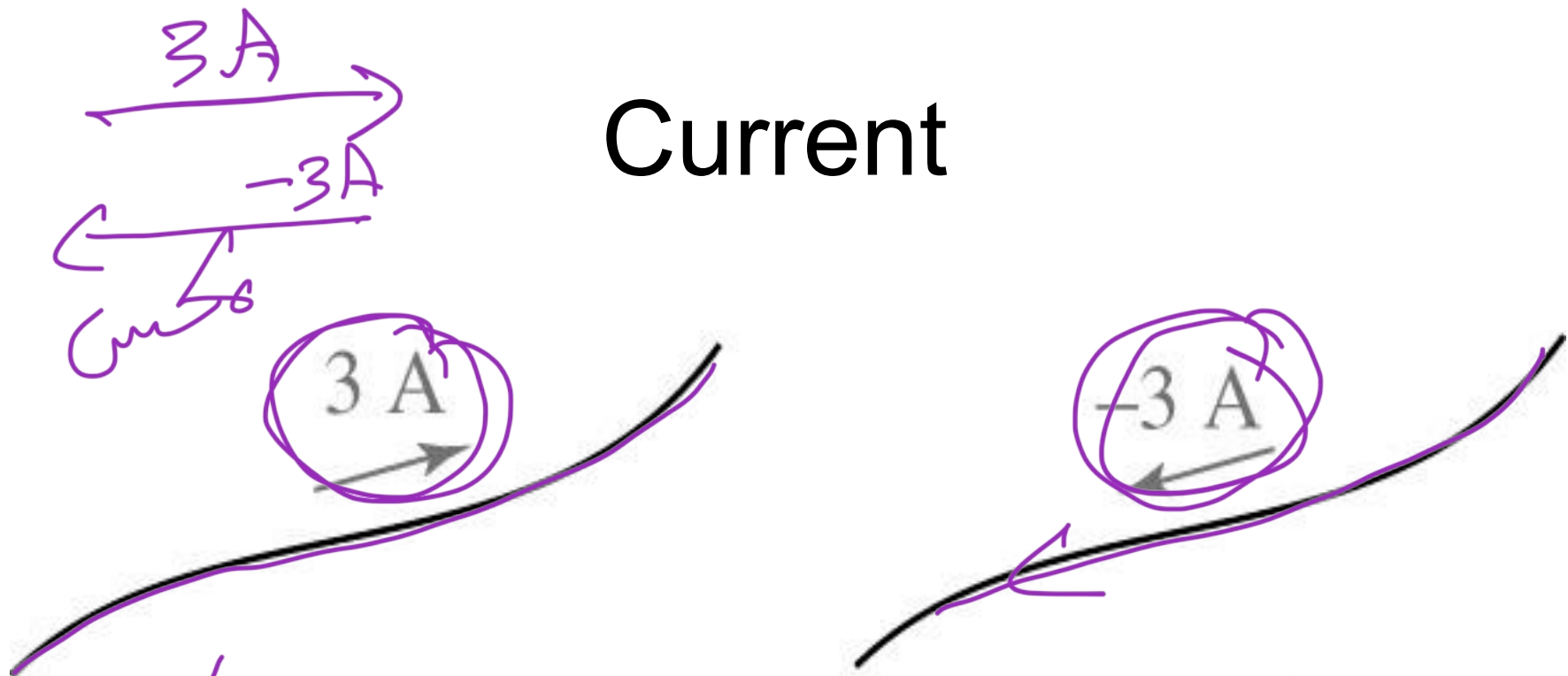

لما نطلع التيار سالبين \Rightarrow معناه منه

(a)

الاتجاه \ominus الختر .

(b)

الاتجاه \ominus الختر .

Example


Q. The charge entering a certain element is shown.
Find the current at $t = 1$ ms.

Solution:

Slope of the line ($t = 0$ ms to $t = 2$ ms):

$$\text{slope} = \frac{\Delta q}{\Delta t} = \frac{30 \text{ mC} - 0 \text{ mC}}{2 \text{ ms} - 0 \text{ ms}} = \frac{30 \cancel{\text{mC}}}{2 \cancel{\text{ms}}} = 15 \text{ mA}.$$

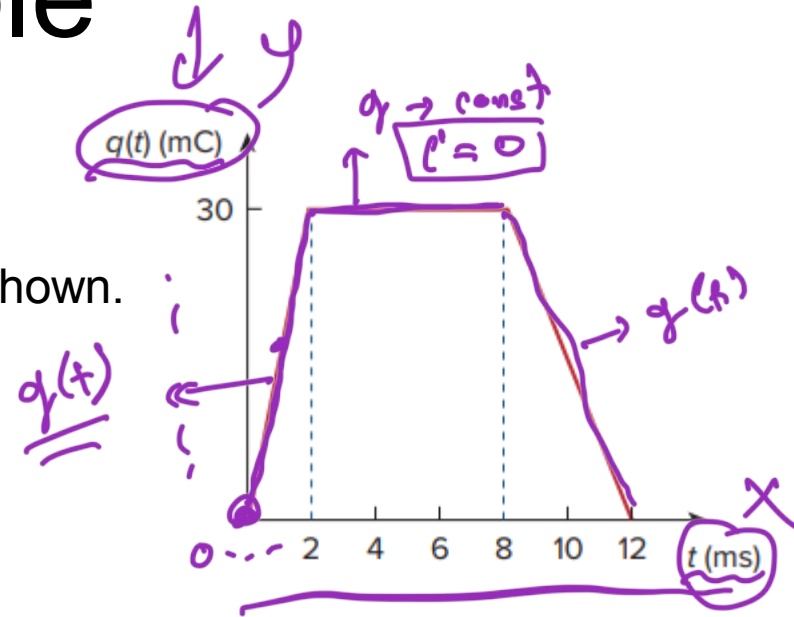Since $t = 1$ ms lies within the linear region ($t = 0$ to $t = 2$ ms),
the current $i(t)$ is equal to the slope of this line:
Thus $i(1 \text{ ms}) = 15 \text{ mA}$.



$$(x, y)$$
$$m = 10^{-3}$$
$$m \text{ A}$$

$$\Rightarrow q(t) - q_1 = m(t - t_1)$$

$$\Rightarrow m = \frac{\Delta q}{\Delta t} = \frac{q_2 - q_1}{t_2 - t_1}$$


$$m = \frac{30 - 0}{2 - 0} = \frac{30}{2}$$

$$m = 15A$$

$$q(t) - 0 = 15(t - 0)$$

$$1(t) = \frac{dq}{dt}$$

$$= 15A \checkmark$$

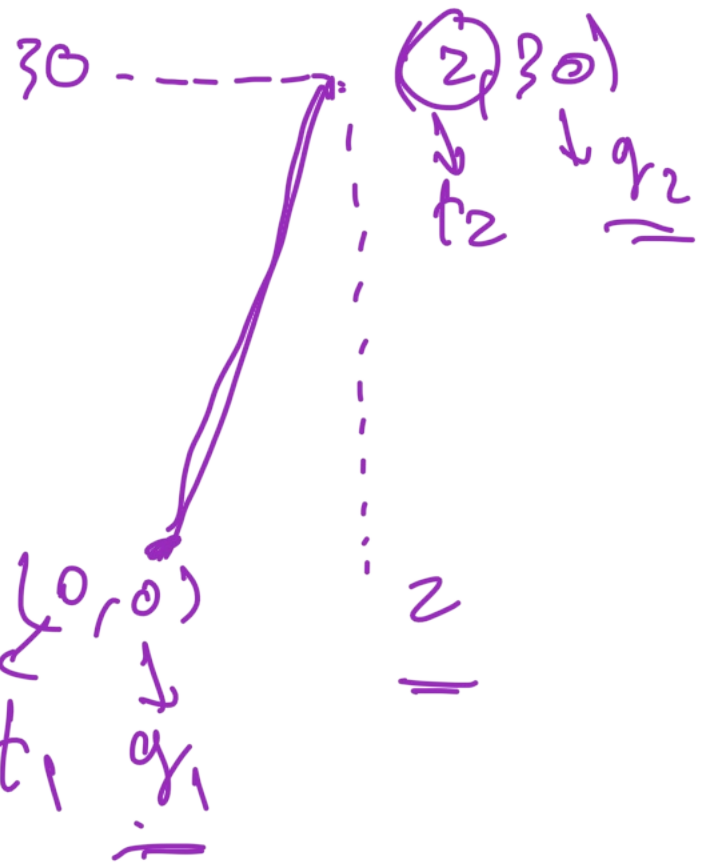


$$\Rightarrow q(t) = \underline{15t}$$

Voltage

- Voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).

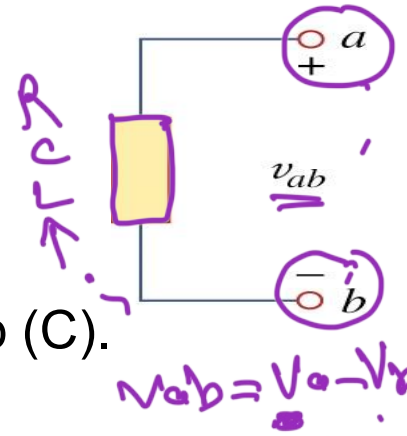- Mathematically, $v_{ab} = \frac{dw}{dq}$ (volt)
 - w is energy in joules (J) and q is charge in coulomb (C).



- Electric voltage, v_{ab} , is always across the circuit element or between two points in a circuit.

- $v_{ab} > 0$ means the potential of a is higher than potential of b.
- $v_{ab} < 0$ means the potential of a is lower than potential of b.

1.5 Power


- Power is the time rate of expending or absorbing energy, measured in watts (W).

- Mathematical expression: $p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$


Passive sign convention:

$$p = vi$$

الجاه التيار

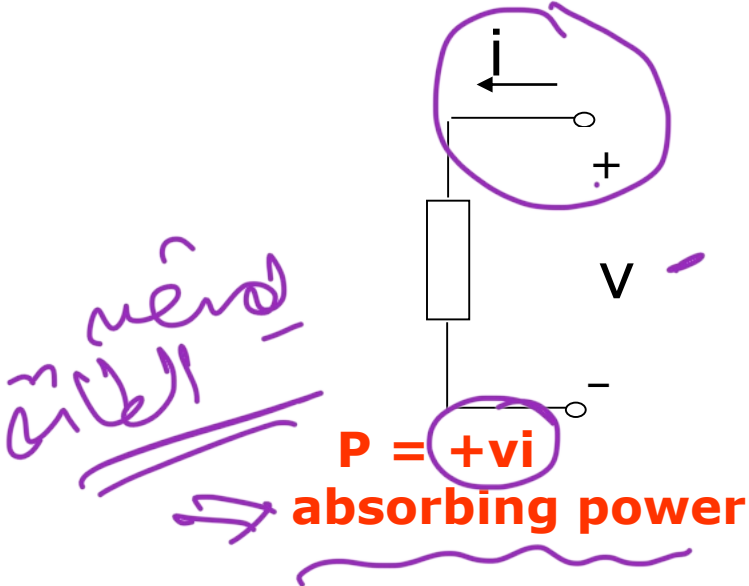

تولد الطاقة

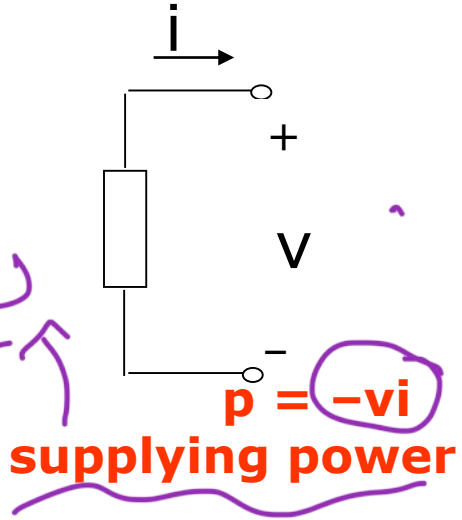


+power absorbed = - power supplied

التيار اذا دخل من \rightarrow $\Rightarrow P = +iV$

التيار اذا دخل من \leftarrow $\Rightarrow P = -iV$



$$P = iV$$

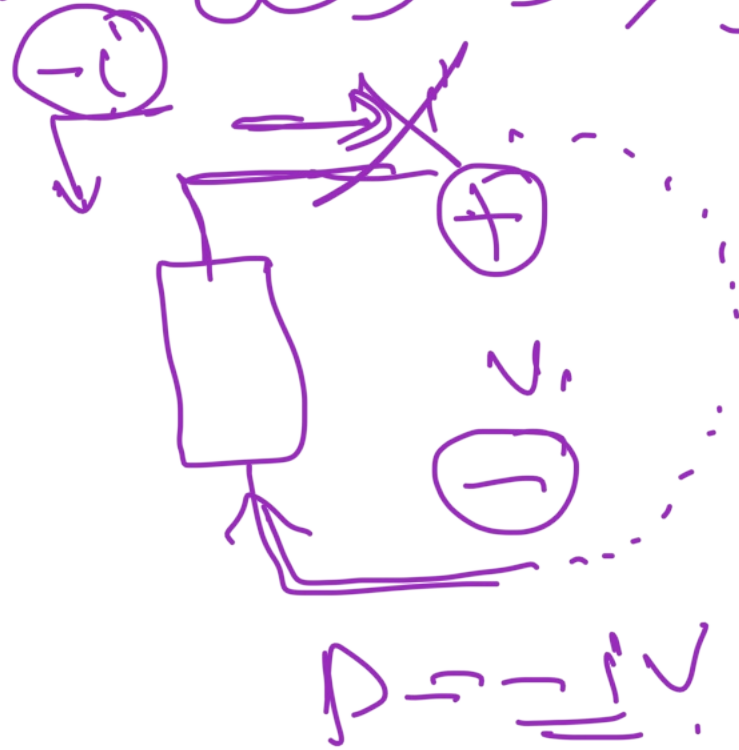


$$P = -iV$$

$P \rightarrow W$

examples

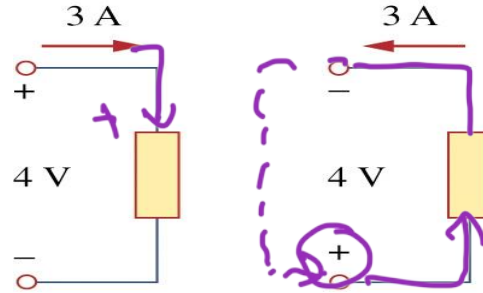- (a) $p = 4 \times 3 = 12W$
- (b) $p = 4 \times 3 = 12W$




(a)


(b)

Both are absorbing power as + current enters + terminal

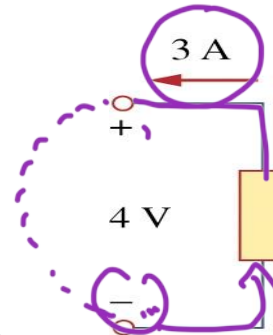- (a) $p = -4 \times 3 = -12W$
- (b) $p = -4 \times 3 = -12W$
- Both are supplying power of 12w
- Absorbing power of +12W is equivalent to a supplying power of -12W.



(a)

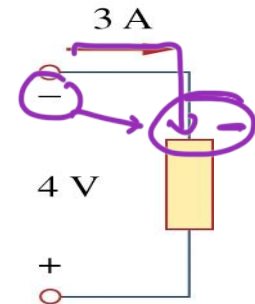

(b)

defining


Circuit elements

توضيرة

تأثير


- Two types passive and active elements
- Active is capable of generating energy while a passive element is not.
- Passive elements: resistors, capacitors and inductors.
- Active elements: generators, batteries and amplifiers

مولد

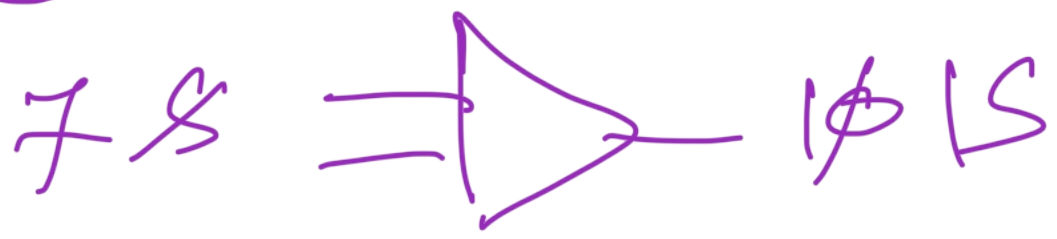


Voltage and current sources

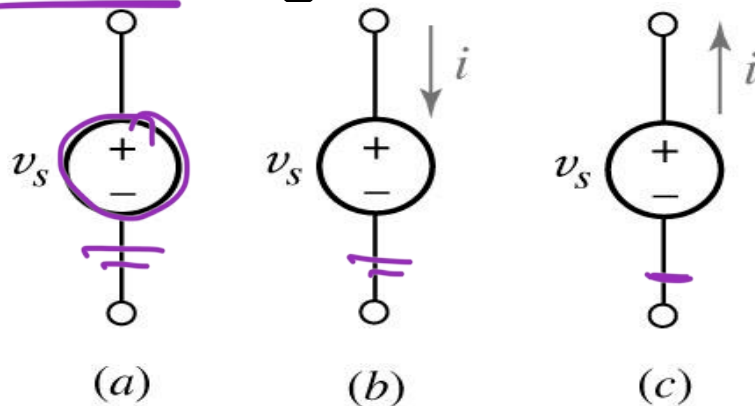- Ideal independent sources: voltage is completely independent of the current or the current is completely independent of the voltage.



Independent voltage source

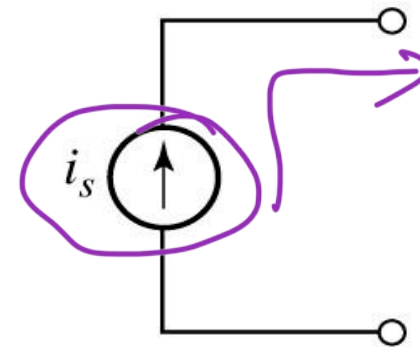


Independent current source


Batteries and generators may be regarded as approximations to ideal voltage sources.

Voltage and current sources

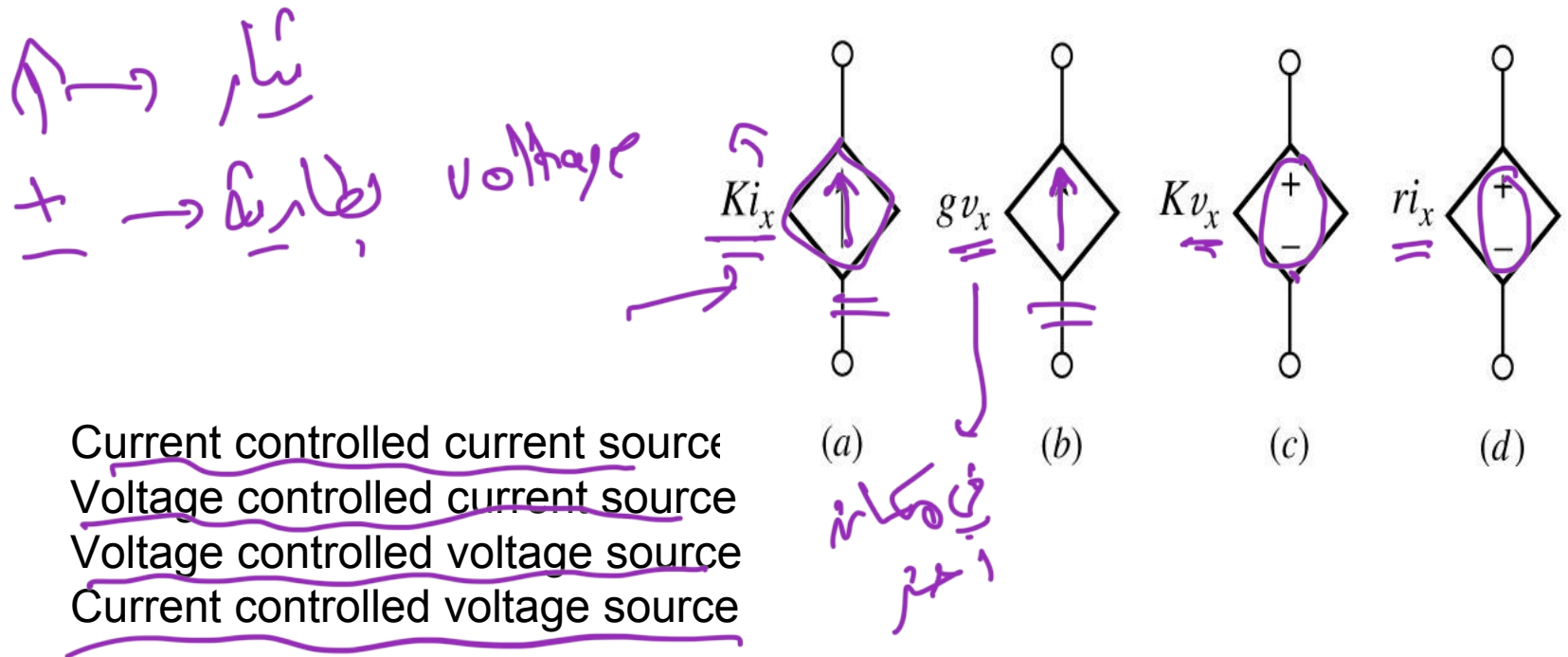
- Ideal dependent (or controlled) sources: the source quantity is controlled by another voltage or current. It is mainly used in modeling electronic devices such as transistor.



Dependent sources

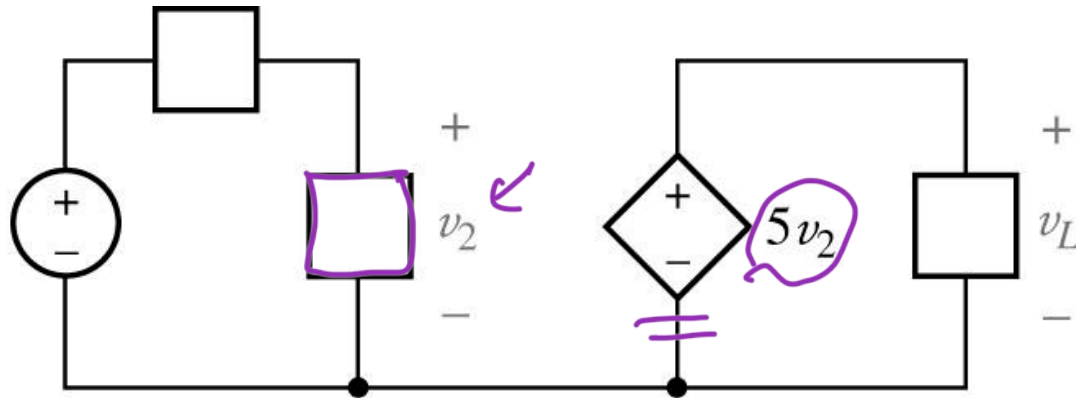

(a)

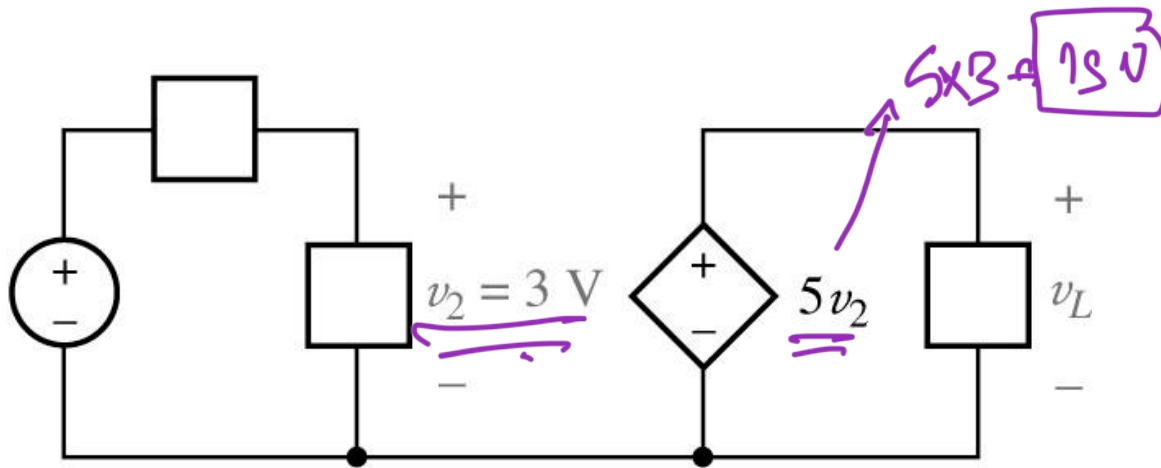


(b)


Networks and circuits

- The interconnection of two or more simple elements forms an electrical network
- If the network contains at least one closed path, it is also an electric circuit. Note that every circuit is a network but not all networks are circuits.

101

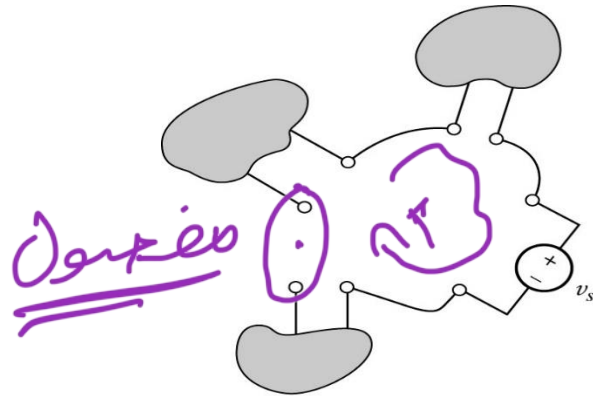

(a) A network that is not a circuit

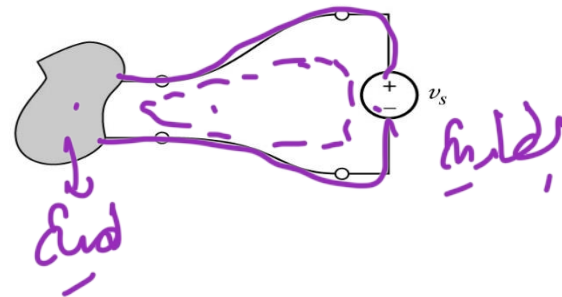

(b) a network that is a circuit

Resistance

القدرة على مقاومة التيار الكهربائي

القدرة على مقاومة التيار الكهربائي
من مرور التيار الكهربائي
المقاومة


- Resistance (R) is the ability to resist current
- Resistivity (ρ) is the measure of a material's natural resistance to current flow. For a wire with length ℓ , cross-section area A then

$$R = \rho \frac{\ell}{A}$$

طول

Resistance unit is Ohm or Ω

Resistivity unit is Ohm.meter or Ωm

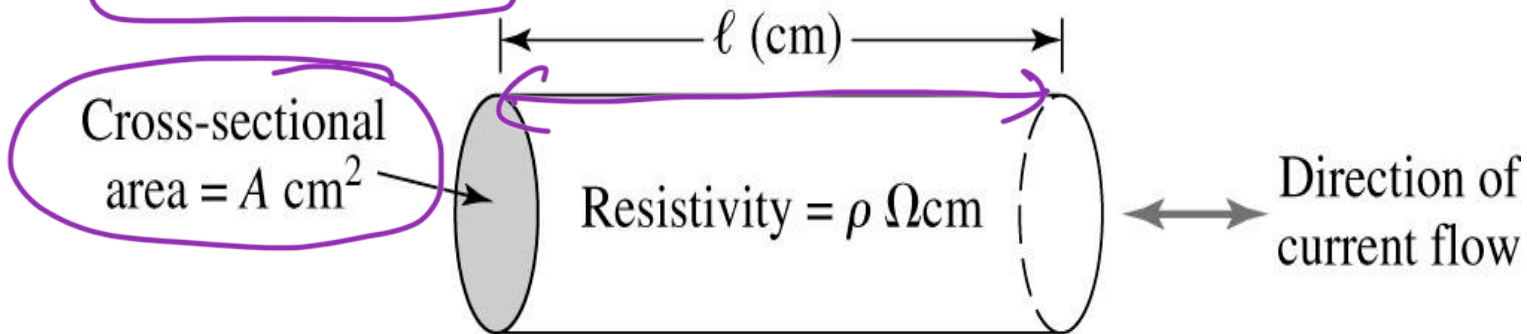

Resistivities of common materials

$10^{-8} = 0,00000001$

TABLE 2.1

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

Handwritten notes:
 - A bracket groups Silver, Copper, Aluminum, and Gold with the word "wires".
 - A bracket groups Carbon, Germanium, and Silicon with the word "chips".
 - A bracket groups Paper, Mica, Glass, and Teflon with the word "discs".

Wire gauge

TABLE 2.4 Some Common Wire Gauges and the Resistance of (Soft) Solid Copper Wire.*

Conductor Size (AWG)	Cross-Sectional Area (mm ²)	Ohms per 1000 ft at 20°C
28	0.0804	65.3
24	0.205	25.7
22	0.324	16.2
18	0.823	6.39
14	2.08	2.52
12	3.31	1.59
6	13.3	0.3952
4	21.1	0.2485
2	33.6	0.1563

* C. B. Rawlins, et al., *Standard Handbook for Electrical Engineering*, 13th ed., D. G. Fink and H. W. Beaty, eds. New York: McGraw-Hill, 1993, p. 4-47.

AWG: American wire gauge which is a standard system of specifying wire size


أهم واحد
بالمعادلة كلها

Ohm's Law

- Ohm's law states that the voltage across a resistor is directly proportional to the current i flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

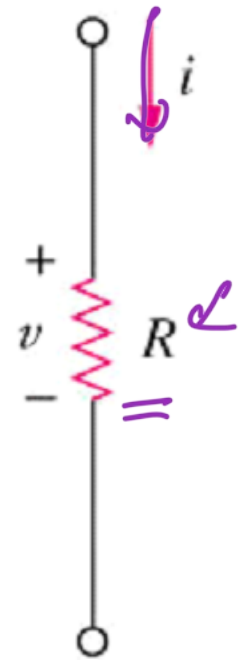- Two extreme possible values of R : 0 (**zero**) and ∞ (**infinite**) are related with two basic circuit concepts: **short circuit** and **open circuit**.




$R = \infty$
open circuit

$R = 0$
short circuit



Resistors

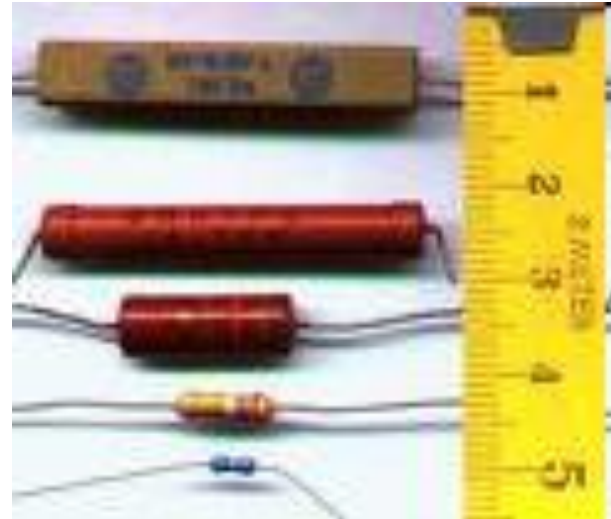


Ohm's law

$$V = IR$$

$$R = \frac{\Delta V}{\Delta I}$$

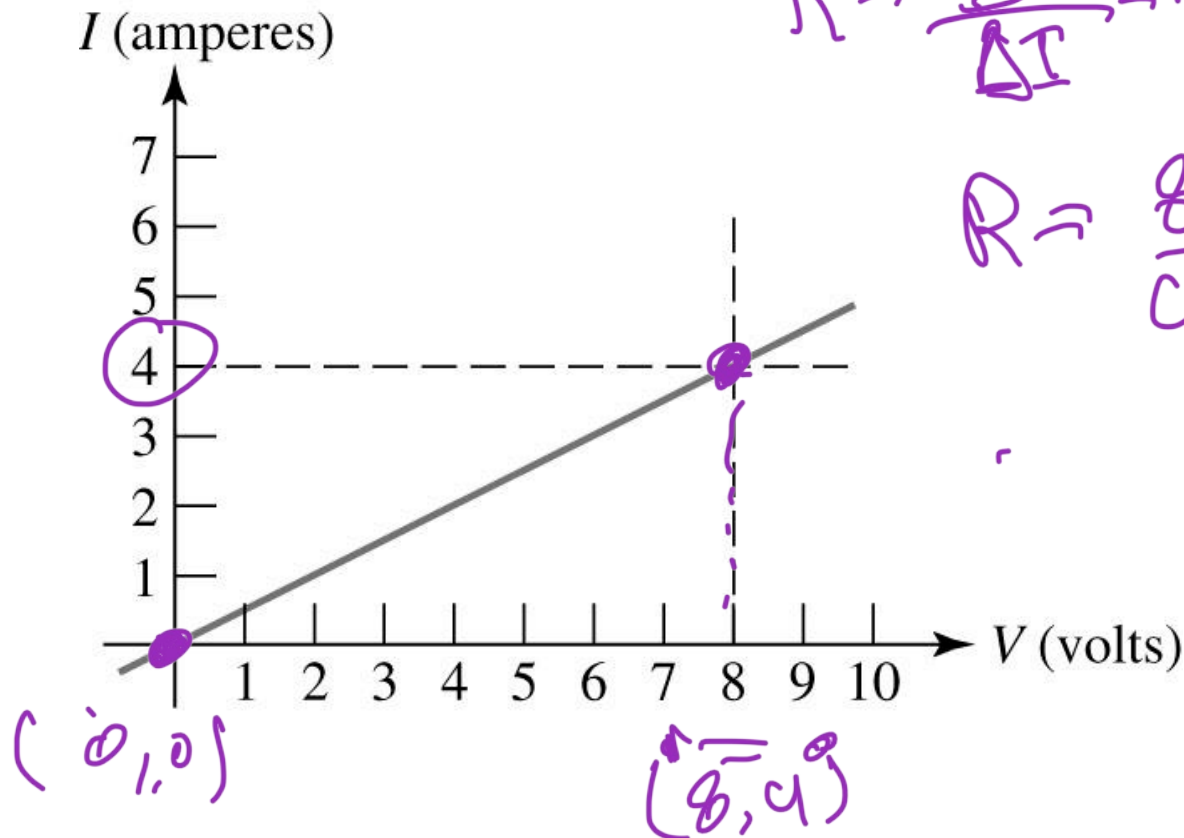- Current and voltage relationship for 2Ω linear resistor



$$R = \frac{\Delta V}{\Delta I} = m = \frac{V_2 - V_1}{I_2 - I_1}$$

$$R = \frac{8 - 0}{4 - 0} = \frac{8}{4} = 2 \Omega$$

قوله

Ohm's law

$$R = \frac{V}{I}$$

- **Conductance** is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in mhos or siemens.

$$G = \frac{1}{R} = \frac{i}{v}$$



- The unit of conductance is mho Ω^{-1} , or siemens S
- **Power = VI = I²R = V²/R**

$$P = VI \rightarrow I^2 R$$

$$P = I^2 R$$

$$V = IR \rightarrow I = \frac{V}{R}$$

$$P = \frac{V \cdot V}{R} = \frac{V^2}{R}$$

$P = \underline{C'V} \rightarrow$ للبيانات المتناثرة

$P = \left[\begin{array}{c} \frac{V^2}{R} \\ \frac{V^2}{R} \end{array} \right] \Rightarrow$ المعادلات

Examples

$$V = IR$$
$$R = \frac{V}{I}$$

1. An electric iron draws 2 A at 120V. Find its resistance.


$$R = \frac{120}{2} = 60 \Omega$$

Solution:

From Ohm's law $R = V/I = 120/2 = 60\Omega$

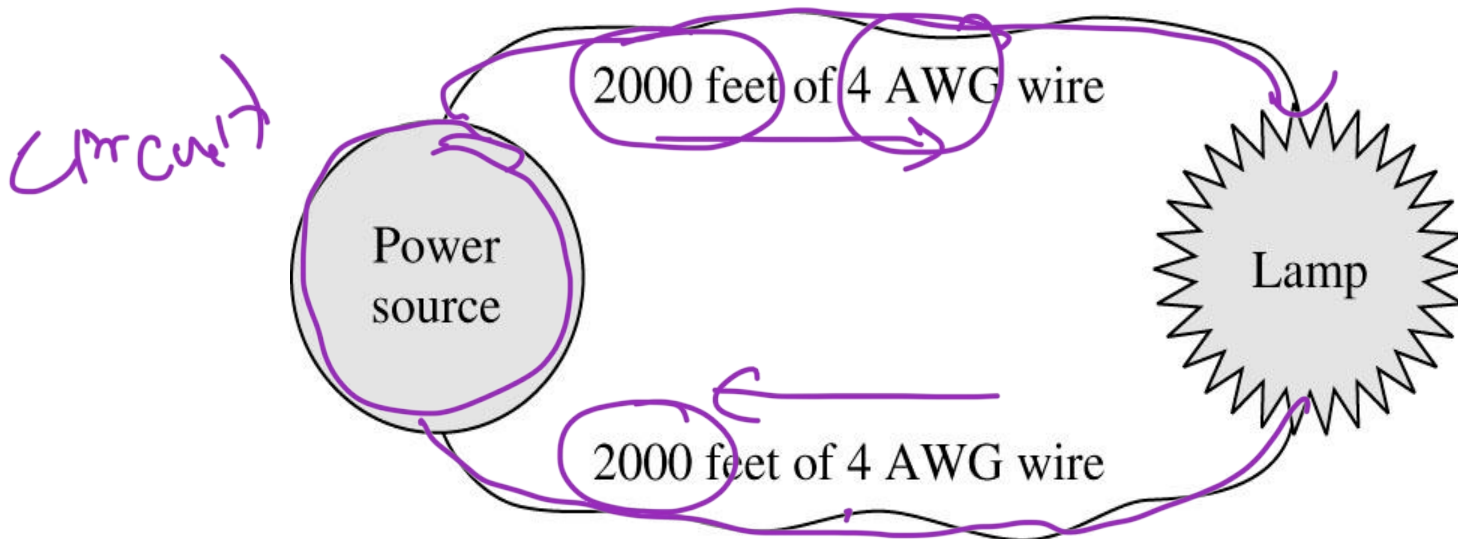example

- A wire is run across a 2000 ft span to a high power lamp that draws 100 A. if 4 AWG wire is used, how much power is dissipated(lost or wasted) within the wire?



4000 ft

$$I' = 100 \text{ A}$$

$$P = I'V = I'^2 R$$

$$R = \cancel{4000} \times \frac{0,2485}{\cancel{1000}} = 4 \times 0,2485 = \boxed{0,994 \Omega}$$

$$P = (100)^2 \times 0,994 = 9940 \text{ W}$$


Eng

$$\Rightarrow 9,94 \times 10^3 \text{ W}$$
$$\Rightarrow \boxed{9,94 \text{ kW}}$$

From table 2.4 that 4 AWG wire is 0.2485Ω per 1000 ft. the total wire is $2000 + 2000 = 4000$ ft.

$$\begin{aligned}\text{Wire resistance} &= 4000\text{ft} \times 0.2485 \Omega / 1000\text{ft} \\ &= 0.994 \Omega\end{aligned}$$
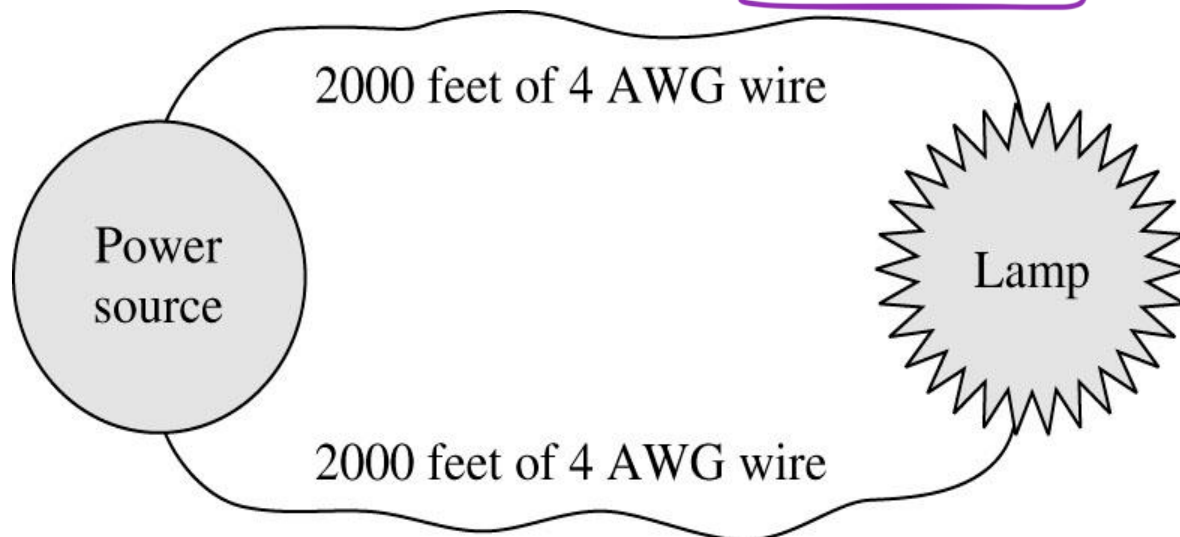
$$\begin{aligned}\text{Power dissipation in the wire} &= I^2R \\ &= (100)^2 \times 0.994 = 9940 \text{ W} = \boxed{9.94\text{kW}}\end{aligned}$$



Example of Electricity Bills

A homeowner consumes 700 kWh in January. Determine the electricity bill for the month using the following residential rate schedule:

Base monthly charge of \$12.00.

First 100 kWh per month at 16 cents/kWh.

Next 200 kWh per month at 10 cents/kWh.

Over 300 kWh per month at 6 cents/kWh.

Solution:

We calculate the electricity bill as follows.

$$\text{Base monthly charge} = \$12.00$$

$$\text{First 100 kWh @ } \$0.16/\text{kWh} = \$16.00$$

$$\text{Next 200 kWh @ } \$0.10/\text{kWh} = \$20.00$$

$$\text{Remaining 400 kWh @ } \$0.06/\text{kWh} = \$24.00$$

$$\text{Total charge} = \$72.00$$

نظام الشرائح

0 → 100 → 1

100 → 200 → 2

200 → 300 → 3

300 → 5

700

~~700 600~~

~~400~~
400

0 → 100 د^ا → 1 × 100 = 100

100 → 200 د^ا → 2 × 100 = 200

200 → 300 د^ا → 3 × 100 = 300

300 > → 5 × 400 = 2000

جواب 2600

مسا $\frac{100}{100}$ ← مسا $\frac{1}{100}$

مسا $\frac{1}{100}$ ← مسا

فاتورة إستهلاك الطاقة الكهربائية

القطاع القطر
إدارة كهرباء
مكتب خدمات
الشرقي الدمام
الخبر

رقم الفاتورة ٢٣٤٠٠١٢٩٨٠٨١	مجمع المها السكني ص.ب. ٠٠١٦٦٤ الخبر ٣١٩٥٢	المشترك العنوان
بداية الفترة ٢٠١٥/١١/٠٢ ١٤٣٧/٠١/٢٠	٠٠٠١	
نهاية الفترة ٢٠١٥/١٢/٠١ ١٤٣٧/٠٢/١٩		
هاتف الاستفسار ٩٢٠٠٠١١٠٠	موقع الشركة www.se.com.sa	هاتف الطوارئ ٩٣٣
شرائح الاستهلاك يتم احتساب الاستهلاك على أساس ٣٠ يوم سكني		

ك. و. س.	مئله
٢٠٠٠	٥
١٤١٩٠	١٠
$2000 \times \frac{5}{100} + 1419 \times \frac{10}{100}$	
١٥٠ + ١٤١,٩	
٢٤١,٩	
٢٥٦,٩	

فاتورة بريدية
٢٤١,٩
+ ١٥
٢٥٦,٩



رقم الحساب	١٠٠٠٠٨١٩٢٢١	رقم الإشتراك	٣١٠١٠٩٩٦٩٧٣
المبلغ المطلوب	٢٥٦,٩٠	رقم العداد	٧١٩٣٦٤٦٥
آخر موعد للداد	١٤٣٧/٠٣/١٣	سعة القاطع	١٠٠
تاريخ الفاتورة	١٤٣٧/٠٢/٢١	القراءة الحالية	٢٤٦٩١٧
تاريخ التوزيع	١٤٣٧/٠٢/٢٤	القراءة السابقة	٢٤٣٤٩٨
تاريخ فصل الكهرباء		معامل الضرب	١,٠٠
قيمة الإستهلاك	٢٤١,٩٠	كمية الإستهلاك	٠,٣٤١٩
خدمة العداد	١٥,٠٠	إجمالي الإستهلاك	٣٤١٩
إستحقاق الفترة	٢٥٦,٩٠	رقم المنطقة	٣١٢٠٠٠٣ ١٢٠٠٠١٠١٢ ٠٠٣٠٧٤٥
رصيد سابق	٠,٠٠		
عداد الأيسام	٣,٠٠		
رصيد دالن	٠,٠٠		
المبلغ المطلوب	٢٥٦,٩٠		

رقم الحساب	رقم الفاتورة	تاريخ الفاتورة
١٠٠٠٠٨١٩٢٢١	٢٣٤٠٠١٢٩٨٠٨١	١٤٣٧/٠٢/٢١
المبلغ المطلوب	٢٥٦,٩٠	

رقم الحساب	رقم الفاتورة	تاريخ الفاتورة
١٠٠٠٠٨١٩٢٢١	٢٣٤٠٠١٢٩٨٠٨١	١٤٣٧/٠٢/٢١
المبلغ المطلوب	٢٥٦,٩٠	



CONSUMPTION TARIFFS

Table shows the New Electricity Tariffs for all categories of consumption as approved by the Council of Ministers' Decree dated 12/12/2017, which has been applied since 1/1/2018 :

Consumption categories (Kwh)	Residential (Halalah / kwh)	Commercial (Halalah / kwh)	Agricultural & Charities (Halalah / kwh)	Governmental (Halalah / kwh)	Industrial (Halalah / kwh)	Private educational facilities, private medical facilities (Halalah / kwh)
1-6000	18	20	16	32	18	18
More than 6000	30	30	20			



Examples

How much energy does a 100-W electric bulb consume in two hours?

Example 1.6

Solution:

$$w = pt = 100 \text{ (W)} \times 2 \text{ (h)} \times 60 \text{ (min/h)} \times 60 \text{ (s/min)}$$
$$= 720,000 \text{ J} = 720 \text{ kJ}$$

This is the same as

$$w = pt = 100 \text{ W} \times 2 \text{ h} = 200 \text{ Wh}$$

watt hour


$$100 \times 2 \times 60 \times 60 \text{ s}$$

$$w = pt$$

$$w = J, \text{ Wh}$$

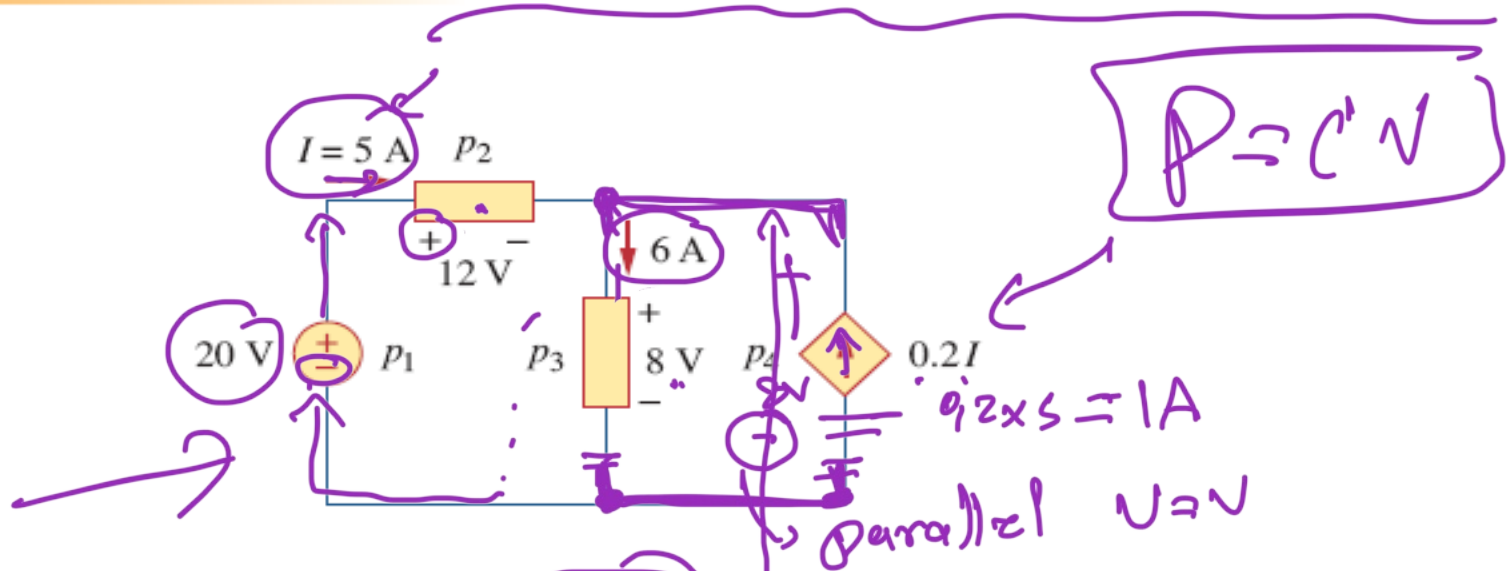Example 1.7

Calculate the power supplied or absorbed by each element in Fig.



$p_1 = 20(-5) = -100 \text{ W}$ Supplied power

$p_2 = 12(5) = 60 \text{ W}$ Absorbed power

$p_3 = 8(6) = 48 \text{ W}$ Absorbed power

$p_4 = 8(-0.2I) = 8(-0.2 \times 5) = -8 \text{ W}$ Supplied power

$p_1 + p_2 + p_3 + p_4 = -100 + 60 + 48 - 8 = 0$

$\sum P = 0 \Rightarrow$ conservation of energy