

$f_{rms} = \sqrt{\frac{1}{T} \int_0^T (f)^2 dt}$

\hat{v} periodic \swarrow
 \swarrow
period

$$v(t) = V_m \sin(\omega t)$$

$$V_{rms} =$$

$$V_m$$

$$\sqrt{\frac{1}{T} \int_0^T [V_m \sin(\omega t)]^2 dt}$$
$$\sqrt{\frac{1}{T} \int_0^T V_m^2 \sin^2(\omega t) dt}$$

$$V_{rms} = V_m \sqrt{\frac{1}{T} \int_0^T \sin^2(\omega t) dt}$$

$$\sin^2 \omega t = \frac{1}{2} - \frac{1}{2} \cos 2\omega t$$

$$\cos^2 \omega t = \frac{1}{2} + \frac{1}{2} \cos 2\omega t$$

$\frac{1}{T} \int_0^T \left(\frac{1}{2} - \frac{1}{2} \cos 2\omega t \right) dt$

$\frac{1}{T} \left[\frac{1}{2}t - \frac{1}{4} \sin(2\omega t) \right]_0^T$

$\frac{1}{T} \left(\frac{1}{2}T - \frac{1}{4} \sin(2\omega T) + \frac{1}{4} \sin(0) \right)$

$\frac{1}{T} \left(\frac{1}{2}T - \frac{1}{4} \sin(2\omega T) \right)$

$\frac{1}{2} - \frac{1}{4T} \sin(2\omega T)$

$\frac{1}{2}$

$$\omega = \frac{2\pi f}{T}$$

$$\rightarrow \omega T = 2\pi$$

$$\sin(\underbrace{2 \cdot 2\pi}_{4\pi}) = 0$$

$$\sin(0) = 0$$

$$V_{rms} = V_m \sqrt{\frac{1}{T} \cdot \frac{1}{2} T} = V_m \sqrt{\frac{1}{2}}$$


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

AC Circuits and AC Analysis

- Solving AC circuits in time domain involves solving differential equations.
- Example, for the given circuit below, what is $V_o(t)$?

$$i_C \Rightarrow C \frac{dv}{dt}$$

$$v_L \Rightarrow L \frac{di}{dt}$$

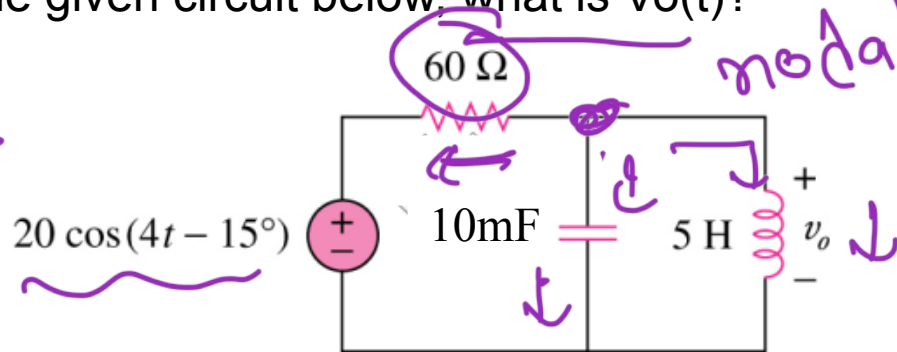

- Writing KCL at V_o node results in.

$$\frac{d^2 v_o}{dt^2} + \frac{5}{3} \frac{dv_o}{dt} + 20v_o = -\frac{400}{3} \sin(4t - 15^\circ)$$

- However, forming and solving the DE in time domain are sometimes very tedious.

- Therefore, AC circuits analysis is done in **Phasor (frequency) domain**.

$$\frac{V_0 - 20 \cos(4t - 15)}{60} + 10m \frac{dV_0}{dt} + \frac{1}{5} \int V_0 dt = 20$$

$$\frac{V_0}{60} + \frac{10m}{60} \frac{dV_0}{dt} + \frac{1}{5} \int V_0 dt = \frac{1}{3} \cos(4t - 15)$$

$$\frac{d^2 V_0}{dt^2} + \frac{dV_0}{dt} \left[\frac{1}{60 \times 10 \times 10^{-3}} \right] + \frac{1}{5 \times 10 \times 10^{-3}} V_0 =$$

$$= \frac{-4}{3 \times 10^{-3} \times 10} \sin(\underline{4t - 15})$$

$$\frac{d^2 v_0}{dt^2} + \frac{5}{3} \frac{dv_0}{dt} + 20 v_0 = -\frac{400}{3} \sin(4t - 15)$$



1-(b) Phasor

1-(b) Phasors

- A **phasor** is a **complex number** that represents the amplitude and phase of a sinusoid (**Polar Form**).
- Phasor is the mathematical equivalent of a sinusoid with **time variable dropped**.
- Phasor representation is based on **Euler's identity**.

$$e^{\pm j\phi} = \cos\phi \pm j\sin\phi \quad \text{Euler's Identity}$$

$$\cos\phi = \text{Re}\{e^{j\phi}\} \quad \text{Real part}$$

$$\sin\phi = \text{Im}\{e^{j\phi}\} \quad \text{Imaginary part}$$

- Given a sinusoid $v(t) = V_m \cos(\omega t + \phi)$.

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re}(V_m e^{j(\omega t + \phi)}) = \text{Re}(V_m e^{j\phi} e^{j\omega t}) = \text{Re}(\mathbf{V} e^{j\omega t})$$

$$\mathbf{V} = V_m e^{j\phi} = V_m \angle \phi = \text{PHASOR REP.}$$

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{V} = V_m \angle \phi$$

(Time Domain Re pr.) (Phasor Domain Representation)

$$v(t) = \text{Re}\{\mathbf{V} e^{j\omega t}\} \quad \text{(Converting Phasor back to time)}$$



Complex Numbers and Mathematical Foundation of Phasor

Complex Numbers

➤ A complex number may be written in RECTANGULAR FORM as:

RECTANGULAR FORM

$$z = x + jy \quad j = \sqrt{-1}, \quad x = \text{Re}(z), \quad y = \text{Im}(z)$$

➤ A second way of representing the complex number is by specifying the MAGNITUDE and r and the ANGLE θ in POLAR form.

POLAR FORM

$$z = x + jy = |z| \angle \phi = r \angle \phi$$

➤ The third way of representing the complex number is the EXPONENTIAL form.

EXPONENTIAL FORM

$$z = x + jy = |z| \angle \phi = r e^{j\phi}$$


$$z = r e^{j\phi}$$

$$r e^{j\phi} = r \cos \phi + j r \sin \phi \quad \text{Euler's Identity}$$

$$r \cos \phi = \text{Re} \{ r e^{j\phi} \} \quad \text{Real part}$$

$$r \sin \phi = \text{Im} \{ r e^{j\phi} \} \quad \text{Imaginary part}$$

Imaginary axis

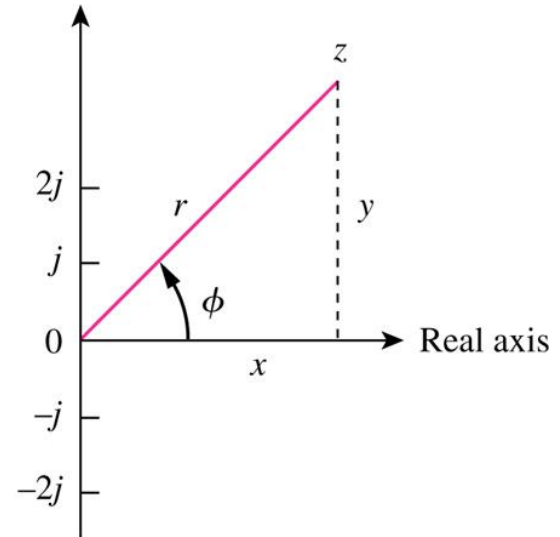

- x is the REAL part.
- y is the IMAGINARY part.
- r is the MAGNITUDE.
- ϕ is the ANGLE.

Complex number

$$j = \underline{\underline{i}} = \sqrt{-1}$$


$$Z = \underline{\underline{x}} + j \underline{\underline{y}}$$

Real part

Imag part

Rectangular form

$$Z = S + 3j$$

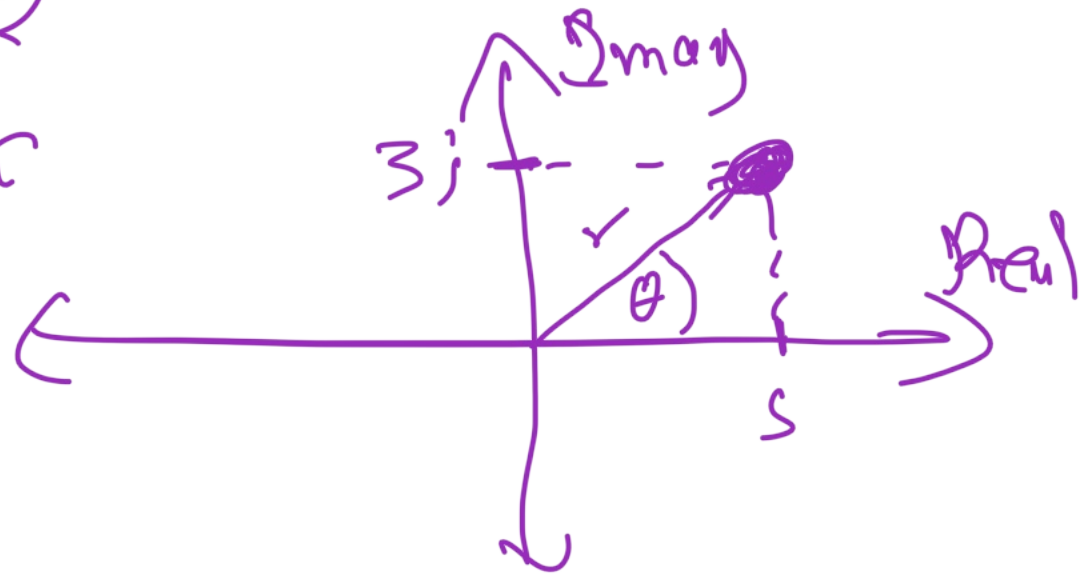

$$r = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right)$$

المركب
المركب

$$\theta = \tan^{-1}\left(\frac{3}{3}\right)$$

$$z = r \angle \theta$$

Polar
Form

Direct into
Polar

$$x = r \cos \theta$$

$$y = r \sin \theta$$

di Polário
rect

$$z = x + jy$$




Complex Number Conversions

- We need to convert COMPLEX numbers from one form to the other form.

$$z = x + jy = r \angle \phi = re^{j\phi} = r(\cos \phi + j \sin \phi)$$

EXPONENTIAL FORM

$$z = x + jy = |z| \angle \phi = re^{j\phi}$$

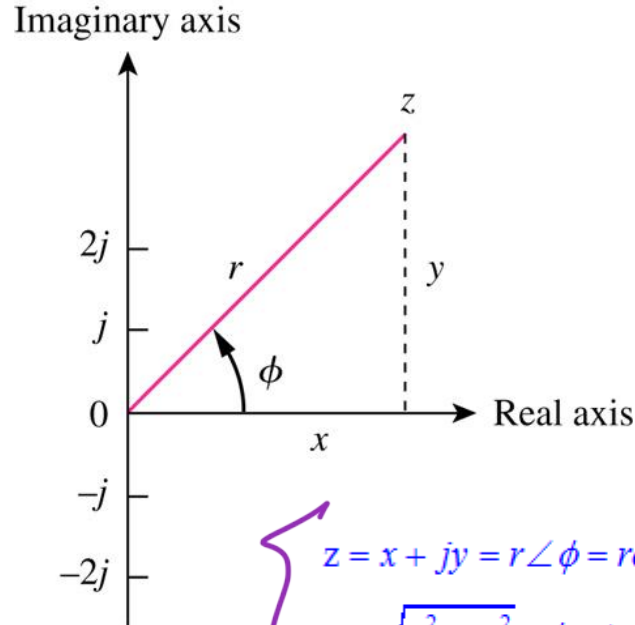

$$z = x + jy = r \angle \phi = re^{j\phi} = r(\cos \phi + j \sin \phi)$$

$$r = \sqrt{x^2 + y^2}, \quad \phi = \tan^{-1} \frac{y}{x} \quad \text{Rectangular to Polar}$$

$$x = r \cos \phi, \quad y = r \sin \phi \quad \text{Polar to Rectangular}$$

Mathematical Operations of Complex Numbers

➤ Mathematical operations on complex numbers may require conversions from one form to other form.



ADDITION: $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

SUBTRACTION: $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

Better performed in Rectangular form

MULTIPLICATION: $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

DIVISION: $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

Better performed in Polar form

RECIPROCAL: $\frac{1}{z} = \frac{1}{r} \angle -\phi$

SQUARE ROOT: $\sqrt{z} = \sqrt{r} \angle \frac{\phi}{2}$

$z = x + jy$

COMPLEX CONJUGATE: $z^* = x - jy = r \angle -\phi = re^{-j\phi}$

Complex Numbers

✓ Example 1:

Evaluate $[(5 + j2)(-1 + j4) - 5\angle 60^\circ]^*$ and $\frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ$

Solution:

$$(a) \quad (5 + j2)(-1 + j4) = -5 + j20 - j2 - 8 = -13 + j18$$

$$5\angle 60^\circ = 2.5 + j4.33$$

$$(5 + j2)(-1 + j4) - 5\angle 60^\circ = -15.5 + j13.67$$

$$[(5 + j2)(-1 + j4) - 5\angle 60^\circ]^* = \underline{\underline{-15.5 - j13.67}} = \underline{\underline{20.67\angle 221.41^\circ}}$$

$$(b) \quad 3\angle 40^\circ = 2.298 + j1.928$$

$$10 + j5 + 3\angle 40^\circ = 12.298 + j6.928 = 14.115\angle 29.39^\circ$$

$$-3 + j4 = 5\angle 126.87^\circ$$

$$\frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} = \frac{14.115\angle 29.39^\circ}{5\angle 126.87^\circ} = 2.823\angle -97.48^\circ$$

$$2.823\angle -97.48^\circ = -0.3675 - j2.8$$

$$10\angle 30^\circ = 8.66 + j5$$

$$\frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ = \underline{\underline{8.293 + j2.2}}$$

کے
الئے
حاسب

Complex Numbers

✓ Example 2:

$$(4\angle 50^\circ)(2\angle -20^\circ) = 4 \cdot 2 \angle (50^\circ + (-20^\circ)) = 8\angle 30^\circ$$

✓ Example 3:

$$\frac{4\angle 50^\circ}{2\angle -20^\circ} = \frac{4}{2} \angle (50^\circ - (-20^\circ)) = 2\angle 70^\circ$$



Back to Phasor



Sinusoids and Phasor

Circuit elements in Phasor domain (frequency domain)

Impedance and admittance

Phasors

- A **phasor** is a complex number that represents the amplitude and phase of a sinusoid (Polar Form).
- Phasor is the mathematical equivalent of a sinusoid with **time variable dropped**.
- Given a sinusoid $v(t) = V_m \cos(\omega t + \phi)$.

$$v(t) = V_m \cos(\omega t + \phi) \xleftrightarrow{\omega} \mathbf{V} = V_m \angle \phi$$

Handwritten notes: "Polar" written above the phasor equation, and a box around the phasor equation.

(Time Domain Repr.)


(Phasor Domain Representation)



Phasor Diagrams

- Amplitude and phase difference are two principal concerns in the study of voltage and current sinusoids.
- Phasor can be defined using either sine or cosine functions.
- By convention, source of the circuit is used as reference (zero phase angle).
- If not stated, cosine function is used as reference and any voltage or current expression is in the form of a sine is changed to a cosine:

NOTE

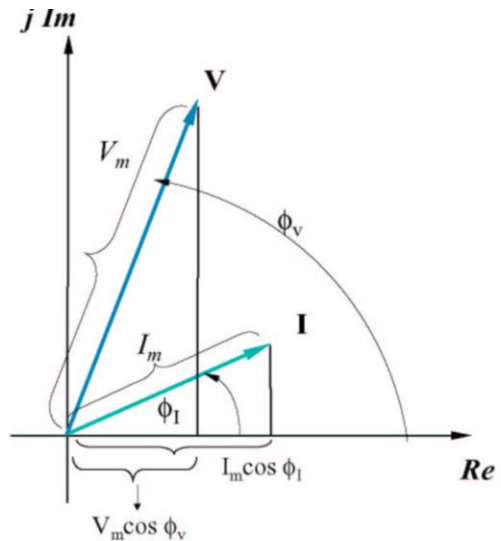

$+ \sin(\omega t) \rightarrow \cos(\omega t - 90^\circ)$

Time Domain Representation	Phasor Domain Rep.
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	$I_m \angle \theta$
$I_m \sin(\omega t + \theta)$	$I_m \angle \theta - 90^\circ$

Phasor diagram

Phasor Diagrams




✓ Graphing phasors

- Positive phase angles are drawn counterclockwise from the axis;
- Negative phase angles are drawn clockwise from the axis.


مخطط متجهات الطاقة

→ متجه

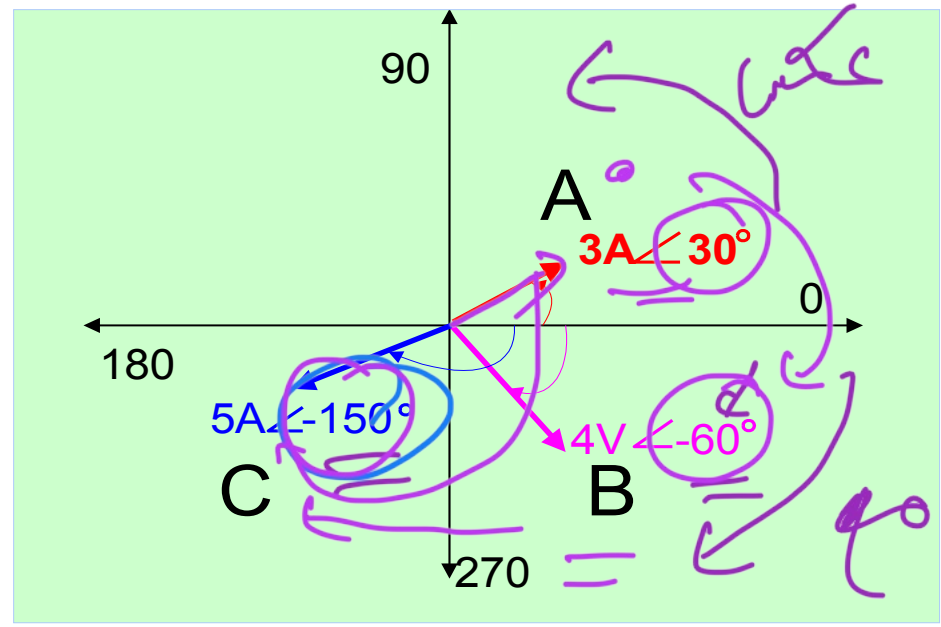

Note:
A leads B
B leads C
C lags A
etc.


A lead C

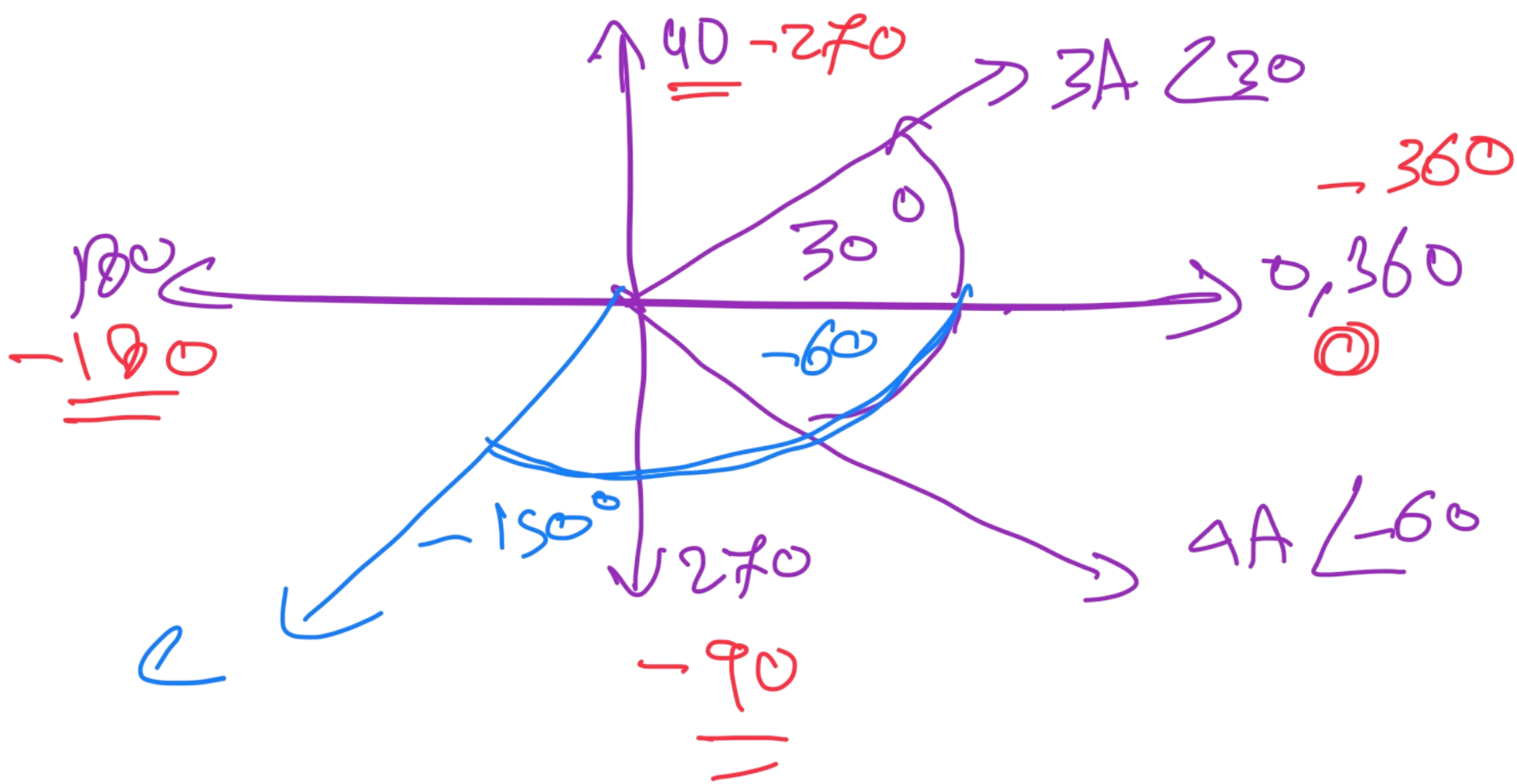

$$A = 230 \rightarrow \theta_1 = -30$$

$$B = 260 \rightarrow \theta_2 = 60$$

$$C = 2150 \rightarrow \theta_3 = 150$$

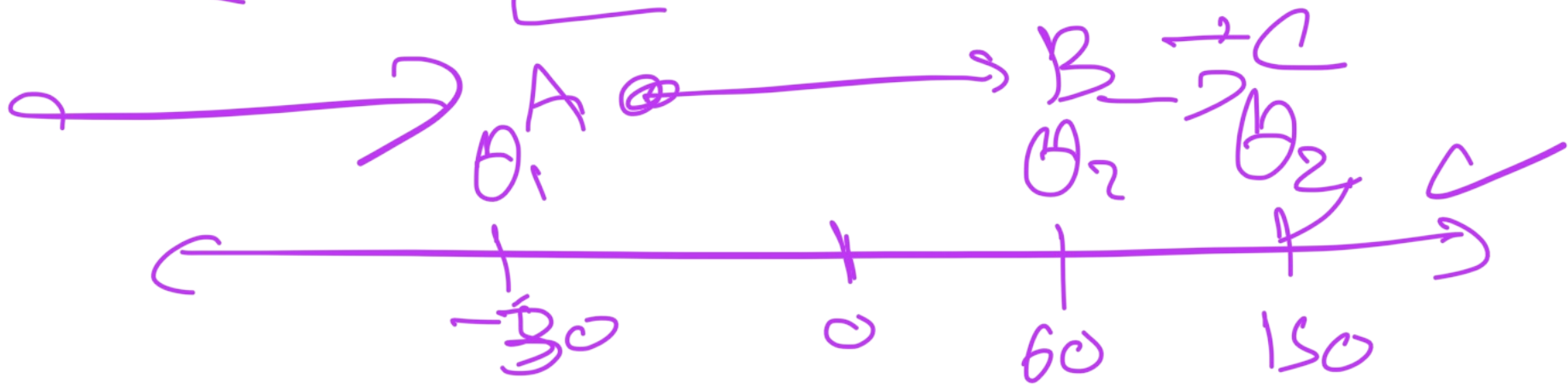


Phasor Diagrams



✓ PHASOR DIAGRAM

- Represents one or more sine waves (of the same frequency) and the relationship between them.
- The arrows A and B rotate together. A leads B or B lags A.

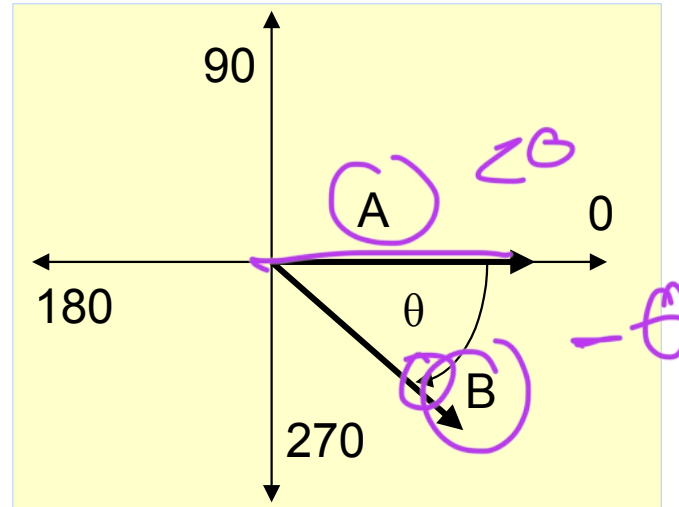

Example 11

Transform the following sinusoids to phasors:

$$i = 6\cos(50t - 40^\circ) \text{ A} \rightarrow 6 \angle -40^\circ$$

$$v = -4\sin(30t + 50^\circ) \text{ V}$$

$$-\sin(\omega t) \rightarrow \cos(\omega t + 90^\circ)$$

$$v = 4\cos(30t + 140^\circ)$$

$$4 \angle 140^\circ$$

Solution:

a. $I = 6 \angle -40^\circ \text{ A}$

b. Since $-\sin(A) = \cos(A+90^\circ)$;

$$v(t) = 4\cos(30t + 50^\circ + 90^\circ) = 4\cos(30t + 140^\circ) \text{ V}$$

Transform to phasor $\Rightarrow V = 4 \angle 140^\circ \text{ V}$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$



Time Domain Versus Phasor Domain

The differences between $v(t)$ and V :

- $v(t)$ is instantaneous or time-domain representation
 V is the frequency or phasor-domain representation.
- $v(t)$ is time dependent, V is not.
- $v(t)$ is always real with no complex term, V is generally complex.



Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.

$$\cos(\omega t)$$

$$\cos(\omega t)$$

$$\cos(\omega t)$$
$$\sin(\omega t)$$

* لو كانت frequency line \Rightarrow يكون كل

اللائحة في frequency domain

* لو كانت frequency line \Rightarrow يكون



Superposition \Leftarrow طريقة دالة



Differentiation and Integration in Phasor Domain



➤ Differentiating a sinusoid is equivalent to multiplying its corresponding phasor by $j\omega$.


$$v(t) = V_m \cos(\omega t + \theta) = \text{Re}[V e^{j\omega t}]$$

$$\frac{dv(t)}{dt} = -\omega V_m \sin(\omega t + \theta) = \omega V_m \cos(\omega t + \theta + 90^\circ)$$

which transforms to the phasor

$$\frac{dv(t)}{dt} = \omega V_m e^{j(\theta + 90^\circ)} = \omega V_m \angle \phi + 90^\circ$$
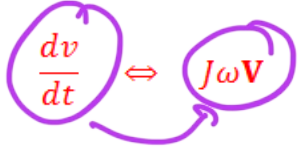
$$\frac{dv(t)}{dt} = \omega e^{j90^\circ} V_m e^{j\theta}$$



$$\begin{aligned} \sin(\omega t \pm 180^\circ) &= -\sin \omega t \\ \cos(\omega t \pm 180^\circ) &= -\cos \omega t \\ \sin(\omega t \pm 90^\circ) &= \pm \cos \omega t \\ \cos(\omega t \pm 90^\circ) &= \mp \sin \omega t \end{aligned}$$



$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$



➤ Integrating a sinusoid is equivalent to dividing its corresponding phasor by $j\omega$.



Differentiation and Integration in Phasor Domain



- Relationship between differential, integral operation in phasor listed as follow:

(Time Domain)		(Phasor Domain)
$v(t) = V_m \cos(\omega t + \phi)$	\Leftrightarrow	$\mathbf{V} = V_m \angle \phi$
$v(t) = V_m \sin(\omega t + \phi)$	\Leftrightarrow	$\mathbf{V} = V_m \angle \phi - 90^\circ$
$\frac{dv}{dt}$	\Leftrightarrow	$J\omega \mathbf{V}$
$\int v dt$	\Leftrightarrow	$\frac{\mathbf{V}}{J\omega}$

Example 9.7: Using Phasor to solve integro-differential equations

Example 9.7

Use phasor approach, determine the current $i(t)$ in a circuit described by the integro-differential equation.

$$4i + 8 \int idt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

➤ Solution:

$$4\mathbf{I} + \frac{8\mathbf{I}}{j\omega} - 3j\omega\mathbf{I} = 50\angle 75^\circ$$

But $\omega = 2$, so

$$\mathbf{I}(4 - j4 - j6) = 50\angle 75^\circ$$
$$\mathbf{I} = \frac{50\angle 75^\circ}{4 - j10} = \frac{50\angle 75^\circ}{10.77\angle -68.2^\circ} = 4.642\angle 143.2^\circ \text{ A}$$

Converting this to the time domain,

$$i(t) = 4.642 \cos(2t + 143.2^\circ) \text{ A}$$



$v(t)$	\longleftrightarrow	$V = V\angle\phi$
$\frac{dv}{dt}$	\longleftrightarrow	$j\omega V$
$\int v dt$	\longleftrightarrow	$\frac{V}{j\omega}$

$$\underline{4i} + 8 \int \underline{i} dt - 3 \frac{di}{dt} = 50 \cos(\underbrace{2t}_{w=2} + 7s)$$

Let \rightarrow freq domain

$$4I + \frac{8I}{jw} - 3Ijw = 50 \angle 7s$$

$$4I - j4I - \underline{6jI} = 50 \angle 7s$$

$$I(4 - 10j) = 50 \angle 7s$$

$$I = \frac{50 \angle 75^\circ}{4 - 10j} = \underline{\underline{-3,717 + j 2,781}}$$







$$I = 4,642 \angle +143,2^\circ \text{ A}$$

$$i(t) = 4,642 \cos(2t + 143,2^\circ) \text{ A}$$

Phasor Relationships for Circuit Elements

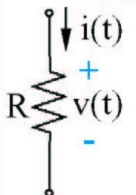➤ Ohm's Law still applies even though the voltage source is AC

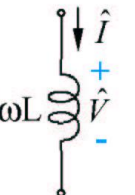Terminal Equations





Time Domain	Frequency Domain
 $v(t) = Ri(t)$	 $\hat{V} = R\hat{I}$ $\hat{I} = G\hat{V}$
 $v(t) = L \frac{di(t)}{dt}$	 $\hat{V} = j\omega L\hat{I}$ $\hat{I} = \frac{1}{j\omega L}\hat{V}$
 $i(t) = C \frac{dv(t)}{dt}$ $v(t) = \frac{1}{C} \int i(t) dt$	 $\hat{V} = \frac{1}{j\omega C}\hat{I}$ $\hat{I} = j\omega C\hat{V}$

$\frac{d}{dt} \rightarrow j\omega$
 $\int \rightarrow \frac{1}{j\omega}$


4

Phasor Relationships for Circuit Elements

A- Resistor:

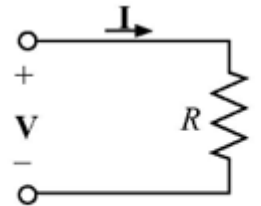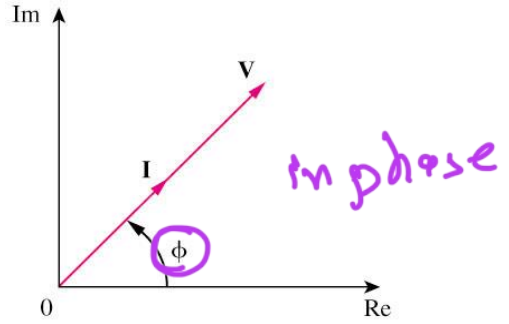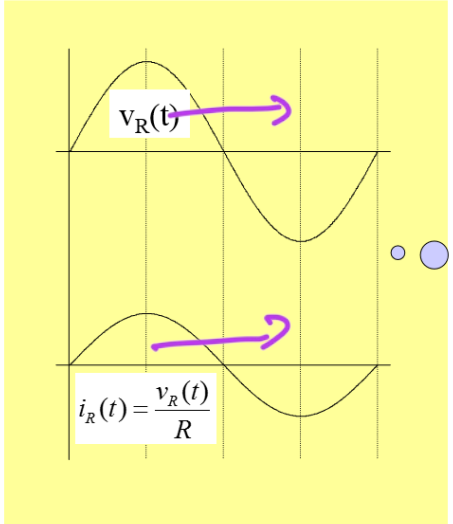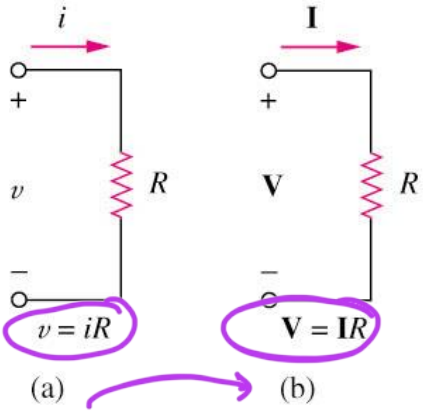

For R, I and V are in phase


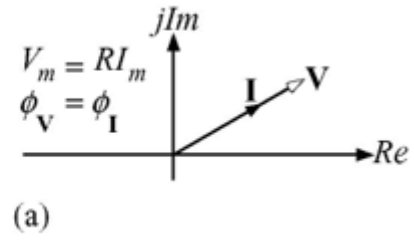


Phasor Relationships for Circuit Elements


*V lags I 90
I leads V*

B- Capacitor:

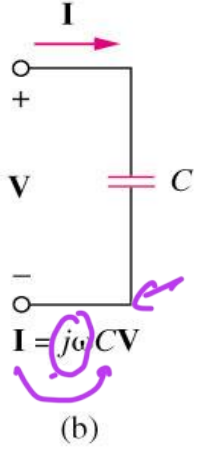
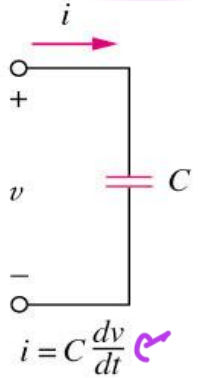
❖ In the Capacitor (C), Voltage **LAGS** charging current by 90° or Charging Current (I) **LEADS** Voltage (E) by 90°



❖ I. C. E.

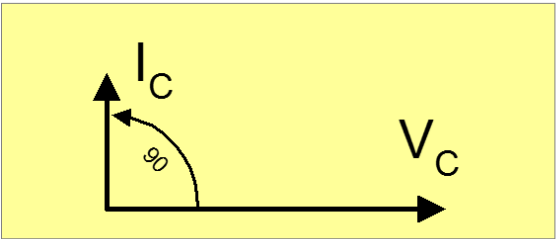


j → 1290

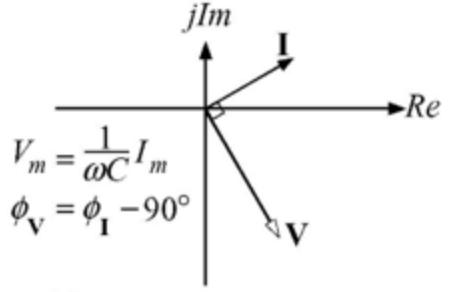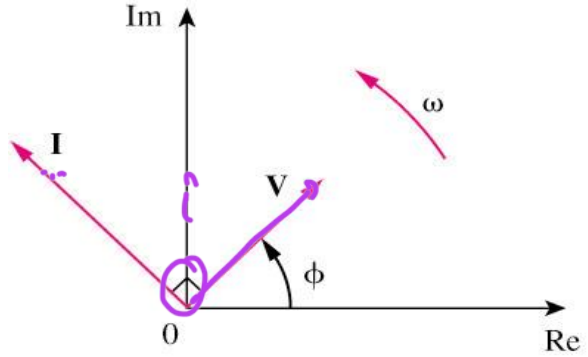


Phasor Relationships for Circuit Elements

B- Capacitor:


$$\frac{1}{j} \Rightarrow -j$$

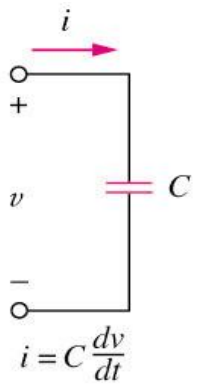

(a)

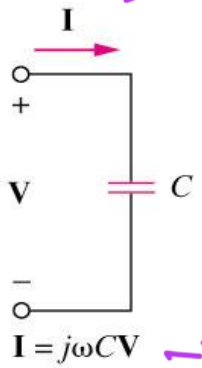

(b)

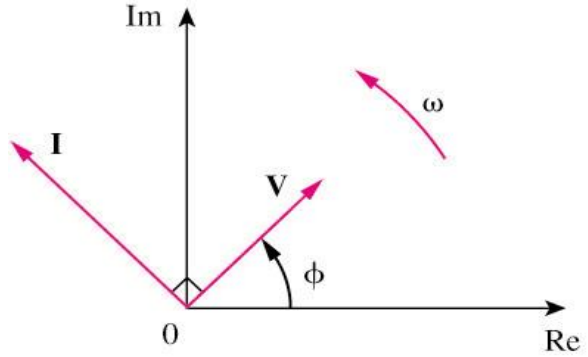

CAPACITIVE REACTANCE

- In resistor, the Ohm's Law is $V=IR$, where R is the opposition to current.
- We will define **Capacitive Reactance**, X_C , as the opposition to current in a capacitor.

$$V = I X_C$$

$$X_C = \frac{1}{\omega C}$$




- X_C will have units of **Ohms**
- Note inverse proportionality to f and C .

$$X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$

Magnitude of X_C


Phasor Relationships for Circuit Elements

B- Capacitor:

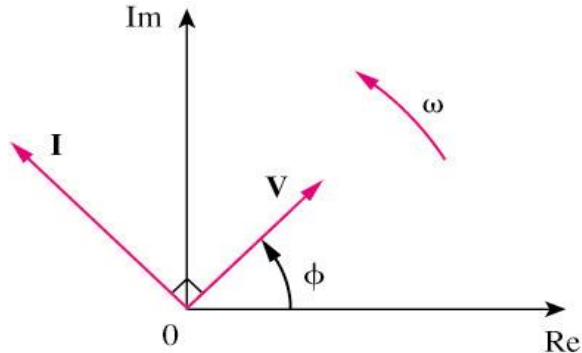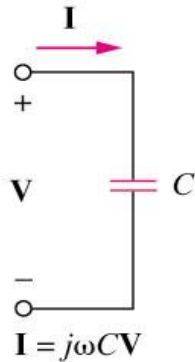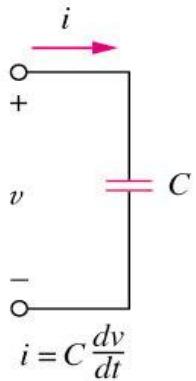

❖ CAPACITIVE REACTANCE


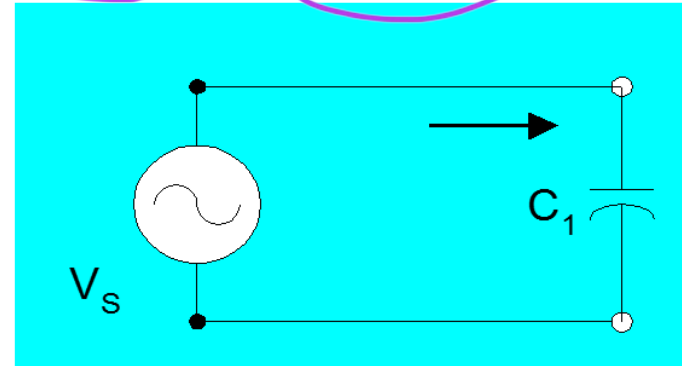
Ex: $f = 500$ Hz, $C = 50 \mu\text{F}$, $X_C = ?$



$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi (500 \text{ Hz}) 50 \mu\text{F}} = 6.4 \Omega$$

Phasor Relationships for Circuit Elements

B- Capacitor:

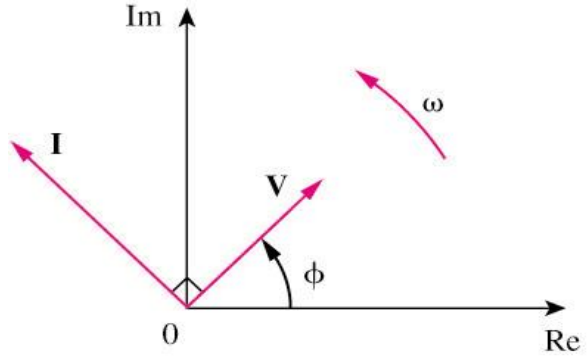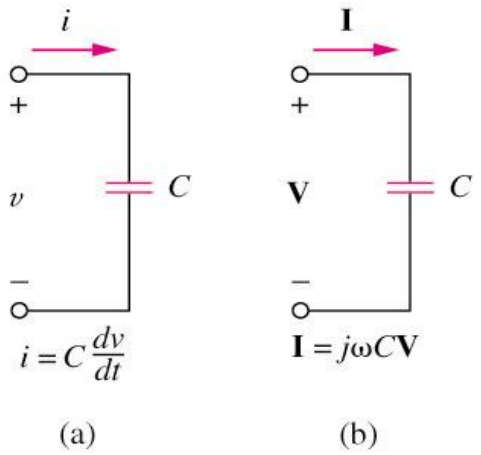

❖ PHASE ANGLE FOR X_C

❖ Capacitive reactance also has a phase angle associated with it.

$$X_C = \frac{V}{I}$$

$$X_C = \frac{V \angle 0^\circ}{I \angle 90^\circ} = Z \angle -90^\circ$$


- ❖ The phase angle for Capacitive Reactance (X_C) will always = -90°
- ❖ X_C may be expressed in POLAR or RECTANGULAR form.

$$X_C \angle -90^\circ \quad \text{or} \quad -jX_C$$


$$Z_C = -jX_C \quad \text{or} \quad Z_C = \frac{1}{j\omega C}$$

Phasor Relationships for Circuit Elements


C-Inductor:

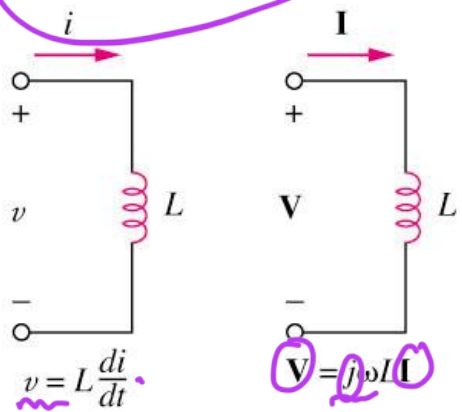

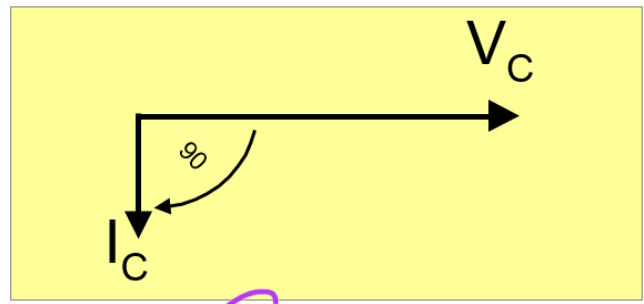❖ In the Inductor (L), Induced Voltage **LEADS** current by 90° or Current (I) **LAGS** Induced Voltage (E) by 90° .






V leads I by 90
I lags V by 90

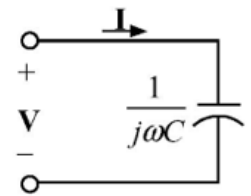




For C, I Leads V by 90°

Graph $v_L(t)$ and $i_L(t)$

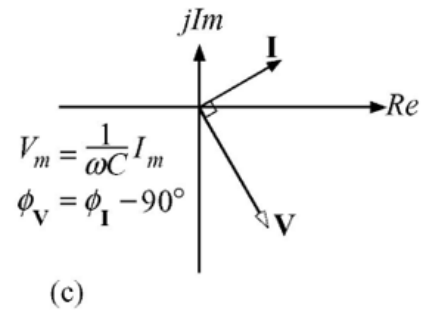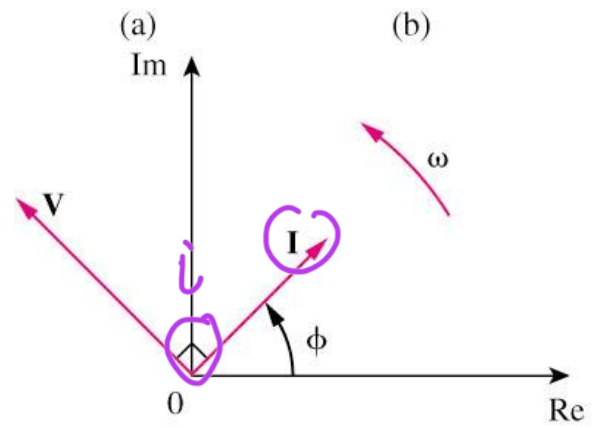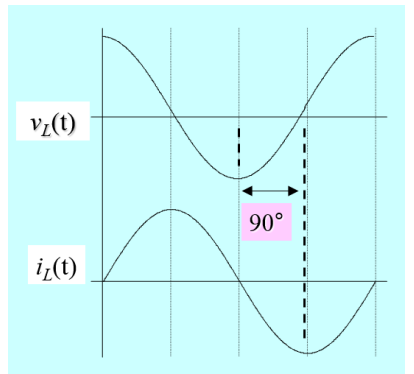

Phasor Relationships for Circuit Elements

C-Inductor:

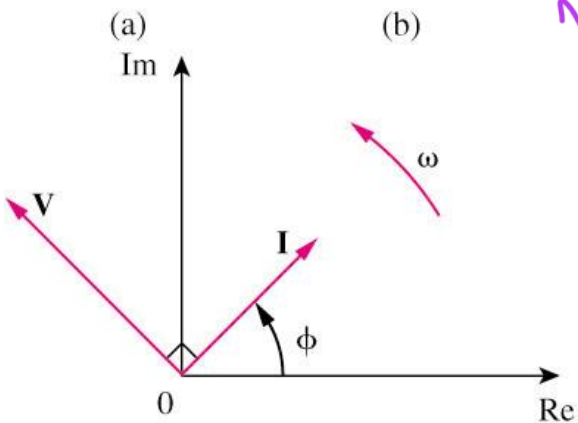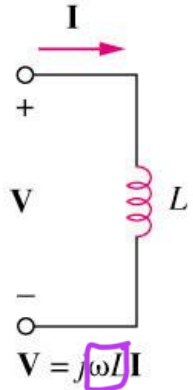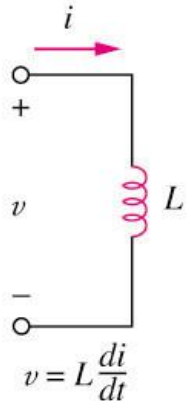

❖ INDUCTIVE REACTANCE

❖ We will define **Inductive Reactance**, X_L , as the opposition to current in an inductor.

$$V = I X_L$$

Handwritten: $V = X_L I$

- ❖ X_L will have units of Ohms (Ω).
- ❖ Note direct proportionality to f and L .



$$X_L = 2\pi fL = \omega L$$

Magnitude of X_L

Handwritten: $V = X_C I$
 $V = X_L I$
 $\frac{1}{\omega C}$
 ωL


Phasor Relationships for Circuit Elements

C-Inductor:

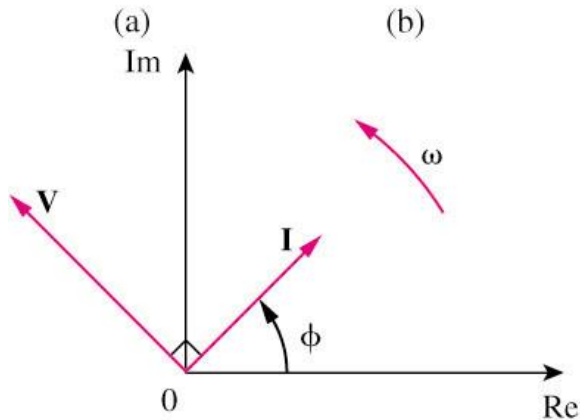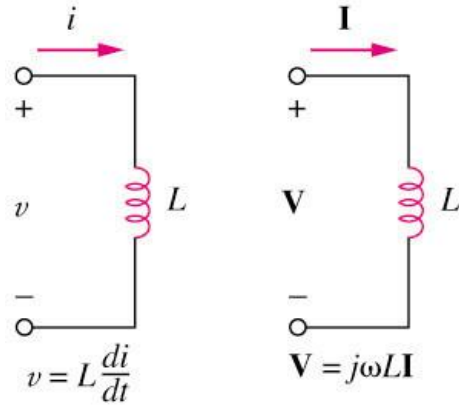

❖ INDUCTIVE REACTANCE



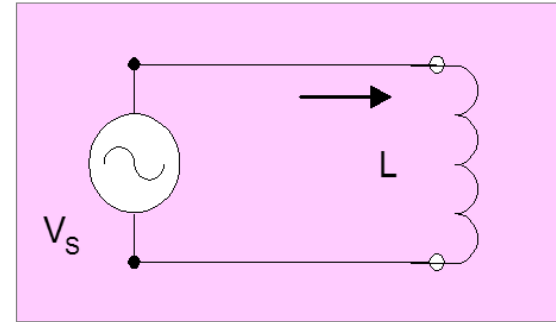
$f = 500 \text{ Hz}$, $C = 500 \text{ mH}$, $X_L = ?$



$$X_L = 2\pi fL = 2\pi(500)(.5) = 1.57k\Omega$$

Phasor Relationships for Circuit Elements

C-Inductor:

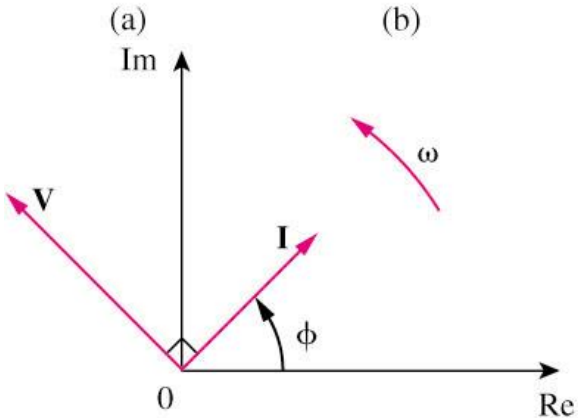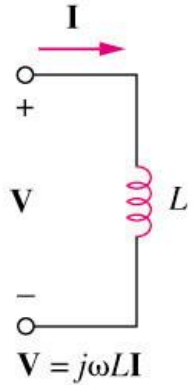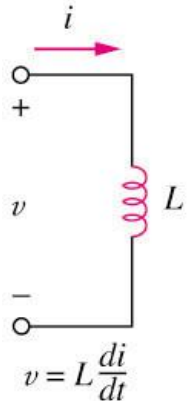

❖ PHASE ANGLE FOR X_L

❖ If \underline{V} is our reference wave:

$$\mathbf{X}_L = \frac{V \angle 0^\circ}{I \angle -90^\circ} = Z \angle +90^\circ$$

- ❖ The phase angle for Inductive Reactance (\mathbf{X}_L) will always = $+90^\circ$
- ❖ \mathbf{X}_L may be expressed in POLAR or RECTANGULAR form.

$$X_L \angle 90^\circ \quad \text{or} \quad jX_L \quad \Omega$$

$$Z_L = jX_L \rightarrow Z_L = j\omega L$$

Phasor Relationships for Circuit Elements



✓ COMPARISON OF X_L & X_C


- ❖ X_L is directly proportional to frequency and inductance.

$$X_L = 2\pi fL = \omega L$$

- ❖ X_C is inversely proportional to frequency and capacitance.

$$X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$

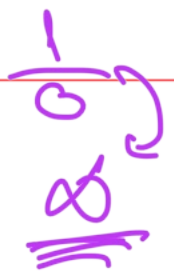Phasor Relationships for Circuit Elements



$\infty \Rightarrow$ open
 $0 \Rightarrow$ short

❖ Frequency effects

❖ Using the reactances of an inductor and a capacitor you can show the effects of low and high frequencies on them.

DC



- DC
- ❖ At low frequencies ($f=0$):
 - an inductor acts like a short circuit.
 - a capacitor acts like an open circuit.
 - ❖ At high frequencies ($f=\infty$):
 - an inductor acts like an open circuit.
 - a capacitor acts like a short circuit.

$$X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$


$$X_L = 2\pi fL = \omega L$$



Example



Represent the below circuit in frequency domain:

Solution:

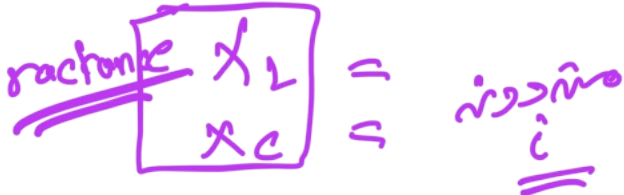

$\omega = 2$ rad/s:

Time domain	Freq domain
$R = 2 \Omega$	$R = 2 \Omega$
$C = 0.25 \text{ F}$	$X_C = -j(1/\omega C) = -j2 \Omega$
$L = 1 \text{ H}$	$X_L = j\omega L = j2 \Omega$
$V_s = 5 \cos 2t$	$V_s = 5 \angle 0^\circ$

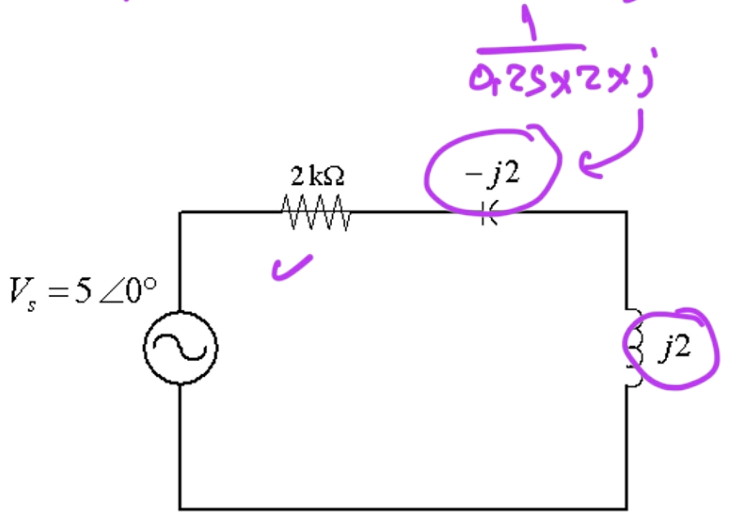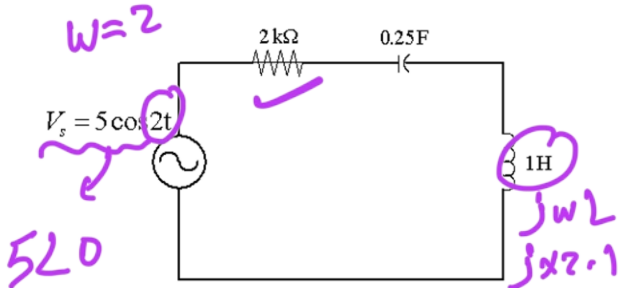

Impedance

$$Z_R = R \quad \Omega$$

$$Z_L = j\omega L \quad \Omega$$

$$Z_C = \frac{1}{j\omega C} \quad \Omega$$

Example 9.8

The voltage $v = 12 \cos(60t + 45^\circ)$ is applied to a 0.1-H inductor. Find the steady-state current through the inductor.

Solution:

For the inductor, $\mathbf{V} = j\omega L\mathbf{I}$, where $\omega = 60 \text{ rad/s}$ and $\mathbf{V} = 12\angle 45^\circ \text{ V}$. Hence,

$$\mathbf{I} = \frac{\mathbf{V}}{j\omega L} = \frac{12\angle 45^\circ}{j60 \times 0.1} = \frac{12\angle 45^\circ}{6\angle 90^\circ} = 2\angle -45^\circ \text{ A}$$

Converting this to the time domain,

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$

$$v(t) = 12 \cos(60t + 45) \quad L = 0,1$$

$$i(t) = \frac{1}{2} \int v(t) dt$$

$$V = 12 \angle 45 \text{ V}$$

$$\omega = 60$$

$$Z_L = j\omega L = j \times 60 \times 0,1 = 6j \ \Omega$$

Frey \hat{v} - \hat{i} \rightarrow \hat{v} \hat{i}

dem \hat{v} \hat{i}

$$V = IZ \quad \Rightarrow \quad I = \frac{V}{Z}$$

$$I = \frac{12 \angle 45^\circ}{6j} = 2 \angle -45^\circ \text{ A}$$

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$

Using phasor to add sinusoids- Example 9.6



Given $i_1(t) = 4 \cos(\omega t + 30^\circ)$ A and $i_2(t) = 5 \sin(\omega t - 20^\circ)$ A find their sum.

Solution:

Here is an important use of phasors—for summing sinusoids of the same frequency. Current $i_1(t)$ is in the standard form. Its phasor is

$$\mathbf{I}_1 = 4 \angle 30^\circ$$

We need to express $i_2(t)$ in cosine form. The rule for converting sine to cosine is to subtract 90° . Hence,

$$i_2(t) = 5 \sin(\omega t - 20^\circ) = 5 \cos(\omega t - 20^\circ - 90^\circ) = 5 \cos(\omega t - 110^\circ)$$

and its phasor is

$$\mathbf{I}_2 = 5 \angle -110^\circ$$

If we let $i = i_1 + i_2$, then

$$\begin{aligned} \mathbf{I} &= \mathbf{I}_1 + \mathbf{I}_2 = 4 \angle 30^\circ + 5 \angle -110^\circ \\ &= 3.464 + j2 - 1.71 - j4.698 = 1.754 - j2.698 \\ &= 3.218 \angle -56.97^\circ \text{ A} \end{aligned}$$



$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$i_1(t) = \underline{4 \cos(\omega t + 30)} \quad \checkmark$$

$$i_2(t) = \underline{5 \sin(\omega t - 20)} - 90$$

$$\hookrightarrow \underline{5 \cos(\omega t - 110)}$$

$$i_1(t) + i_2(t)$$

Polar



Freq
Down

$$\left. \begin{array}{l} i_1 = 4 \angle 30 \\ i_2 = 5 \angle -110 \end{array} \right\}$$

$$i_T = i_1 + i_2 = (4 \angle 30^\circ) + (5 \angle -110^\circ)$$

$$3,218 \angle -56,98^\circ$$

$$i_T(t) = 3,218 \cos(\omega t - 56,98^\circ) \text{ A}$$





Impedance and Admittance

A-Impedance

$$R = \frac{V}{I}$$

□ The impedance Z of a circuit is the ratio of the phasor voltage V to the phasor current I, measured in ohms Ω.

$$Z = \frac{V}{I} = R + jX$$

➤ Impedance is a complex quantity:

- R = Real part of Z = Resistance
- X = Imaginary part of Z = Reactance

X_L, X_C

Impedances of passive elements	
Element	Impedance
R	$Z = R$
L	$Z = j\omega L$
C	$Z = \frac{1}{j\omega C} = \frac{-j}{\omega C}$

□ Impedance in polar form:

$$Z = \frac{V}{I} = R + jX = |Z| \angle \theta$$

$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1} \frac{X}{R}$$


$$R = |Z| \cos \theta$$

$$X = |Z| \sin \theta$$



➤ The Reactance may be positive or negative:

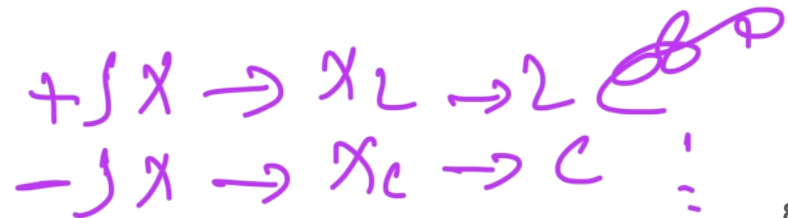- It is Inductive if X is positive.
- It is Capacitive if X is negative.



A-Impedance

IMPEDANCES SUMMARY

Impedance	Phasor form:	Rectangular form
<u>Z_R</u>	$R \angle 0^\circ$	$R + j0$
<u>Z_L</u>	$X_L \angle 90^\circ$	$0 + jX_L$
<u>Z_C</u>	$X_C \angle -90^\circ$	$0 - jX_C$

$$Z_L = j\omega L = jX_L$$

$$Z_C = \frac{-j}{\omega C} = -jX_C$$

$$X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$



B- ADMITTANCE



- ✓ The reciprocal of impedance.
- ✓ Symbol is Y.
- ✓ Measured in Siemens (S).

$$Y = \frac{1}{Z} = \frac{I}{V}$$



➤ Admittance is a complex quantity:

$$Y = G \pm jB$$

- G = Real part of Y : Conductance
- B = Imaginary part of Y : Susceptance

Z AND Y OF PASSIVE ELEMENTS

ELEMENT	IMPEDANCE	ADMITTANCE
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = -j\frac{1}{\omega C}$	$Y = j\omega C$

$$\frac{1}{j\omega C}$$

$$\psi = \frac{1}{2} = \frac{1}{R + jX} = G - jB$$

~~$$\frac{1}{R + jX} = \frac{1}{R} - j\frac{1}{X}$$~~




C-TOTAL IMPEDANCE FOR AC CIRCUITS

Resistance


- To compute total circuit impedance in AC circuits, use the same techniques as in DC.
- The **only difference** is that instead of using resistors, you now have to use **complex impedance, Z** .

❖ For series connected impedances:

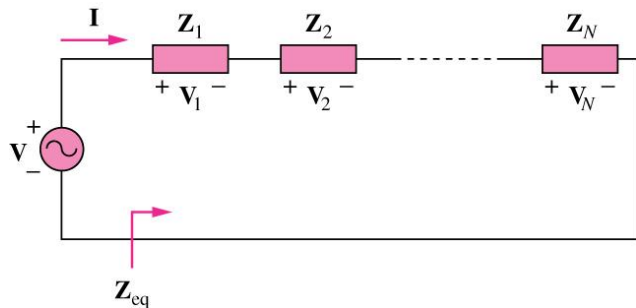

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N \quad (\text{Equivalent Impedance})$$

❖ Total impedance for parallel circuit:

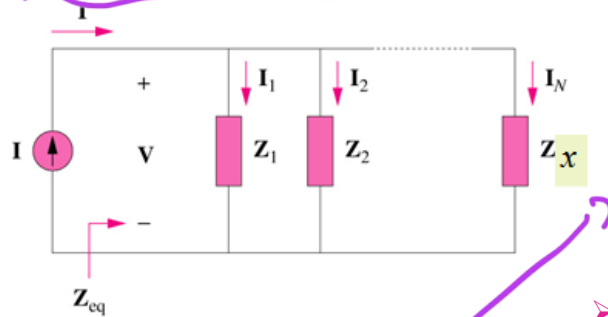

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$$

- The impedance can be easily computed from the admittance:

$$\frac{1}{Z_{total}} = \sum \frac{1}{Z_x} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_x} \Rightarrow$$


$$Z_{total} = \left(\sum \frac{1}{Z_x} \right)^{-1} = \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_x} \right)^{-1}$$

$$Z_{total} = \frac{1}{Y_{total}} = [Y_{total}]^{-1}$$

$$\therefore Y_{total} = (Y_1 + Y_2 + \dots + Y_x)$$


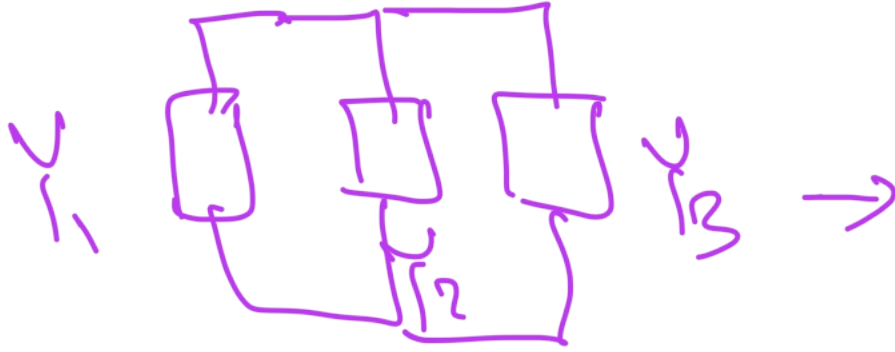
$$Z = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$



$$Y = Y_1 + Y_2 + Y_3$$

$$Y_1 = \frac{1}{Z_1} \quad Y_2 = \frac{1}{Z_2} \quad Y_3 = \frac{1}{Z_3}$$


$$Z = \frac{1}{Y_{tot}}$$



C-TOTAL IMPEDANCE FOR AC CIRCUITS

1-Example of series circuit:

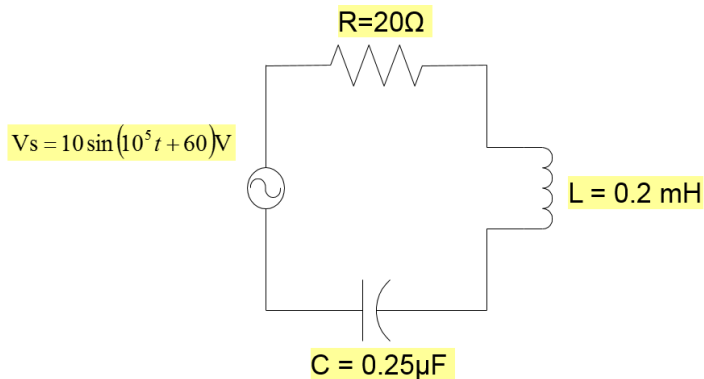- a- Find Total Impedance
- b- Draw Impedance Triangle (Phasor Diagram).
- c- Find i_s , v_R , v_C , v_L
- d- Find v_R , v_C , v_L using Voltage Divider





✓ Solution

- a- The total Impedance

$$\begin{aligned} Z_T &= \sum Z_R + Z_L + Z_C \\ &= 20 + j20 + (-j40) \\ &= (20 - j20) \Omega \\ &= 28.28 \angle -45^\circ \Omega \end{aligned}$$

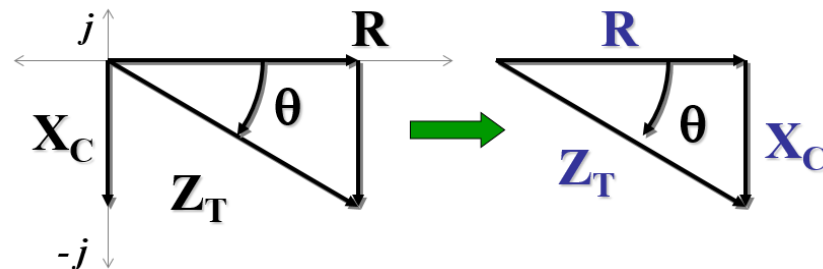- b- The Impedance Triangle (Phasor Diagram)



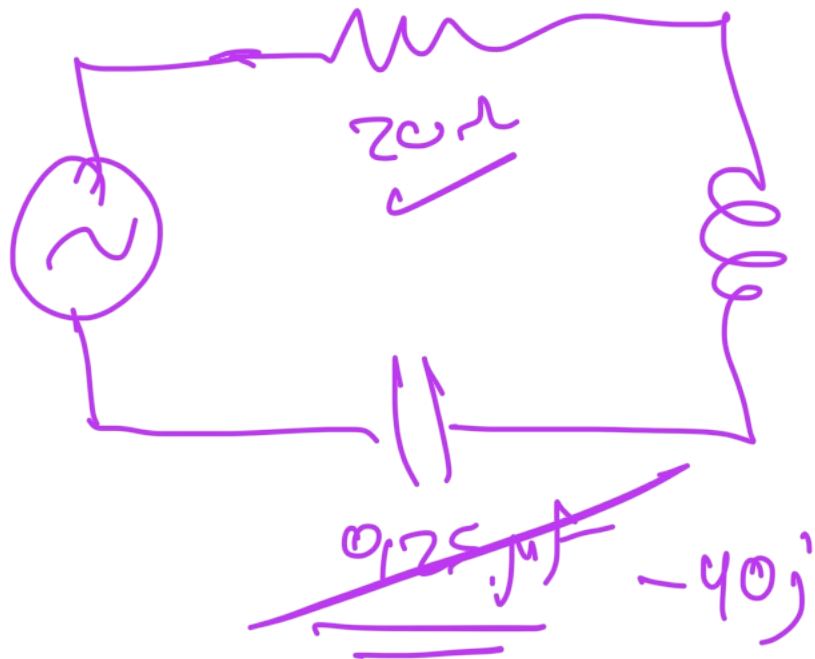

$0,25 \times 10^{-6} \times 10^6$

~~$0,2 mH$~~
 z_{0j}


$$v = 10 \sin(10^6 t + 60)$$

 $\omega = 10^6$

$$z_R = R$$

$$z_L = j\omega L$$

$$z_C = \frac{1}{j\omega C}$$

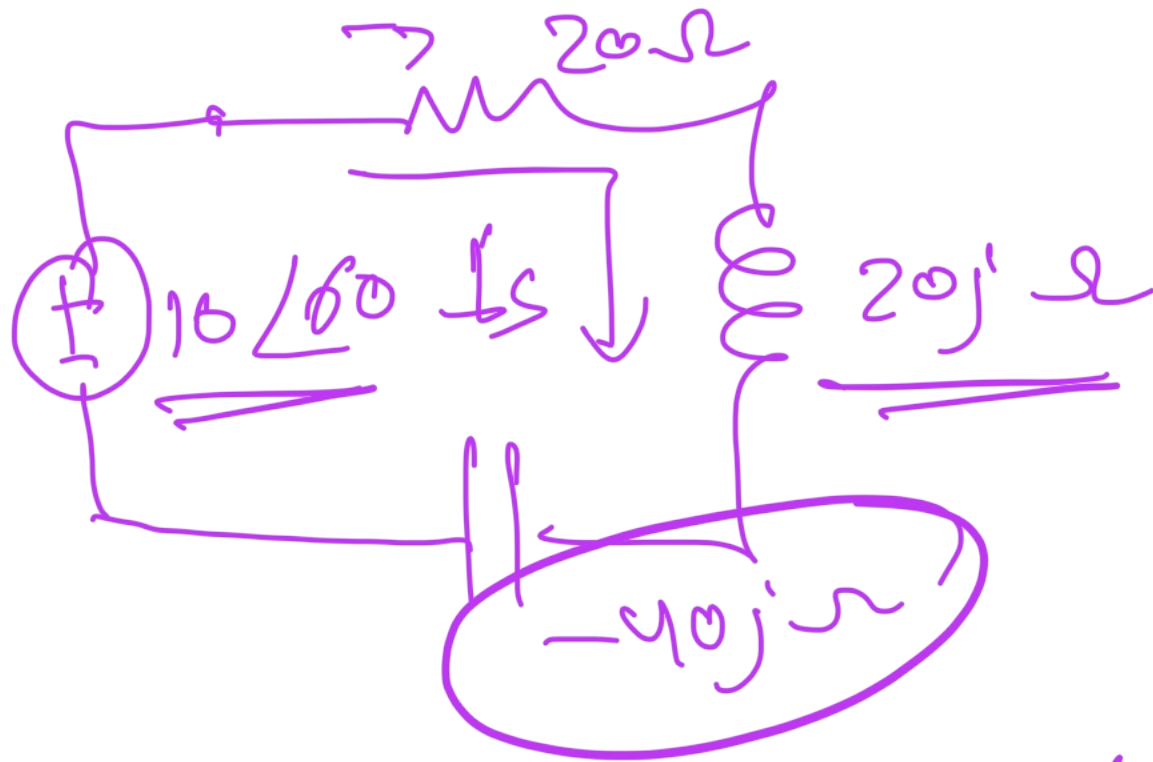

Series

$$V_s = I_s Z_T \Rightarrow I_s = \frac{V_s}{Z_T}$$

$$I_s = \frac{10 \angle 60^\circ}{20 + 20j - 40j} = 0,354 \angle 105^\circ \text{ A}$$

$$V_R = IR = 0,354 \angle 105^\circ \times 20 = \underline{\underline{7,08 \angle 105^\circ}}$$

$$V_L = IZ_L = 0,354 \angle 105^\circ \times 20j = \underline{\underline{7,08 \angle 165^\circ}}$$

$$V_C = IZ_C = 0,354 \angle 105^\circ \times -j40 = \underline{\underline{14,16 \angle 15^\circ}}$$

Voltage divider Series

$$V_R = \frac{20}{20 + 20j - 40j} \times 10 \angle 60^\circ = 7.08 \angle 10^\circ$$

$$V_L = \frac{20j}{20 + 20j - 40j} \times 10 \angle 60^\circ = 7.08 \angle -16^\circ$$

$$V_C = \frac{-40j}{20 + 20j - 40j} \times 10 \angle 60^\circ = 14.16 \angle 1^\circ$$



C-TOTAL IMPEDANCE FOR AC CIRCUITS $-180 \leq \theta \leq 180$


1-Example of series circuit:

a- Find Total Impedance

b- Draw Impedance Triangle (Phasor Diagram)

c- Find i_s , v_R , v_C , v_L

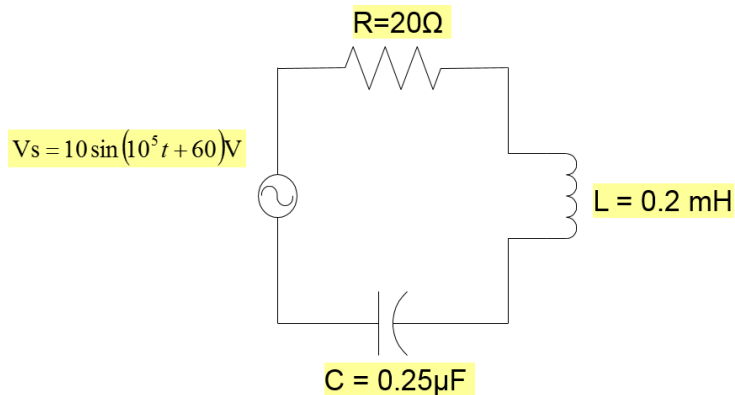d- Find v_R , v_C , v_L using Voltage Divider



✓ Solution

➤ c- i_s , v_R , v_C , v_L :

$$i_s = \frac{v_s}{Z_T} = \frac{10 \angle 60^\circ}{28.28 \angle -45^\circ} = 353 \angle 105^\circ \text{ mA}$$

$$v_s = i_s \cdot Z_R = (353 \angle 105^\circ \text{ mA}) \cdot (20 \Omega) = 7 \angle 105^\circ \text{ V}$$

$$v_L = i_s \cdot Z_L = (353 \angle 105^\circ \text{ mA}) \cdot (20 \angle 90^\circ \Omega) = 7 \angle 195^\circ \text{ V}$$

$$v_C = i_s \cdot Z_C = (353 \angle 105^\circ \text{ mA}) \cdot (40 \angle -90^\circ \Omega) = 7 \angle 15^\circ \text{ V}$$



C-TOTAL IMPEDANCE FOR AC CIRCUITS


1-Example of series circuit:

a- Find Total Impedance

b- Draw Impedance Triangle (Phasor Diagram)

c- Find i_s , v_R , v_C , v_L

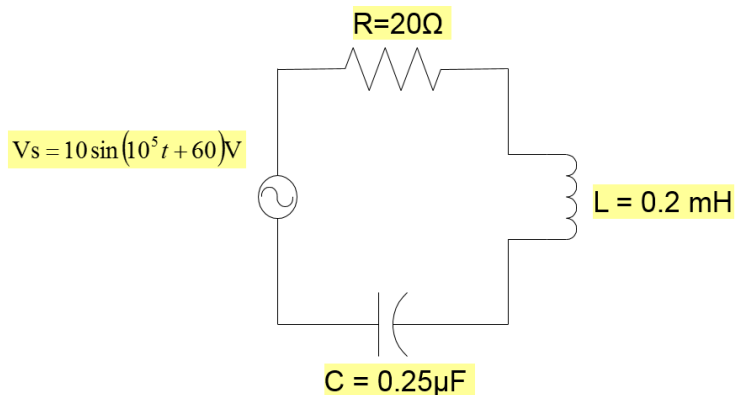d- Find v_R , v_C , v_L using Voltage Divider



✓ Solution

➤ d- Find v_R , v_C , v_L using Voltage Divider

➤ Voltage divider still works, too.

$$v_R = \frac{Z_R}{Z_T} v_s = \frac{(20 \Omega \angle 0^\circ)}{(28.28 \angle -45^\circ)} \cdot 10 \text{ V} \angle 60^\circ = 7 \angle 105^\circ$$
$$v_L = \frac{Z_L}{Z_T} v_s = \frac{(20 \Omega \angle 90^\circ)}{(28.28 \angle -45^\circ)} \cdot 10 \text{ V} \angle 60^\circ = 7 \angle 195^\circ$$
$$v_C = \frac{Z_C}{Z_T} v_s = \frac{(20 \Omega \angle -90^\circ)}{(28.28 \angle -45^\circ)} \cdot 10 \text{ V} \angle 60^\circ = 7 \angle 15^\circ$$



C-TOTAL IMPEDANCE FOR AC CIRCUITS


2-Example of Parallel circuit:

a- Find the total Impedance

b- Draw Impedance Triangle (Phasor Diagram)

c- Find i_s , v_R , v_C , v_L

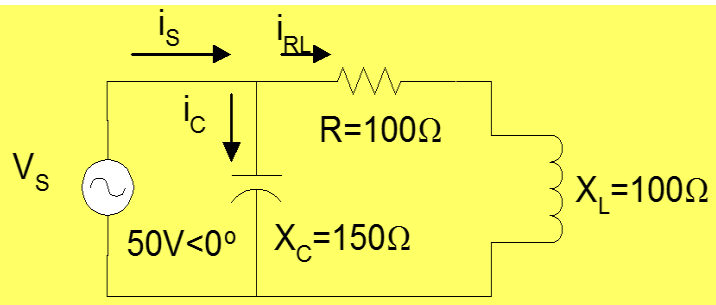d- Find v_R , v_C , v_L using Voltage Divider



✓ Solution ➤ a- The total Impedance

➤ The circuit given is already in frequency domain:


$$Z_R = 100\Omega \angle 0^\circ = 100 \Omega$$

$$Z_C = 150\Omega \angle -90^\circ = -j150 \Omega$$

$$Z_L = 100\Omega \angle 90^\circ = j100 \Omega$$



➤ **Circuit simplification**

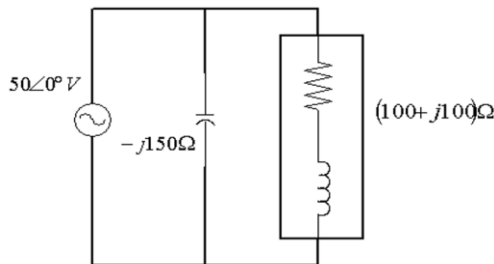



C-TOTAL IMPEDANCE FOR AC CIRCUITS


2-Example of Parallel circuit:

a- Find the total Impedance

b- Draw Impedance Triangle (Phasor Diagram)


c- Find i_s , v_R , v_C , v_L

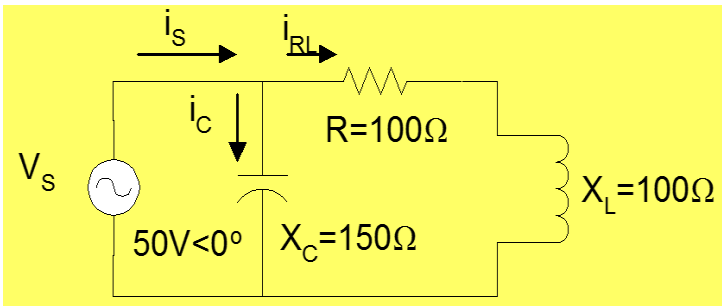d- Find v_R , v_C , v_L using Current Divider



✓ Solution ➤ a- The total Impedance

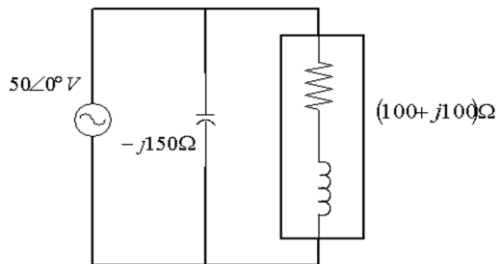➤ The circuit given is already in frequency domain:



$$\begin{aligned} Z_{total} &= (Z_C) \parallel (Z_R + Z_L) \\ &= (150 \angle -90^\circ) \parallel [(100) + (100 \angle 90^\circ)] \\ &= (150 \angle -90^\circ) \parallel (100 + j100) \\ &= (150 \angle -90^\circ) \parallel (141.42 \angle 45^\circ) \end{aligned}$$

$$\begin{aligned} \therefore Z_{total} &= [Y_{total}]^{-1} \\ &= \left[\frac{1}{150 \angle -90^\circ} + \frac{1}{141.42 \angle 45^\circ} \right]^{-1} \end{aligned}$$

$$\therefore Z_{total} = \left(\frac{1}{150} (\cos(90^\circ) + j \sin(90^\circ)) + \frac{1}{141.42} (\cos(-45^\circ) + j \sin(-45^\circ)) \right)^{-1}$$

$$= (0.005 + j0.0016)^{-1}$$

$$= \left(\sqrt{0.005^2 + 0.0016^2} \angle \tan^{-1}\left(\frac{0.0016}{0.005}\right) \right)^{-1}$$

$$= (0.00524 \angle 17.744^\circ)^{-1} \approx 190 \angle -18^\circ$$

$$\therefore Z_{total} \approx 180 - j60 \Omega$$



C-TOTAL IMPEDANCE FOR AC CIRCUITS


2-Example of Parallel circuit:

a- Find the total Impedance

b- Draw Impedance Triangle (Phasor Diagram)



c- Find i_s , v_R , v_C , v_L

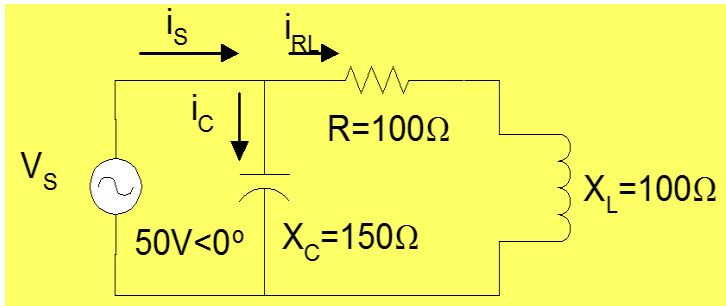d- Find v_R , v_C , v_L using Current Divider



✓ Solution ➤ b- The Impedance Triangle (Phasor Diagram)
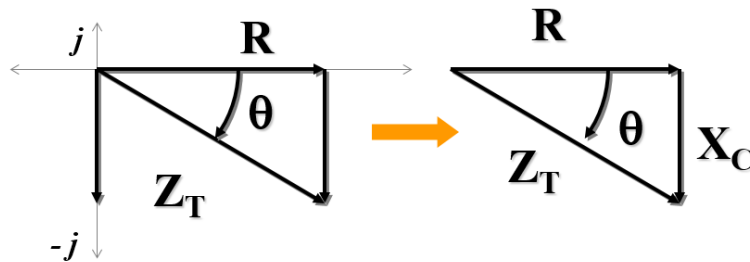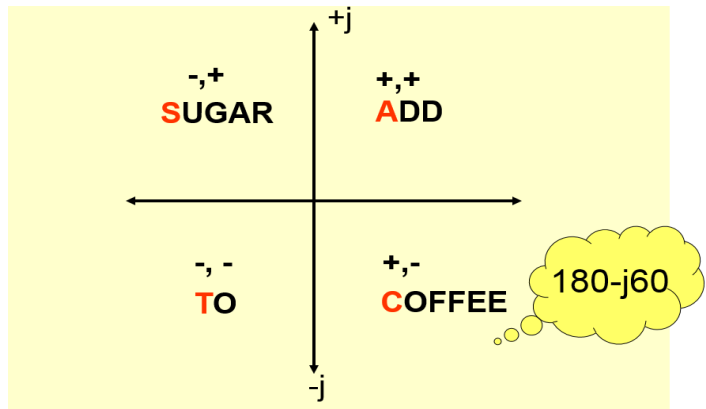
$$\therefore Z_{total} \simeq 180 - j60 \Omega$$





C-TOTAL IMPEDANCE FOR AC CIRCUITS


2-Example of Parallel circuit:

a- Find the total Impedance

b- Draw Impedance Triangle (Phasor Diagram)

c- Find i_s , v_R , v_C , v_L

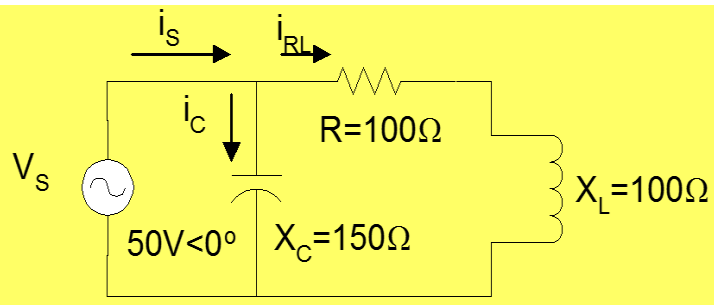d- Find v_R , v_C , v_L using Current Divider



✓ Solution ➤ c- i_s , v_R , v_C , v_L :

$$\therefore Z_{total} \simeq 180 - j60 \Omega$$

$$i_s = \frac{v_s}{Z_T} = \frac{50 \angle 0^\circ}{190 \angle -18^\circ} = 263 \angle 18^\circ \text{ mA}$$

$$v_S = v_C = (v_R + v_L) = 50 \angle 0^\circ \text{ V}$$

$$\Rightarrow i_C = \frac{v_S}{Z_C} = \frac{50 \angle 0^\circ}{150 \angle -90^\circ} = 333 \angle 90^\circ \text{ mA}$$

$$\Rightarrow i_{RL} = \frac{v_S}{Z_R + Z_L} = \frac{50 \angle 0^\circ}{100 + (100 \angle -90^\circ)} = 353 \angle -45^\circ \text{ mA}$$



C-TOTAL IMPEDANCE FOR AC CIRCUITS


2-Example of Parallel circuit:

a- Find the total Impedance

b- Draw Impedance Triangle (Phasor Diagram)

c- Find i_s , v_R , v_C , v_L

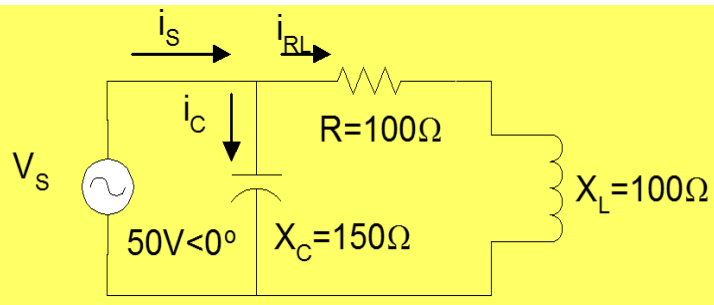d- Find v_R , v_C , v_L using Current Divider



✓ Solution ➤ d- Find v_R , v_C , v_L using Current Divider

$$i_c = \frac{Z_T}{Z_C} i_S = \frac{(190 \angle -18^\circ)}{(150 \angle -90^\circ)} \cdot (263 \angle 18^\circ \text{ mA})$$
$$= 333 \angle 90^\circ \text{ mA}$$

$$i_{RL} = \frac{Z_T}{Z_R + Z_L} i_S = \frac{(190 \angle -18^\circ)}{(100)(100 \angle 90^\circ)} \cdot (263 \angle 18^\circ \text{ mA})$$
$$= 353 \angle -45^\circ \text{ mA}$$



D-Impedance as a Function of Frequency

- The Impedance Z of a circuit is a function of the frequency.

Element	Impedance
L	$Z = j\omega L$
C	$Z = \frac{1}{j\omega C}$

- Inductor is **SHORT CIRCUIT** at DC and **OPEN CIRCUIT** at high frequencies.
Capacitor is **OPEN CIRCUIT** at DC and **SHORT CIRCUIT** at high frequencies.

$$Z_L = j\omega L$$


$$Z_L \rightarrow 0 \quad \omega \rightarrow 0 \quad (\text{Short at DC})$$

$$Z_L \rightarrow \infty \quad \omega \rightarrow \infty \quad (\text{Open as } \omega \rightarrow \infty)$$


$$Z_C = \frac{1}{j\omega C}$$

$$Z_C \rightarrow \infty \quad \omega \rightarrow 0 \quad (\text{Open at DC})$$
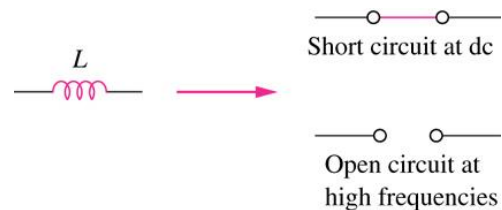
$$Z_C \rightarrow 0 \quad \omega \rightarrow \infty \quad (\text{Open as } \omega \rightarrow \infty)$$



(a)

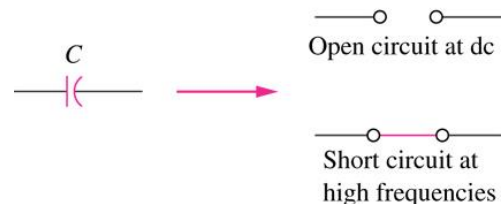

(b)



AC Analysis Techniques

AC Analysis Techniques



- Both **KVL** and **KCL** are hold in Phasor domain or more commonly called frequency domain.
- Moreover, the variables to be handled are phasors, which are complex numbers.
- All the mathematical operations involved are now in complex domain.
- **All DC circuit analysis principles apply to AC circuits.**
 - Voltage Division
 - Current Division
 - Circuit Reduction
 - Impedance equivalence
 - Y-Delta Transformation

Example 22: Voltage Divider Rule

➤ Calculate the v_0 in the given circuit

➤ Solution:

In the frequency domain,

the voltage source is $V_s = 10\angle 75^\circ$

the 0.5-H inductor is $j\omega L = j(10)(0.5) = j5$

the $\frac{1}{20}$ -F capacitor is $\frac{1}{j\omega C} = \frac{1}{j(10)(1/20)} = -j2$

Let $Z_1 =$ impedance of the 0.5-H inductor in parallel with the 10- Ω resistor


and $Z_2 =$ impedance of the (1/20)-F capacitor

$$Z_1 = 10 \parallel j5 = \frac{(10)(j5)}{10 + j5} = 2 + j4 \quad \text{and} \quad Z_2 = -j2$$

$$V_o = Z_2 / (Z_1 + Z_2) V_s$$


$$V_o = \frac{-j2}{2 + j4 - j2} (10\angle 75^\circ) = \frac{-j(10\angle 75^\circ)}{1 + j} = \frac{10\angle(75^\circ - 90^\circ)}{\sqrt{2}\angle 45^\circ} = 7.071\angle -60^\circ$$

$$v_o(t) = \underline{\underline{7.071 \cos(10t - 60^\circ) \text{ V}}}$$

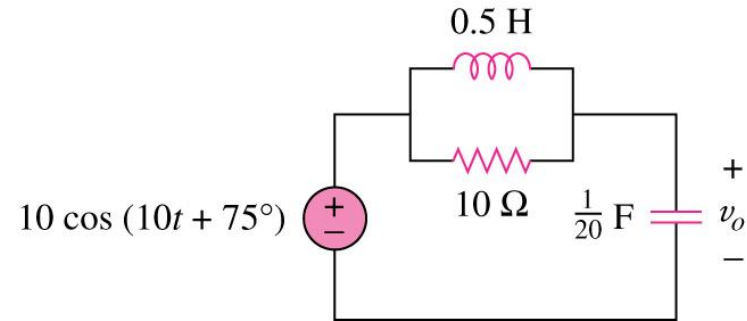


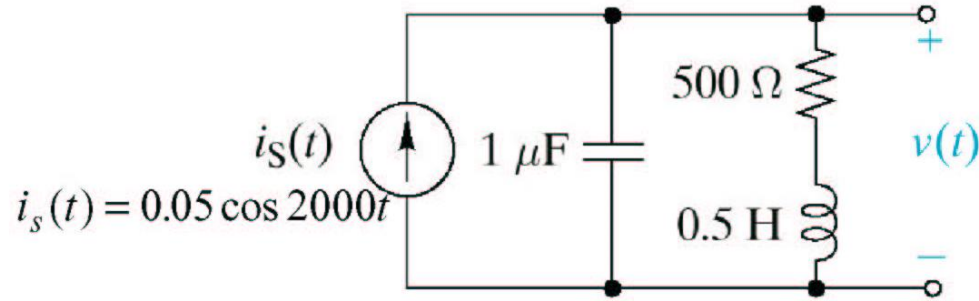Example 23: Current Divider Rule

Find I_1 and I_2 in phasor domain, then convert them into time domain




Solution:

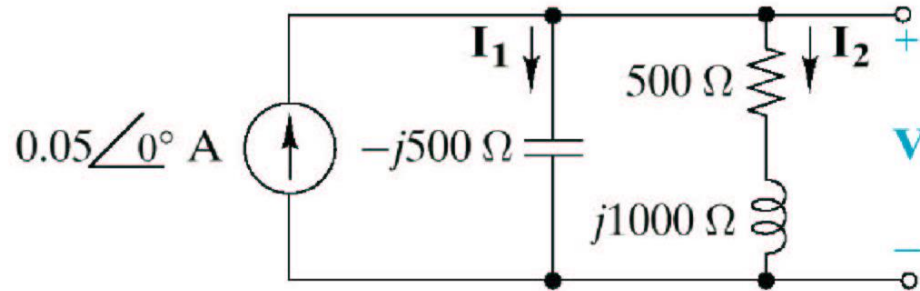

Example 23: Current Divider Rule

Solution (Cont.):

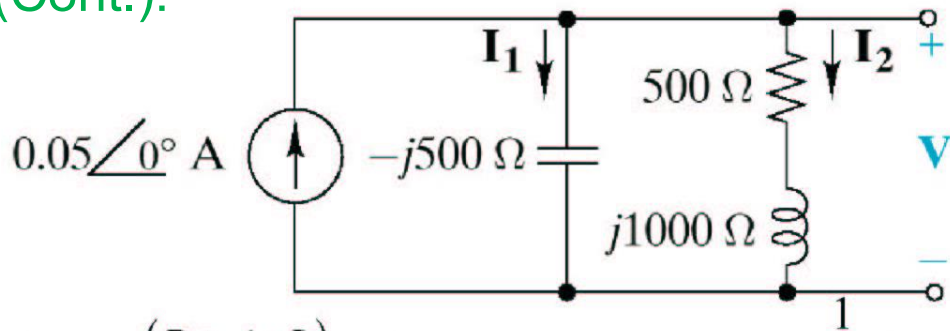

$$\hat{I}_1 = \frac{(R + j\omega L)}{R + j\omega L + \frac{1}{j\omega C}} \hat{I}$$

$$\hat{I}_1 = \frac{(500 + j1000)}{500 + j1000 - j500} 0.05 \angle 0^\circ$$

$$I_1 = 0.079 \angle 18.4^\circ \text{ A}$$

$$i_1(t) = 79 \cos(2000t + 18.4^\circ) \text{ mA}$$


$$\hat{I}_2 = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} \hat{I}$$

$$\hat{I}_2 = \frac{-j500}{500 + j1000 - j500} 0.05 \angle 0^\circ$$

$$I_2 = 0.03535 \angle -135^\circ \text{ A}$$

$$i_2(t) = 35.35 \cos(2000t - 135^\circ) \text{ mA}$$

Delta-Wye ($\Delta - Y$) Transformation

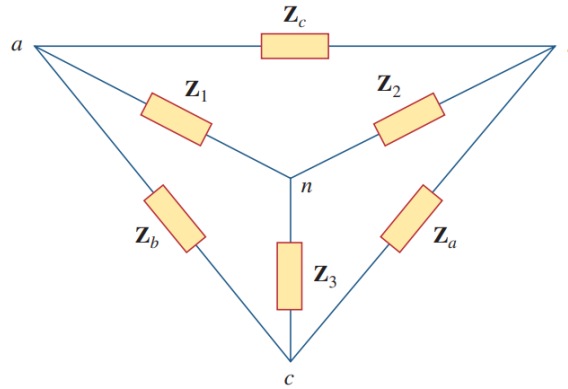

Y- Δ Conversion:

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

Δ -Y Conversion:

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

Example 24- ($\Delta - Y$) Transformation

Find current \mathbf{I} in the circuit

Solution:

$$\mathbf{Z}_{an} = \frac{j4(2 - j4)}{j4 + 2 - j4 + 8} = \frac{4(4 + j2)}{10} = (1.6 + j0.8) \Omega$$



$$\mathbf{Z}_{bn} = \frac{j4(8)}{10} = j3.2 \Omega, \quad \mathbf{Z}_{cn} = \frac{8(2 - j4)}{10} = (1.6 - j3.2) \Omega$$

The total impedance at the source terminals is

$$\begin{aligned} \mathbf{Z} &= 12 + \mathbf{Z}_{an} + (\mathbf{Z}_{bn} - j3) \parallel (\mathbf{Z}_{cn} + j6 + 8) \\ &= 12 + 1.6 + j0.8 + (j0.2) \parallel (9.6 + j2.8) \\ &= 13.6 + j0.8 + \frac{j0.2(9.6 + j2.8)}{9.6 + j3} \\ &= 13.6 + j1 = 13.64 \angle 4.204^\circ \Omega \end{aligned}$$


The desired current is
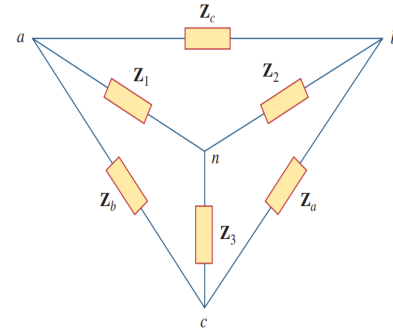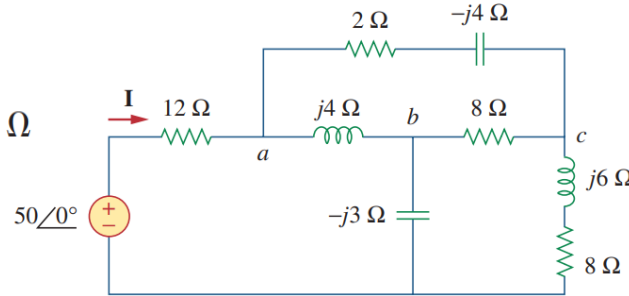
$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{50 \angle 0^\circ}{13.64 \angle 4.204^\circ} = 3.666 \angle -4.204^\circ \text{ A}$$




Δ -Y Conversion:
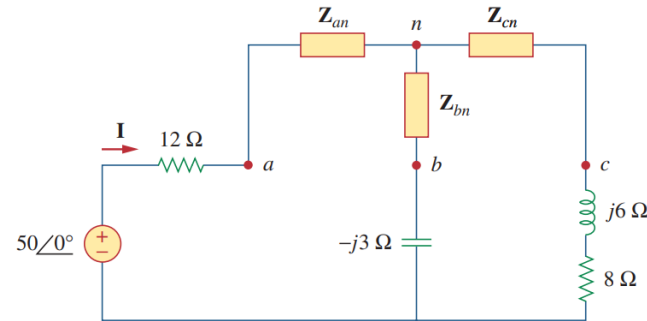
$$\begin{aligned} \mathbf{Z}_1 &= \frac{\mathbf{Z}_b \mathbf{Z}_c}{\mathbf{Z}_a + \mathbf{Z}_b + \mathbf{Z}_c} \\ \mathbf{Z}_2 &= \frac{\mathbf{Z}_c \mathbf{Z}_a}{\mathbf{Z}_a + \mathbf{Z}_b + \mathbf{Z}_c} \\ \mathbf{Z}_3 &= \frac{\mathbf{Z}_a \mathbf{Z}_b}{\mathbf{Z}_a + \mathbf{Z}_b + \mathbf{Z}_c} \end{aligned}$$





Frequency Domain Analysis (Using Phasor)



Nodal Analysis
Mesh Analysis
Superposition,
Source transformation
Thevenin theorem, and
Norton theorem

Example 25- Nodal Analysis

Find i_x in the following circuit using nodal analysis

Solution

We first convert the circuit to the frequency domain:

$$20 \cos 4t \Rightarrow 20 \angle 0^\circ, \quad \omega = 4 \text{ rad/s}$$

$$1 \text{ H} \Rightarrow j\omega L = j4$$

$$0.5 \text{ H} \Rightarrow j\omega L = j2$$



$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j2.5$$

Applying KCL at node 1,

$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$

or

$$(1 + j1.5)\mathbf{V}_1 + j2.5\mathbf{V}_2 = 20$$

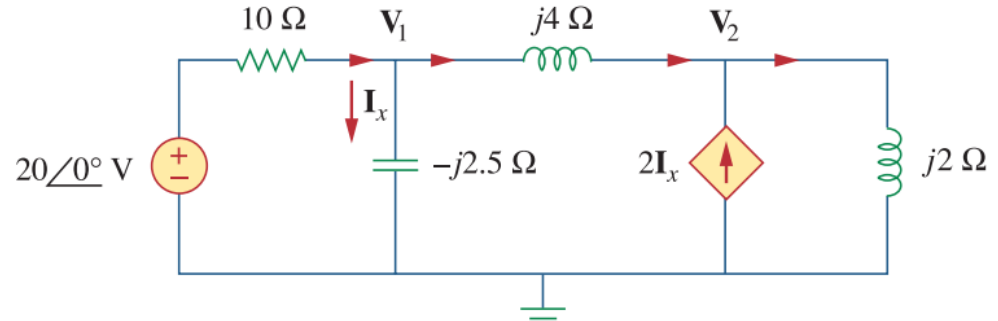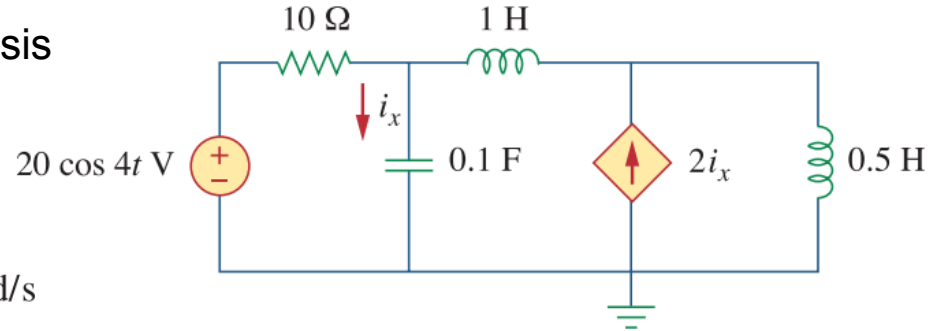

Example 25- Nodal Analysis

Find i_x in the following circuit using nodal analysis

Solution (continue)

At node 2,


$$(1 + j1.5)V_1 + j2.5V_2 = 20$$

$$2\mathbf{I}_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

But $\mathbf{I}_x = V_1 / -j2.5$. Substituting this gives

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$11V_1 + 15V_2 = 0$$

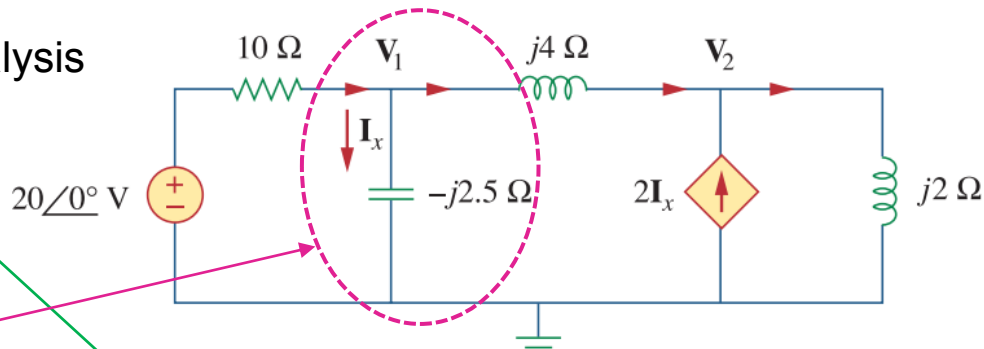

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$V_1 = 18.97 / \underline{18.43^\circ} \text{ V}$$

$$V_2 = 13.91 / \underline{198.3^\circ} \text{ V}$$

The current \mathbf{I}_x is given by

$$\mathbf{I}_x = \frac{V_1}{-j2.5} = \frac{18.97 / \underline{18.43^\circ}}{2.5 / \underline{-90^\circ}} = 7.59 / \underline{108.4^\circ} \text{ A}$$

$$\longrightarrow i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

Example 26- Mesh Analysis

Find I_o in the following circuit using mesh analysis

Solution

Applying KVL to mesh 1, we obtain

$$\begin{aligned} &\text{➤ } 8I_1 + j10(I_1 - I_3) - 2j(I_1 - I_2) = 0 \\ (8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 &= 0 \end{aligned}$$


$$\text{For mesh 2, } \text{➤ } 20\angle 90^\circ + 4I_2 - j2(I_2 - I_3) - j2(I_2 - I_1) = 0$$

$$(4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0$$

For mesh 3, $I_3 = 5$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$
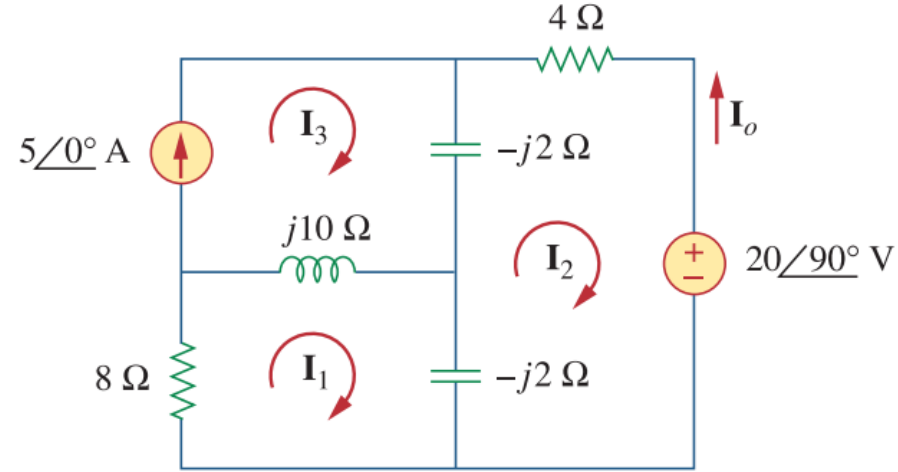
$$I_2 = \frac{\Delta_2}{\Delta} = \frac{416.17\angle -35.22^\circ}{68} = 6.12\angle -35.22^\circ \text{ A} \longrightarrow I_o = -I_2 = 6.12\angle 144.78^\circ \text{ A}$$




Superposition Theorem

When a circuit has sources operating at different frequencies,


- The separate phasor circuit for each frequency must be solved independently, and
- The total response is the sum of time-domain responses of all the individual phasor circuits.

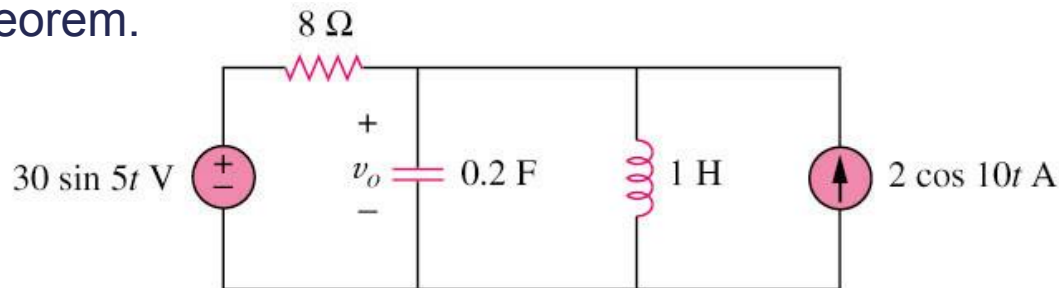Example Calculate v_o in the circuit of figure shown below using the superposition theorem.




Answer: $V_o = 4.631 \sin(5t - 81.12) + 1.051 \cos(10t - 86.24) \text{ V}$

Source Transformation

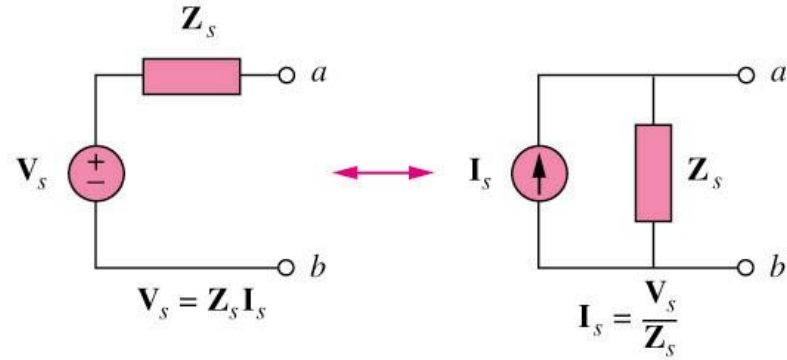

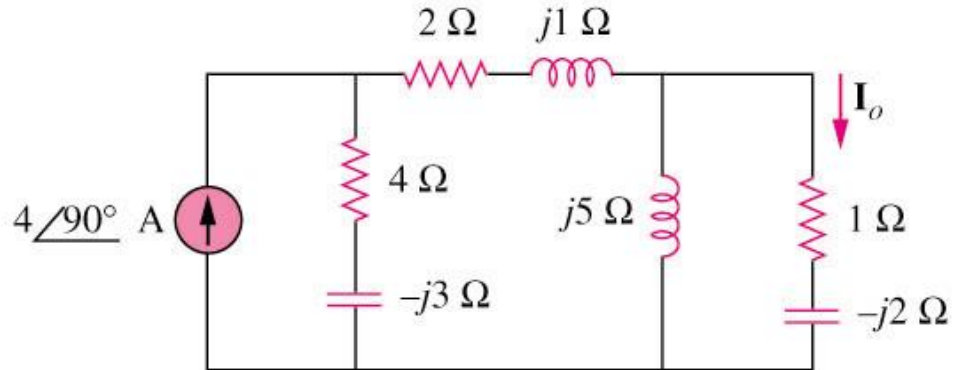
Example Find I_o in the circuit of figure below using the concept of source transformation.




Answer: $I_o = \underline{3.288 + j99.46 \text{ A}}$

Thevenin and Norton Theorems in AC circuits

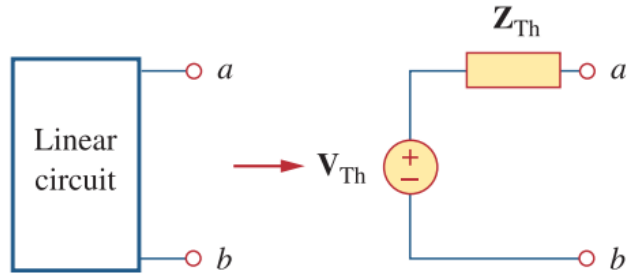- Thevenin's and Norton theorems are applied to ac circuits in the same way as they are to DC circuits
- The **ONLY additional effort** is the need to manipulate **complex numbers**.



Thevenin equivalent.

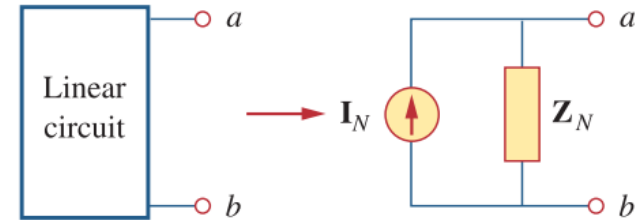


Norton equivalent.

Where; $V_{Th} = V_{ab-OC}$ is the **open circuit voltage (PHASOR)** between terminals a-b, $I_N = I_{ab-SC}$ is the **short circuit current (PHASOR)** through the terminals a-b, and Z_{Th} is the **input or equivalent IMPEDANCE** at the terminals **when the independent source are turn off**.


How to Find Thevenin Equivalent Circuit in AC circuits

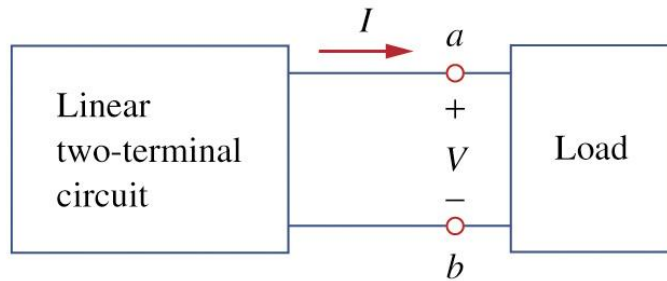- ❖ First, **Open the circuit** (remove the load) at the **points** of interest **a-b**
 - 1- V_{th} = Open circuit voltage (keep all sources intact). Note: V_{th} is Phasor
 - 2- Z_{th} = Open circuit **equivalent Impedance** appears at terminals **a-b** while all **independent sources=0** (voltage source=SC, current source=OC).



Original Circuit

≡

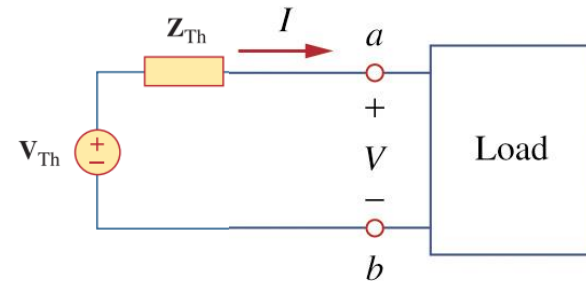

Thevenin equivalent circuit

Example 10.8- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.


Solution

1- For Z_{th}

$$\mathbf{Z}_1 = -j6 \parallel 8 = \frac{-j6 \times 8}{8 - j6} = 2.88 - j3.84 \Omega$$

$$\mathbf{Z}_2 = 4 \parallel j12 = \frac{j12 \times 4}{4 + j12} = 3.6 + j1.2 \Omega$$

$$\mathbf{Z}_{Th} = \mathbf{Z}_1 + \mathbf{Z}_2 = 6.48 - j2.64 \Omega$$

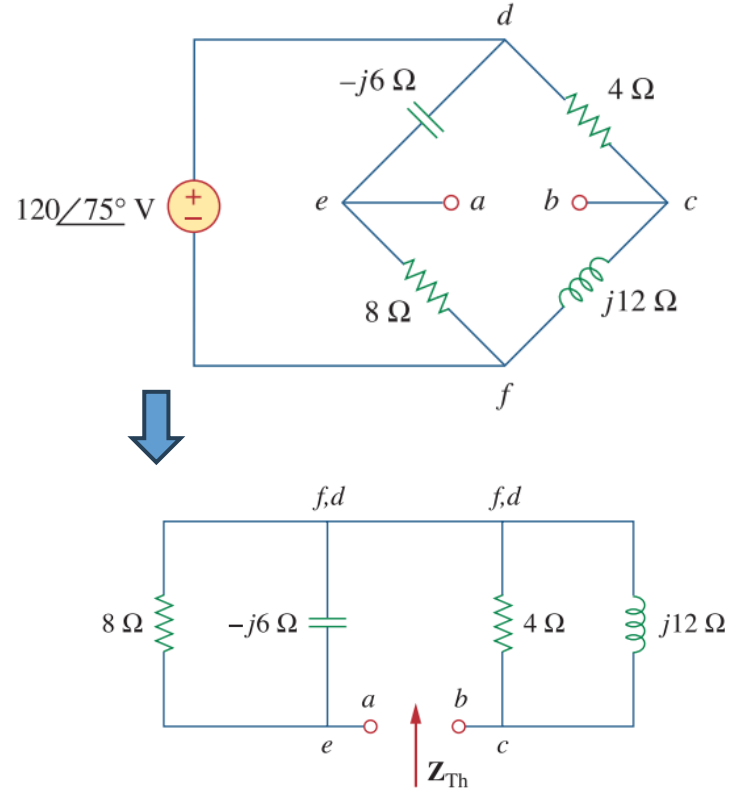

Example 10.8- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution (continue)



2- For V_{th}

$$\mathbf{I}_1 = \frac{120 \angle 75^\circ}{8 - j6} \text{ A}, \quad \mathbf{I}_2 = \frac{120 \angle 75^\circ}{4 + j12} \text{ A}$$

Applying KVL around loop $bcdeab$

$$\mathbf{V}_{Th} - 4\mathbf{I}_2 + (-j6)\mathbf{I}_1 = 0$$

$$\begin{aligned} \mathbf{V}_{Th} = 4\mathbf{I}_2 + j6\mathbf{I}_1 &= \frac{480 \angle 75^\circ}{4 + j12} + \frac{720 \angle 75^\circ + 90^\circ}{8 - j6} \\ &= 37.95 \angle 3.43^\circ + 72 \angle 201.87^\circ \\ &= -28.936 - j24.55 = 37.95 \angle 220.31^\circ \text{ V} \end{aligned}$$

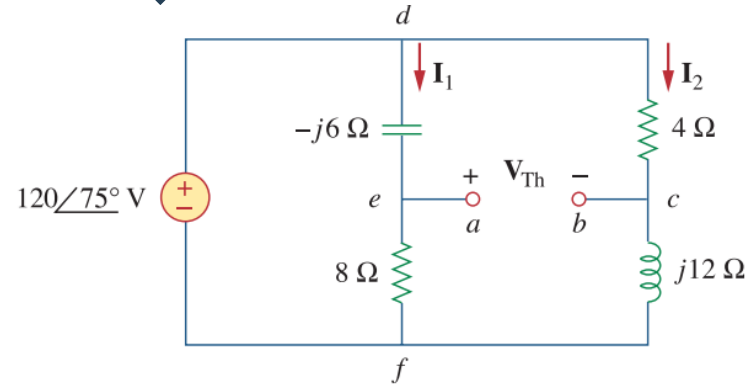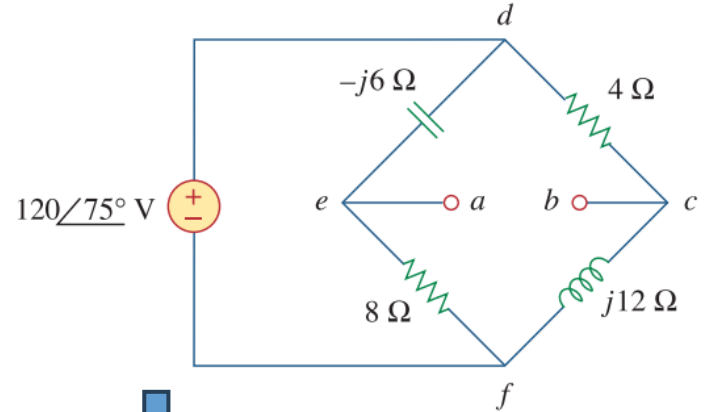

Example 10.9- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution

1- For V_{th}

To find V_{Th} , we apply KCL at node 1

$$15 = \mathbf{I}_o + 0.5\mathbf{I}_o \quad \Rightarrow \quad \mathbf{I}_o = 10 \text{ A}$$

Applying KVL to the loop on the right-hand side



$$-\mathbf{I}_o(2 - j4) + 0.5\mathbf{I}_o(4 + j3) + \mathbf{V}_{Th} = 0$$

or

$$\mathbf{V}_{Th} = 10(2 - j4) - 5(4 + j3) = -j55$$

Thus, the Thevenin voltage is

$$\mathbf{V}_{Th} = 55 \angle -90^\circ \text{ V}$$

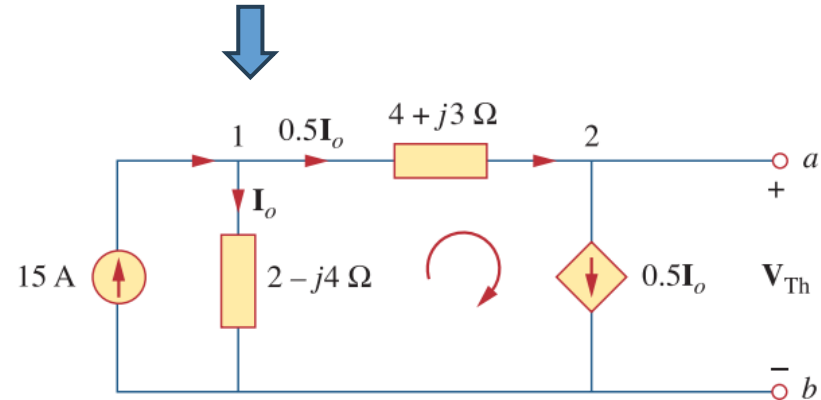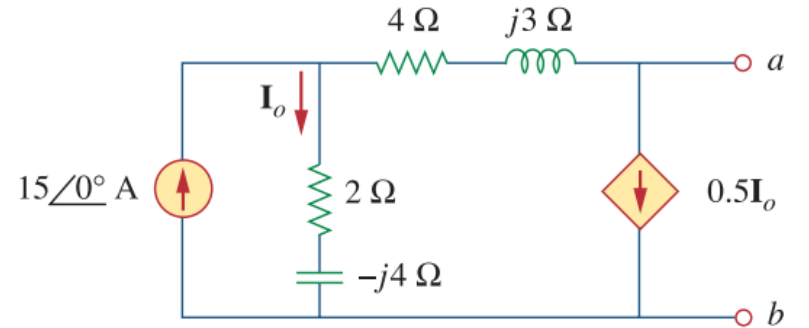

Example 10.9- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution (continue)

2- For Z_{th}

To obtain Z_{Th} , we remove the independent source. Due to the presence of the dependent current source, we connect a 3-A current source (3 is an arbitrary value chosen for convenience here, a number divisible by the sum of currents leaving the node) to terminals $a-b$



$$3 = \mathbf{I}_o + 0.5\mathbf{I}_o \quad \Rightarrow \quad \mathbf{I}_o = 2 \text{ A}$$

Applying KVL to the outer loop in Fig. 10.26(b) gives

$$\mathbf{V}_s = \mathbf{I}_o(4 + j3 + 2 - j4) = 2(6 - j)$$

The Thevenin impedance is
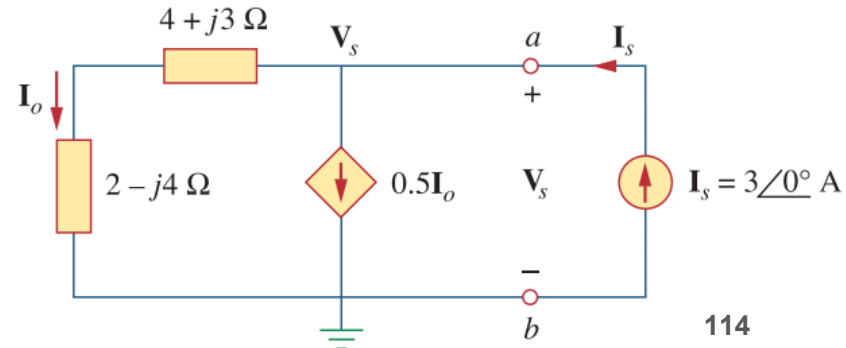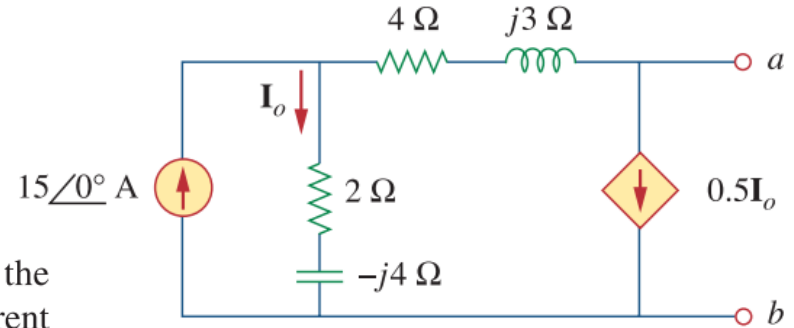
$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_s}{\mathbf{I}_s} = \frac{2(6 - j)}{3} = 4 - j0.6667 \Omega$$



Trigonometric Identities



- Sine and cosine form conversions.

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$


$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$


Where

$$C = \sqrt{A^2 + B^2} \quad \text{and} \quad \theta = \tan^{-1} \frac{B}{A}$$

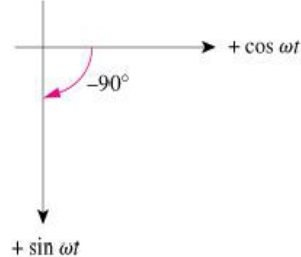Graphically relating sine and cosine functions.


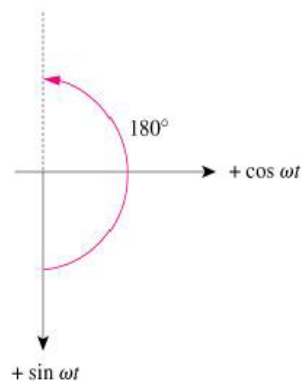
$$\cos(\omega t - 90^\circ) = \sin \omega t$$



$$\sin(\omega t + 180^\circ) = -\sin \omega t$$



End of Lecture



Questions?