

$$Z_3 = \frac{8 \times j^4}{10} = 3,2j$$

Frequency Domain Analysis (Using Phasor)

Nodal Analysis ✓
Mesh Analysis ✓
Superposition, ✓
Source transformation ✓
Thevenin theorem, and
Norton theorem ✓

Phasor
complex

Example 25- Nodal Analysis

Find i_x in the following circuit using nodal analysis

Solution

We first convert the circuit to the frequency domain:



$$\begin{aligned}
 20 \cos 4t &\Rightarrow 20 \angle 0^\circ, & \omega &= 4 \text{ rad/s} \\
 1 \text{ H} &\Rightarrow j\omega L = j4 \\
 0.5 \text{ H} &\Rightarrow j\omega L = j2 \\
 0.1 \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j2.5
 \end{aligned}$$

Applying KCL at node 1,

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

or

$$(1 + j1.5)V_1 + j2.5V_2 = 20$$

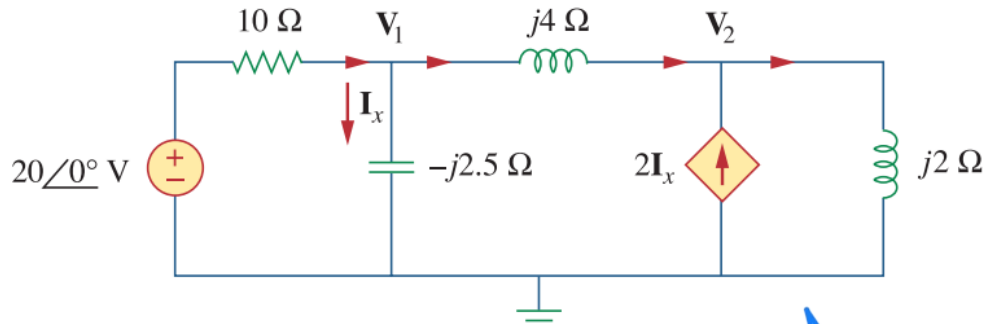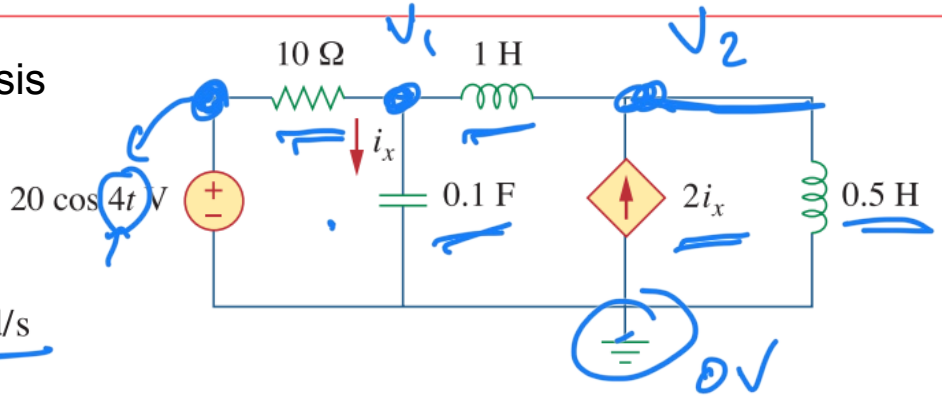

$$Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$

node ②

$$\frac{V_2}{j4} + \frac{V_2 - 0}{j2} + -2(0,4jV_1) = 0$$

$$\boxed{\frac{-11}{20}j} V_1 + \boxed{\frac{-2}{10}j} V_2 = \boxed{0} \rightarrow \text{②}$$

$$V_1 = \frac{ED - BF}{AD - BC} = \underline{18 + j6} \text{ V} = 18,97 \angle 18,43^\circ \text{ V}$$

$$V_2 = \frac{AF - EC}{AD - BC} = \underline{-13,2 - j4,4} \text{ V} = 13,91 \angle -16,57^\circ \text{ V}$$

$$\vec{I}_X = j_{0,4} \times (18 + j6) = 7,589 \angle 108,43$$

$$i_X(t) = 7,589 \cos(4t + 108,43) \text{ A}$$

Example 25- Nodal Analysis

Find i_x in the following circuit using nodal analysis

Solution (continue)

$$(1 + j1.5)V_1 + j2.5V_2 = 20$$


At node 2,

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

But $I_x = V_1 / -j2.5$. Substituting this gives

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$11V_1 + 15V_2 = 0$$

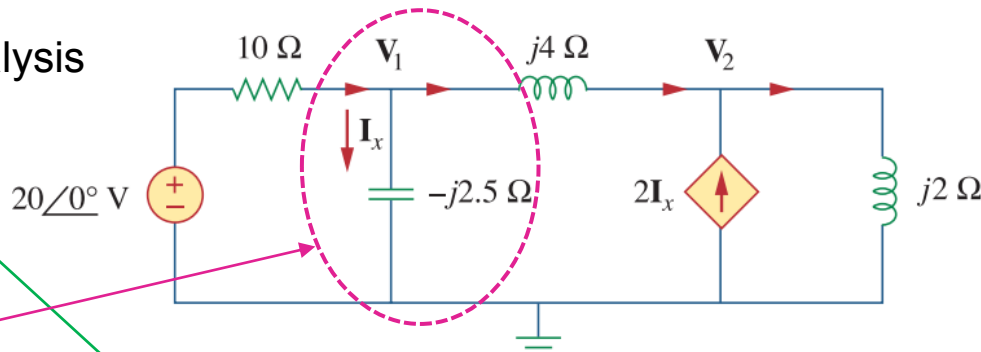

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

E
F

$$V_1 = 18.97 / \underline{18.43^\circ} \text{ V}$$

$$V_2 = 13.91 / \underline{198.3^\circ} \text{ V}$$

The current I_x is given by

$$I_x = \frac{V_1}{-j2.5} = \frac{18.97 / \underline{18.43^\circ}}{2.5 / \underline{-90^\circ}} = 7.59 / \underline{108.4^\circ} \text{ A}$$

$$\longrightarrow i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

Example 26- Mesh Analysis

Find I_o in the following circuit using mesh analysis

Solution

Applying KVL to mesh 1, we obtain

$$\begin{aligned} &\text{➤ } 8I_1 + j10(I_1 - I_3) - 2j(I_1 - I_2) = 0 \\ (8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 &= 0 \end{aligned}$$


$$\text{For mesh 2, } \text{➤ } 20\angle 90^\circ + 4I_2 - j2(I_2 - I_3) - j2(I_2 - I_1) = 0$$

$$(4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0$$

For mesh 3, $I_3 = 5$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$
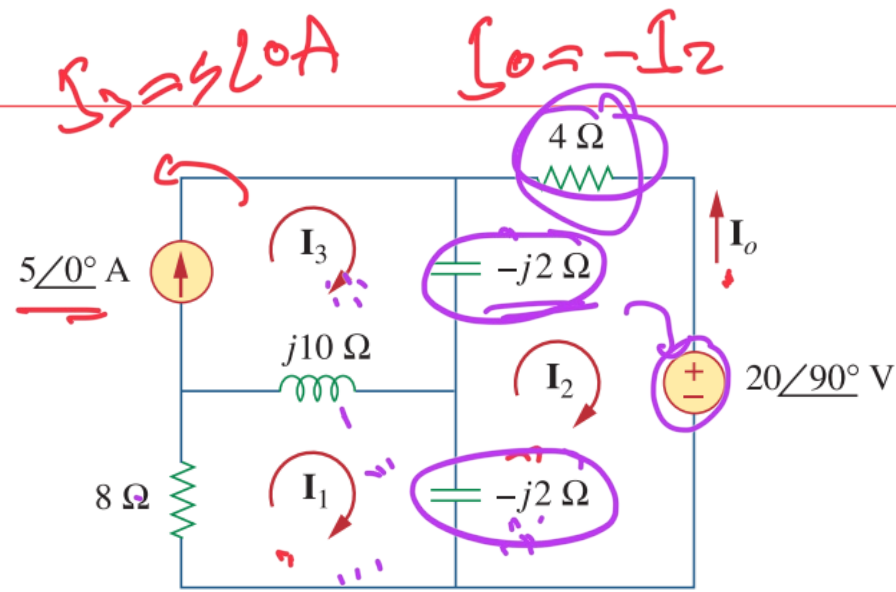
$$I_2 = \frac{\Delta_2}{\Delta} = \frac{416.17 \angle -35.22^\circ}{68} = 6.12 \angle -35.22^\circ \text{ A} \longrightarrow I_o = -I_2 = 6.12 \angle 144.78^\circ \text{ A}$$



mesh ①

$$(8 + 8j)I_1 + (j2)I_2 - \underbrace{10\angle 90^\circ}_{F} = 0$$

$$\boxed{(8 + 8j)I_1 + (j2)I_2 = 50j} \rightarrow \text{①}$$

A B F

mesh ②

$$+(j2)I_1 + (4 - 4j)I_2 + \underbrace{j2(s)}_{F} + \underbrace{20\angle 90^\circ}_{F} = 0$$

$$\Rightarrow \boxed{(j2)I_1 + (4 - 4j)I_2 = -j30} \rightarrow \text{②}$$

C D F

$$I_1 = \frac{ED - BF}{AD - BC} = 3,59 \angle_{SS} A$$

$$I_2 = \frac{AF - EC}{AD - BC} = 6,12 \angle_{-3S, 22} A$$

$$I_0 = -I_2 = 6,12 \angle_{144, 78} A$$

Superposition Theorem


When a circuit has sources operating at different frequencies,

- The separate phasor circuit for each frequency must be solved independently, and
- The total response is the sum of time-domain responses of all the individual phasor circuits.

Example Calculate v_o in the circuit of figure shown below using the superposition theorem.

$$Z_L = j\omega L$$
$$Z_C = \frac{1}{j\omega C}$$

$\omega = 5$
Short

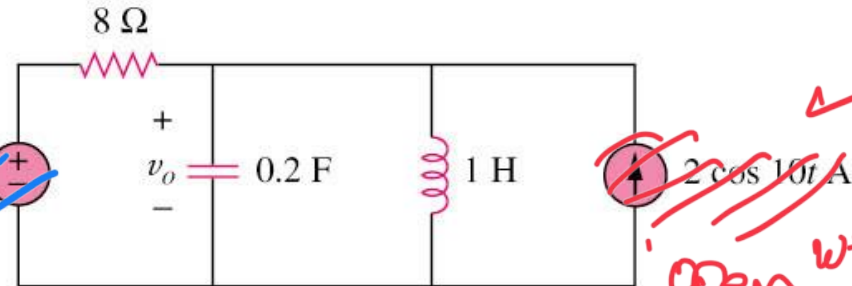

open $\omega = 10$

Answer: $v_o = 4.631 \sin(5t - 81.12) + 1.051 \cos(10t - 86.24) \text{ V}$




$$= \underline{\underline{-1,25j \Omega}}$$

voltage divider

$$V_o' = \frac{-1,25j}{-1,25j + 8} \cdot 30$$

$$V_o' = 4,631 \angle -89,12 \text{ V}$$

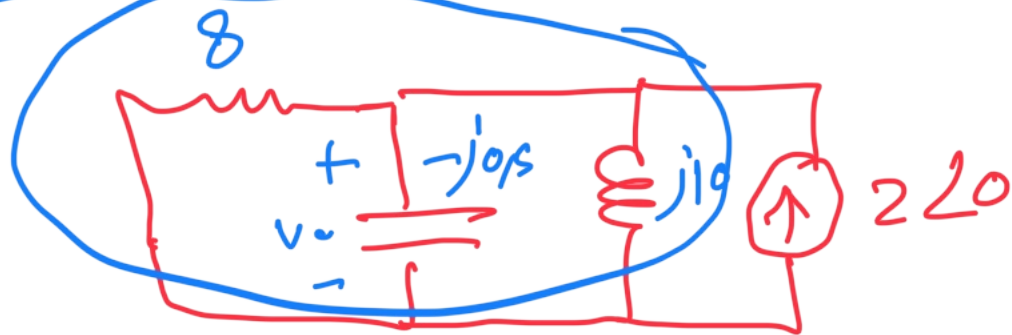

$$Z_T = \frac{1}{\frac{1}{8} + \frac{1}{-0,5j} + \frac{1}{j10}}$$



$$Z_T = 0,525 \angle -86,24 \Omega$$

$$V_0'' = 2 \times \frac{2}{\pi} = 1,05 \angle -86,24$$

$$V_0 = 4,631 \sin(\omega t - 81,12) + 1,05 \cos(\omega t - 86,24)$$

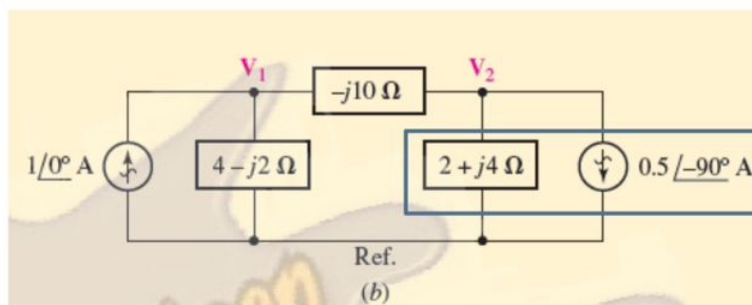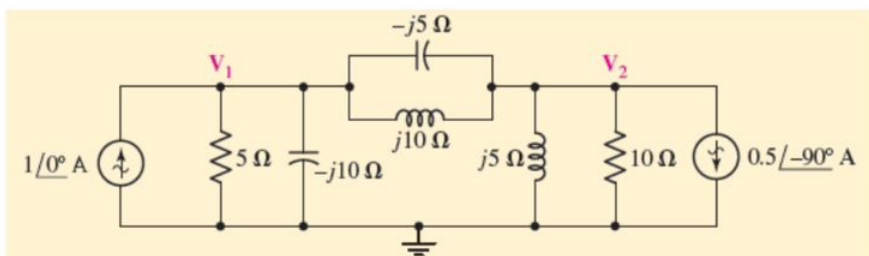Example 27: Superposition Theorem

- Calculate v_1 in the circuit of figure shown below using the superposition theorem.



Answer:

First we redraw the circuit as Fig. *b* where each pair of parallel impedances is replaced by a single equivalent impedance. That is, $5 \parallel -j10 \Omega$ is $4 - j2 \Omega$; $j10 \parallel -j5 \Omega$ is $-j10 \Omega$; and $10 \parallel j5$ is equal to $2 + j4 \Omega$.

To find V_1 , we first activate only the left source and find the partial response, V_{1L} . The $1/0^\circ$ source is in parallel with an impedance of

$$(4 - j2) \parallel (-j10 + 2 + j4) \text{ and we have: } V_{1L} = (4 - j2) * i_1$$

so that

$$\begin{aligned} V_{1L} &= 1/0^\circ \frac{(4 - j2)(-j10 + 2 + j4)}{4 - j2 - j10 + 2 + j4} \\ &= \frac{-4 - j28}{6 - j8} = 2 - j2 \text{ V} \end{aligned}$$


With only the right source active, current division and Ohm's law yield : $V_{1R} = (4 - j2) * i_1'$

$$V_{1R} = (-0.5/-90^\circ) \left(\frac{2 + j4}{4 - j2 - j10 + 2 + j4} \right) (4 - j2) = -1 \text{ V}$$


Summing, then,

$$V_1 = V_{1L} + V_{1R} = 2 - j2 - 1 = 1 - j2 \text{ V}$$

Source Transformation

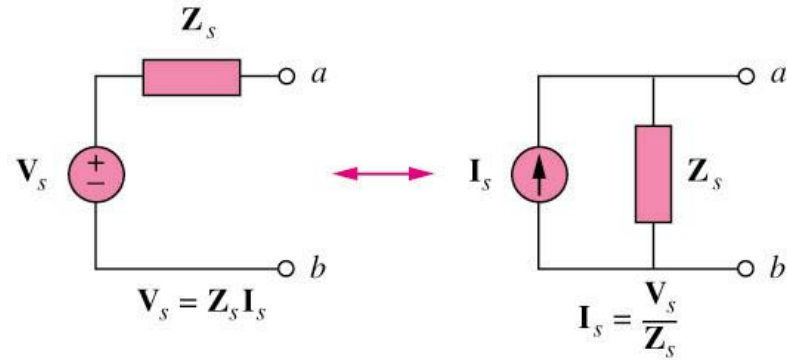

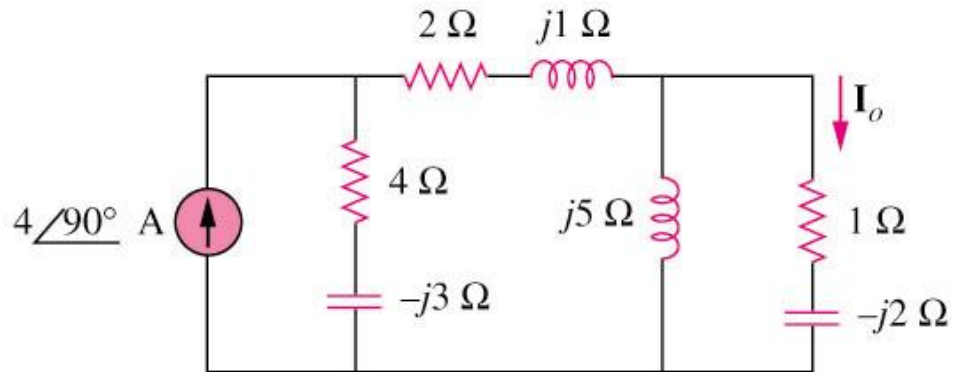
Example Find I_o in the circuit of figure below using the concept of source transformation.




Answer: $I_o = \underline{3.288 + j99.46 \text{ A}}$

Thevenin and Norton Theorems in AC circuits

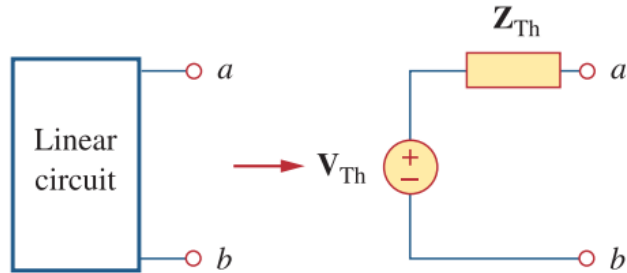- Thevenin's and Norton theorems are applied to ac circuits in the same way as they are to DC circuits
- The **ONLY additional effort** is the need to manipulate **complex numbers**.



Thevenin equivalent.

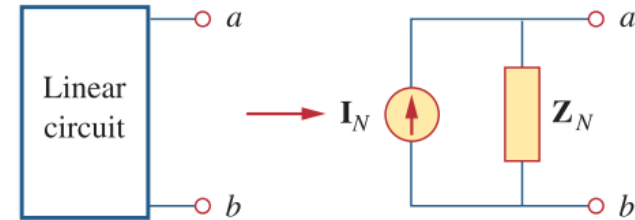


Norton equivalent.

Where; $V_{Th} = V_{ab-OC}$ is the **open circuit voltage (PHASOR)** between terminals a-b, $I_N = I_{ab-SC}$ is the **short circuit current (PHASOR)** through the terminals a-b, and Z_{Th} is the **input or equivalent IMPEDANCE** at the terminals **when the independent source are turn off**.


How to Find Thevenin Equivalent Circuit in AC circuits

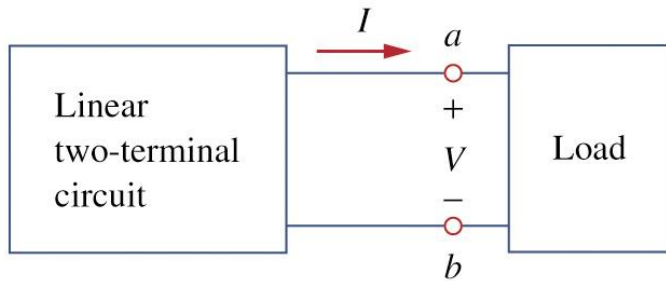- ❖ First, **Open the circuit** (remove the load) at the **points** of interest **a-b**
- 1- V_{th} = Open circuit voltage (keep all sources intact). Note: V_{th} is Phasor
- 2- Z_{th} = Open circuit **equivalent Impedance** appears at terminals **a-b** while all **independent sources=0** (voltage source=SC, current source=OC).



Original Circuit

≡

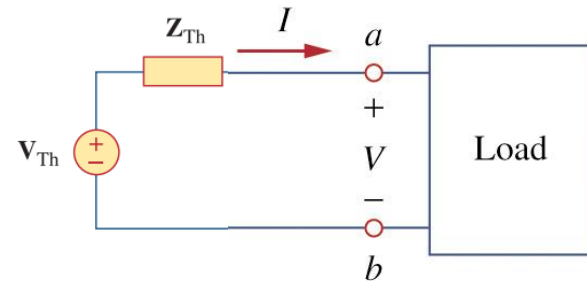

Thevenin equivalent circuit

Example 10.8- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.


Solution

1- For Z_{th}

$$\mathbf{Z}_1 = -j6 \parallel 8 = \frac{-j6 \times 8}{8 - j6} = 2.88 - j3.84 \Omega$$

$$\mathbf{Z}_2 = 4 \parallel j12 = \frac{j12 \times 4}{4 + j12} = 3.6 + j1.2 \Omega$$

$$\mathbf{Z}_{Th} = \mathbf{Z}_1 + \mathbf{Z}_2 = 6.48 - j2.64 \Omega$$

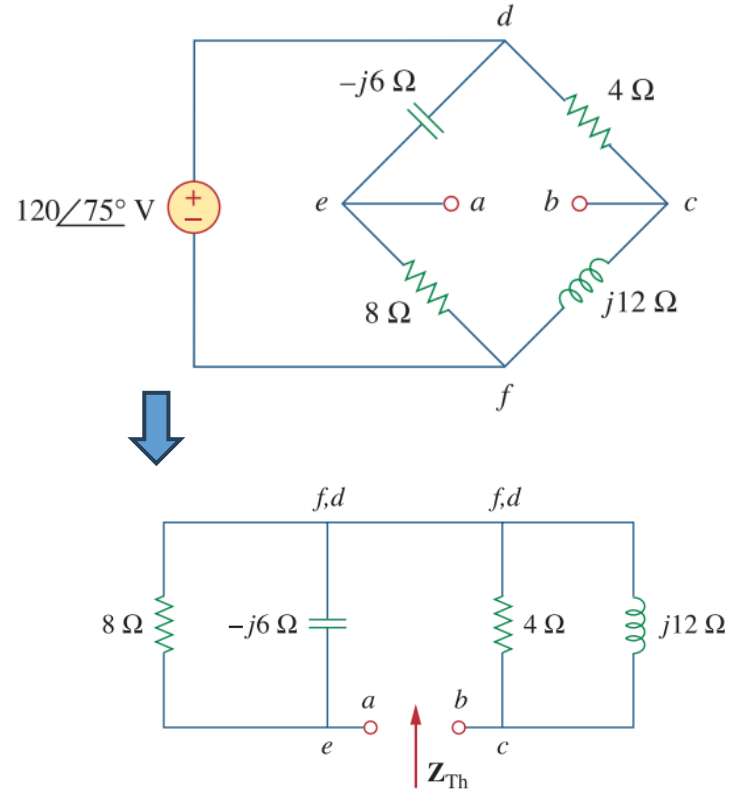

Example 10.8- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution (continue)



2- For V_{th}

$$\mathbf{I}_1 = \frac{120 \angle 75^\circ}{8 - j6} \text{ A}, \quad \mathbf{I}_2 = \frac{120 \angle 75^\circ}{4 + j12} \text{ A}$$

Applying KVL around loop $bcdeab$

$$\mathbf{V}_{Th} - 4\mathbf{I}_2 + (-j6)\mathbf{I}_1 = 0$$

$$\begin{aligned} \mathbf{V}_{Th} = 4\mathbf{I}_2 + j6\mathbf{I}_1 &= \frac{480 \angle 75^\circ}{4 + j12} + \frac{720 \angle 75^\circ + 90^\circ}{8 - j6} \\ &= 37.95 \angle 3.43^\circ + 72 \angle 201.87^\circ \\ &= -28.936 - j24.55 = 37.95 \angle 220.31^\circ \text{ V} \end{aligned}$$

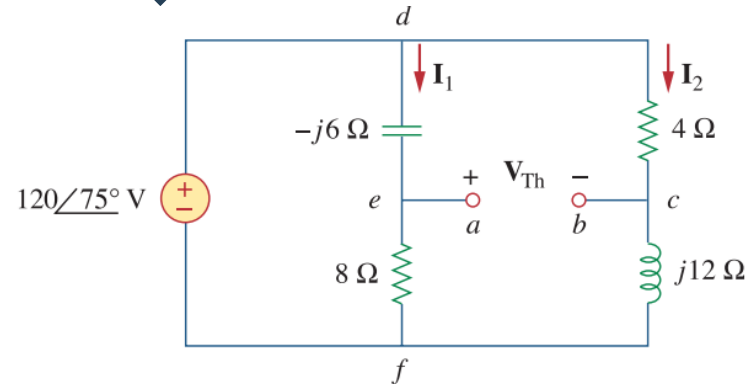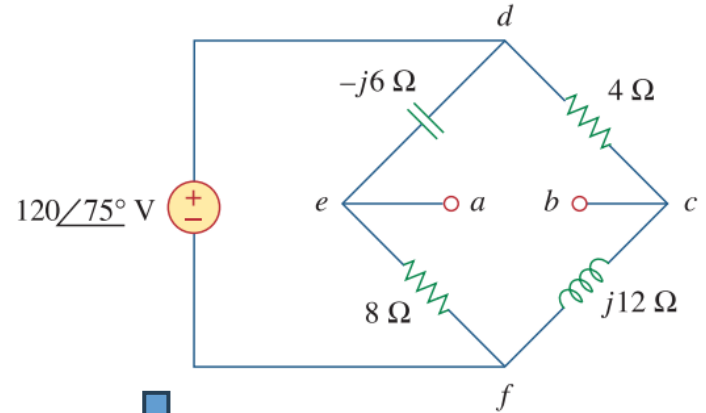

Example 10.9- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution

1- For V_{th}

To find V_{Th} , we apply KCL at node 1

$$15 = \mathbf{I}_o + 0.5\mathbf{I}_o \quad \Rightarrow \quad \mathbf{I}_o = 10 \text{ A}$$

Applying KVL to the loop on the right-hand side



$$-\mathbf{I}_o(2 - j4) + 0.5\mathbf{I}_o(4 + j3) + \mathbf{V}_{Th} = 0$$

or

$$\mathbf{V}_{Th} = 10(2 - j4) - 5(4 + j3) = -j55$$

Thus, the Thevenin voltage is

$$\mathbf{V}_{Th} = 55 \angle -90^\circ \text{ V}$$

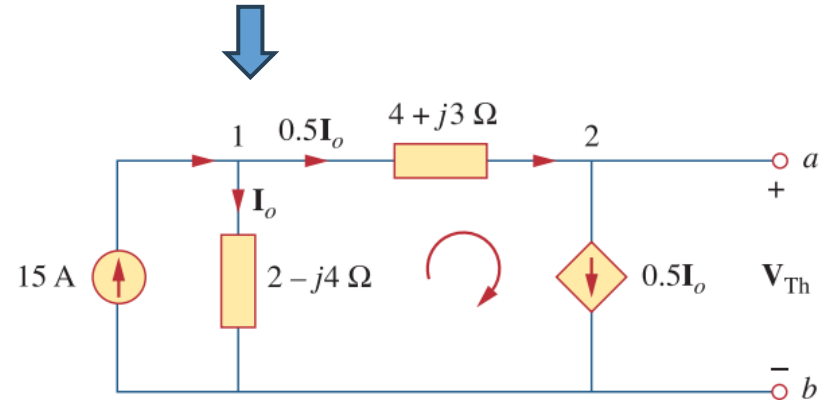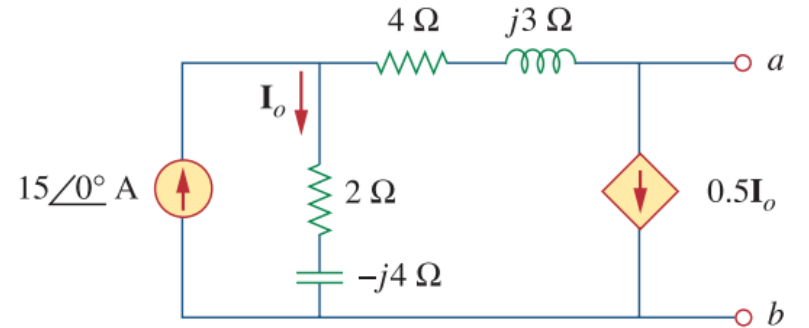

Example 10.9- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution (continue)

2- For Z_{th}

To obtain Z_{Th} , we remove the independent source. Due to the presence of the dependent current source, we connect a 3-A current source (3 is an arbitrary value chosen for convenience here, a number divisible by the sum of currents leaving the node) to terminals $a-b$



$$3 = \mathbf{I}_o + 0.5\mathbf{I}_o \quad \Rightarrow \quad \mathbf{I}_o = 2 \text{ A}$$

Applying KVL to the outer loop in Fig. 10.26(b) gives

$$\mathbf{V}_s = \mathbf{I}_o(4 + j3 + 2 - j4) = 2(6 - j)$$

The Thevenin impedance is
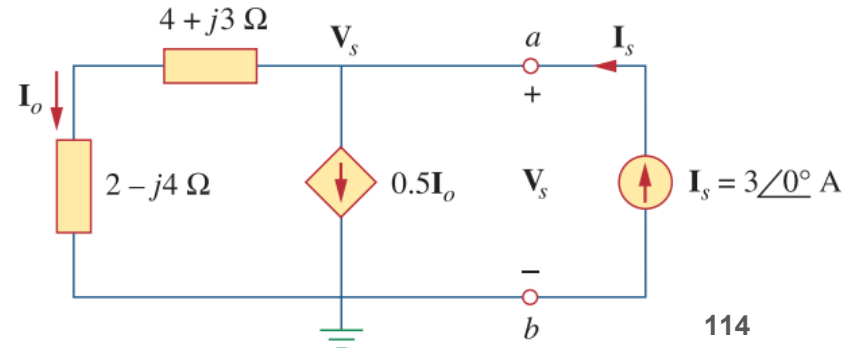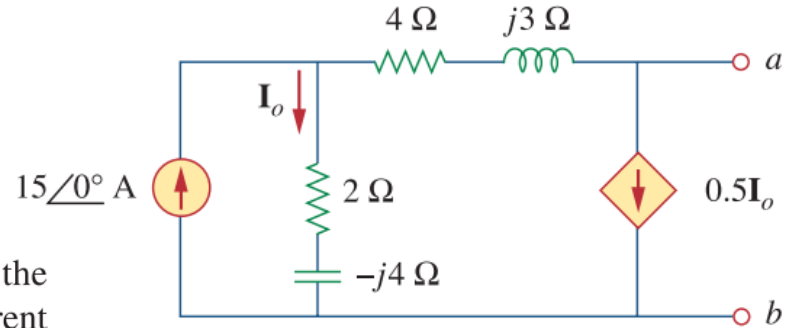
$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_s}{\mathbf{I}_s} = \frac{2(6 - j)}{3} = 4 - j0.6667 \Omega$$



Trigonometric Identities



- Sine and cosine form conversions.

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$


$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$


Where

$$C = \sqrt{A^2 + B^2} \quad \text{and} \quad \theta = \tan^{-1} \frac{B}{A}$$

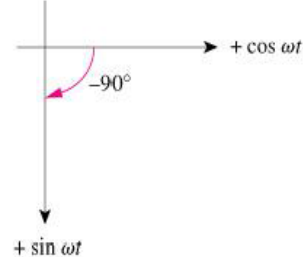Graphically relating sine and cosine functions.


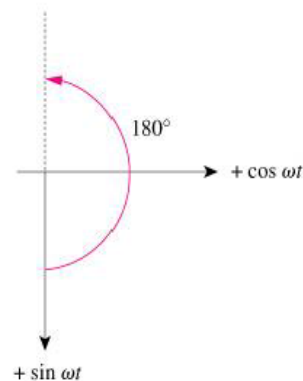
$$\cos(\omega t - 90^\circ) = \sin \omega t$$



$$\sin(\omega t + 180^\circ) = -\sin \omega t$$



End of Lecture



Questions?