
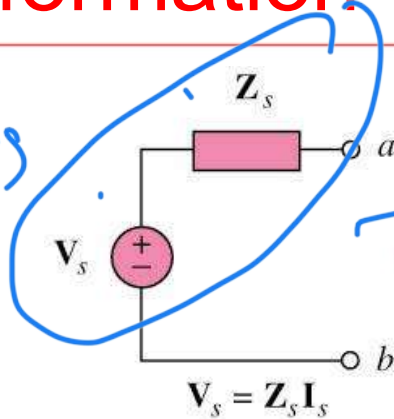


# Source Transformation

series

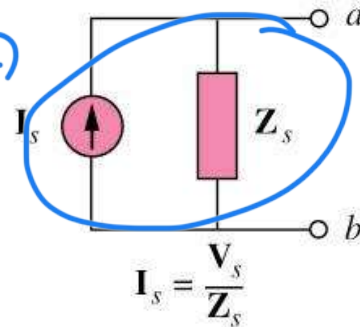


parallel




**Example** Find  $I_o$  in the circuit of figure below using the concept of source transformation.

parallel

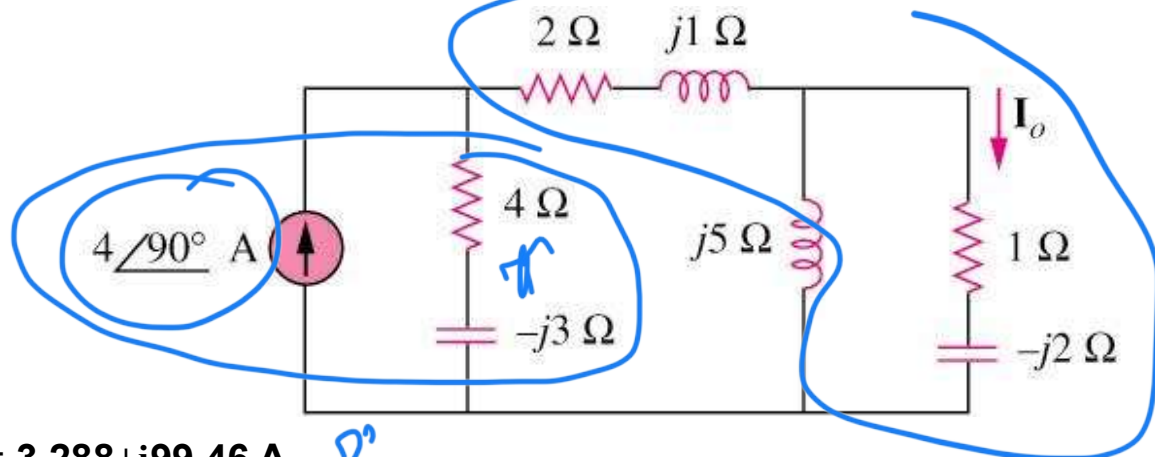


**Answer:**  $I_o = 3.288 + j99.46 \text{ A}$
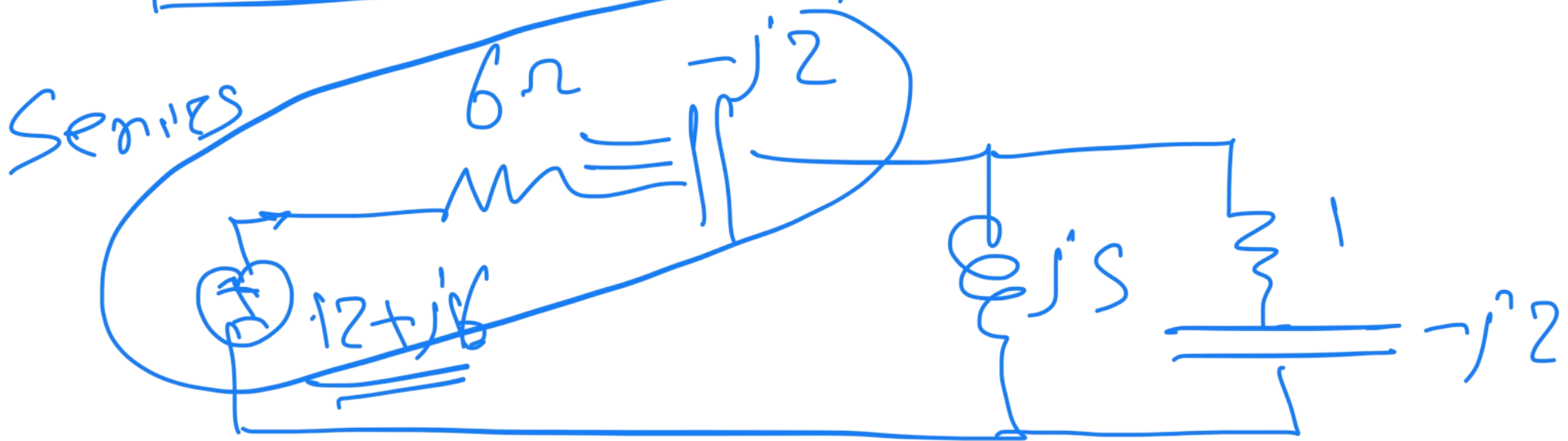
$$V = 100 \angle 90^\circ = 4 \angle 90^\circ \times (4 - j3)$$


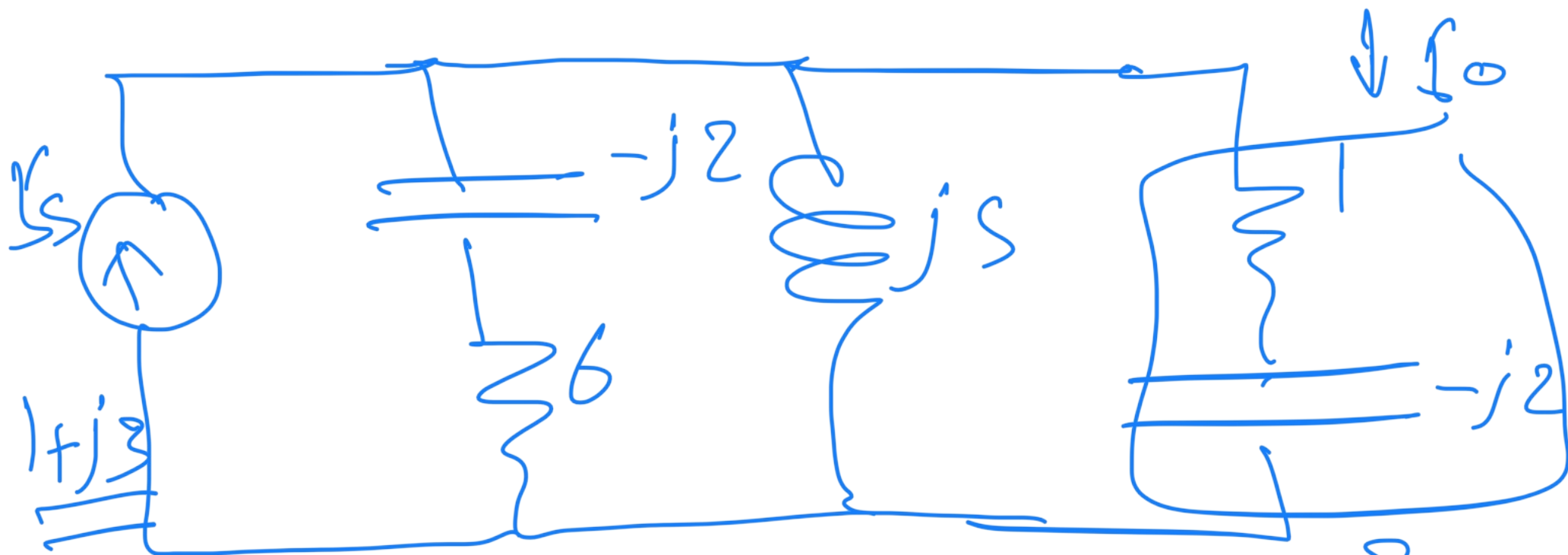
$$I = \frac{V}{Z} \Rightarrow \frac{12 + j16}{6 - j2} = 1 + j3$$



Current divider parallel  $Z_1$

$$I_o = \frac{Z_{eq} \times I_s}{Z_1}$$

$$Z_{eq} = \frac{1}{\frac{1}{6-j2} + \frac{1}{j5} + \frac{1}{1-j2}}$$


$$= \frac{40}{37} - j \frac{50}{37} \Omega$$

$$I_0 = \frac{* (1+j3)}{1-j2}$$


$$\Rightarrow \begin{aligned} & -\textcircled{1}, 541 + j3, 2 \text{ A A} \\ & = 3, 29 \angle 100^\circ \text{ A} \end{aligned}$$
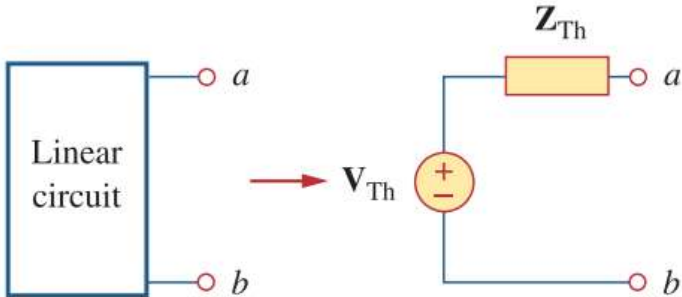
# Thevenin and Norton Theorems in AC circuits

- Thevenin's and Norton theorems are applied to ac circuits in the same way as they are to DC circuits
- The **ONLY additional effort** is the need to manipulate **complex numbers**.



Thevenin equivalent.

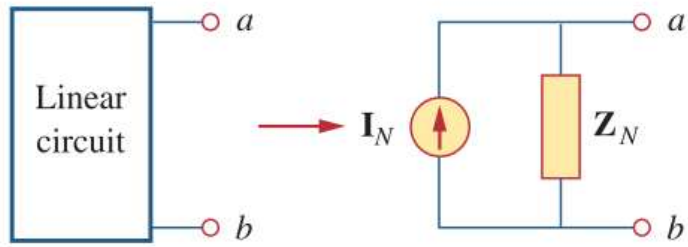


Norton equivalent.

Where:  $V_{Th} = V_{ab-OC}$  is the **open circuit voltage (PHASOR)** between terminals a-b,  
 $I_N = I_{ab-SC}$  is the **short circuit current (PHASOR)** through the terminals a-b, and  
 $Z_{Th}$  is the input or equivalent **IMPEDANCE** at the terminals **when the independent source are turn off**.

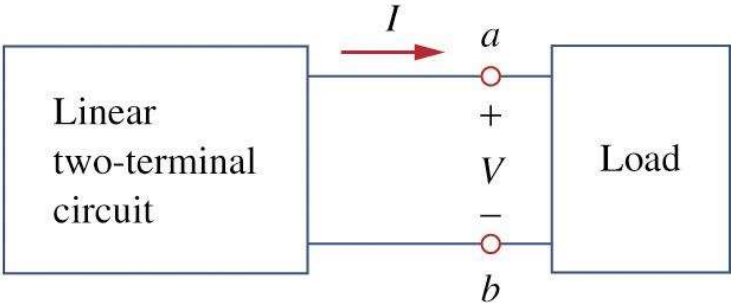
# How to Find Thevenin Equivalent Circuit in AC circuits

- ❖ First, **Open the circuit** (remove the load) at the **points** of interest **a-b**
- 1-  $V_{th}$  = Open circuit voltage (keep all sources intact). Note:  $V_{th}$  is Phasor
- 2-  $Z_{th}$  = Open circuit **equivalent Impedance** appears at terminals **a-b** while all **independent sources=0** (voltage source=**SC** , current source=**OC**).



Original Circuit

≡

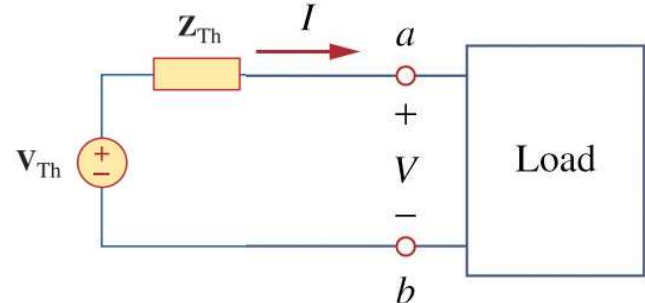

Thevenin equivalent circuit

## Example 10.8- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.


Solution


1- For  $Z_{th}$

$$\mathbf{Z}_1 = -j6 \parallel 8 = \frac{-j6 \times 8}{8 - j6} = 2.88 - j3.84 \Omega$$



$$\mathbf{Z}_2 = 4 \parallel j12 = \frac{j12 \times 4}{4 + j12} = 3.6 + j1.2 \Omega$$
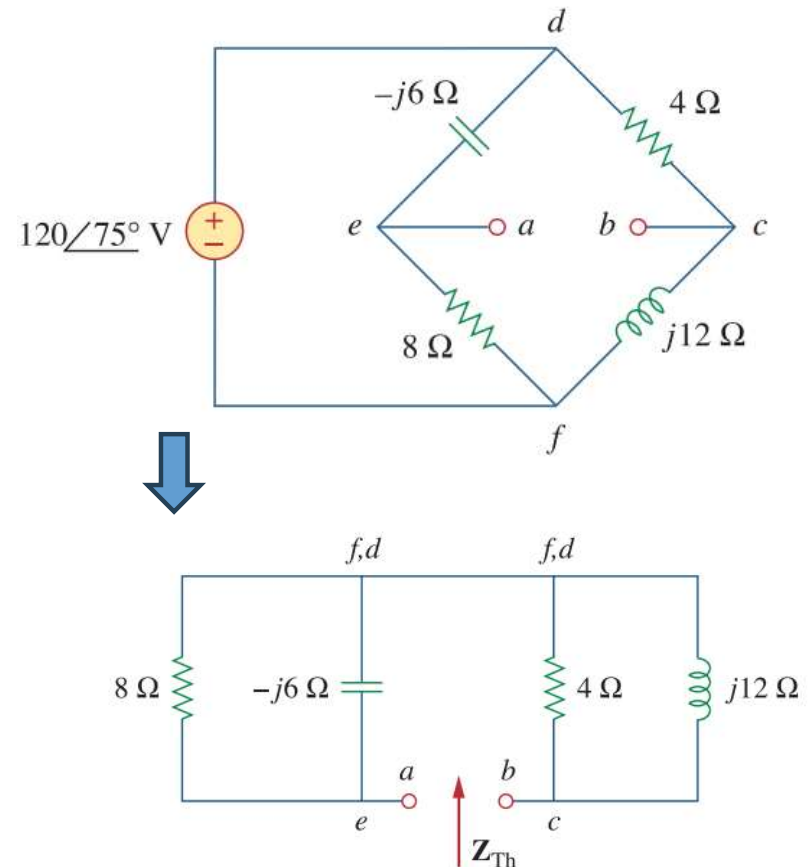
$$\mathbf{Z}_{Th} = \mathbf{Z}_1 + \mathbf{Z}_2 = 6.48 - j2.64 \Omega$$



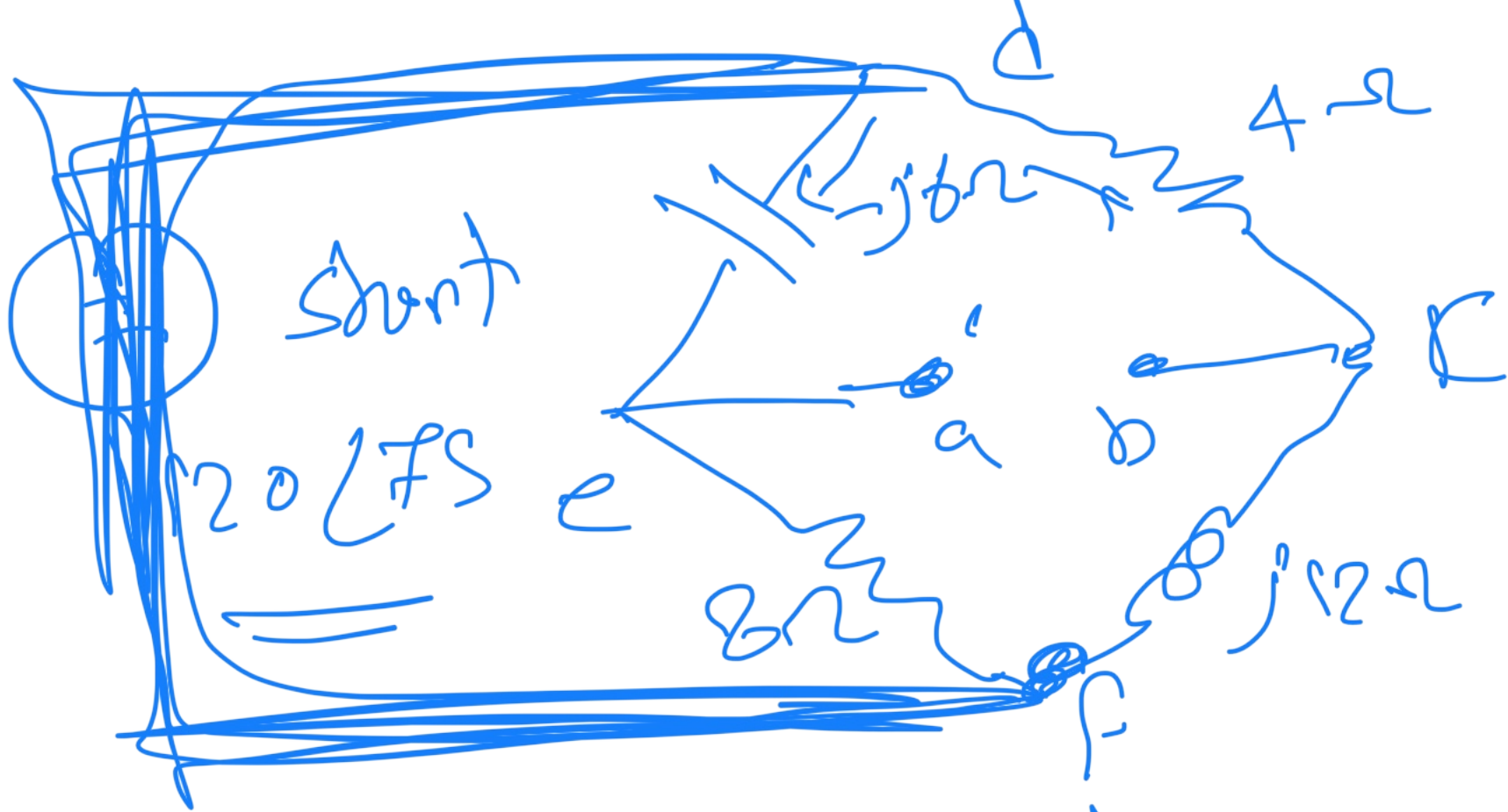

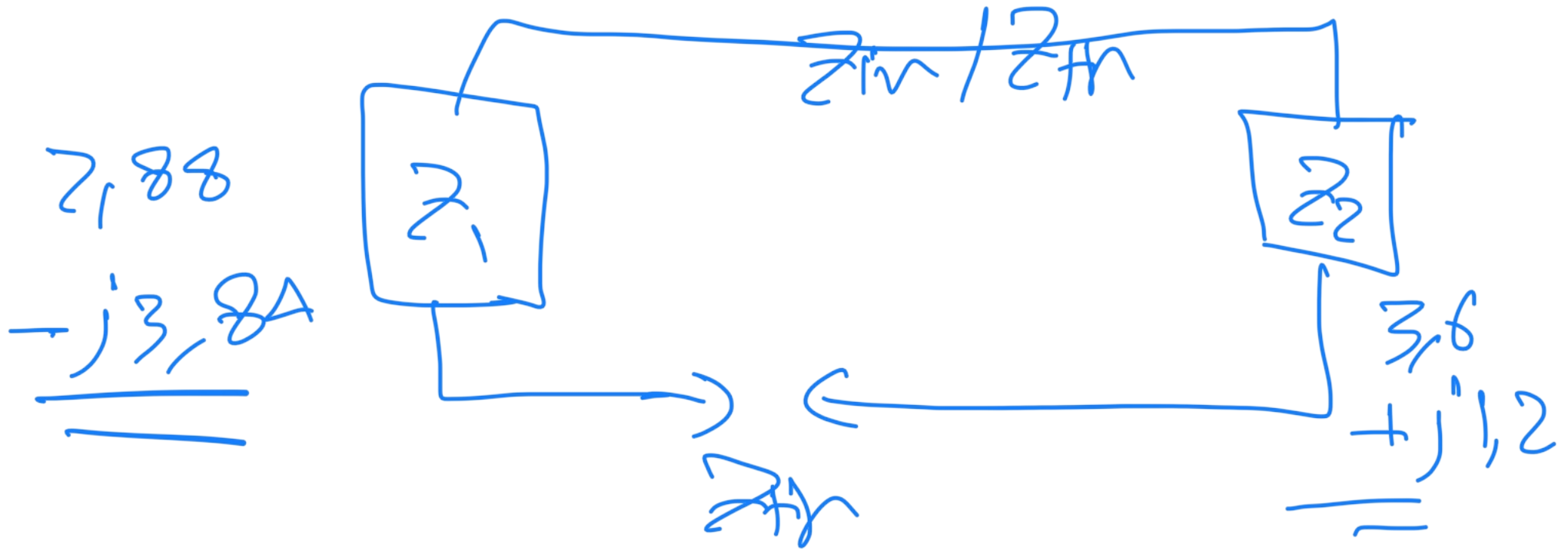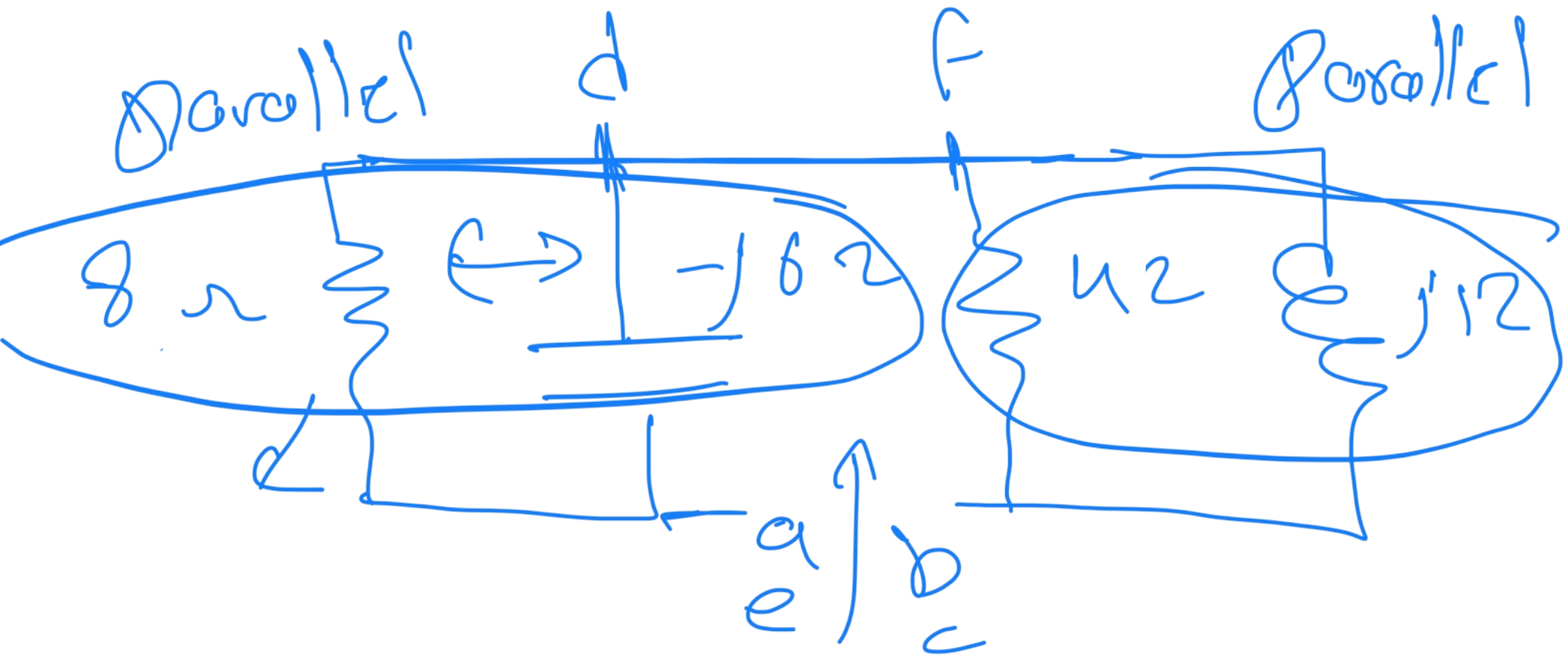① 2th All ind source  
 → Turn off cell ind source



$$Z_{th} = Z_1 + Z_2$$

$$2,88 - j3,84 + 3,6 + j1,2$$

$$Z_{th} = 6,48 - j2,64 \Omega$$

# Example 10.8- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution (continue)

2- For  $V_{th}$


$$\mathbf{I}_1 = \frac{120 \angle 75^\circ}{8 - j6} \text{ A}, \quad \mathbf{I}_2 = \frac{120 \angle 75^\circ}{4 + j12} \text{ A}$$


Applying KVL around loop  $bcdeab$

$$V_{Th} - 4\mathbf{I}_2 + (-j6)\mathbf{I}_1 = 0$$

$$\begin{aligned} V_{Th} = 4\mathbf{I}_2 + j6\mathbf{I}_1 &= \frac{480 \angle 75^\circ}{4 + j12} + \frac{720 \angle 75^\circ + 90^\circ}{8 - j6} \\ &= 37.95 \angle 3.43^\circ + 72 \angle 201.87^\circ \\ &= -28.936 - j24.55 = 37.95 \angle 220.31^\circ \text{ V} \end{aligned}$$

$37.95 \angle -139.6^\circ$

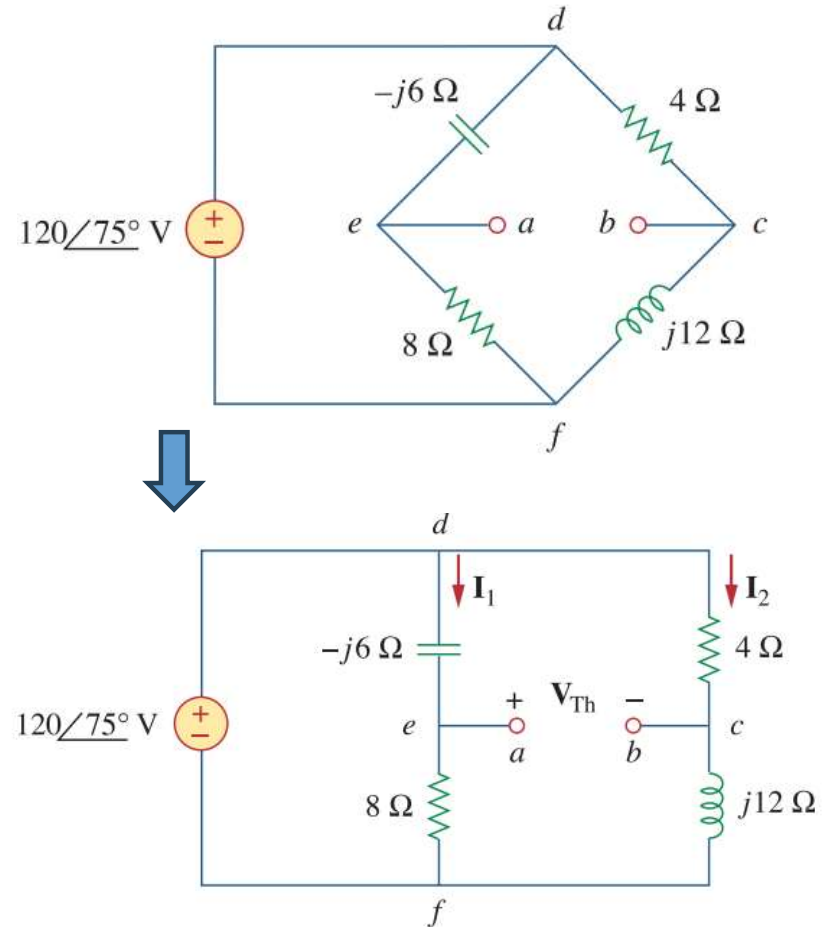

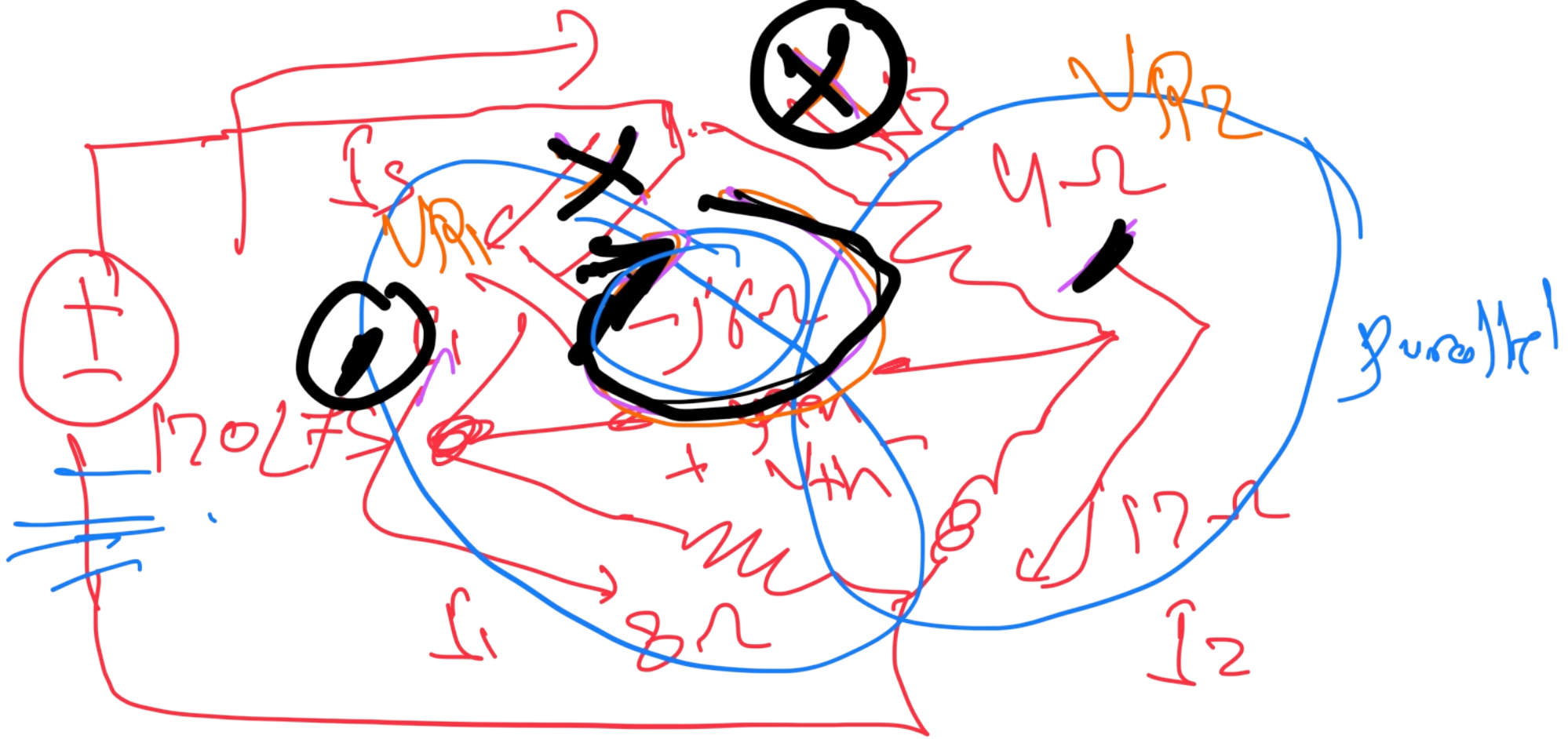

$$I_1 = \frac{120 \angle 75^\circ}{8 - j6} = -4,47 + j11,14$$

$$I_2 = \frac{120 \angle 75^\circ}{9 + j12} = 9,47 + j0,56$$

$$-V_{th} - V_{R_1} + V_{R_2} = 0$$

$$V_{th} = V_{R_2} - V_{R_1}$$

$$4I_2 + j6I_1$$

$$V_{th} = 37,96 \angle -139,71^\circ \text{ V}$$

# Example 10.9- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

## Solution

### 1- For $V_{th}$

To find  $V_{Th}$ , we apply KCL at node 1

$$15 = I_o + 0.5I_o \Rightarrow I_o = 10 \text{ A}$$

Applying KVL to the loop on the right-hand side




$$-I_o(2 - j4) + 0.5I_o(4 + j3) + V_{Th} = 0$$

or

$$V_{Th} = 10(2 - j4) - 5(4 + j3) = -j55$$

Thus, the Thevenin voltage is
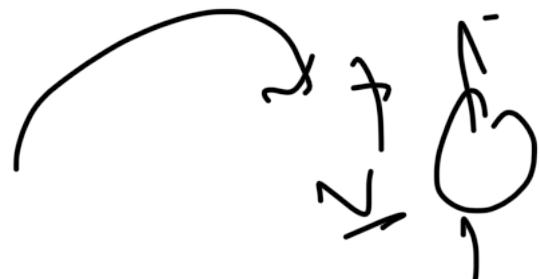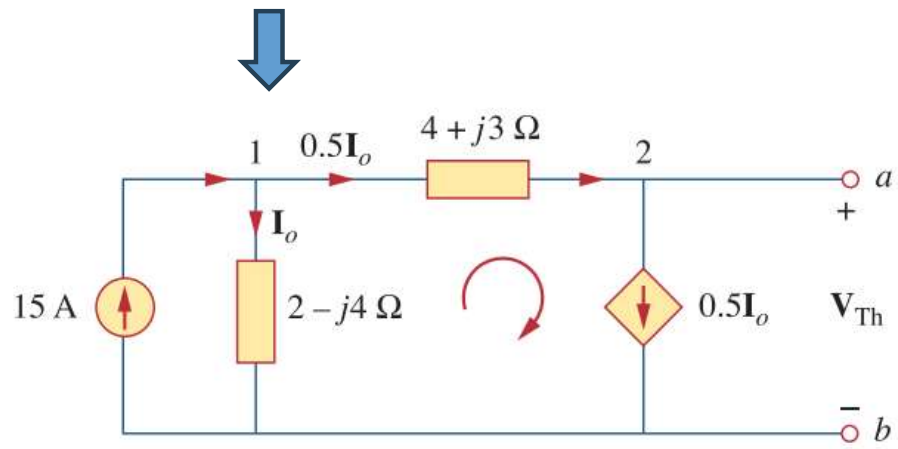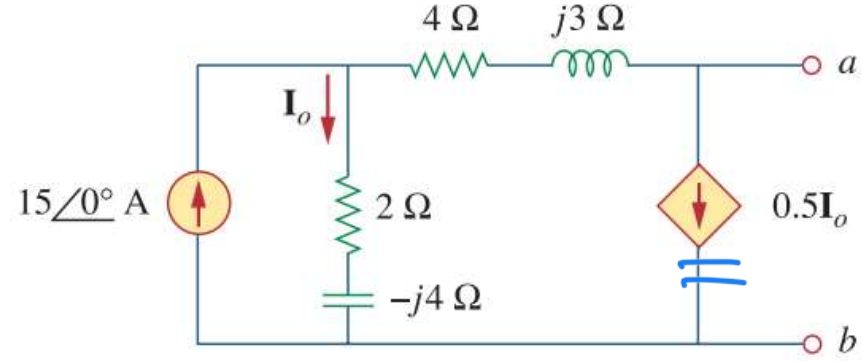
$$V_{Th} = 55 \angle -90^\circ \text{ V}$$






$$\rightarrow \underline{10} [2 - j4] + 5 [4 + j3] + V_o = 0$$

$$V_o = 10 [2 - j4] - 5 [4 + j3]$$
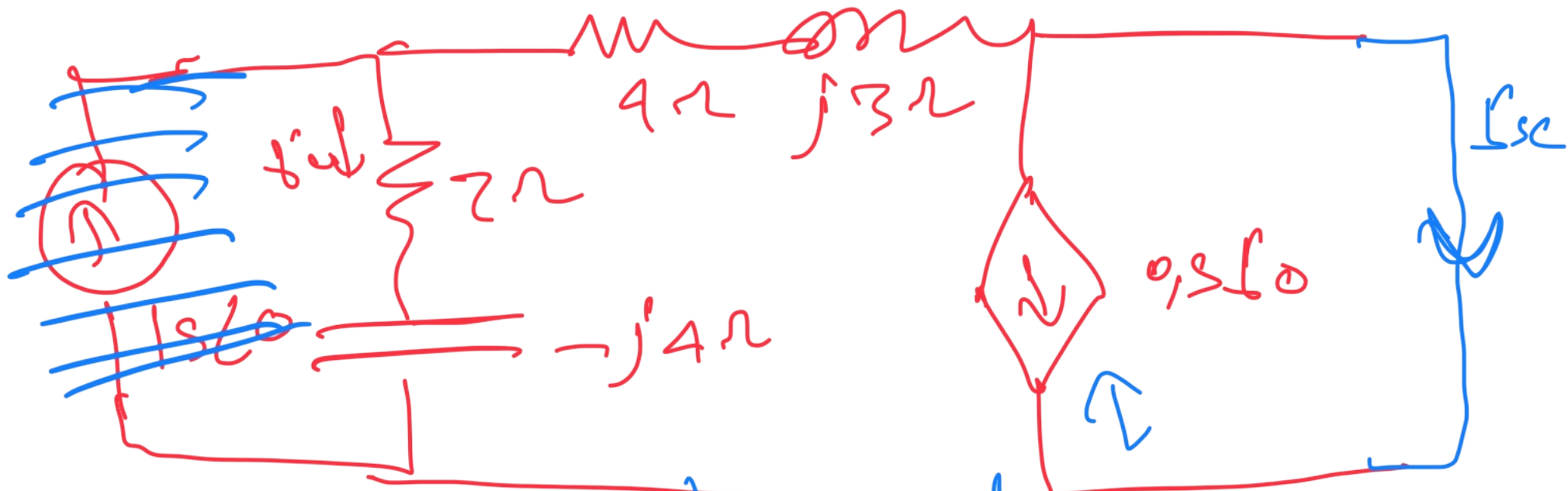
$$V_o = -55j = 55 \angle -90^\circ \text{ V}$$



Short circuit  
 $4\Omega \cdot j3\Omega$

Turn off  
 full and source



$$Z_{in} = \frac{V_s}{I_s}$$

1cc2  $\Rightarrow 1 = i_0 + 0,5 I_0$   
 $1,5 I_0 = 1$

$$I_0 = \frac{1}{1,5} = \frac{2}{3} A$$

$$\underline{\underline{-V_s + \frac{2}{3} [4 + j3 + 2 - j4] = 0}}$$

$$V_S = 4 - \frac{2j}{3} \text{ V}$$

$$\Rightarrow Z_{in} = \frac{4 - j\frac{2}{3}}{1 \angle 0}$$

$$Z_{in} = 4 - j\frac{2}{3} \Omega$$

# Example 10.9- Thevenin Equivalent Circuit

Obtain the Thevenin equivalent at terminals a-b of the following circuit.

Solution (continue)

2- For  $Z_{th}$

To obtain  $Z_{Th}$ , we remove the independent source. Due to the presence of the dependent current source, we connect a 3-A current source (3 is an arbitrary value chosen for convenience here, a number divisible by the sum of currents leaving the node) to terminals  $a-b$



$$3 = I_o + 0.5I_o \Rightarrow I_o = 2 \text{ A}$$

Applying KVL to the outer loop in Fig. 10.26(b) gives

$$V_s = I_o(4 + j3 + 2 - j4) = 2(6 - j)$$

The Thevenin impedance is
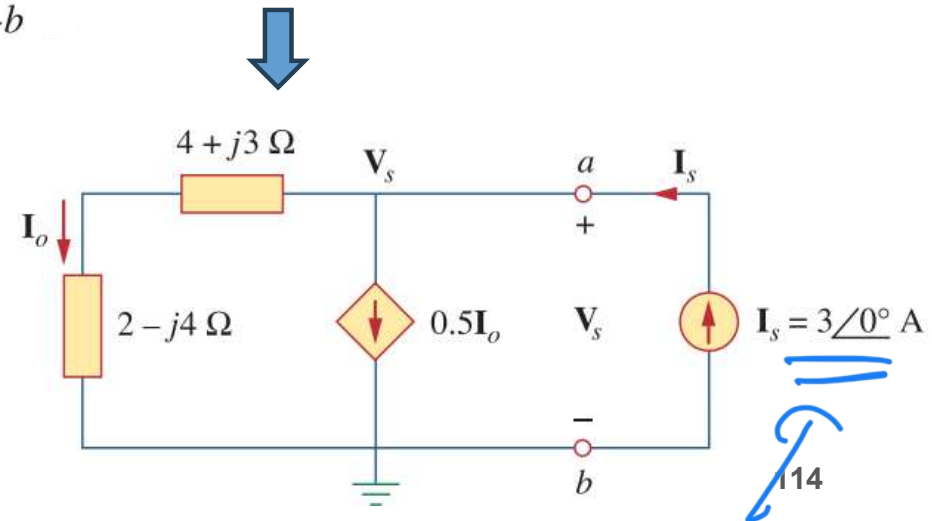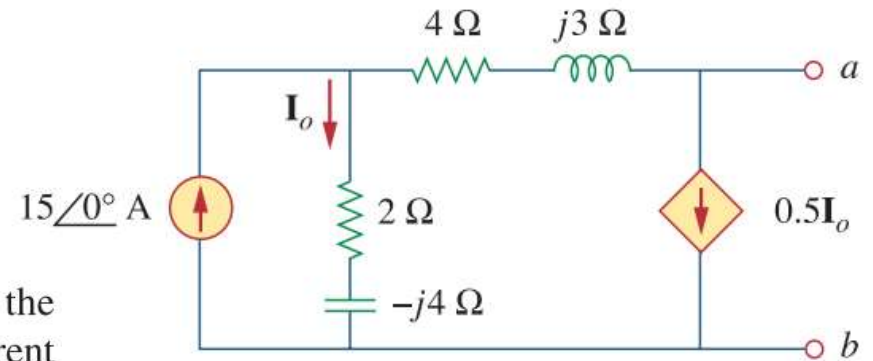
$$Z_{Th} = \frac{V_s}{I_s} = \frac{2(6 - j)}{3} = 4 - j0.6667 \Omega$$



# Trigonometric Identities



➤ Sine and cosine form conversions.

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$


$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$


Where

$$C = \sqrt{A^2 + B^2} \quad \text{and} \quad \theta = \tan^{-1} \frac{B}{A}$$

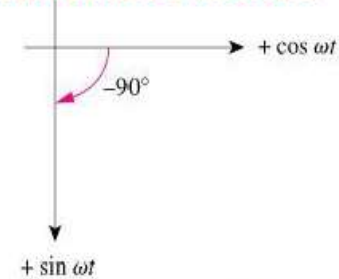Graphically relating sine and cosine functions.


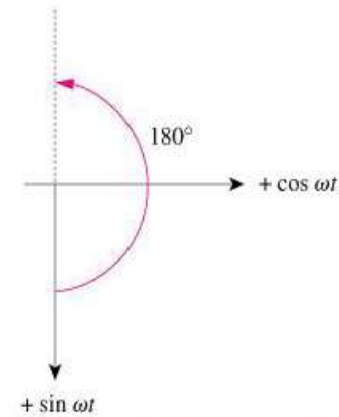
$$\cos(\omega t - 90^\circ) = \sin \omega t$$



$$\sin(\omega t + 180^\circ) = -\sin \omega t$$



End of Lecture



---

Questions?