

EE 210 ELECTRIC CIRCUITS II

Lecture 1

Mutual Inductance and Transformers

Dr. A. Zidouri




Magnetically Coupled Circuits



- The circuits studied so far can be considered as conductively coupled, since loops affect each other by current conduction.
- When two loops with or without contact affect each other through magnetic fields, they are said to be magnetically coupled.
- The transformer is a device designed based on the concept of magnetic coupling.
- In preparation for the study of transformers, we will first make a brief recap of self inductance and then discuss the concept of mutual inductance.

Faraday's Law

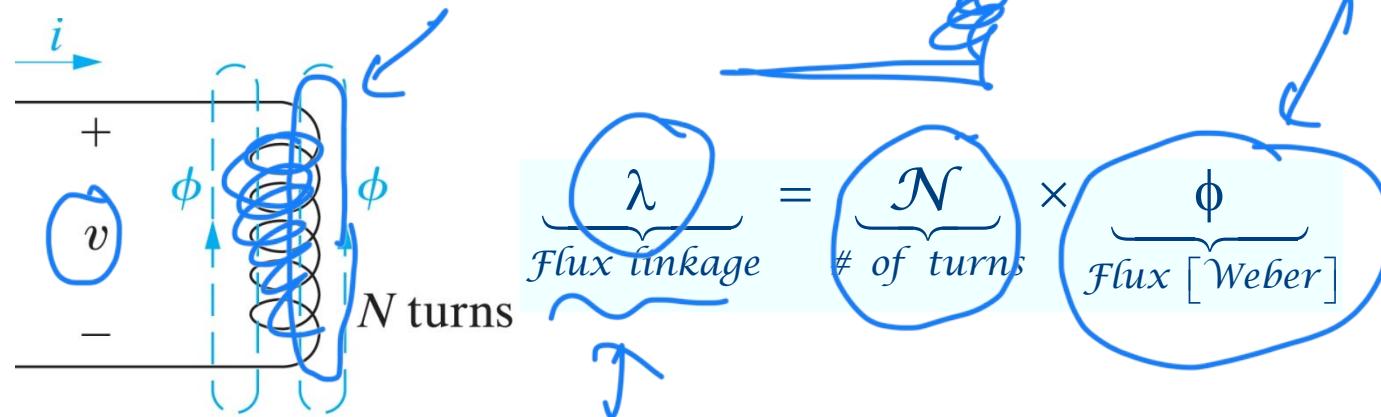

- Consider a coil of \mathcal{N} turns, through which a current i is flowing.
- **Faraday's Law:** The voltage induced in the coil is given by the rate-of-change of the flux linkage:

$$v(t) = \frac{d\lambda(t)}{dt} = \boxed{\mathcal{N} \frac{d\phi(t)}{dt}}$$

Self Inductance



- The magnitude of the flux is given by:

$$\phi = \mathcal{P} \times \mathcal{N} \times i; \quad \mathcal{P}: \text{permeance of the field occupied by the flux}$$

- The permeance is flux-dependent for magnetic materials (like iron, nickel, cobalt), whereas it is constant for nonmagnetic materials.

- When the core material of the coil is nonmagnetic:

$$v(t) = \mathcal{N} \frac{d\phi(t)}{dt} = \mathcal{N}^2 \mathcal{P} \times \frac{di(t)}{dt}$$

$$\mathcal{N} \mathcal{N} \mathcal{P} \quad i(t)$$


- The proportionality constant is the self-inductance:

$$\mathcal{L} = \mathcal{N}^2 \mathcal{P}$$

$$v_L(t) = L \frac{di}{dt}$$

AC
T
NP
'(h)

Magnetically-Coupled Coils

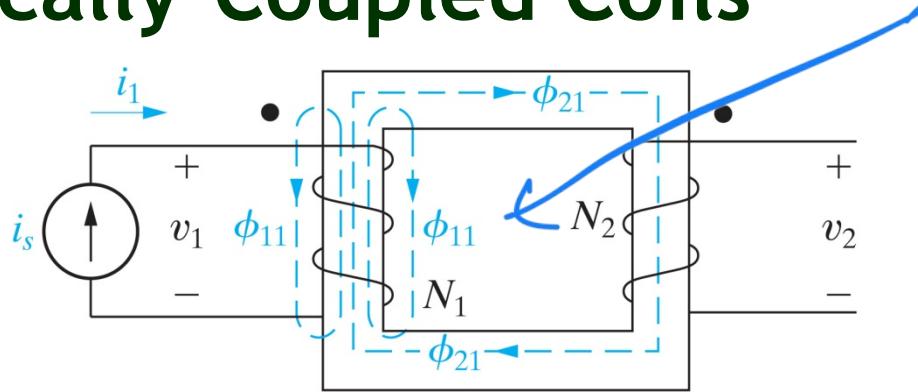


- Now consider two neighboring coils wound on a nonmagnetic core, with a current in the first one:

$$\underbrace{\phi_1}_{\text{total flux}} = \underbrace{\mathcal{P}_{11}\mathcal{N}_1 \times \vec{i}_1}_{\phi_{11}: \text{flux linking coil-1}} + \underbrace{\mathcal{P}_{21}\mathcal{N}_1 \times \vec{i}_1}_{\phi_{21}: \text{flux linking coil-2}} = \underbrace{(\mathcal{P}_{11} + \mathcal{P}_{21})\mathcal{N}_1 \times \vec{i}_1}_{\mathcal{P}_1}$$

- Using Faraday's law, we find:
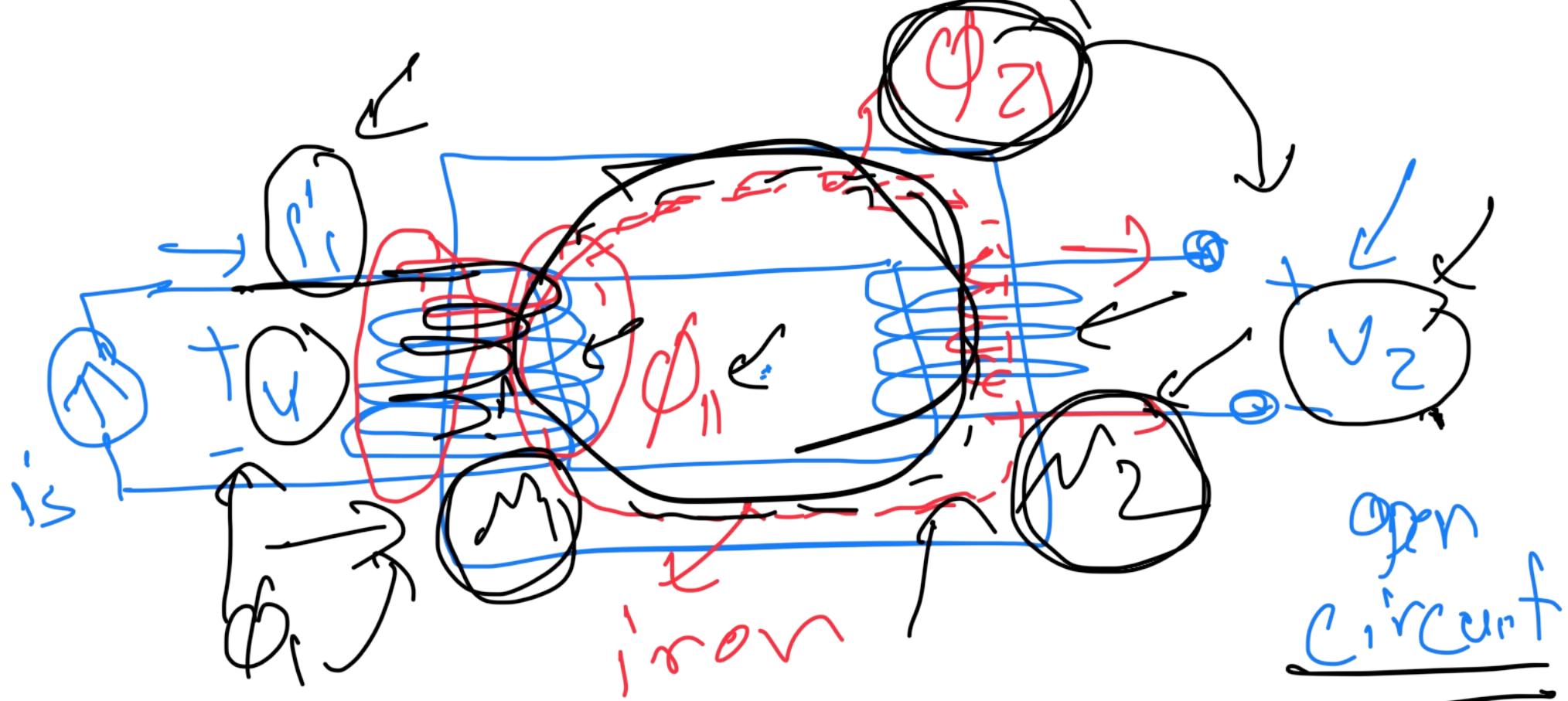
$$\nu_1(t) = \mathcal{N}_1 \frac{d\phi_1(t)}{dt} = \underbrace{\mathcal{N}_1^2 \mathcal{P}_1}_{\mathcal{L}_1} \frac{d\vec{i}_1(t)}{dt}; \quad \nu_2(t) = \mathcal{N}_2 \frac{d\phi_{21}(t)}{dt} = \underbrace{\mathcal{N}_2 \mathcal{N}_1 \mathcal{P}_{21}}_{\mathcal{M}_{21}} \frac{d\vec{i}_1(t)}{dt}$$



$$\text{total flux} = \phi_{11} + \phi_{21}$$

$$\phi_1 = \underbrace{P_{11} \underline{N_1} \underline{C_1}}_{\mathcal{R}} + \underbrace{P_{21} \underline{\cancel{N_1 C_1}}}_{\mathcal{R}} + \underbrace{\phi_{21}}_{\mathcal{R}}$$

$$N_1 C_1 (P_{11} + P_{21}) = \underline{\underline{P_1 N_1 C_1}}$$

$$N_1(t) = N_1 \underbrace{\partial \phi_1}_{\partial t} \rightarrow L_1$$


$$v_1(t) = \underbrace{N_1 N_1 P_1}_{\mathcal{R}} \frac{\partial C_1}{\partial t}$$

$$V_2(t) = N_2 \frac{\partial \mathcal{G}_{21}}{\partial t}^T$$

$$V_2(t) = \begin{matrix} \text{Diagram of three coupled oscillators:} \\ \text{N}_2 \quad \text{M}_1 \quad \text{P}_2 \\ \text{M}_2 \quad \text{Mutual} \quad \text{Seduct} \end{matrix} \frac{\partial \mathcal{C}_1}{\partial f}$$

$$N_2(t) = M_2 \frac{\partial \mathcal{C}_1}{\partial t}$$

Mutual Inductance

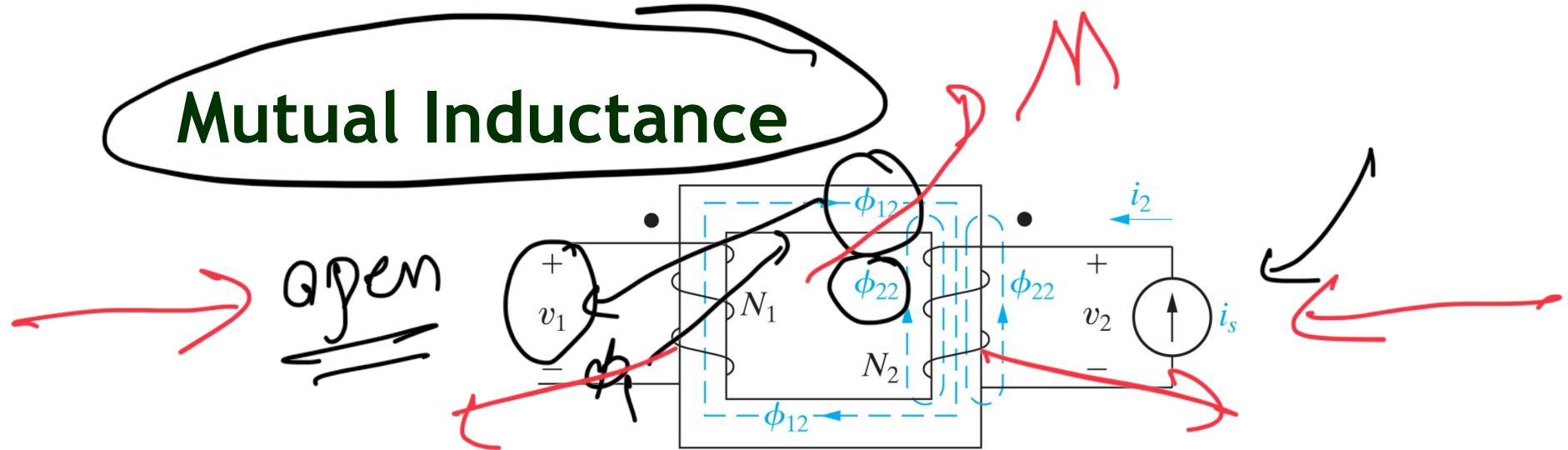

- When the current is fed to the second coil:

$$v_2(t) = \mathcal{N}_2 \frac{d\phi_2(t)}{dt} = \underbrace{\mathcal{N}_2^2 \mathcal{P}_2}_{\mathcal{L}_2} \frac{di_2(t)}{dt}; \quad v_1(t) = \mathcal{N}_1 \frac{d\phi_1(t)}{dt} = \underbrace{\mathcal{N}_1 \mathcal{N}_2 \mathcal{P}_{12}}_{\mathcal{M}_{12}} \frac{di_2(t)}{dt}$$

- For nonmagnetic core materials, we have:

$$\mathcal{P}_{12} = \mathcal{P}_{21} \Rightarrow \mathcal{M}_{12} = \mathcal{M}_{21} = \mathcal{M}$$

- \mathcal{L}_1 and \mathcal{L}_2 are the self inductances, whereas \mathcal{M} is the mutual inductance between the coils.

The Coefficient of Coupling

κ

- Recall the inductance expressions:

$$\mathcal{L}_1 = \mathcal{N}_1^2 \mathcal{P}_1 \text{ and } \mathcal{L}_2 = \mathcal{N}_2^2 \mathcal{P}_2 \Rightarrow \mathcal{L}_1 \mathcal{L}_2 = \mathcal{N}_1^2 \mathcal{N}_2^2 \mathcal{P}_1 \mathcal{P}_2$$

- For nonmagnetic core materials, we have:

$$\mathcal{P}_{21} = \mathcal{P}_{12} \Rightarrow \mathcal{L}_1 \mathcal{L}_2 = \underbrace{(\mathcal{N}_1 \mathcal{N}_2 \mathcal{P}_{12})^2}_{\mathcal{M}^2} \underbrace{\left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)}_{1/\kappa^2}$$

- Coupling is quantified by the **coefficient of coupling**:

$$\kappa = \left(\left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right) \right)^{-1/2} \in [0, 1]; \quad \mathcal{M} = \kappa \sqrt{\mathcal{L}_1 \mathcal{L}_2}$$

$\kappa \in (0.5, 1)$: tightly coupled; $\kappa \in (0, 0.5)$: loosely coupled



ω

$$0 \leq k \leq 1$$

\downarrow

F

$$0 \leq k \leq \omega, S \rightarrow$$


loosely
coupled

weak

$$\omega, S \leq k \leq 1 \rightarrow$$


highly
coupled

Voltage Polarity and the Dot Convention

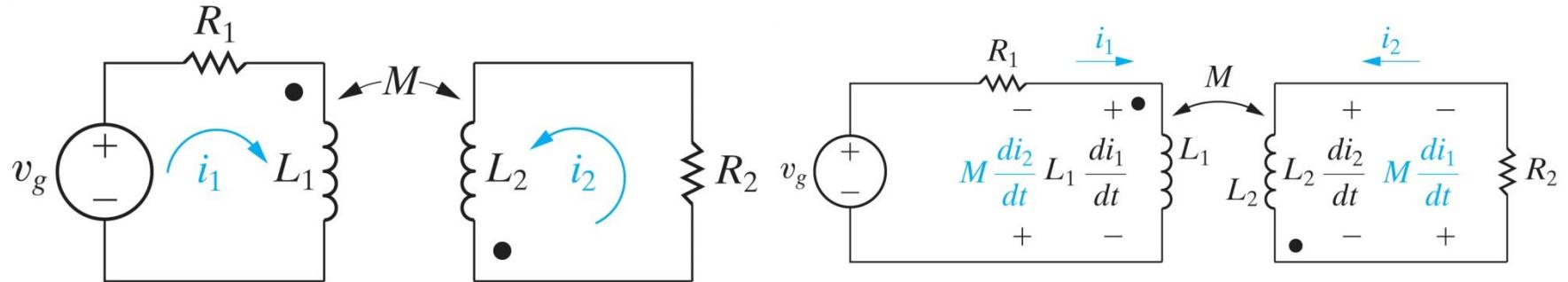


- The polarity of self-induced voltage is identified from the direction of the current.
- The polarity of the mutually-induced voltage is identified based on the dot convention.
- **Dot convention:** When the current enters (leaves) the dotted terminal of a coil, the polarity of the voltage it induces in the other coil is positive (negative) at its dotted terminal.

Application of the Dot Convention

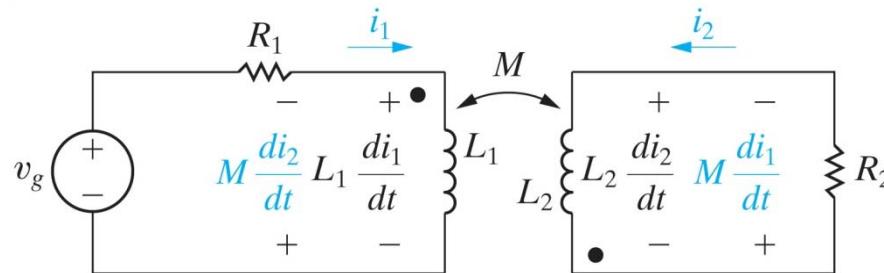

- The easiest way to analyze circuits containing mutual inductance is to use mesh currents.
- KVL is then applied with the addition of the mutually induced voltage with appropriate polarity:
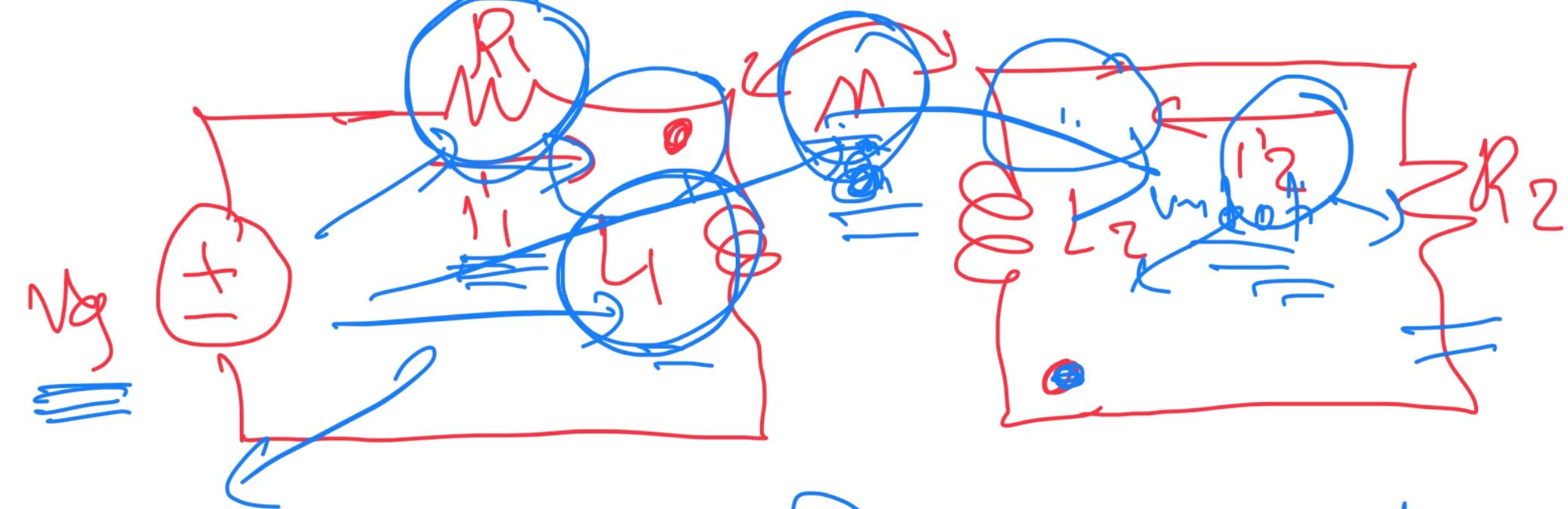
$$\begin{aligned} v_g &= \mathcal{R}_1 i_1 + \mathcal{L}_1 \frac{di_1}{dt} - \mathcal{M} \frac{di_2}{dt} \\ 0 &= \mathcal{R}_2 i_2 + \mathcal{L}_2 \frac{di_2}{dt} - \mathcal{M} \frac{di_1}{dt} \end{aligned}$$




إذا دخل أحدهما
عنبر $\frac{dC}{dt}$ $\neq 0$ فالآخر $\frac{dC}{dt} \neq 0$

$$Vg = R_1 i_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$


$$0 = R_2 i_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Equivalent Circuit for Mutual Inductance

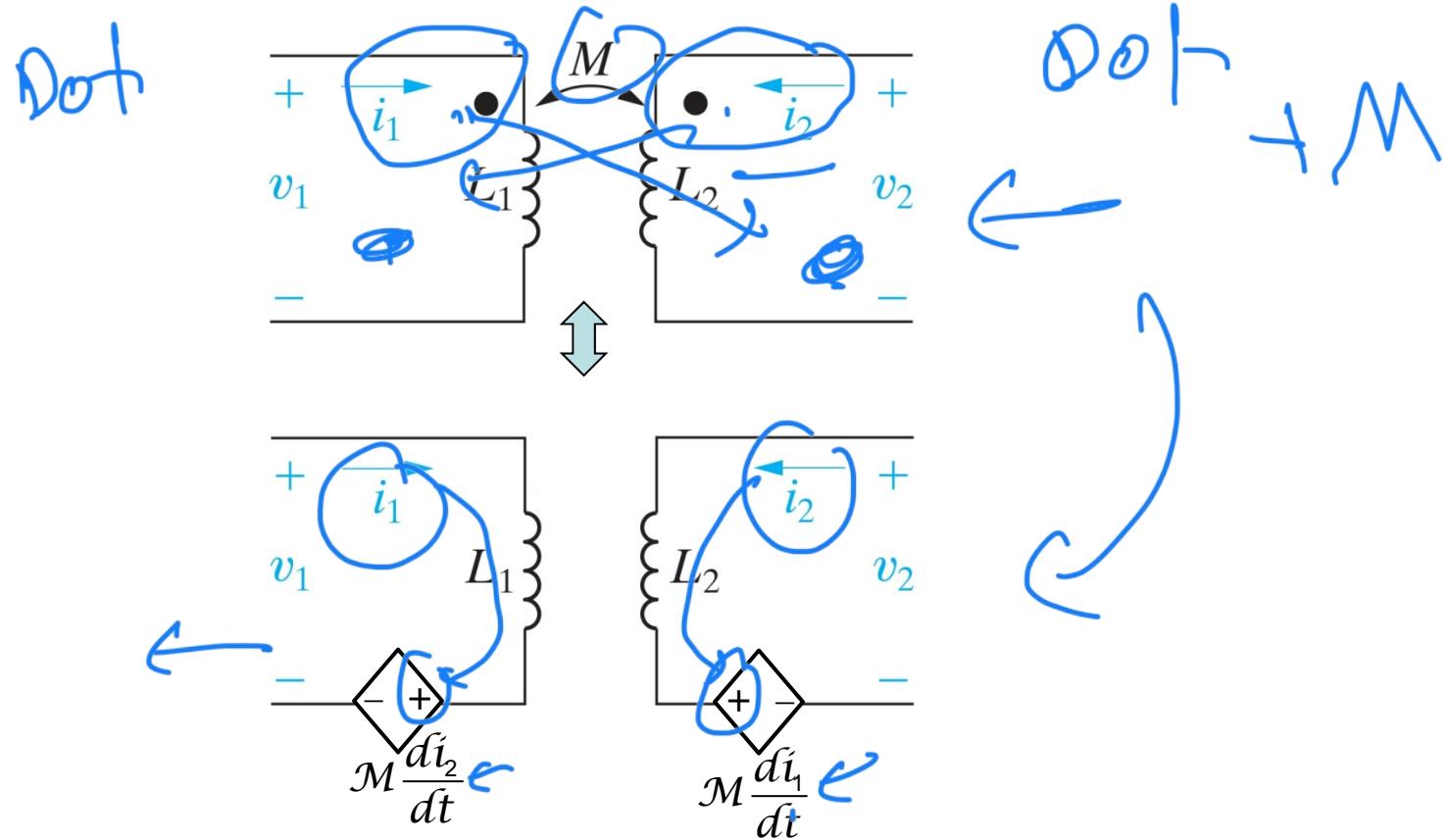


- The dependent source voltages are determined by the derivatives of the currents. The polarities of the sources are identified from the dot convention.

Example: Mesh Current Equations

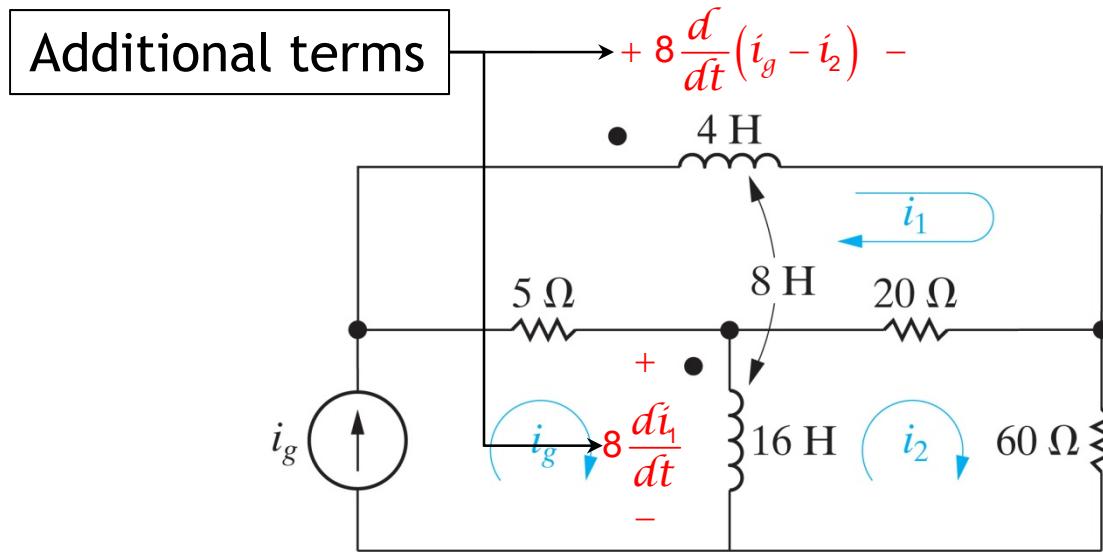

$$i_1 \text{ mesh} : 4 \frac{d i_1}{d t} + 8 \frac{d}{d t} (i_g - i_2) + 20 (i_1 - i_2) + 5 (i_1 - i_g) = 0$$
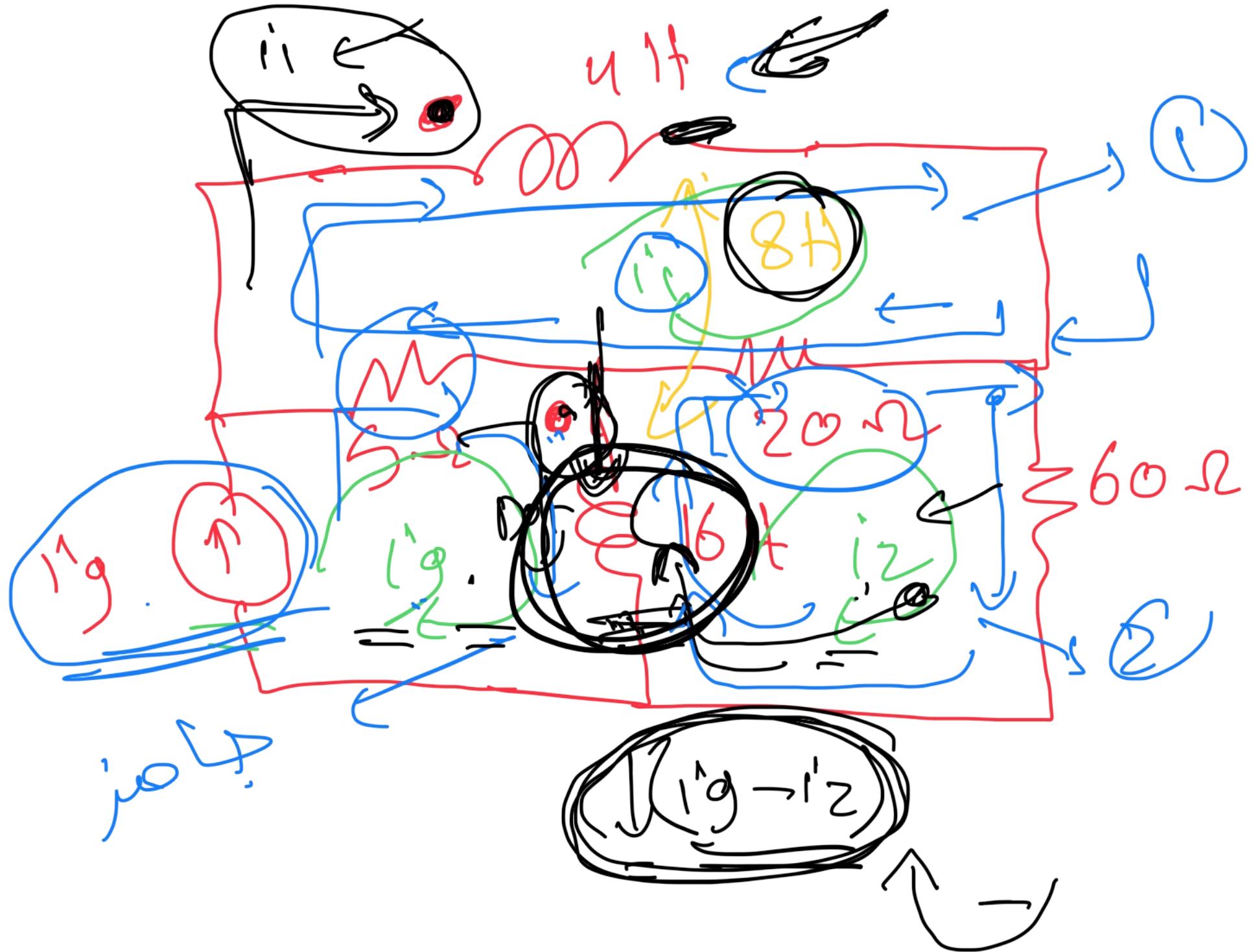
$$i_2 \text{ mesh} : 20 (i_2 - i_1) + 60 i_2 + 16 \frac{d}{d t} (i_2 - i_g) - 8 \frac{d i_1}{d t} = 0$$



mesh $\neq 1$

$$20(i_1 - i_2) + 5(i_1 - i_g) = 0$$


$$+ u \frac{\partial i_1}{\partial t} + 8 \frac{\partial}{\partial t}(i_g - i_2) = 0$$

mesh $\neq 2$

$$60i_2 + 16 \frac{\partial}{\partial t}(i_2 - i_g) + 20(i_2 - i_1) - 8 \frac{\partial}{\partial t}i_1 = 0$$


Procedure for Determining Dot Markings

- Arbitrarily select and mark a terminal, say D, with a dot.
- Assign a current i_D to it.
- Determine the direction of the induced magnetic flux, ϕ_D , based on the right-hand rule.
- Arbitrarily pick a terminal of the second coil, say A, and apply the same steps again.
- If the directions ϕ_A and ϕ_D are the same, then place a dot on A.
- If the directions are opposite, place a dot on the other terminal.

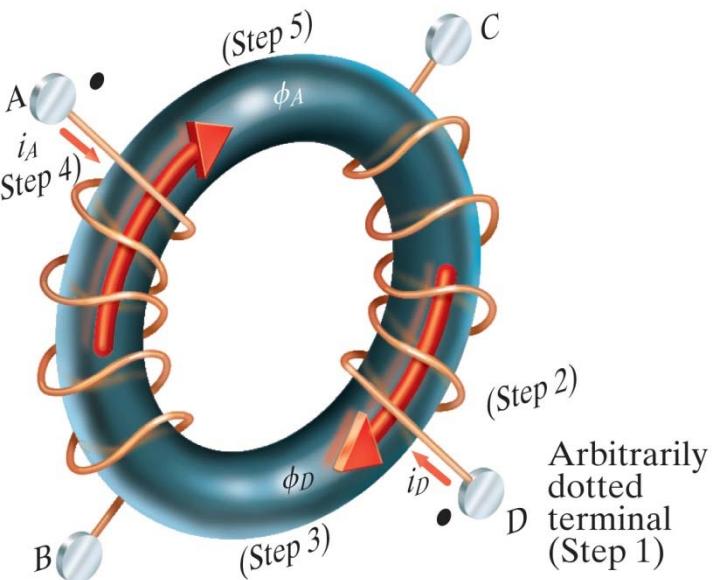

Experimental Setup for Dot Marking


AC
=

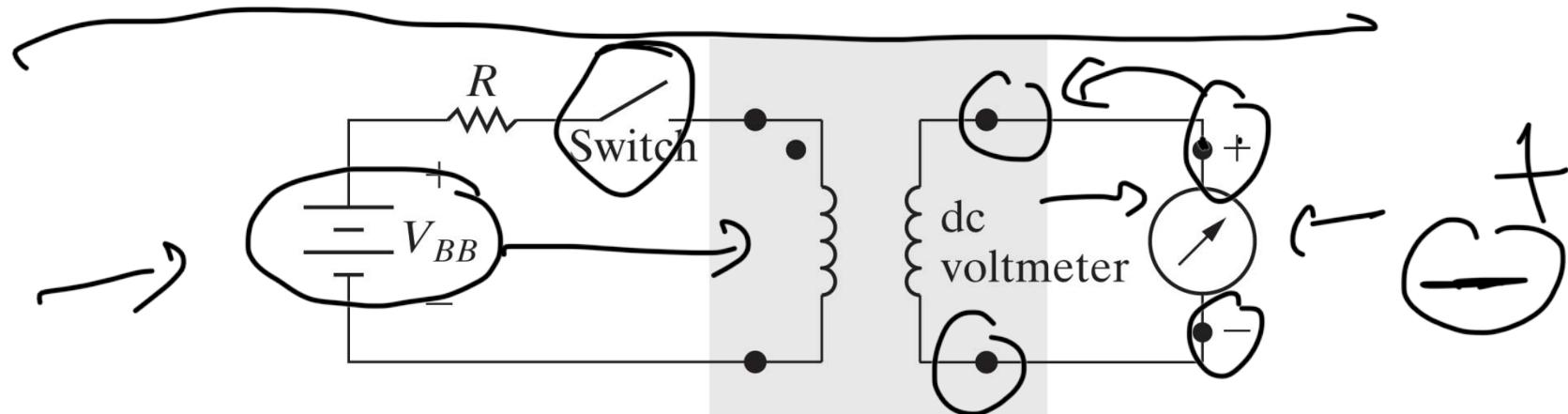

- Put a dot on the terminal to which the resistor is connected.
- Observe the momentary deflection of the DC voltmeter when the switch is closed.
- If it is upscale/downscale, put a dot on the terminal connected to the positive/negative terminal of the voltmeter.

$$W_L = \frac{1}{2} L c'^2$$

Energy Calculations

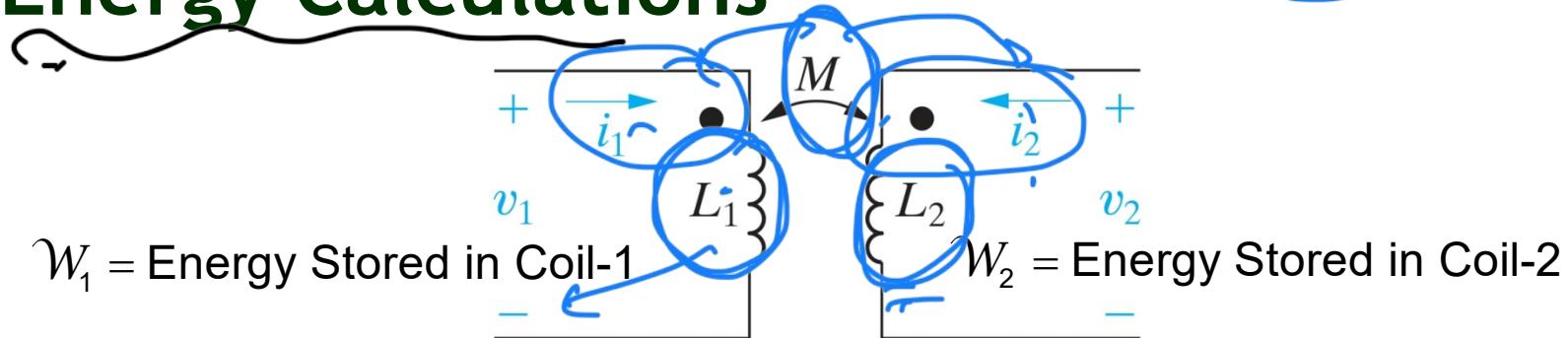

➤ Assume zero initial energy.

➤ Increase i_1 from zero to I_1 :

$$\mathcal{W}_1^1 = \int_{i_1=0}^{i_1=I_1} i_1 \cdot \mathcal{L}_1 \frac{di_1}{dt} dt = \int_0^{I_1} \mathcal{L}_1 i_1 di_1 = \frac{1}{2} \mathcal{L}_1 I_1^2; \quad \mathcal{W}_2^1 = 0$$

➤ Keep $i_1 = I_1$ constant; increase i_2 from zero to I_2 :

$$\mathcal{W}_1^2 = \int_{i_2=0}^{i_2=I_2} I_1 \cdot \mathcal{M}_{12} \frac{di_2}{dt} dt = I_1 I_2 \mathcal{M}_{12}; \quad \mathcal{W}_2^2 = \int_{i_2=0}^{i_2=I_2} i_2 \cdot \mathcal{L}_2 \frac{di_2}{dt} dt = \frac{1}{2} \mathcal{L}_2 I_2^2$$

➤ Total energy stored in the coils:

$$\mathcal{W} = \mathcal{W}_1^1 + \mathcal{W}_1^2 + \mathcal{W}_2^1 + \mathcal{W}_2^2 = \frac{1}{2} \mathcal{L}_1 I_1^2 + \frac{1}{2} \mathcal{L}_2 I_2^2 + \mathcal{M}_{12} I_1 I_2$$

$$\mathcal{M} = \mathcal{M}_{12} = \mathcal{M}_{21}$$

Total Energy Stored in the Coils

- Total energy stored in the coils at time t (with the dot marking not specified) :

$$W(t) = \frac{1}{2} \mathcal{L}_1 i_1^2(t) + \frac{1}{2} \mathcal{L}_2 i_2^2(t) \pm \mathcal{M}_{12} i_1(t) i_2(t)$$

- When the order of the procedure is reversed:

$$W(t) = \frac{1}{2} \mathcal{L}_1 i_1^2(t) + \frac{1}{2} \mathcal{L}_2 i_2^2(t) \pm \mathcal{M}_{21} i_1(t) i_2(t)$$

Self
Mutual

- For linear coupling media $\mathcal{M}_{12} = \mathcal{M}_{21} = \mathcal{M}$, which means that the total energies stored are the same.
- Determining the sign: If both currents are entering or leaving the dotted terminals, then the sign is positive; otherwise the sign is negative.

+
=

→ plus work is
dot is minus is
axis right, left

↖
↖
↗
↗



undot

dot leads
no right dot

Positivity of the Total Energy

- Consider finding the i_2 that minimizes \mathcal{W} :

$$\begin{aligned}\mathcal{W}(i_2) &= \frac{1}{2} \mathcal{L}_1 i_1^2 + \frac{1}{2} \mathcal{L}_2 i_2^2 \pm \mathcal{M} i_1 i_2 \\ \Rightarrow \frac{d\mathcal{W}(i_2)}{di_2} &= \mathcal{L}_2 i_2 \pm \mathcal{M} i_1 \text{ and } \frac{d^2\mathcal{W}(i_2)}{di_2^2} = \mathcal{L}_2 > 0\end{aligned}$$


- Equate the first derivative to zero find the minimum:

$$\mathcal{L}_2 i_2^\circ \pm \mathcal{M} i_1 = 0 \Rightarrow i_2^\circ = \mp \frac{\mathcal{M}}{\mathcal{L}_2} i_1 = \mp k \sqrt{\frac{\mathcal{L}_1}{\mathcal{L}_2}} i_1$$

- Since the energy is \geq its minimum value, we have:


$$\mathcal{W}(i_2) \geq \mathcal{W}(i_2^\circ) = \frac{1}{2} \mathcal{L}_1 i_1^2 + \left(\frac{1}{2} \mathcal{L}_2 i_2^\circ \pm \mathcal{M} i_1 \right) i_2^\circ = \frac{1}{2} (1 - k^2) \mathcal{L}_1 i_1^2 \geq 0$$

Transformers

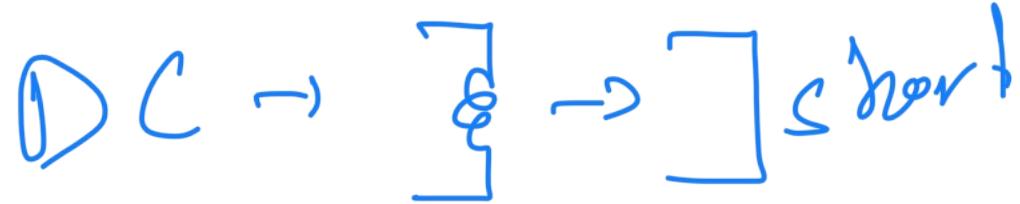


- Transformer is a device based on magnetic coupling.
- In communication circuits, transformers are used to match impedances and eliminate DC signals.
- In power circuits, transformers are used to establish AC voltage levels that facilitate the transmission, distribution and consumption of electrical power.
- We will first analyze the steady-state behavior of the linear transformer, which is common in communication systems.
- We will then study the ideal transformer, which models the ferromagnetic transformer used in power systems.


Transformers

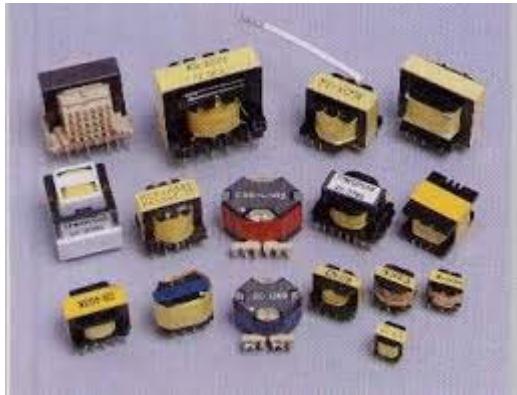


The Linear Transformer

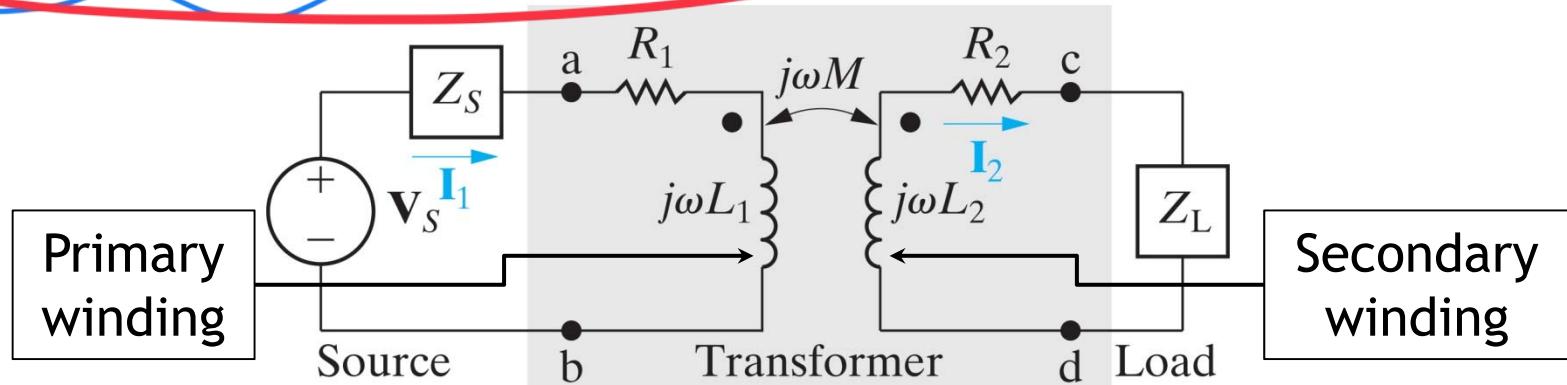

\mathcal{R}_1	Resistance of the primary winding
\mathcal{R}_2	Resistance of the secondary winding
\mathcal{L}_1	Self-inductance of the primary winding
\mathcal{L}_2	Self-inductance of the secondary winding
\mathcal{M}	Mutual inductance
\mathcal{V}_s	Source voltage
Z_s	Source impedance
Z_L	Load impedance
I_1	Primary current
I_2	Secondary current

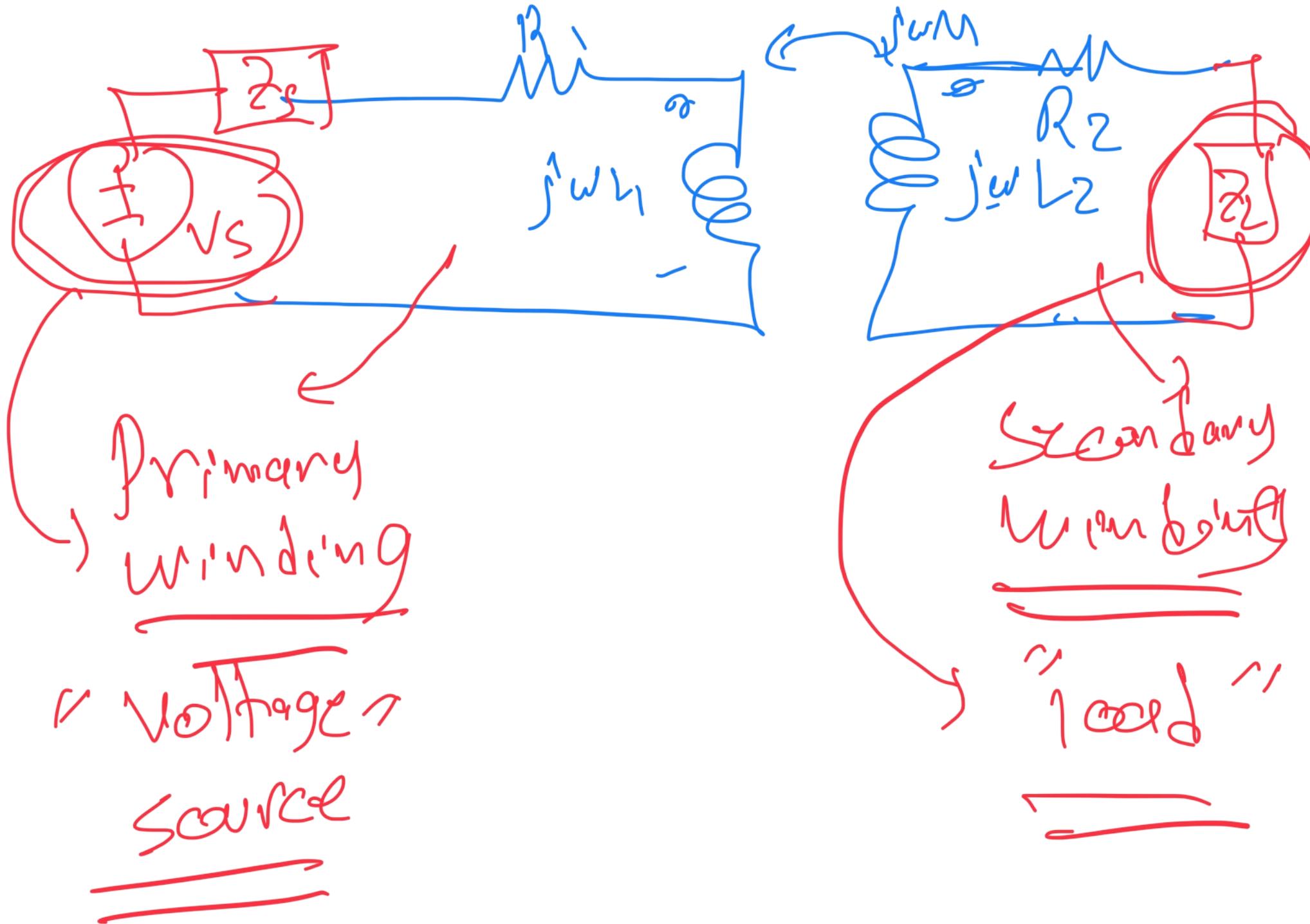

Analysis of a Linear Transformer

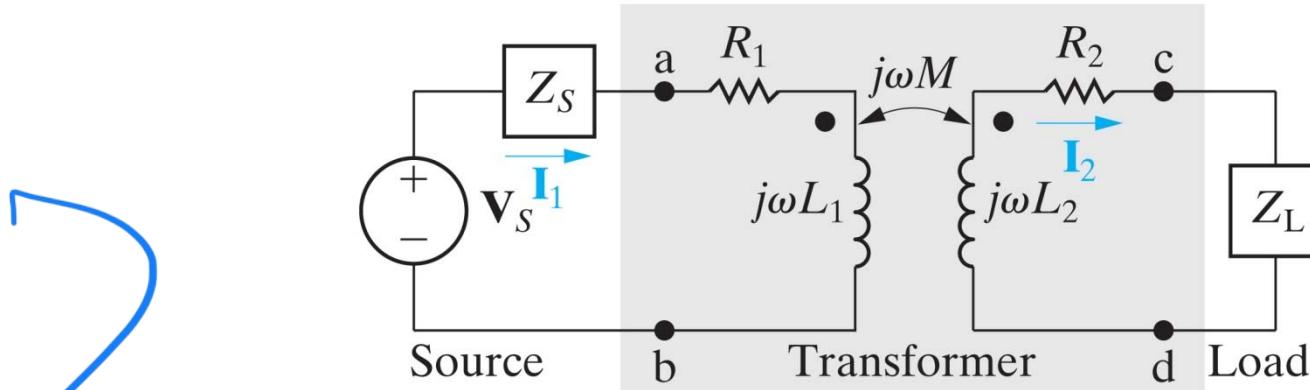

➤ Phasor analysis is adapted easily: $dx/dt \leftrightarrow j\omega \times \mathbf{x}$



$$\underbrace{(Z_s + R_1 + j\omega L_1)}_{Z_{11}} \mathbf{I}_1 - j\omega M \mathbf{I}_2 = \mathbf{V}_s$$

$Z_{11} \leftarrow$ Self impedance of the primary

$$\underbrace{(Z_L + R_2 + j\omega L_2)}_{Z_{22}} \mathbf{I}_2 - j\omega M \mathbf{I}_1 = 0$$

$Z_{22} \leftarrow$ Self impedance of the secondary

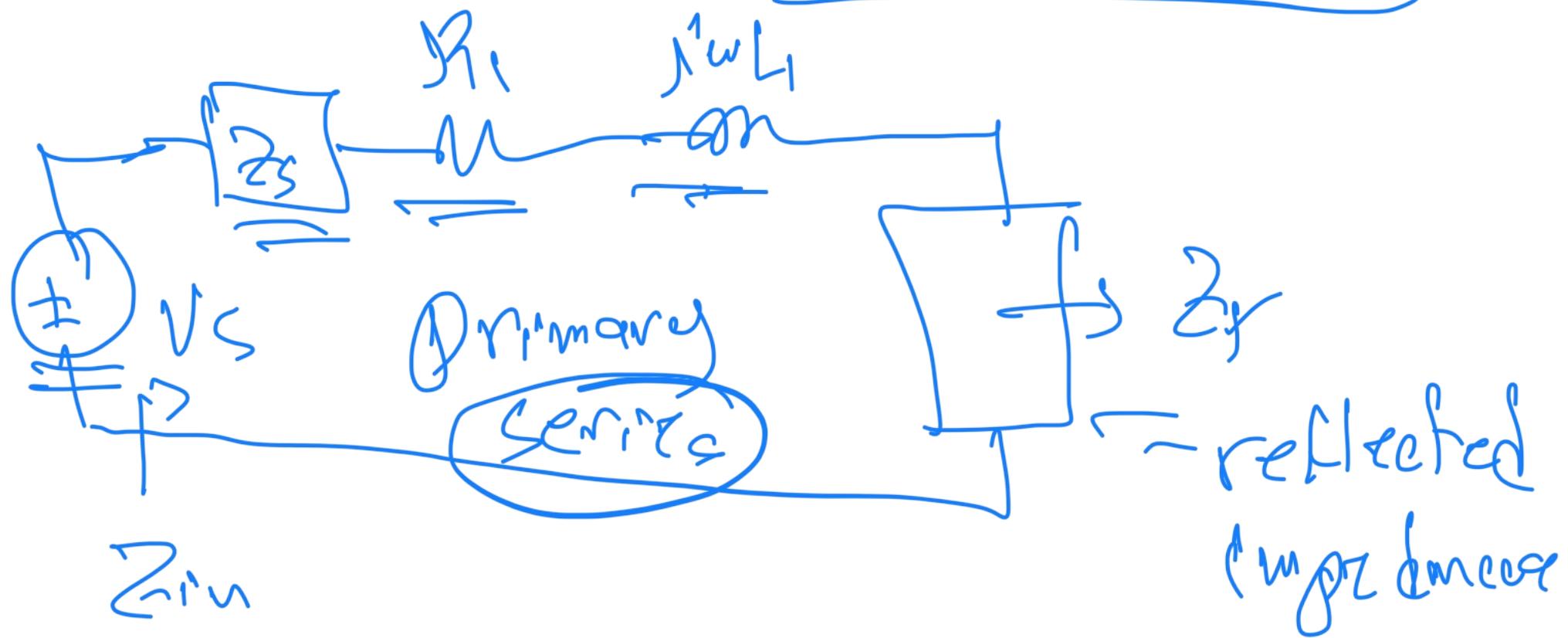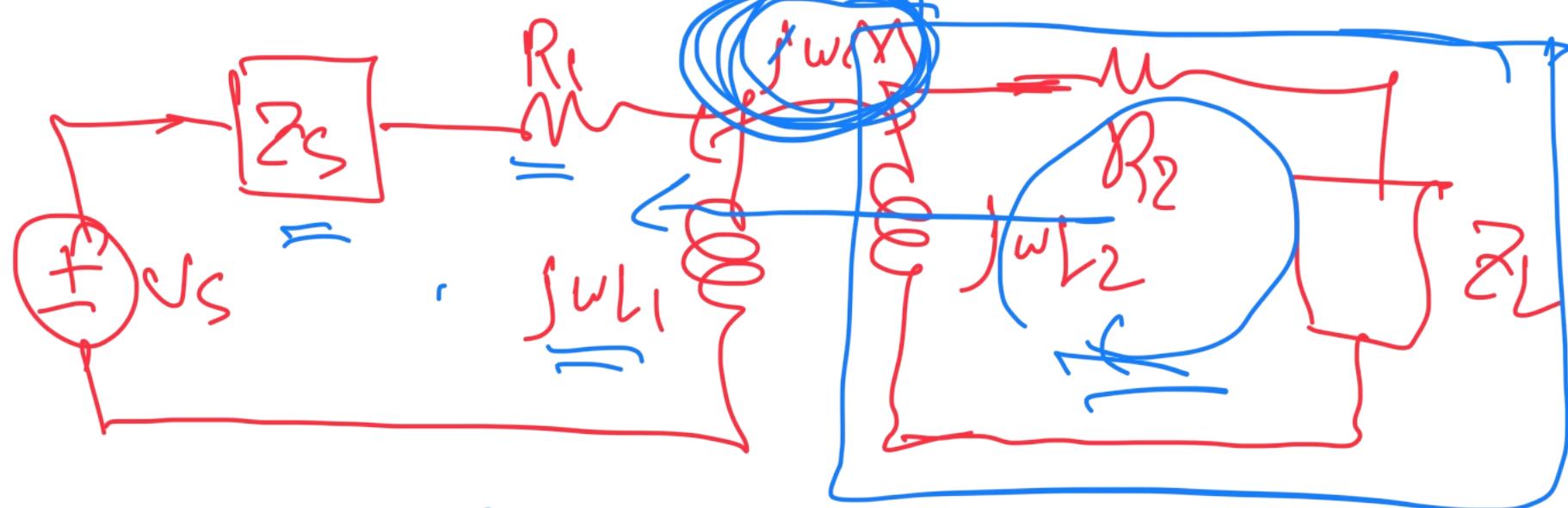
$$\Rightarrow \mathbf{I}_2 = \frac{j\omega M}{Z_{22}} \mathbf{I}_1 \quad \text{and} \quad \mathbf{I}_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} \mathbf{V}_s$$



$$Z_f = \frac{w^2 M^2}{R_2 + jwL_2 + 2L}$$

$$Z_{in} = Z_f + R_1 + jwL_1 + 2r$$

The Impedance Seen by the Source

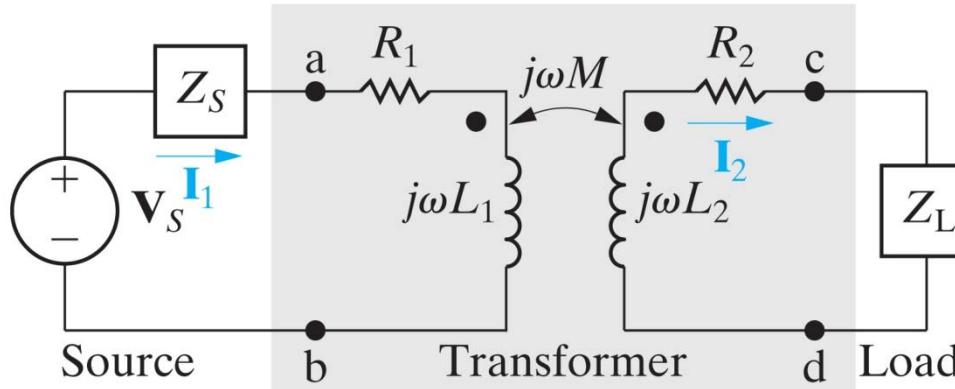

- The impedance seen from the nodes a and b is:

$$Z_{ab} = \frac{\mathcal{V}_s}{I_1} - Z_s = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s = \mathcal{R}_1 + j\omega \mathcal{L}_1 + \frac{\omega^2 M^2}{\mathcal{R}_2 + j\omega \mathcal{L}_2 + Z_L}$$

Z_r : Reflected impedance

- A key role of the transformer is thus revealed:
Changing the impedance seen by the source:

$$Z_L \rightarrow Z_{ab} = \mathcal{R}_1 + j\omega \mathcal{L}_1 + Z_r (Z_L)$$

The Reflected Impedance

- Impedance of the second coil plus load is transmitted to the primary side via the mutual inductance:

$$Z_r = \frac{\omega^2 \mathcal{M}^2}{R_2 + j\omega L_2 + Z_L}$$

- When the load impedance is $Z_L = R_L + jX_L$, we have:

$$Z_r = \frac{\omega^2 \mathcal{M}^2}{(R_2 + R_L)^2 + (\omega L_2 + X_L)^2} [(R_2 + R_L) - j(\omega L_2 + X_L)]$$

Scaling Factor

- The impedance is thus conjugated and then scaled during the reflection.


$$Z_V = \frac{\omega^2 M^2}{R_2 + \cancel{\omega L Z} + \cancel{Z_L}} \leftarrow Z_L = R_L + j \frac{X_L}{\cancel{=}}$$

Scaling factor \rightarrow

$$\frac{\omega^2 M^2}{(R_2 + R_L)^2 + (\omega L_2 + X_L)^2}$$

$$Z_V = f \times [(R_2 + R_L) - j(\omega L_2 + X_L)]$$

Example: Linear Transformer Circuit

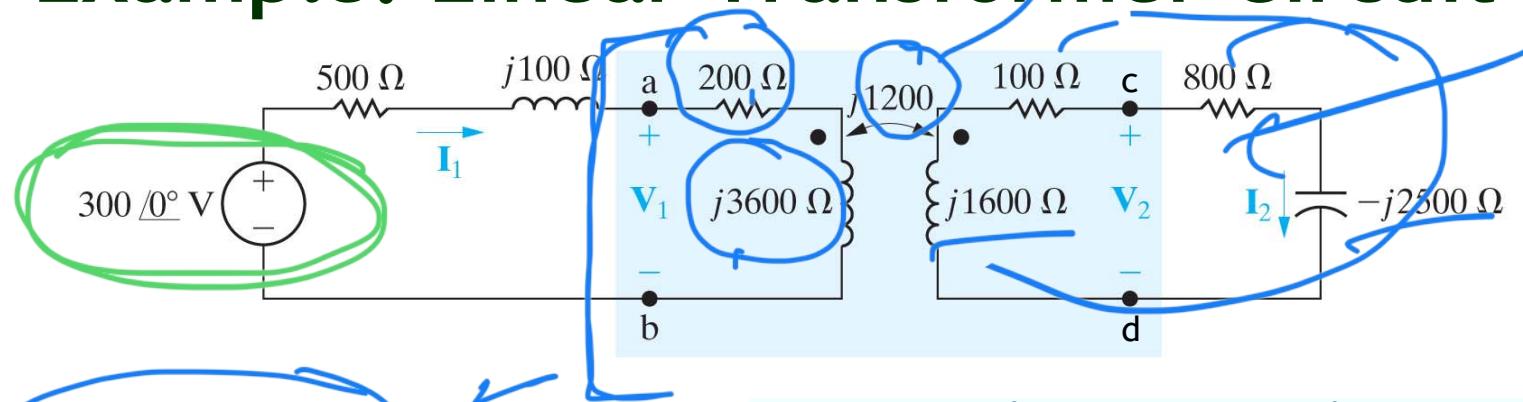

- Scaling factor:
- Reflected impedance:
- Impedance seen from a - b:
- Thevenin equivalent seen from c - d:

$$= \frac{1200^2}{|800+100+1600j-2500j|^2} = \frac{1200^2}{|900-900j|^2} = \frac{1200^2}{900^2+900^2} = \frac{8}{9}$$

$$= \frac{8}{9}(900 + 900j) = 800 + 800j \Omega$$


$$= 200 + 3600j + 800 + 800j = 1000 + 4400j \Omega$$

$$Z_{th} = 100 + 1600j + \frac{1200^2}{700^2 + 3700^2} (700 - 3700j)$$

$$= 171.09 + 1224.26j \Omega$$

$$V_{th} = 1200j \times \frac{300}{500 + 200 + (100 + 3600)j}$$

$$= 95.6 \angle 10.71^\circ V$$

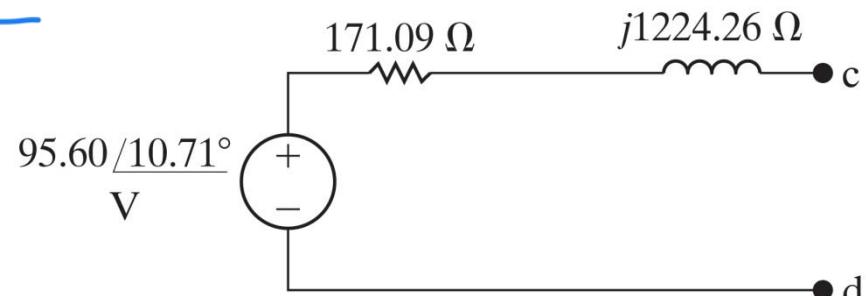

Scaling factor

$$Z_f = \frac{w^2 M^2}{R_2 + j w L_2 + j C}$$

$$Z_f = \frac{1200^2}{100 + 800 + j 2500 + j 1600} \rightarrow j 900$$

Real Part Imag Part

$$f = \frac{1200^2}{900^2 + 900^2} = \frac{8}{9}$$


$$Z_g = \frac{1200^2}{100 + 300 - j2500 + j1600}$$

$$Z_g = 800 + j800$$


$$200 \quad j3600$$

$$800 + j800$$

$$200 + j3600 + 800 + j3600$$

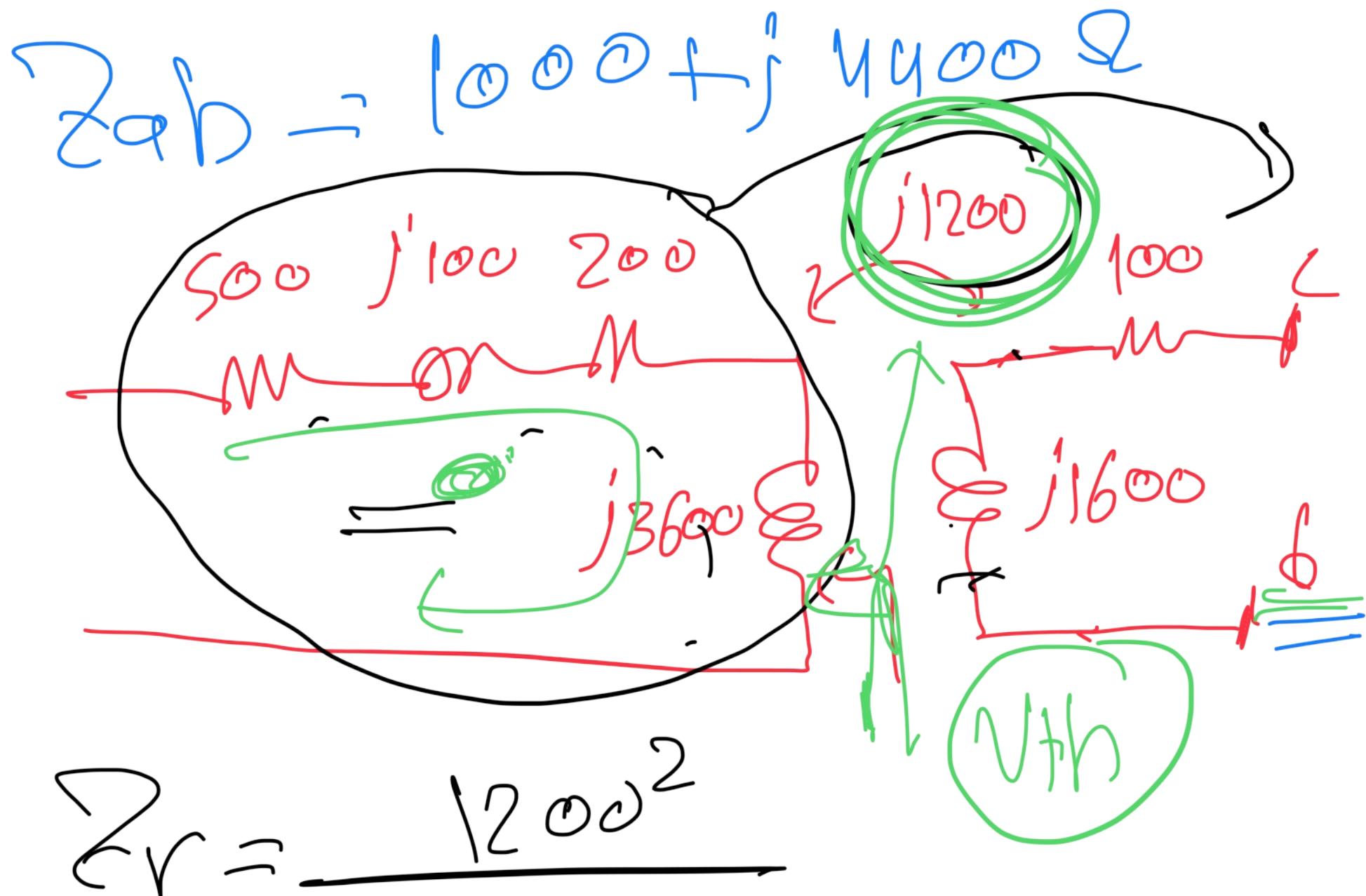

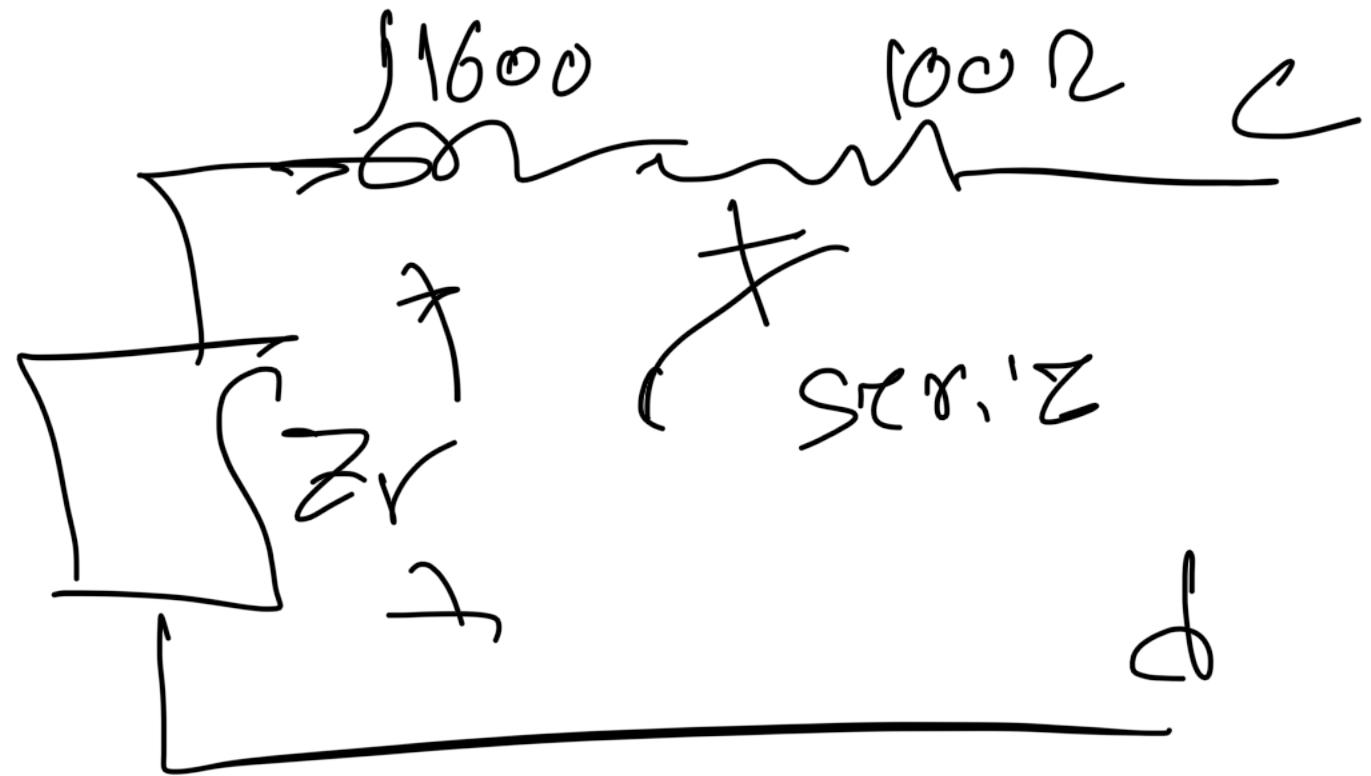
$$Z_L = \frac{1200^2}{500 + j100 + 200 + j3600}$$




$$Z_0 = 71,086 - j375,71 \Omega$$
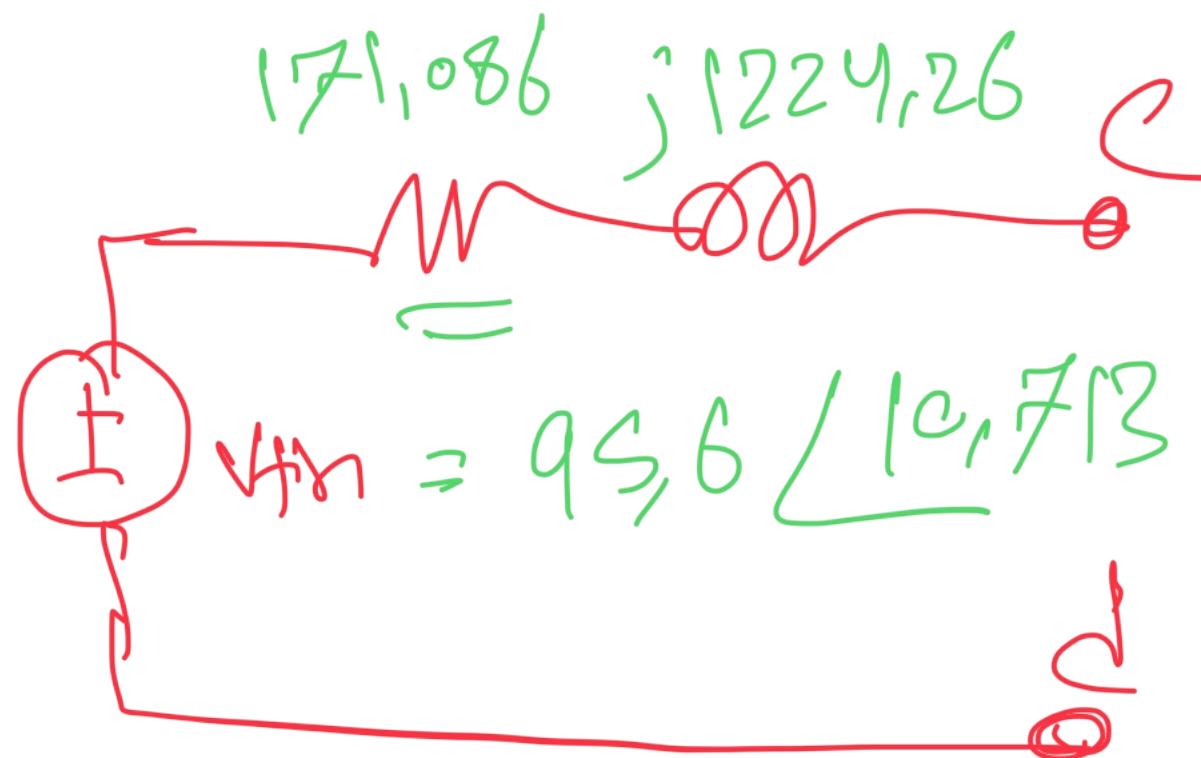
$$Z_{cd} = 171,086 \cancel{+ j1724,76 \Omega} + \cancel{j1724,76 \Omega}$$




$$\begin{aligned}
 V_{th} &= \frac{j1200}{500 + j100 + 200 + j3600} \times 300 \\
 &\equiv 95,6 \angle 10,713
 \end{aligned}$$

The Ideal Transformer

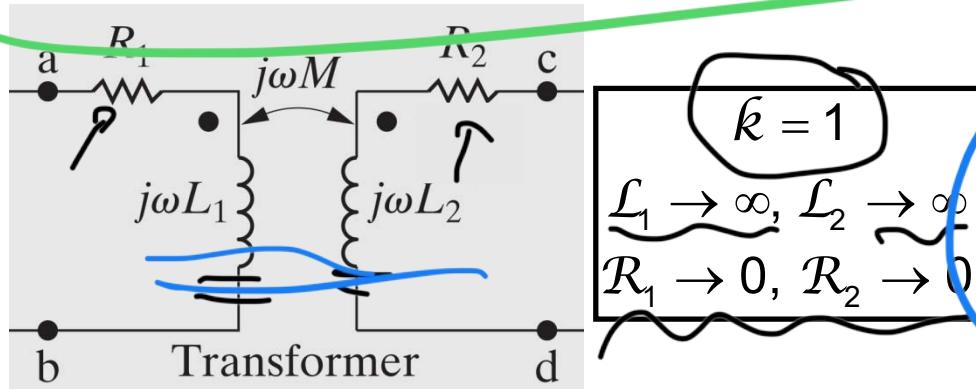

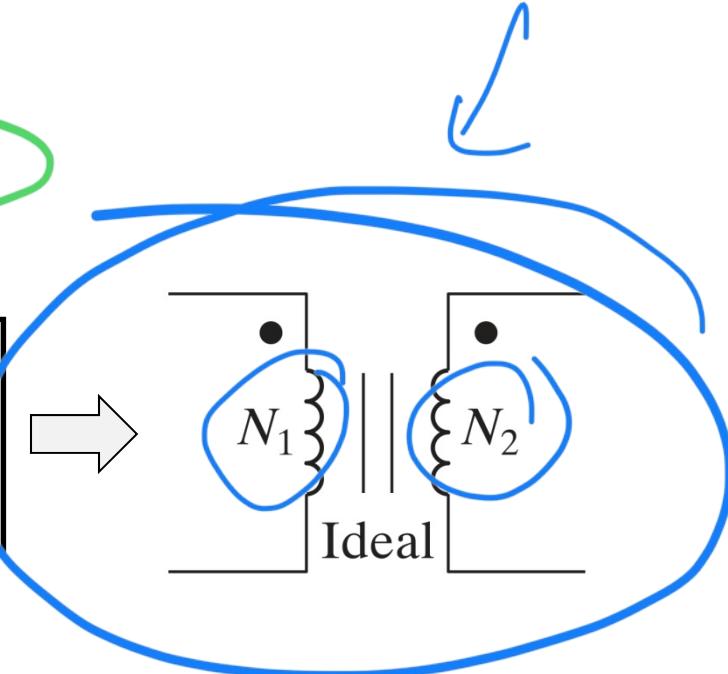
$$\begin{aligned}
 k &= 1 \\
 L_1 &\rightarrow \infty, L_2 \rightarrow \infty \\
 R_1 &\rightarrow 0, R_2 \rightarrow 0
 \end{aligned}$$



- An ideal transformer consists of two magnetically coupled coils having N_1 and N_2 turns respectively, and exhibiting the following three properties:
 - The coefficient of coupling is unity. $k = 1$
 - The self-inductance of each coil is infinite.
 - The coil losses, due to parasitic resistances, are negligible. $R = 0$

Analysis of the Limit Values

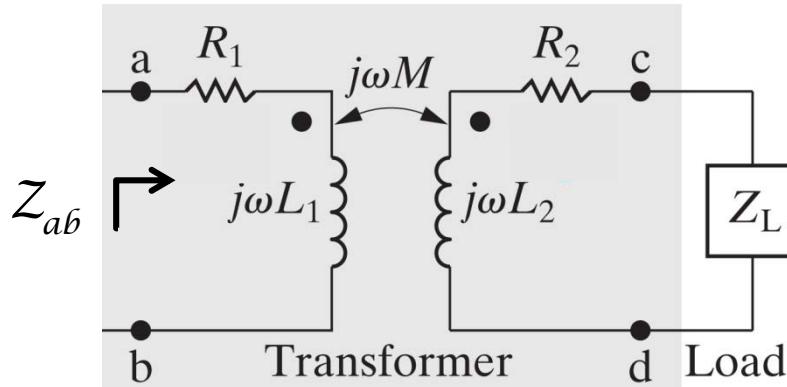

$$Z_{ab} = \underbrace{\mathcal{R}_1 + \frac{\omega^2 \mathcal{M}^2 (\mathcal{R}_2 + \mathcal{R}_L)}{(\mathcal{R}_2 + \mathcal{R}_L)^2 + (\omega \mathcal{L}_2 + \mathcal{X}_L)^2}}_{\mathcal{R}_{ab}} + j \underbrace{\left(\omega \mathcal{L}_1 - \frac{\omega^2 \mathcal{M}^2 (\omega \mathcal{L}_2 + \mathcal{X}_L)}{(\mathcal{R}_2 + \mathcal{R}_L)^2 + (\omega \mathcal{L}_2 + \mathcal{X}_L)^2} \right)}_{\mathcal{X}_{ab}}$$

➤ Setting $\mathcal{M}^2 = \mathcal{L}_1 \mathcal{L}_2$ and letting $\mathcal{L}_1 \rightarrow \infty$, $\mathcal{L}_2 \rightarrow \infty$, we find:

$$\mathcal{R}_{ab} = \mathcal{R}_1 + \left(\frac{\mathcal{L}_1}{\mathcal{L}_2} \right) \left(\frac{(\mathcal{R}_2 + \mathcal{R}_L)}{(\mathcal{R}_2 + \mathcal{R}_L)^2 / (\omega \mathcal{L}_2)^2 + (1 + \mathcal{X}_L / (\omega \mathcal{L}_2))^2} \right) \rightarrow \mathcal{R}_1 + \left(\frac{\mathcal{L}_1}{\mathcal{L}_2} \right) (\mathcal{R}_2 + \mathcal{R}_L)$$


$$\mathcal{X}_{ab} = \left(\frac{\mathcal{L}_1}{\mathcal{L}_2} \right) \left(\frac{(\mathcal{R}_2 + \mathcal{R}_L)^2 / (\omega \mathcal{L}_2) + \mathcal{X}_L + \mathcal{X}_L^2 / (\omega \mathcal{L}_2)}{(\mathcal{R}_2 + \mathcal{R}_L)^2 / (\omega \mathcal{L}_2)^2 + (1 + \mathcal{X}_L / (\omega \mathcal{L}_2))^2} \right) \rightarrow \left(\frac{\mathcal{L}_1}{\mathcal{L}_2} \right) \mathcal{X}_L$$

➤ As $k \rightarrow 1$, the two permeances \mathcal{P}_1 , \mathcal{P}_2 become equal:

$$\frac{\mathcal{L}_1}{\mathcal{L}_2} = \frac{\mathcal{N}_1^2 \mathcal{P}_1}{\mathcal{N}_2^2 \mathcal{P}_2} \rightarrow \left(\frac{\mathcal{N}_2}{\mathcal{N}_1} \right)^2 = a^2; \quad a: \text{turns ratio}$$

$$a = \frac{\mathcal{N}_2}{\mathcal{N}_1}$$

Ideal Transformer Relations

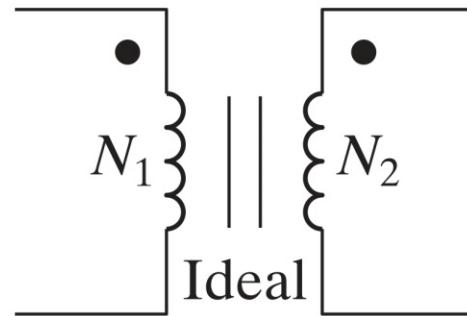


- The voltages of the primary and secondary windings of an ideal transformer are related as:

$$\left| \frac{\mathcal{V}_1}{\mathcal{N}_1} \right| = \left| \frac{\mathcal{V}_2}{\mathcal{N}_2} \right|$$

- The currents of the primary and secondary windings of an ideal transformer are related as:

$$|I_1 \mathcal{N}_1| = |I_2 \mathcal{N}_2|$$

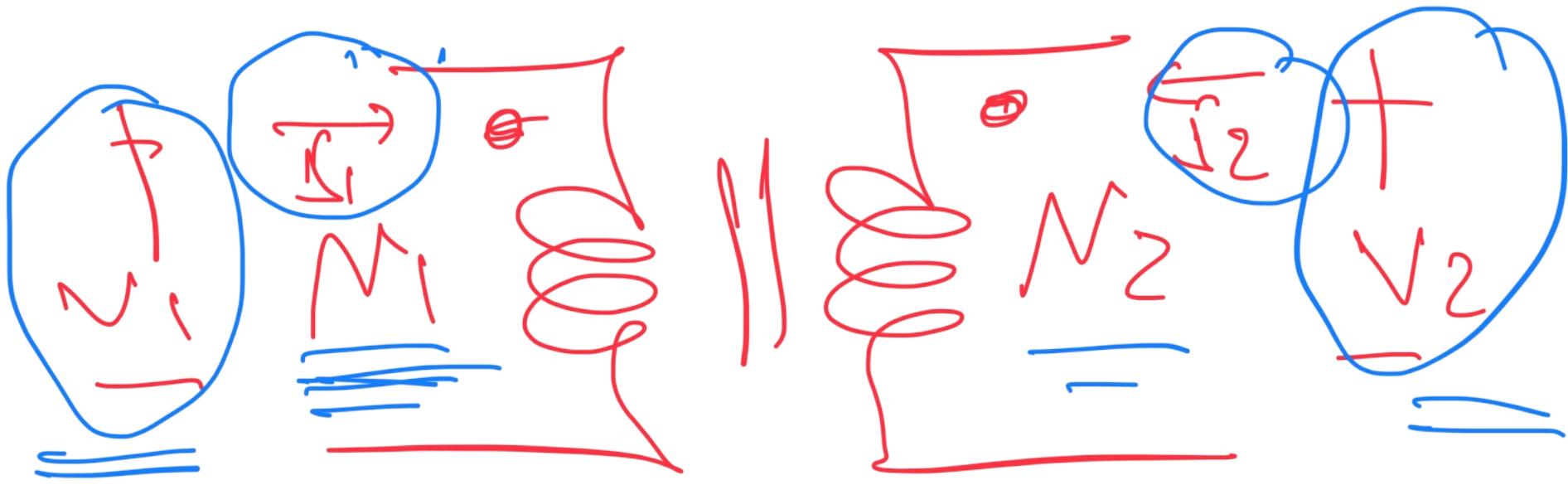- The polarities are determined via the dot convention.




$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

$$\frac{L_1}{L_2} = \frac{N_2}{N_1}$$

Below the equations, there are two diagrams. The first diagram shows a red vertical line with a red arrow pointing upwards, and a blue horizontal line with a blue arrow pointing to the right. The second diagram shows a blue horizontal line with a blue arrow pointing to the right, and a red vertical line with a red arrow pointing upwards.

Determining the Voltage-Current Ratios

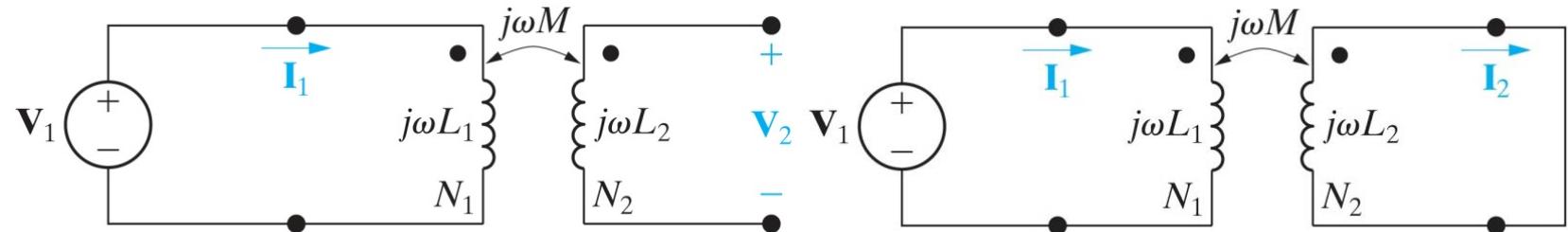

- The voltage ratio is determined using the left circuit:

Since $I_2 = 0$, we have $\mathcal{V}_2 = j\omega M I_1 = \frac{j\omega M}{j\omega L_1} \mathcal{V}_1$.


With $M = \sqrt{L_1 L_2}$, it follows that $\frac{\mathcal{V}_1}{\mathcal{V}_2} = \sqrt{\frac{L_1}{L_2}} = \sqrt{\frac{\mathcal{N}_1^2 \mathcal{P}}{\mathcal{N}_2^2 \mathcal{P}}} = \frac{\mathcal{N}_1}{\mathcal{N}_2}$.

- The current ratio is determined using the right circuit:


Since $\mathcal{V}_2 = 0$, we have $j\omega M I_1 - j\omega L_2 I_2 = 0$.

With $M = \sqrt{L_1 L_2}$, it follows that $\frac{I_1}{I_2} = \sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{\mathcal{N}_2^2 \mathcal{P}}{\mathcal{N}_1^2 \mathcal{P}}} = \frac{\mathcal{N}_2}{\mathcal{N}_1}$.


Determining the Polarities

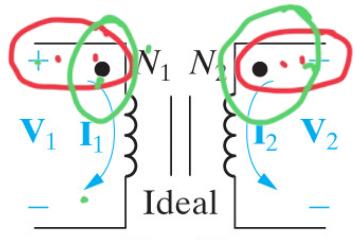

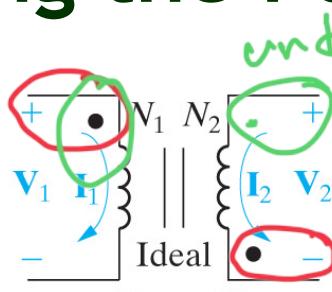
$$\rightarrow \frac{V_1}{N_1} = \frac{V_2}{N_2}, \\ N_1 I_1 = -N_2 I_2$$


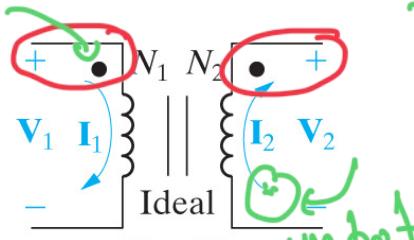
$$\frac{V_1}{N_1} = \frac{V_2}{N_2}, \\ N_1 I_1 = N_2 I_2$$



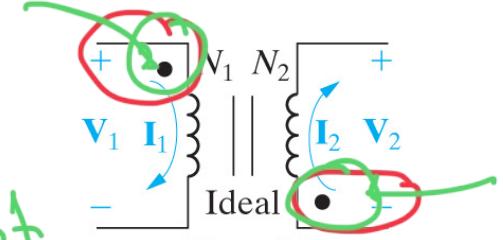
$$\frac{V_1}{N_1} = \frac{V_2}{N_2}, \\ N_1 I_1 = N_2 I_2$$



$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}, \\ N_1 I_1 = -N_2 I_2$$

- If the coil voltages are both positive or negative at the dot-marked terminal, use a plus sign in the voltage ratio; otherwise, use a minus sign.
- If the coil currents are both directed into or out of the dot-marked terminal, use a minus sign in the current ratio; otherwise, use a plus sign.

Ideal Transformer for Impedance Matching

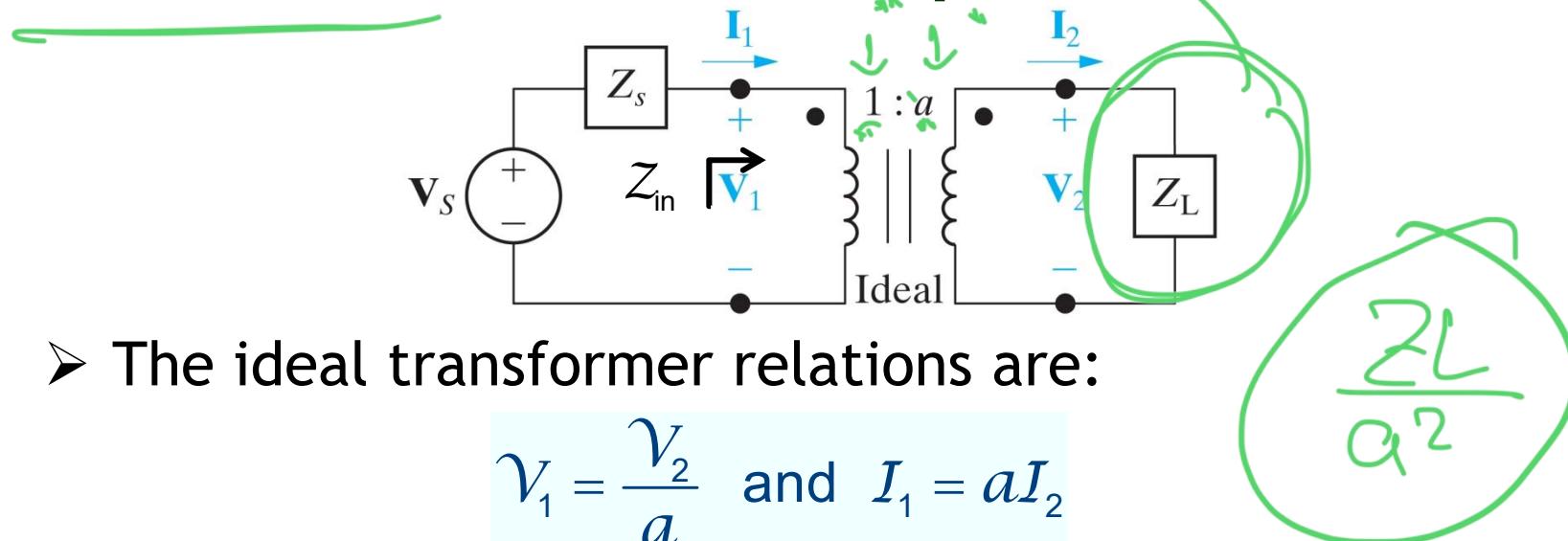

- The ideal transformer relations are:


$$V_1 = \frac{V_2}{a} \text{ and } I_1 = aI_2$$

- Then the impedance seen by the practical source is:

$$Z_{in} = \frac{V_1}{I_1} = \frac{1}{a^2} \frac{V_2}{I_2} = \frac{1}{a^2} Z_L$$

- The practical version of the ideal transformer is the ferromagnetic core transformer. It is used to match the magnitude of Z_L to the magnitude of Z_s .

Example: Ideal Transformer Circuit

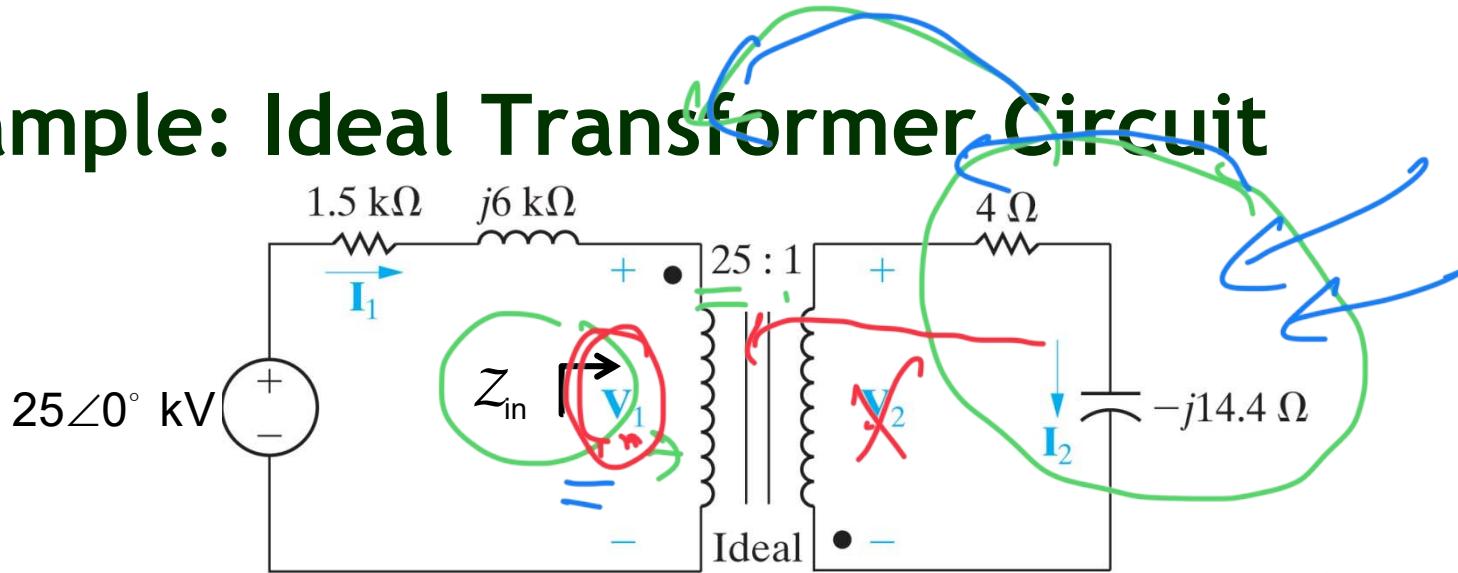

➤ Z_{in} : $= (25)^2 (4 - j14.4) = 2.5 - j9 \text{ k}\Omega$

~~$$\frac{Z_S}{Z_S} : \frac{1}{Z_S}$$~~

➤ V_1 : $= \frac{2.5 - j9.0}{4.0 - j3.0} 25 \text{ kV} = 46.703.85 \angle -37.61^\circ$


~~$$1 : 1$$~~

➤ V_2 : $= -V_1 / 25 = 1868.15 \angle 142.39^\circ$

➤ I_2 : $= -\frac{25 \text{ kV}}{4 - j3} \times 25 = 125 \angle 216.87^\circ \text{kA}$

$$Z_{in} = \frac{U - jIu, y}{(0, ou)^2} = 250 \Omega - j9000 \Omega$$

$$Z_{in} = \underline{Z_s} - j9 \Omega$$

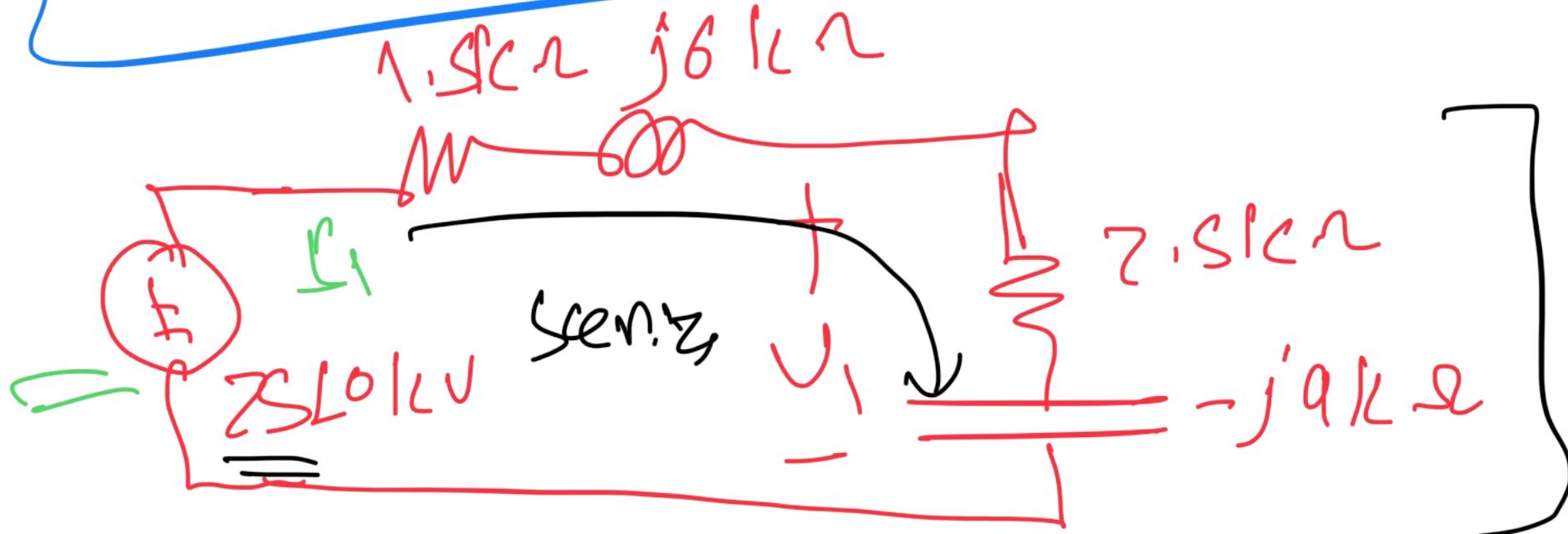

\Rightarrow Voltage Divider

~~N_1~~

$$N_1 = \frac{2 \cdot S - j9}{1, S + j6 + 2 \cdot S - j9} \times 2S \text{ k}$$

$$N_1 = 37 - j 28 \text{ S kV}$$




$$V_1 = 16,7 \angle -37,61^\circ \text{ V}$$

$$I_1 = \frac{N}{Z_{in}} = \frac{2S_k}{(1,5 + j6 + 2S - ja)k}$$

$$I_1 = 4 + j3 \text{ A}$$

$$= 5136,87 \text{ A}$$



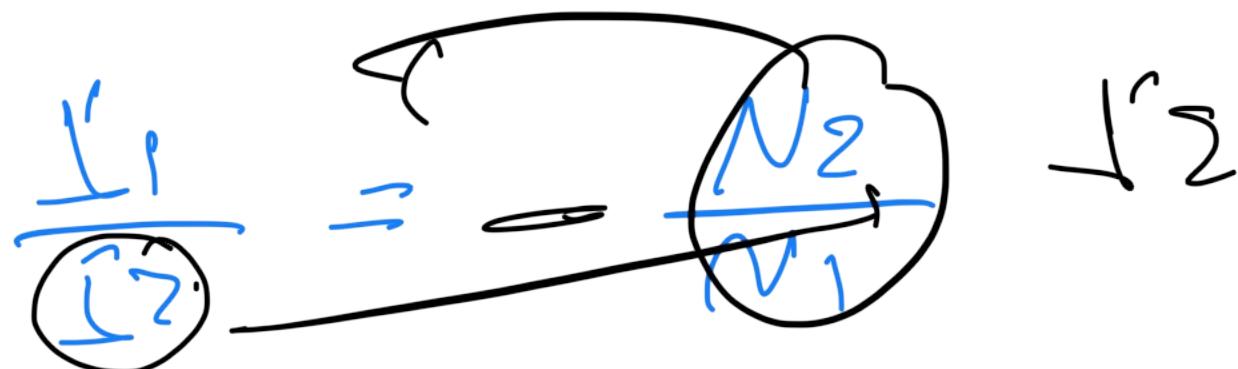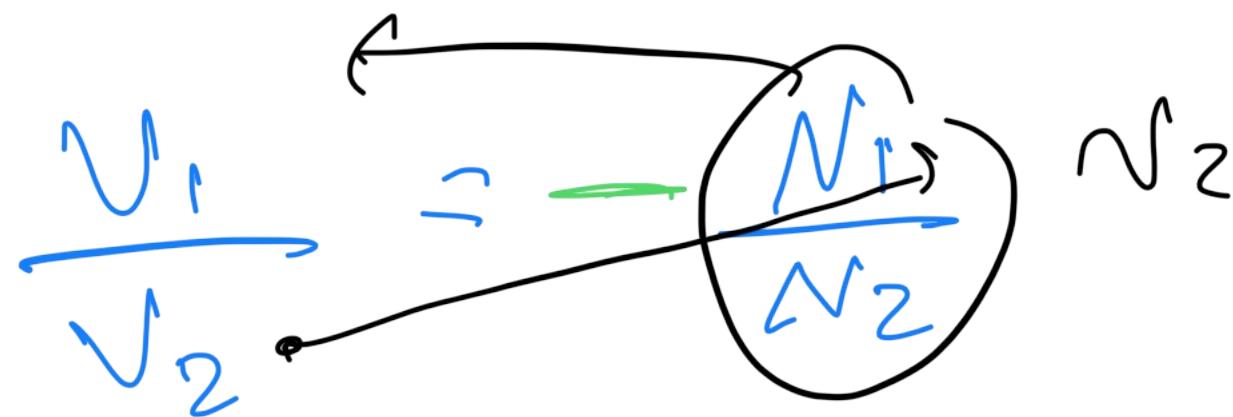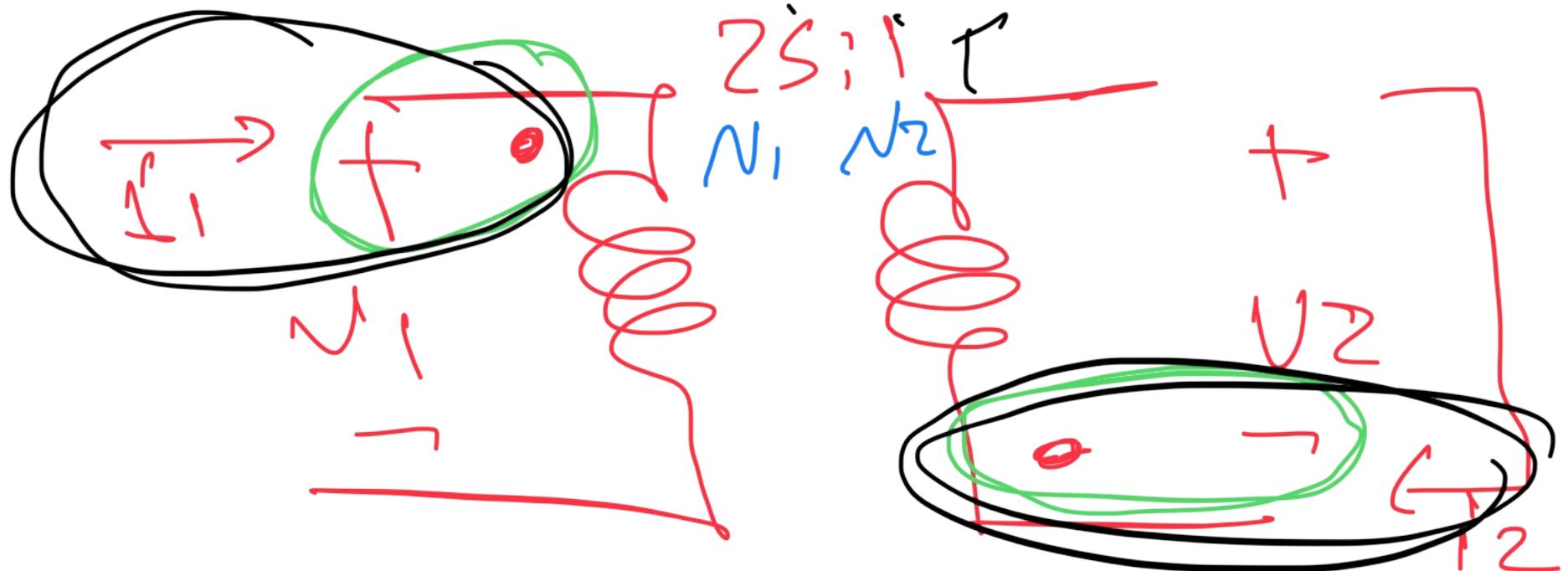

$$\Rightarrow V_2 = -\frac{N_2}{N_1} V_1$$

$$N_2 = -\frac{1}{25} \times 16,7 \underbrace{-37,6}_{\text{in}}$$

$$V_2 = -1,48 + j 1,14 \text{ kV}$$


$$V_2 = 1,868 \underbrace{143\text{V}}_{\text{in}} \text{ kV}$$

$$i_2 = -\frac{N_1}{N_2} i_1$$

$$i_2 = \left(-\frac{25}{1} \right) (5 \angle 36.8^\circ)$$

$$i_2 = -100 - j75 \text{ A}$$

$$\rightarrow 12S \angle 43.12^\circ$$

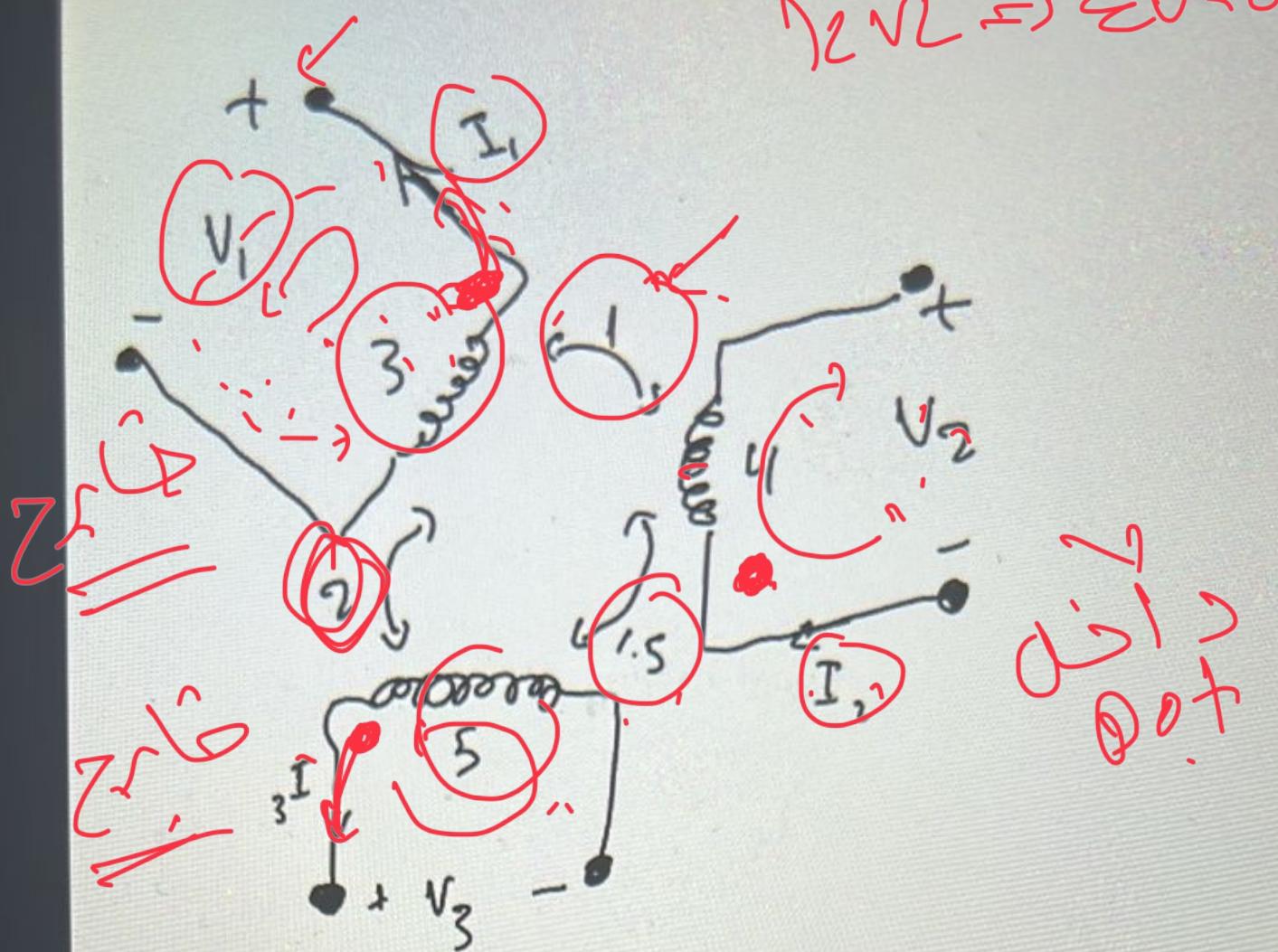

$$V_1 + 3 \frac{dI_1}{dt} - \frac{dI_2}{dt} + 2 \frac{dI_3}{dt} = 0 \Rightarrow$$

$$V_1 = -3 \frac{dI_1}{dt} + \frac{dI_2}{dt} - 2 \frac{dI_3}{dt}$$

$$V_2 + 4 \frac{dI_2}{dt} - \frac{dI_1}{dt} - 1.5 \frac{dI_3}{dt}$$

$$V_2 = \frac{dI_1}{dt} - 4 \frac{dI_2}{dt} + 1.5 \frac{dI_3}{dt}$$

$$V_3 + 5 \frac{dI_3}{dt} + 2 \frac{dI_1}{dt} - 1.5 \frac{dI_2}{dt}$$

$$V_3 = -2 \frac{dI_1}{dt} + 1.5 \frac{dI_2}{dt} - 5 \frac{dI_3}{dt}$$

$$+ V_1 + 3 \frac{\partial C_1}{\partial t} \stackrel{?}{=} 1 \frac{\partial C_2}{\partial t} \stackrel{?}{=} 2 \frac{\partial C_2}{\partial t}$$