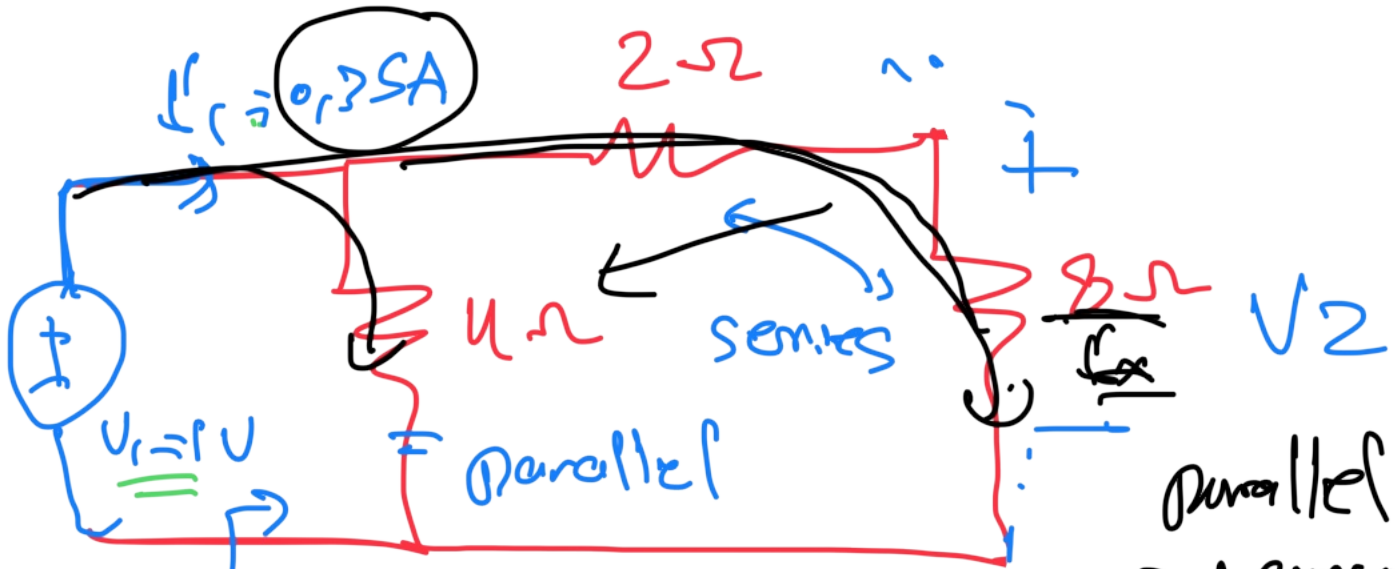


# Find Z parameter



parallel  
 $\rightarrow$  current divider

1

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$I_2 = 0$  open

$$Z_{11} = \frac{V_1}{I_1}$$

$$Z_{21} = \frac{V_2}{I_1}$$
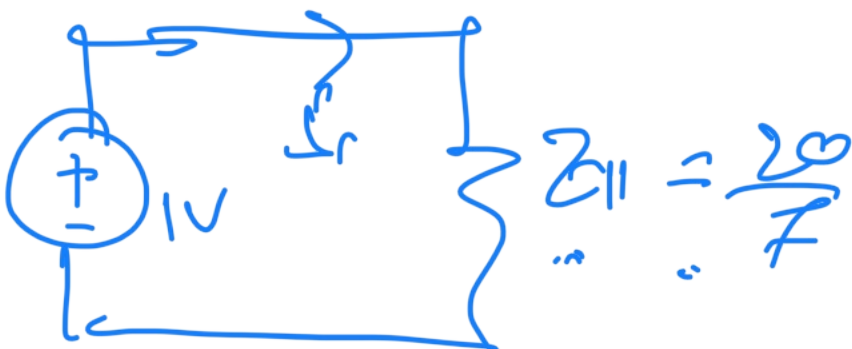
$$Z_{11} = \frac{1}{\frac{1}{4} + \frac{1}{2+8}} = \frac{20}{7} \Omega \leftarrow$$



$$I_1 = \frac{V}{Z_{total}}$$

$$I_1 = 0,35A$$

$$I_x = \frac{4}{4+2+8} \times 0,3S = 0,1A$$

$$V_2 = 8 \times 0,1 = 0,8V$$

$$Z_{11} = \frac{20}{7} \Omega$$

$$Z_{21} = \frac{0,8}{0,3S} = \frac{16}{7} \Omega$$



$$V_1 = I_1 Z_{11} + I_2 Z_{12}$$

$$V_2 = I_1 Z_{21} + I_2 Z_{22}$$

$I_1 \rightarrow \infty$  open

$$Z_{12} = \frac{V_1}{I_2}$$

$$Z_{22} = \frac{V_2}{I_2}$$

$$Z_{22} = \frac{1}{\frac{1}{8} + \frac{1}{4+2}} = \frac{24}{7} \Omega$$

$$I_2 = \frac{V_2}{Z_{22}} = \frac{1}{24/7} = \frac{7}{24} \text{ A} \quad \checkmark$$


$$I_y = \frac{8}{8+2+4} \times \frac{7}{24} = \frac{1}{6}$$

$$V_1 = 4 \times \frac{1}{6} = \frac{2}{3} \text{ V}$$

$$Z_{12} = \frac{2/3}{7/24} = 16/7$$

$$Z = \begin{bmatrix} \frac{20}{7} & 16/7 \\ 16/7 & 7/12 \end{bmatrix} \Omega$$

# Find Z parameter

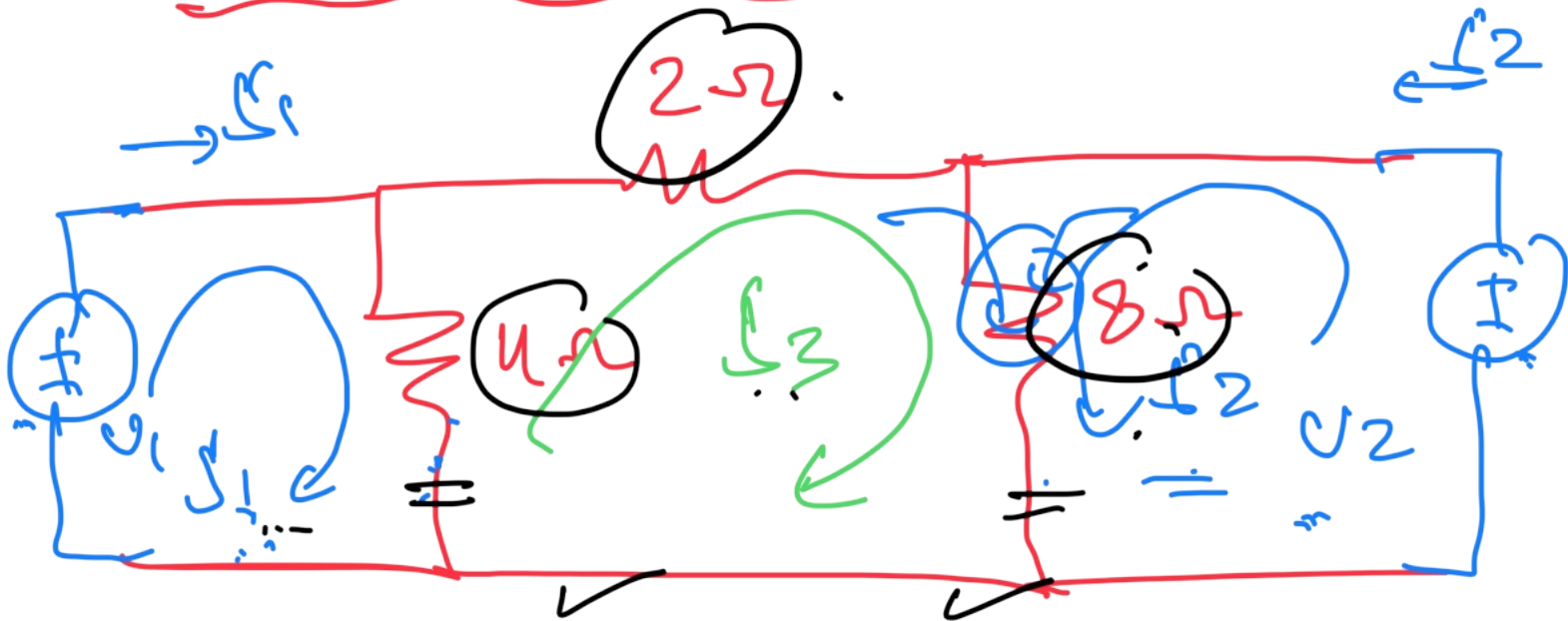

$$\begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{cases} \rightarrow Z \rightarrow V_{\text{mesh}}$$

$$\begin{aligned} \text{mesh (1)} & \quad 4I_1 + 0I_2 - 4I_3 = V_1 \\ \text{mesh (2)} & \quad 0I_1 + 8I_2 + 8I_3 = V_2 \\ \text{mesh (3)} & \quad -4I_1 + 8I_2 + 14I_3 = 0 \end{aligned}$$

$$I_3 = \frac{4I_1}{14} - \frac{8I_2}{14} \rightarrow \text{put in } Z_{21} I_1$$

$$V_1 = 4I_1 - \frac{4 \times 4 I_1}{14} + 11 \times \frac{8 I_2}{14}$$


$$V_1 = \frac{20}{7} I_1 + \frac{16}{7} I_2$$

$$V_2 = \frac{8 I_2}{14} + \frac{8 \times 4 I_1}{14} - \frac{8 \times 8 I_2}{14}$$

$$V_2 = \frac{16}{7} I_1 + \frac{24}{7} I_2$$

$$Z = \begin{bmatrix} \frac{20}{7} & \frac{16}{7} \\ \frac{16}{7} & \frac{24}{7} \end{bmatrix} \Omega$$

# Find Z parameter

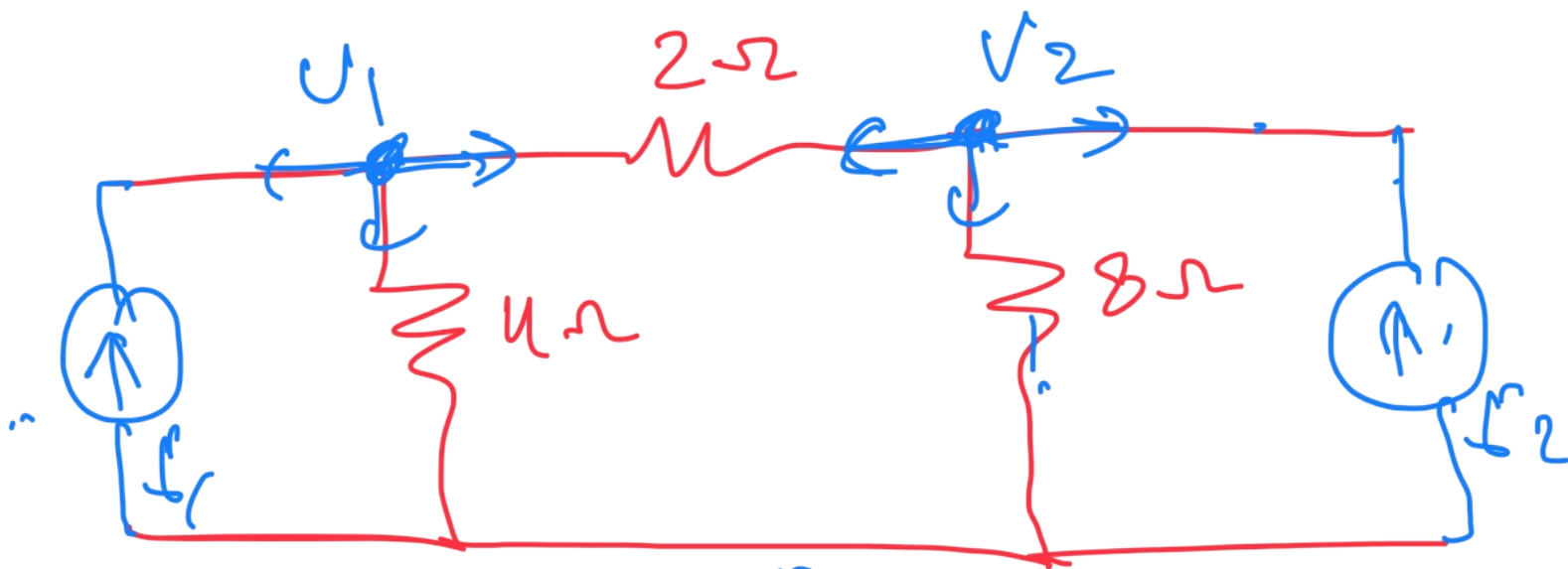

$$\begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned} \quad \left. \begin{array}{l} \rightarrow Y \rightarrow I \\ \text{Node} \end{array} \right\}$$

node (1)  $-I_1 + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$

$$\Rightarrow I_1 = \frac{3}{4} V_1 - \frac{1}{2} V_2 \quad \rightarrow (1)$$

node (2)  $-I_2 + \frac{V_2}{8} + \frac{V_2 - V_1}{2} = 0$

$$I_2 = \frac{1}{2} V_1 + \frac{5}{8} V_2 \quad \rightarrow (2)$$

$$y = \begin{bmatrix} \frac{3}{4} = 0,75 & \cdot & \cdot & \cdot & \frac{-1}{2} = -0,5 \\ \frac{-1}{2} = -0,5 & \cdot & \cdot & \cdot & \frac{5}{8} = 0,625 \end{bmatrix}_{2 \times 2}$$

$$z = y^{-1} \quad \text{or} \quad y = z^{-1}$$

mode  $\rightarrow 6 \rightarrow 1 \rightarrow 5$

shift  $\rightarrow RCL \rightarrow A \rightarrow AC$

shift  $\rightarrow 4 \rightarrow 3 \rightarrow$  mode  $\rightarrow x^{-1} \rightarrow \equiv$

Mat A

$$\begin{bmatrix} \frac{20}{7} \\ \frac{16}{7} \end{bmatrix}_{20,57}$$

$$\begin{bmatrix} \frac{16}{7} \\ \frac{24}{7} \end{bmatrix}$$

inv inv  $\square$