

# Electric Circuits I


## Chapter 1: Basic Concepts of Electric Circuits Part 1: Circuit Variables

EE 2010 – Credits : 4

د/ ارحاب يوسف

Assistant Professor in Electrical Engineering Dept.,

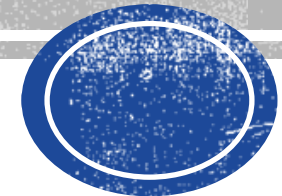Faculty of Engineering, Prince Sattam Bin Abdel Aziz University



## The Overall Goal

**Chapter 1** aims to establish a solid understanding of the basic concepts, principles, and analysis techniques in electric circuits, providing a foundation for further study in the field.

# The Main Topics

## Part 1: Circuit Variables:

- **Circuit Variables:** Introducing the basic variables used in circuit analysis, such as voltage, current, and power.
- **Circuit Analysis:** An Overview: Providing an overview of circuit analysis techniques and methodologies.
- **Voltage and Current:** Explaining the concepts of voltage and current and their relationship in electric circuits.
- **The Ideal Basic Circuit Element:** Introducing the ideal basic circuit elements, such as resistors, capacitors, and inductors.
- **Power and Energy:** Discussing the concepts of power and energy in electric circuits and their calculation methods.

## Part 2: Circuit Elements:


- **Voltage and Current Sources:** Explaining different types of voltage and current sources used in circuits.
- **Ohm's Law:** Describing Ohm's law, which relates voltage, current, and resistance in a circuit.
- **Kirchhoff's Laws:** Introducing Kirchhoff's laws, which are fundamental principles used for circuit analysis.
- **Analysis of Circuit Containing Dependent Sources:** Discussing the analysis of circuits that contain dependent sources, which are sources whose values depend on other circuit variables.

# 1- Introduction

In the field of electrical engineering, our primary focus is on the transmission and exchange of energy between different locations. In order to accomplish this, an interconnection of electrical devices are required.

An electric circuit is a system of interconnected components, where each component is called an **element**.

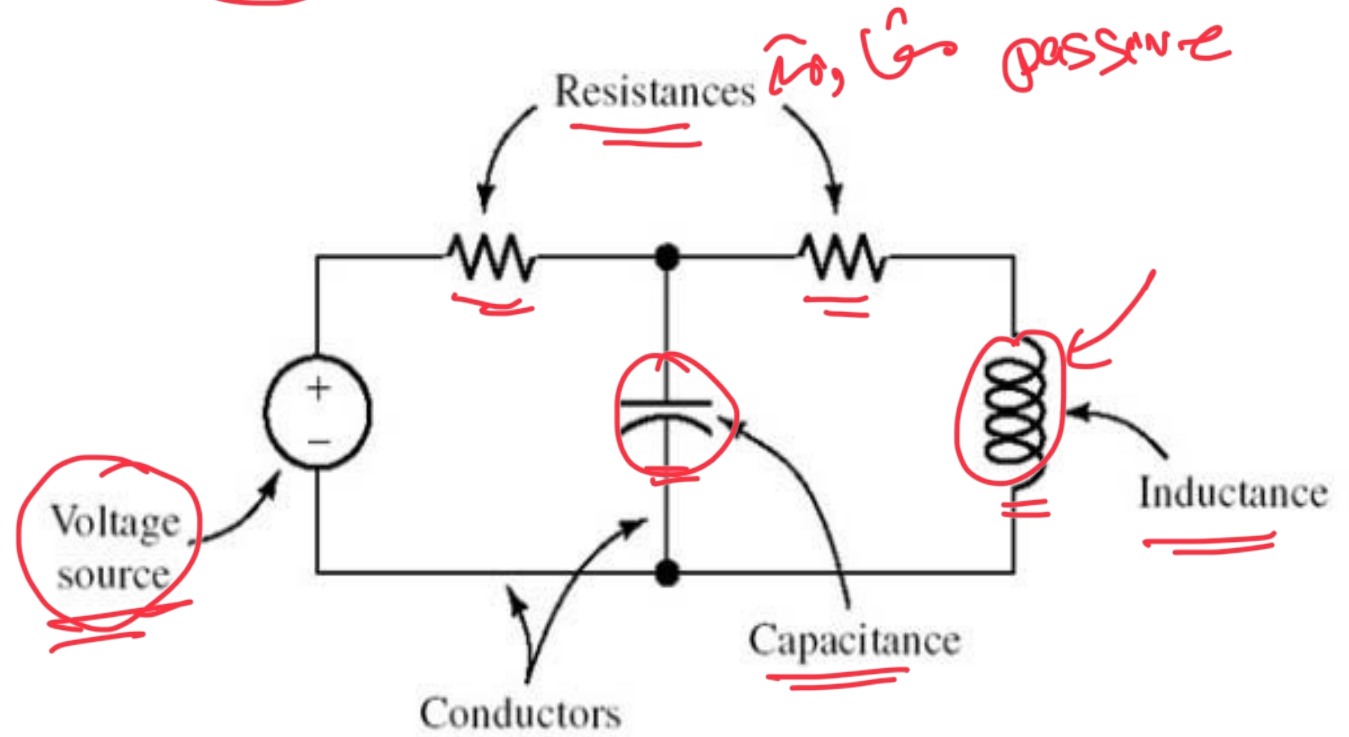In fact, Electrical circuits are composed of electrical generators (**sources**) and components that can be passive, non-reactive such as resistors or reactive passive such as capacities and inductions.



## 2- Circuit variables

The circuit variables are : **Current, Voltage, Power and Energy; (I, V, P, E)**

### a) **Voltage (V)**

**Definition:** Voltage, also known as electric potential difference, is the force that drives the electric current (the energy per unit charge)

**Symbol:** V

→ **Unit:** Volt(V)

**Formula:**  $V = \frac{dW}{dq}$ , V: voltage in volt, W: the energy in Joule, q: the charge in Coulomb

شحنة q ، مقدار التيار في الحيز  
لنقل الإلكترونات

## 2- Circuit variables

### b) Current (I)

**Definition:** Electric current in the flow of electric charge through a conductor, It is measured in amperes (A),

**Symbol:** I

**Unit:** Ampere (A)

**Formula:**  $I = \frac{dq}{dt}$ , I: the current in Ampere, q: the charge in Coulomb, t: the time in second

# Reminder of Knowledge

[https://www.youtube.com/watch?v=MUh\\_dOcqqVw](https://www.youtube.com/watch?v=MUh_dOcqqVw)

Electric current is defined as the flow of electric charge through a conductor.

**The direction of a current is opposite to the direction of electron flow.**

The SI unit of electric current is the ampere (A).

One ampere is equivalent to one coulomb of electric charge passing through a point in a circuit per second.

Mathematically, electric current ( $I$ ) is expressed as:


$$i = \frac{dq}{dt},$$

where

$i$  = the current in amperes,

$q$  = the charge in coulombs,

$t$  = the time in seconds.

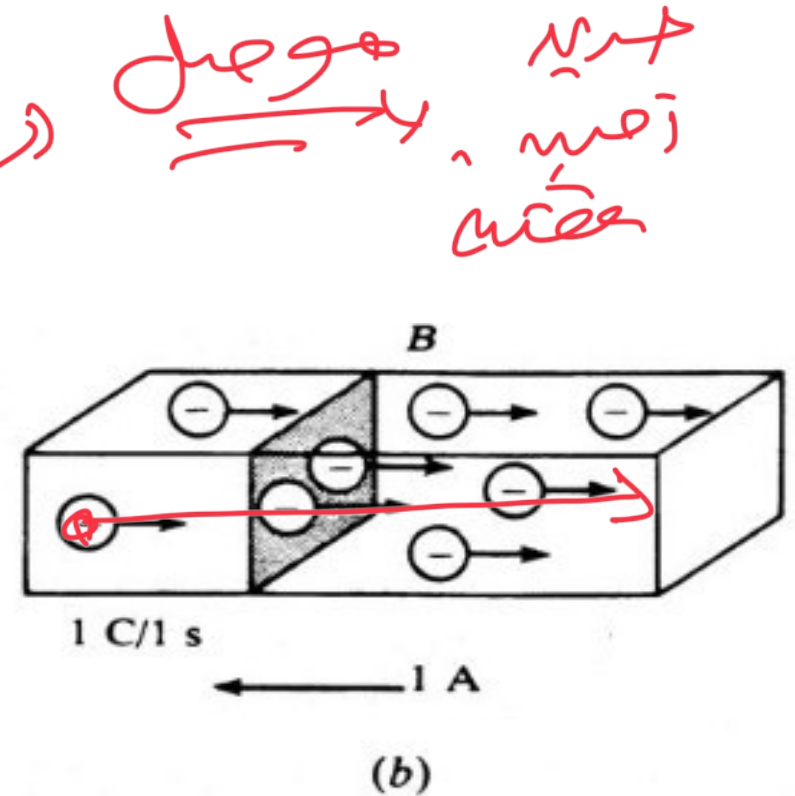

Negative ions

## Reminder of Knowledge


<https://www.youtube.com/watch?v=7VEdfuE9bic>

The flow of electric charge can occur in two main types:

- 1- **Direct current (DC)**, where the charge flows consistently in one direction,
- 2- **Alternating current (AC)**, where the charge periodically reverses direction.

والتي

ثابت الاتجاه


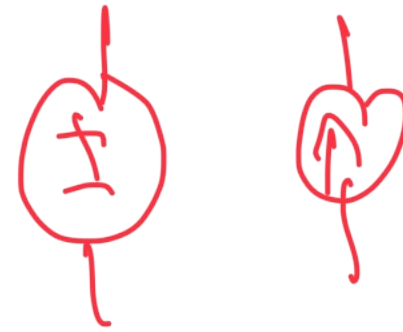


DC

AC

تغير الاتجاه والقيمة

Circuits 2

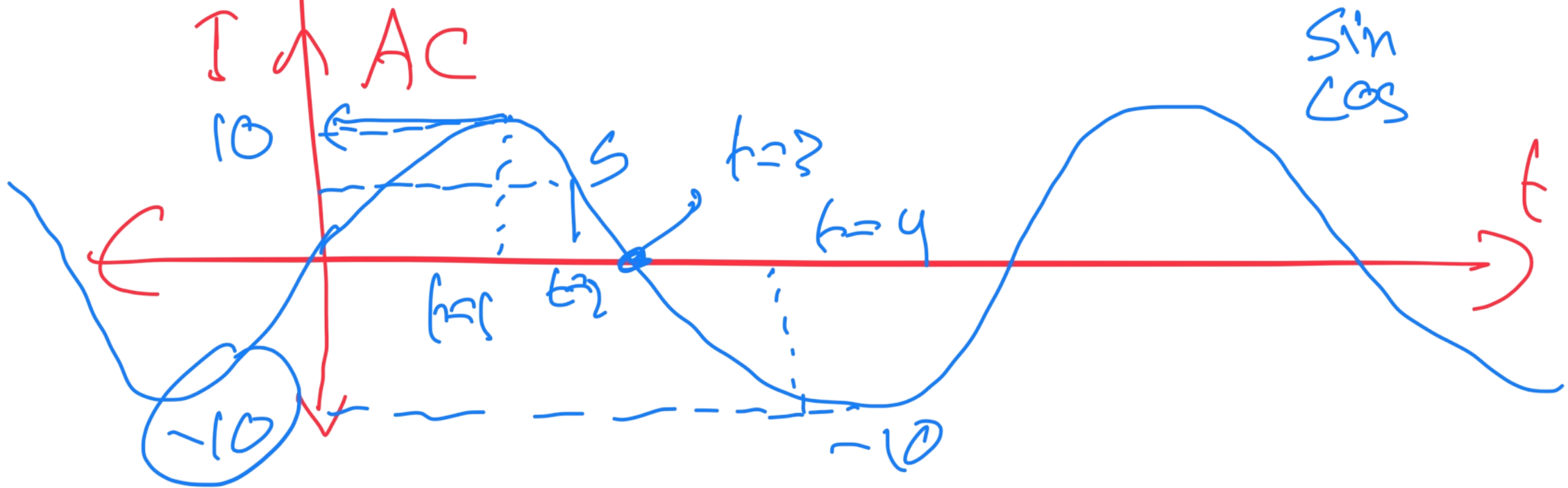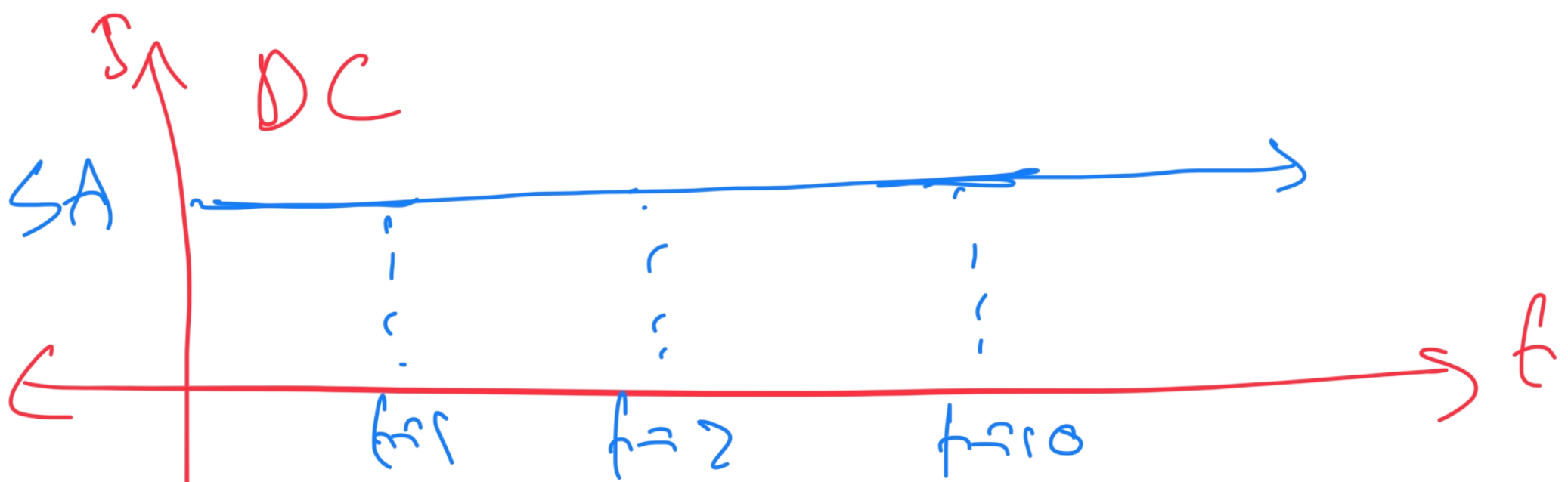

## 2- Circuit variables

### c) Power (P)

**Definition:** the power is the rate of energy consumption or production per unit time,

**Symbol:** P

**Unit:** Watt (W)

**Formula:**  $P = \frac{dW}{dt}$ , P: the power in Watt, W: the energy in Joule, t: the time in second

$$P = \frac{dW}{dt} = \frac{dW}{dq} * \frac{dq}{dt} = V * I$$

$$\underline{1 \text{ W}} = \underline{1 \text{ J/s}}$$

$$P = VI$$

## 2- Circuit variables

### d) Energy (E)

**Definition:** energy refers to the capacity to do work through the movement of electric charge,

**Symbol:** E

**Unit:** Joule (J)

**Formula:**  $W = P * t$ , E: the energy in Joule, P: the power in Watt, t: the time in second

1 second

$$\frac{J}{s} \cdot s = J$$

## 2- Circuit variables

### Passive sign convention

Current direction and voltage polarity play a major role in determining the sign of power.

Whenever the reference direction for the current in an element is in the direction of the reference voltage drop across the element (as in Fig. 1.5), use a positive sign in any expression that relates the voltage to the current. Otherwise, use a negative sign.


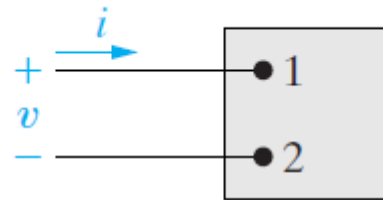


Figure 1.5 ▲ An ideal basic circuit element.

◀ Passive sign convention

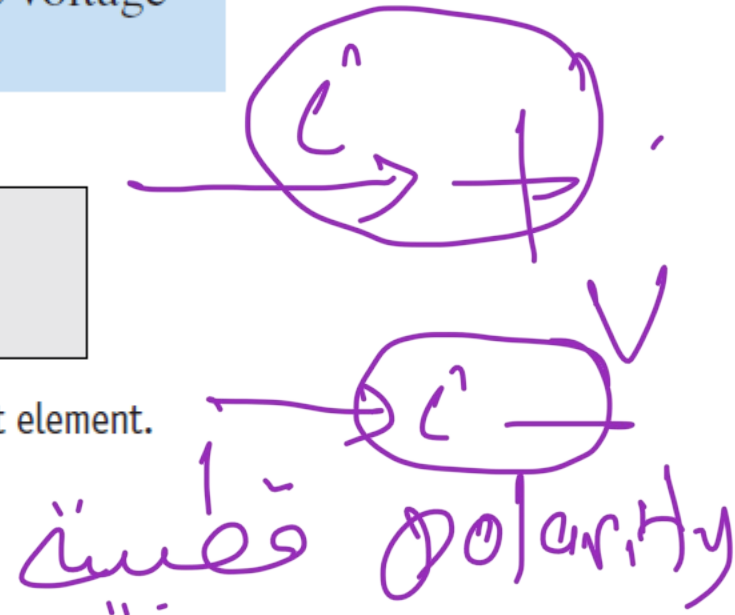

أنواع الأدوات :-



لـ نوع power  
نوع power

⇔ مبدأ حق الطاقة

$P = \boxed{+} V C'$

absorbed & dissipated alone

$R = \text{power} \leftarrow$

$V, I \Rightarrow$  "أحيا"

$P = \boxed{-} V C'$

supplying

$\text{power} \leftarrow$

"أحيا"

## 2- Circuit variables

### Passive sign convention

Current direction and voltage polarity play a major role in determining the sign of power.

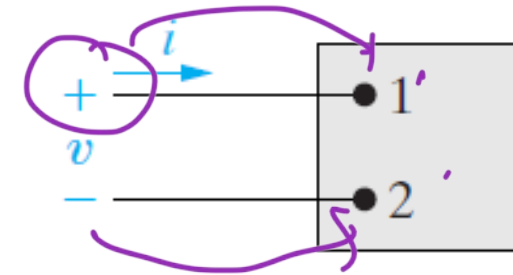


Figure 1.5 ▲ An ideal basic circuit element.

TABLE 1.4 Interpretation of Reference Directions in Fig. 1.5

#### Positive Value

$v$  voltage drop from terminal 1 to terminal 2

*or*

voltage rise from terminal 2 to terminal 1

$i$  positive charge flowing from terminal 1 to terminal 2

*or*

negative charge flowing from terminal 2 to terminal 1

#### Negative Value

voltage rise from terminal 1 to terminal 2

*or*

voltage drop from terminal 2 to terminal 1

positive charge flowing from terminal 2 to terminal 1

*or*

negative charge flowing from terminal 1 to terminal 2


## 2- Circuit variables

### Passive sign convention


Current direction and voltage polarity play a major role in determining the sign of power.

By the passive sign convention, current enters through the positive polarity of voltage.


(a) absorbing ; (b) supplying

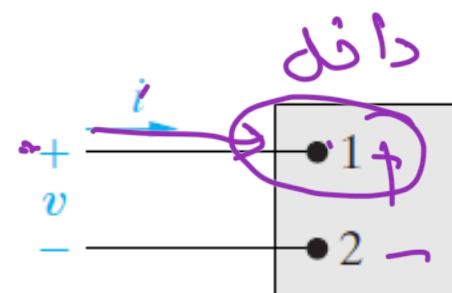


$$(a) p = vi$$

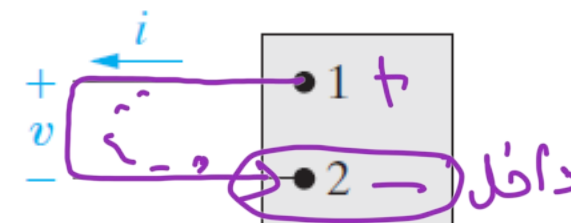

$$(b) p = -vi$$

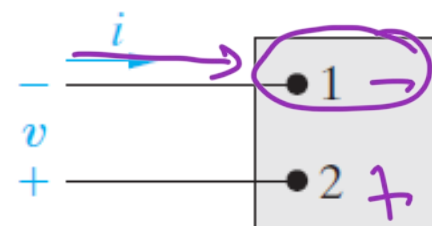

$$(c) p = -vi$$

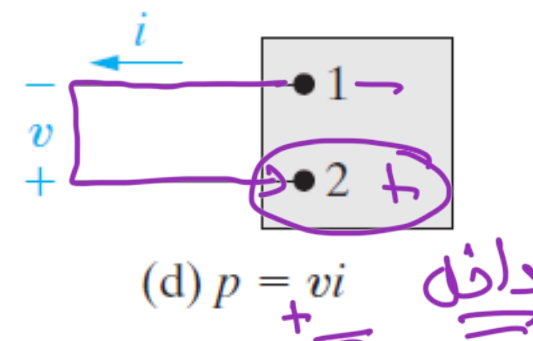

$$(d) p = vi$$

**Figure 1.6** ▲ Polarity references and the expression for power.


If the power is positive (that is, if  $p > 0$ ), power is being delivered to the circuit inside the box. If the power is negative (that is, if  $p < 0$ ), power is being extracted from the circuit inside the box.

## 2- Circuit variables
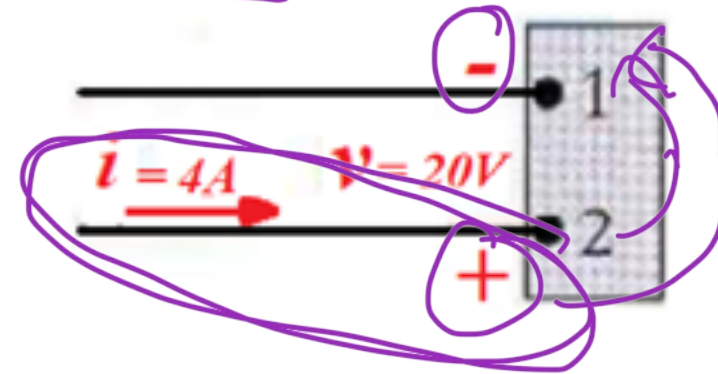
### Example 1 (problem 1.5)

Assume that a 20 V voltage drop occurs across an element from terminal 2 to terminal 1 and that the current of 4 A enters terminal 2.

- Specify the values of  $v$  and  $i$  for the polarity references shown below.
- How much power is the circuit absorbing?
- State whether the circuit inside the box is absorbing or delivering power.



a)



b)

$$P = +V\hat{C} = 4 \times 20 = \underline{\underline{80\text{ W}}}$$

c)



P (+)  $\Rightarrow$  absorbing power

عند عكس  
 الاتجاه النفاذ  
 تغيير إشارته فقط

$\rightarrow \hat{c}$   
 $\leftarrow \hat{c}$

عند عكس القطبية  
 تغيير الإشارة ~~فقط~~

$SV \quad \begin{matrix} + \\ - \end{matrix} \Rightarrow \begin{matrix} - \\ + \end{matrix} \quad \begin{matrix} -SV \\ + \end{matrix}$

## 2- Circuit variables

### Solution

a)  
-voltage drop of 20 V from terminal 2 to terminal 1

-current of 4 A enters terminal 2 Circuit

(a):  $v = -20V$  and  $i = -4A$

Circuit (b):  $v = -20V$  and  $i = 4A$

Circuit (c):  $v = 20V$  and  $i = -4A$

Circuit (d):  $v = 20V$  and  $i = 4A$

b)

$$p = vi = (-20) \times (-4) = 80 \text{ W for (a).}$$


$$p = -vi = -(-20) \times (4) = 80 \text{ W for (b).}$$

$$p = -vi = -(20) \times (-4) = 80 \text{ W for (c).}$$


$$p = vi = (20) \times (4) = 80 \text{ W for (d).}$$

c)

$p > 0$  so, the box is absorbing power

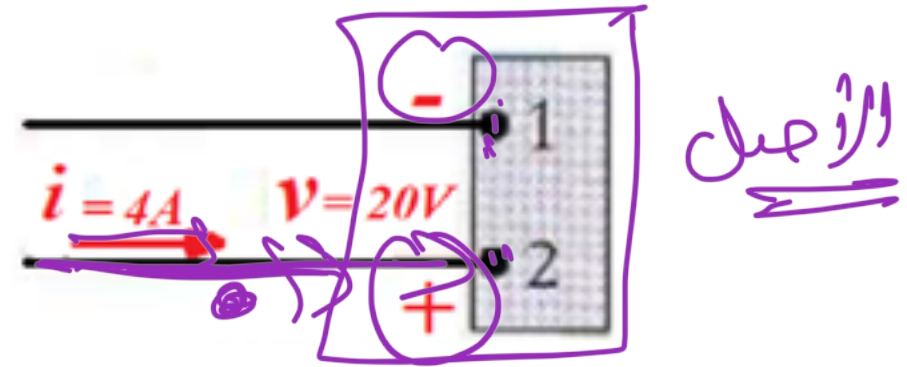

التيار

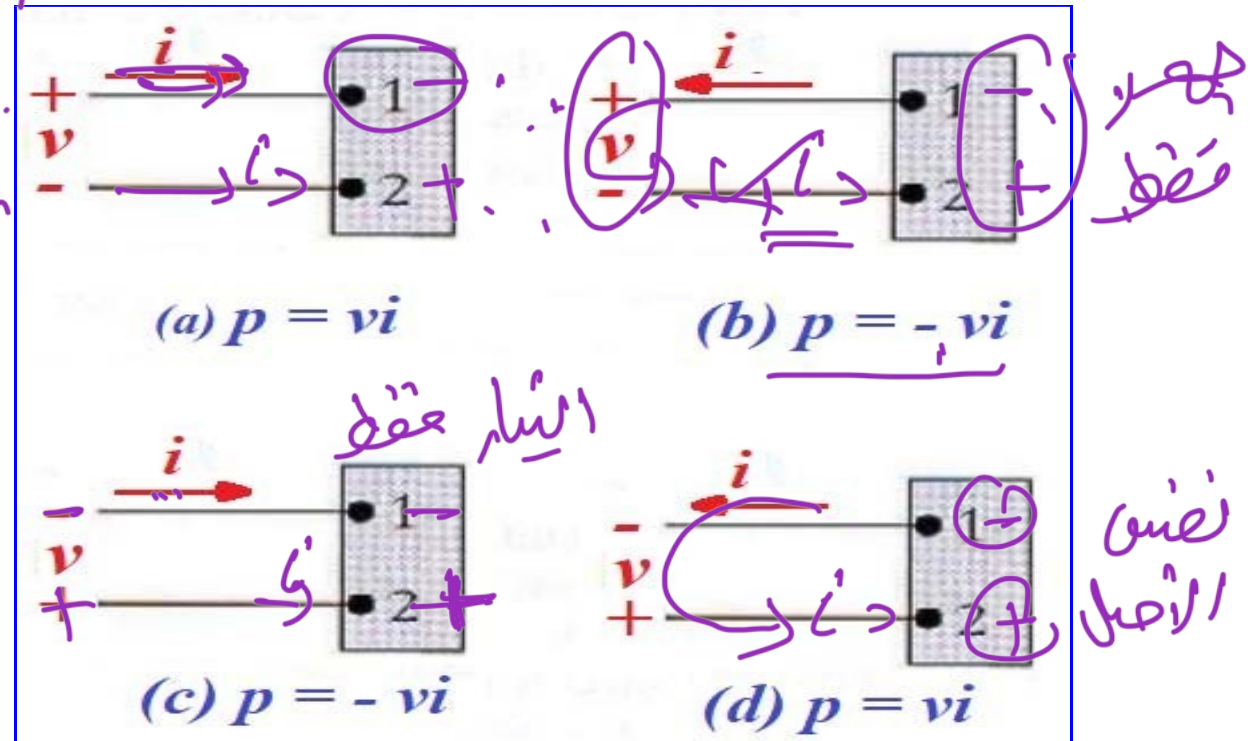

$$i' = 4 \text{ A}$$

$$V = 20 \text{ V}$$

$$a) \quad P = + V i' \Rightarrow P = (-4)(-20) = 80 \text{ W}$$

$$b) \quad P = - V i' \Rightarrow P = - (4)(-20) = 80 \text{ W}$$

$$c) \quad P = - V i' \Rightarrow P = - (-4)(20) = 80 \text{ W}$$

$$d) \quad P = + V i' \Rightarrow P = + (4)(20) = 80 \text{ W}$$

## 2- Circuit variables

### Example 2: Problem 1 in HW

The numerical values for the currents and voltages in the circuit in Fig. P1.29 are given in Table P1.29. Find the total power developed in the circuit.

TABLE P1.29

| Element | Voltage (V) | Current (mA) |
|---------|-------------|--------------|
| a       | 40          | -4           |
| b       | -24         | -4           |
| c       | -16         | 4            |
| d       | -80         | -1.5         |
| e       | 40          | 2.5          |
| f       | 120         | -2.5         |

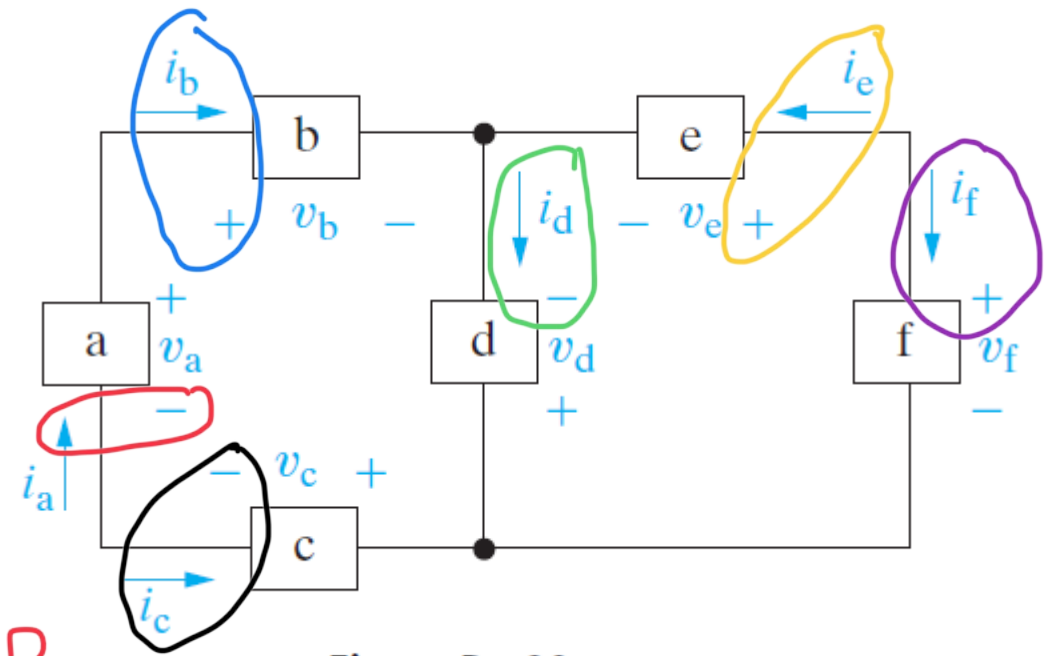


Figure P1.29

دائما للسؤال تعاملو  
مع الدارة

$$P_a = -i_a v_a = -(-4\text{m})(40) = + \underline{\underline{160\text{ mW}}}$$

$$P_b = + i_b v_b = + (-4\text{m})(-24) = + \underline{\underline{96\text{ mW}}}$$

$$P_c = -i_c v_c = -(4\text{m})(-16) = + \underline{\underline{64\text{ mW}}}$$

$$P_d = -i_d v_d = + (1.5\text{m})(-80) = - \underline{\underline{120\text{ mW}}}$$

$$P_e = + i_e v_e = + (2.5\text{m})(40) = + \underline{\underline{100\text{ mW}}}$$

$$P_f = + i_f v_f = + (-2.5\text{m})(120) = - \underline{\underline{300\text{ mW}}}$$

$$\Rightarrow \sum P_+ = 160 + 96 + 64 + 100 = 420 \text{ mW}$$

absorption

$$\Rightarrow \sum P_- = -120 + -300 = -420 \text{ mW}$$

dev

$$\sum P_{\text{abs}} = \sum P_{\text{dev}}$$

erhöhenkeit = (erhöhen)

$$\Rightarrow \boxed{\sum P = 0} \Rightarrow \text{valid equation}$$

## 2- Circuit variables

### Solution

We use the passive sign convention to determine whether the power equation is  $p = vi$  or  $p = -vi$  and substitute into the power equation the values for  $v$  and  $i$ , as shown below:

$$p_a = -v_a i_a = -(40)(-4 \times 10^{-3}) = 160 \text{ mW}$$

$$p_b = v_b i_b = (-24)(-4 \times 10^{-3}) = 96 \text{ mW}$$

$$p_c = -v_c i_c = -(-16)(4 \times 10^{-3}) = 64 \text{ mW}$$

$$p_d = -v_d i_d = -(-80)(-1.5 \times 10^{-3}) = -120 \text{ mW}$$

$$p_e = v_e i_e = (40)(2.5 \times 10^{-3}) = 100 \text{ mW}$$

$$p_f = v_f i_f = (120)(-2.5 \times 10^{-3}) = -300 \text{ mW}$$

We can add the positive powers together and the negative powers together — if the power balances, these power sums should be equal:

$$\sum P_{\text{dev}} = 120 + 300 = 420 \text{ mW};$$

$$\sum P_{\text{abs}} = 160 + 96 + 64 + 100 = 420 \text{ mW}$$

Thus, the power balances and the total power absorbed in the circuit is 420 mW.

# **Electric Circuits I**


## **Chapter 2: Circuit Elements**


**EE 2010 – Credits : 4**

**د/ ارحاب يوسف**

**Assistant Professor in Electrical Engineering Dept.,**

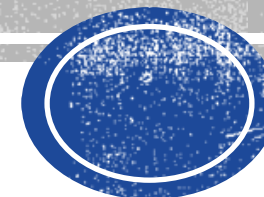**Faculty of Engineering, Prince Sattam Bin Abdel Aziz University**



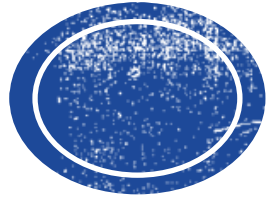

# **Chapter 2: Basic Concepts of Electric Circuits**

## **Part 2: Circuit Elements**



## Introduction

There are two types of elements found in electric circuits: passive elements and active elements.

- An **active element** is capable of generating energy  
Example: **batteries, generators and operational amplifiers,**
- A **passive element** is not.  
Example: **resistors, capacitors and inductors**


The most important active elements are **voltage or current sources** that generally deliver power to the circuit connected to them,

There are two types of sources: **independent and dependent sources**

### a) Passive elements



**Resistance**

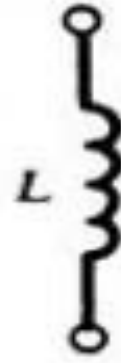

**Inductance**



**Capacitor**


### b) Active elements

- ✓ Independent sources
- ✓ Dependent sources


# Independent voltage and current sources
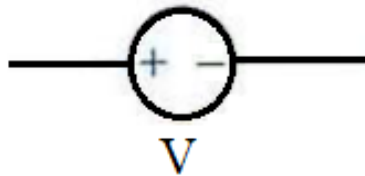
## 1) Independent sources

- Ideal independent voltage source is a circuit that maintains prescribed voltage across its terminals regardless of the current flowing in those terminals
- Ideal independent current source is a circuit that maintains prescribed current through its terminals regardless of the voltage across those terminals.



Ideal independent voltage source

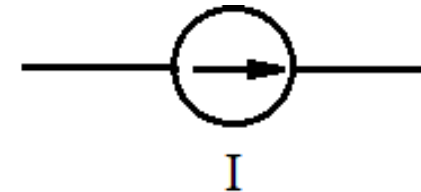

Ideal independent current source

# Dependent voltage and current sources

## Dependent sources

The dependent source establishes a voltage or a current in the circuit whose value depends on the value of voltage or current elsewhere in the circuit.

(a) voltage-controlled voltage source


$\mu$ : is a multiplying constant dimensionless

$V_x$ : controlling voltage


(b) current-controlled voltage source

$\rho$ : is a multiplying constant V/A


$i_x$ : controlling current

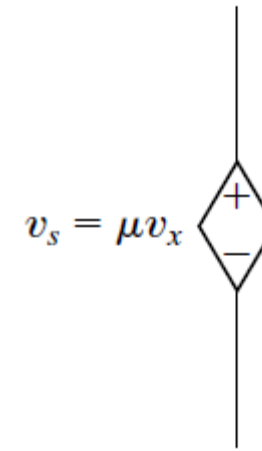

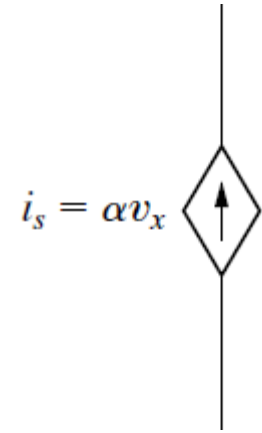
an ideal dependent  
voltage-controlled  
voltage source



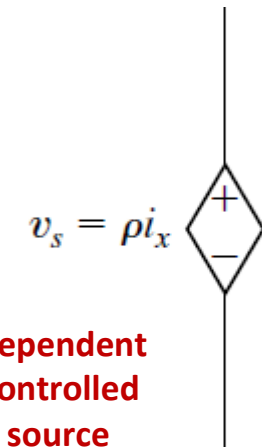An ideal dependent  
voltage-controlled  
current source



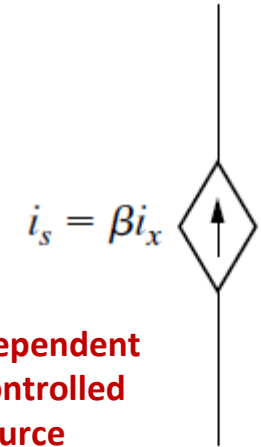an ideal dependent  
current-controlled  
voltage source



an ideal dependent  
current-controlled  
current source

## ■ Dependent voltage and current sources

### Dependent sources

The dependent source establishes a voltage or a current in the circuit whose value depends on the value of voltage or current elsewhere in the circuit

(c) voltage-controlled current source


$\alpha$ : is a multiplying constant A/V

$V_x$ : controlling voltage


(c) current-controlled current source

$\beta$ : is a multiplying dimensionless


$i_x$ : controlling current

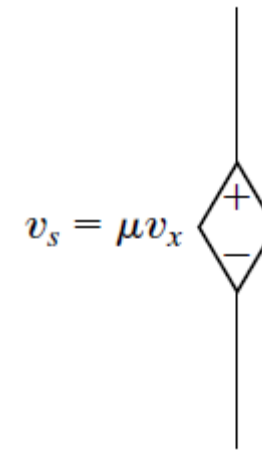

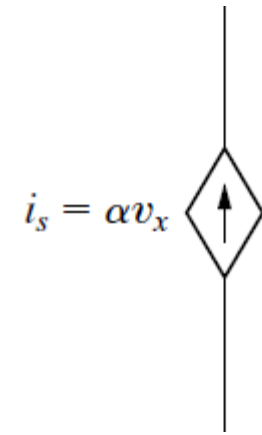
an ideal dependent  
voltage-controlled  
voltage source



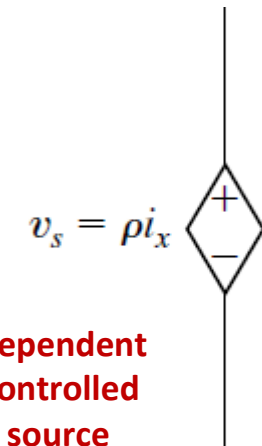An ideal dependent  
voltage-controlled  
current source



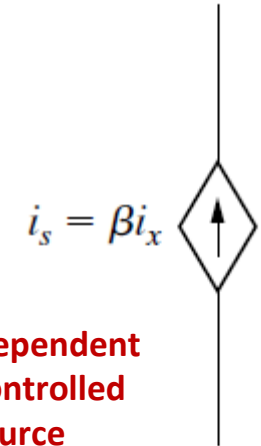
an ideal dependent  
current-controlled  
voltage source



an ideal dependent  
current-controlled  
current source

## Interconnections of independent sources

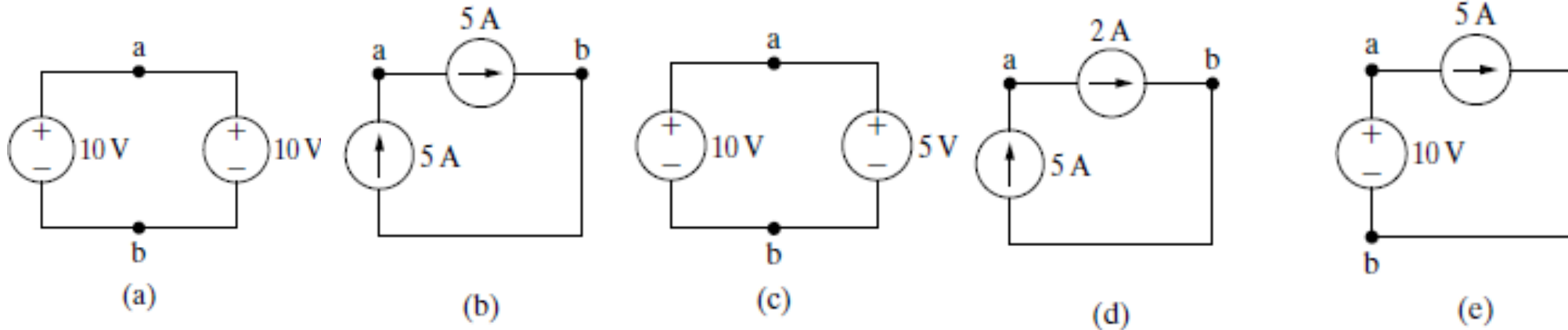**Problem 2.1:** Using the definitions of ideal independent voltage and current sources, the following connections may be valid or invalid or not permissible,







Connection (a) is valid.  
Connection (b) is valid.

Connection (c) is not permissible.  
Connection (d) is not permissible.

Connection (e) is valid.


## Interconnections of dependent and independent sources

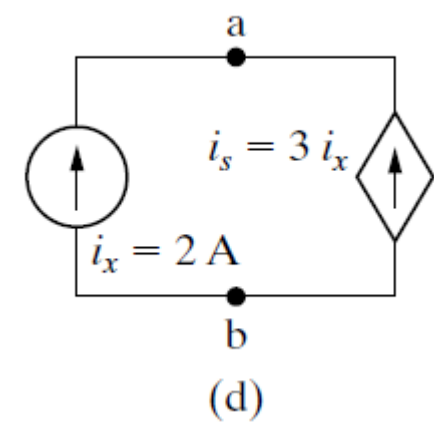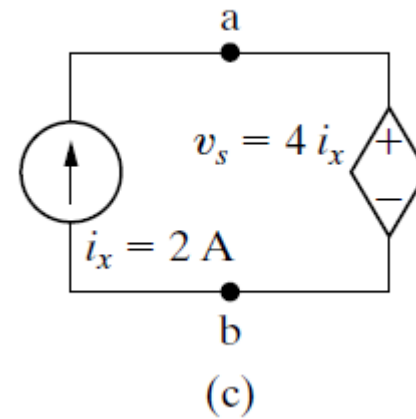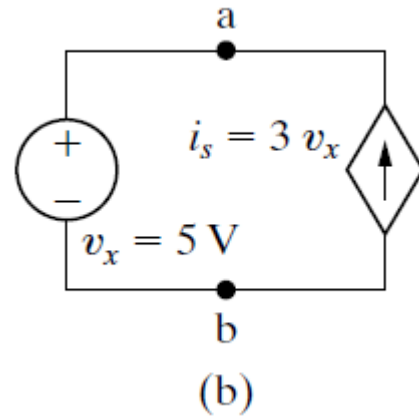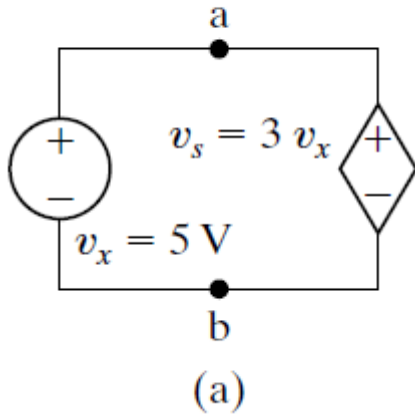**Problem 2.2:** Using the definitions of ideal independent and dependent sources, in the following some connections are valid and some others are invalid,




# Interconnections of dependent and independent sources

## Problem 2.2: answer

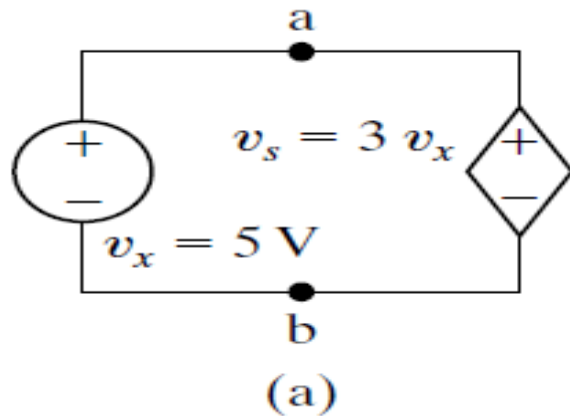

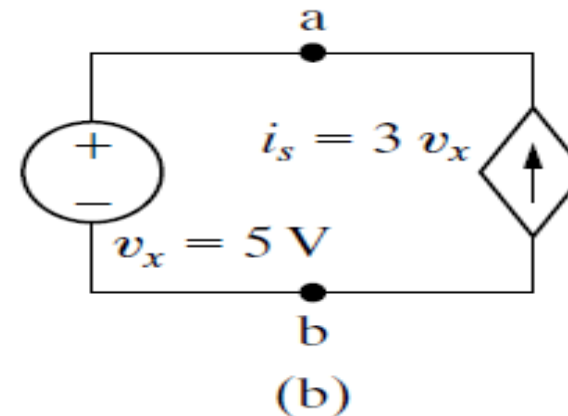**(a): invalid.**

Reason: The independent voltage source supplies 5 V and the dependent voltage source supplies 15 V although they supply voltage across the same pair of terminals a, b.




**(b): valid.**

Reason: An ideal voltage source supplies the same voltage regardless of current, and an ideal current source supplies the same current regardless of voltage.


# Interconnections of dependent and independent sources

## Problem 2.2: answer

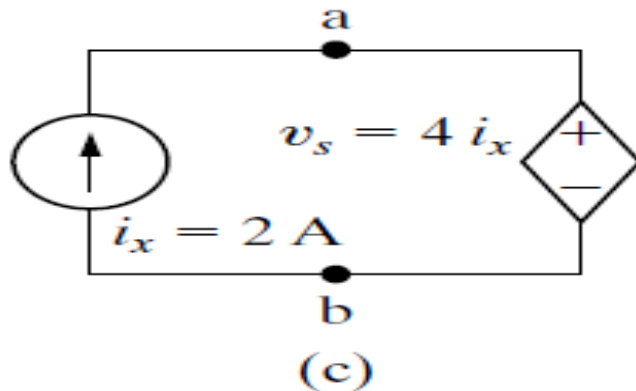

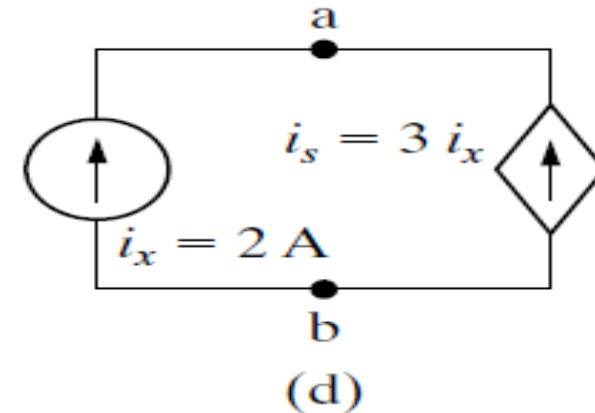**(c): valid.**

Reason: An ideal voltage source supplies the same voltage regardless of current, and an ideal current source supplies the same current regardless of voltage.




**(d): invalid.**

Reason: The independent source supplies 2 A and the dependent source supplies 6 A although they supply current through the same pair of terminals a, b.

### Example 3

For the circuit shown,

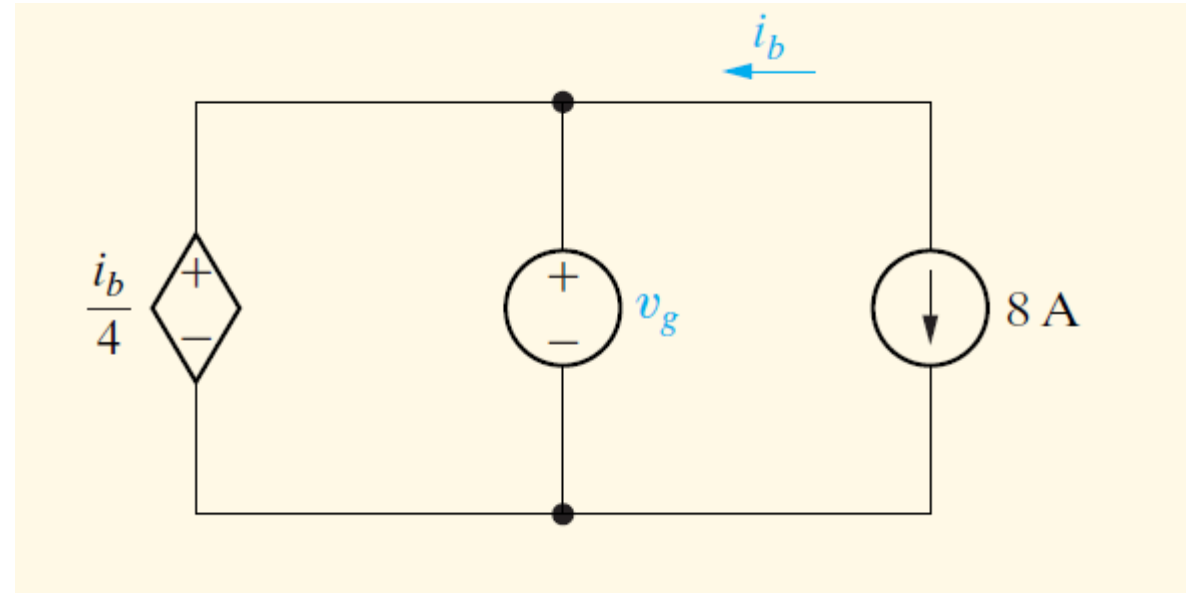- a) What value of  $v_g$  is required in order for the interconnection to be valid?
- b) For this value of  $v_g$ , find the power associated with the 8 A source.



### Solution

a)  $V_g = i_b/4 = -8/4 = -2 \text{ V},$


b)  $P_{8A} = + V_g \times 8 = -2 \times 8 = -16 \text{ W (delivered)}$

**Answer:** (a)  $-2 \text{ V};$   
(b)  $-16 \text{ W (16 W delivered)}$
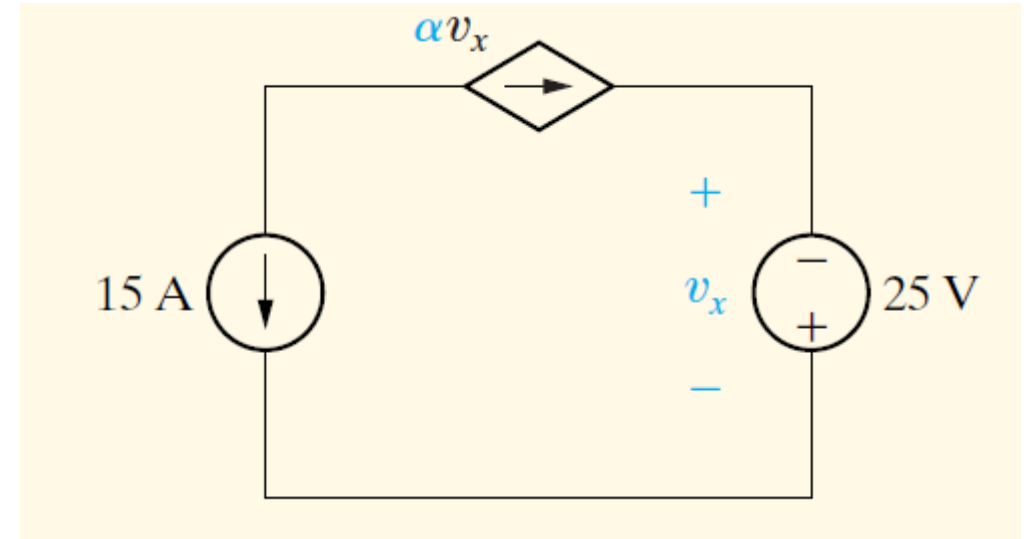
## Example 4

For the circuit shown,

- What value of  $\alpha$  is required in order for the interconnection to be valid?
- For the value of  $\alpha$  calculated in part (a), find the power associated with the 25 V source.



## Solution

a)  $V_X = -25$ ,

$\alpha \cdot V_X = -15$ ,

$\alpha = -15/V_X$

$\alpha = -15/(-25)$

$\alpha = 0.6 \text{ A/V}$

b)  $P_{25V} = 25 \times 15 = +375 \text{ W}$  (absorbed)

## 2-3 Electrical Resistance (Ohm's Law)

For purpose of circuit analysis, we must reference the current in the resistor to the terminal voltage as shown in the following figures:

If we choose the first figure, the relationship between the voltage and current is:


Ohm's law ►

$$v = iR,$$

$v$  = the voltage in volts,

$i$  = the current in amperes,

$R$  = the resistance in ohms.

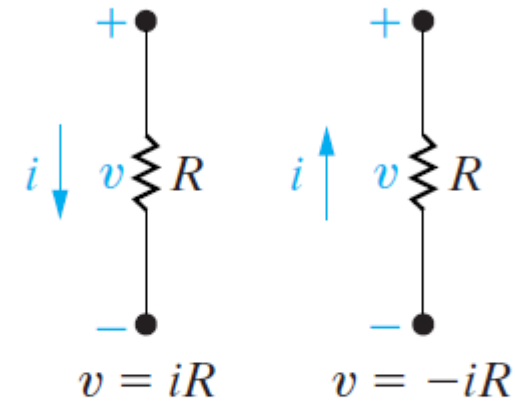

**Figure 2.6** ▲ Two possible reference choices for the current and voltage at the terminals of a resistor, and the resulting equations.

## 2-3 Electrical Resistance (Ohm's Law)

**Ohm's law** is the algebraic relationship between voltage and current for a resistor. In SI units, resistance is measured in ohms. The Greek letter omega (  $\Omega$  ) is the standard symbol for an ohm.

**Ohm's law** expresses the voltage as a function of the current. However, from Eq. 2.1, expressing the current as a function of the voltage also is convenient. Thus,

$$i = \frac{v}{R},$$

$$i = -\frac{v}{R}.$$

The reciprocal of the resistance is referred to as **conductance**, is symbolized by the letter  $G$ , and is measured in siemens (S). Thus,

$$G = \frac{1}{R} \text{ S}$$

## 2-3 Electrical Resistance (Ohm's Law)

### Power in resistance

We may calculate the power at the terminals of a resistor in several ways. The first approach is to use the defining equation and simply calculate the product of the terminal voltage and current.

$$p = vi$$



$$p = vi = (iR)i$$

Power in a resistor in terms of current ►

$$p = i^2 R.$$

Power in a resistor in terms of voltage ►


$$p = \frac{v^2}{R}.$$

$$p = \frac{i^2}{G},$$
$$p = v^2 G.$$


### Example 2.3
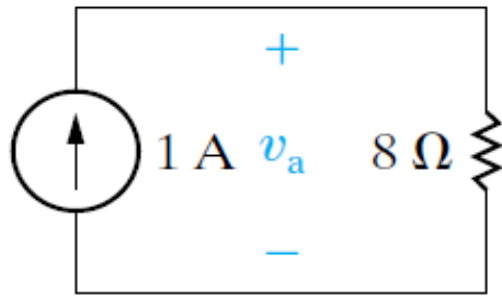
### Calculating Voltage, Current, and Power for a Simple Resistive Circuit


In each circuit in Fig. 2.8, either the value of  $v$  or  $i$  is not known.




(a)

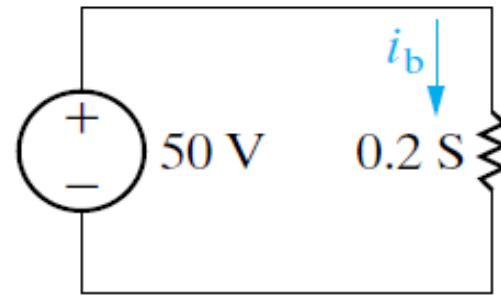

(b)

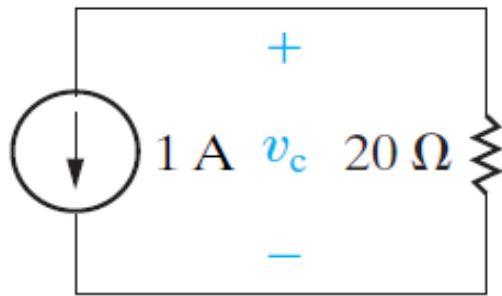

(c)

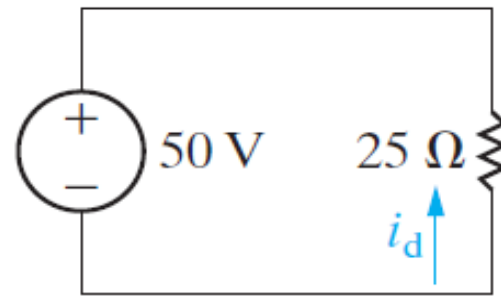


(d)

a) Calculate the values of  $V$  and  $i$ .

b) Determine the power dissipated in each resistor

**Figure 2.8** ▲ The circuits for Example 2.3.

## Solution

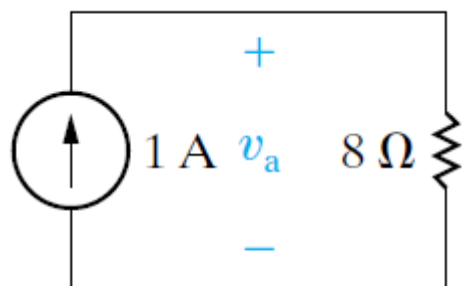


(a)

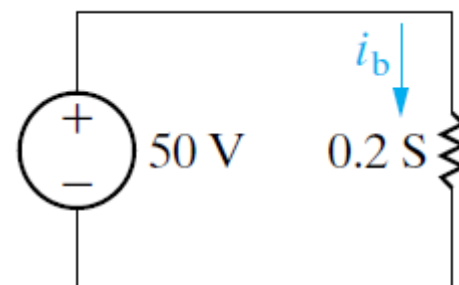a) The voltage  $v_a$  in Fig. 2.8(a) is a drop in the direction of the current in the resistor. Therefore,

$$v_a = (1)(8) = 8 \text{ V.}$$

$$p_{8\Omega} = \frac{(8)^2}{8} = (1)^2(8) = 8 \text{ W,}$$




(b)

The current  $i_b$  in the resistor with a conductance of 0.2 S in Fig. 2.8(b) is in the direction of the voltage drop across the resistor. Thus

$$i_b = (50)(0.2) = 10 \text{ A.}$$

$$p_{0.2S} = (50)^2(0.2) = 500 \text{ W,}$$

## Solution

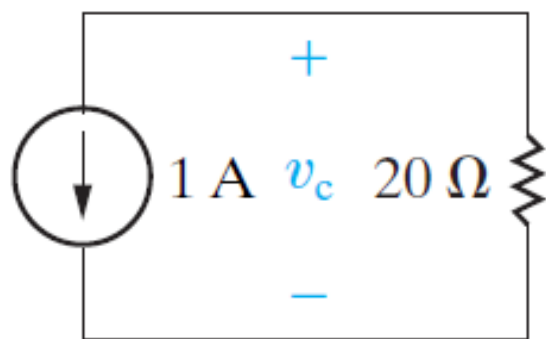


(c)

The voltage  $v_c$  in Fig. 2.8(c) is a rise in the direction of the current in the resistor. Hence

$$v_c = -(1)(20) = -20 \text{ V.}$$
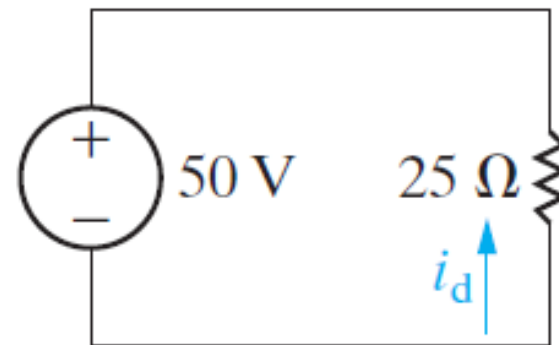
$$p_{20\Omega} = \frac{(-20)^2}{20} = (1)^2(20) = 20 \text{ W,}$$



(d)

The current  $i_d$  in the  $25 \Omega$  resistor in Fig. 2.8(d) is in the direction of the voltage rise across the resistor. Therefore


$$i_d = \frac{-50}{25} = -2 \text{ A.}$$

$$p_{25\Omega} = \frac{(50)^2}{25} = (-2)^2(25) = 100 \text{ W.}$$

### Example 4 (problem2.3)

For the circuit shown,

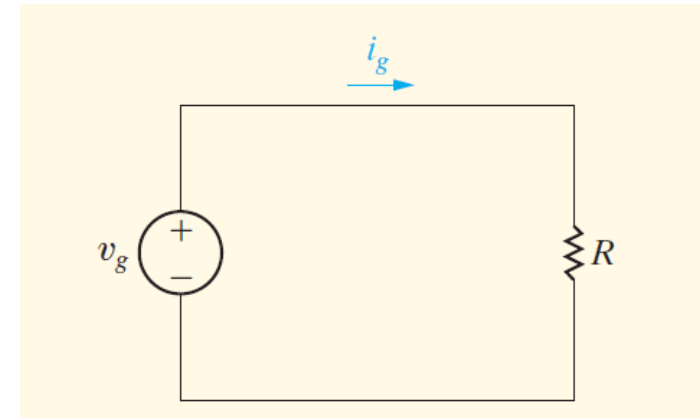- a) If  $v_g = 1 \text{ kV}$  and  $i_g = 5 \text{ mA}$ , find the value of  $R$  and the power absorbed by the resistor.
- b) If  $i_g = 75 \text{ mA}$  and the power delivered by the voltage source is  $3 \text{ W}$ , find  $v_g$ ,  $R$ , and the power absorbed by the resistor.
- c) If  $R = 300 \Omega$  and the power absorbed by  $R$  is  $480 \text{ mW}$ , find  $i_g$  and  $v_g$ .



**Answer:** (a)  $200 \text{ k}\Omega$ ,  $5 \text{ W}$ ;  
(b)  $40 \text{ V}$ ,  $533.33 \Omega$ ,  $3 \text{ W}$ ;  
(c)  $40 \text{ mA}$ ,  $12 \text{ V}$ .

### Example 4 (problem2.3)

For the circuit shown,

- a) If  $v_g = 1 \text{ kV}$  and  $i_g = 5 \text{ mA}$ , find the value of  $R$  and the power absorbed by the resistor.
- b) If  $i_g = 75 \text{ mA}$  and the power delivered by the voltage source is  $3 \text{ W}$ , find  $v_g$ ,  $R$ , and the power absorbed by the resistor.
- c) If  $R = 300 \Omega$  and the power absorbed by  $R$  is  $480 \text{ mW}$ , find  $i_g$  and  $v_g$ .

### Solution

a)  $V_g = i_g R$ ,  $R = V_g / i_g = 1000 / 0.005 = \mathbf{200 \text{ k}\Omega}$

$P = (i_g)^2 \cdot R = (0.005)^2 \times 2 \times 10^5 = \mathbf{5W}$

b)  $P_G = V_g \cdot i_g$ ,  $V_g = P_G / i_g$

$V_g = 3 / 0.075 = \mathbf{40 \text{ V}}$

$R = V_g / i_g = 40 / 0.075 = \mathbf{533.33 \Omega}$

$P = (i_g)^2 \cdot R = (0.075)^2 \times 533.33 = \mathbf{3W}$

c)  $P = (i_g)^2 \cdot R$   $i_g = \mathbf{40 \text{ mA}}$


So,  $i_g = (P_G / R)^{1/2} = (0.48 / 300)^{1/2}$

$V_g = i_g R = 0.04 \times 300 = \mathbf{12 \text{ V}}$

### Example 4 (problem2.4)

For the circuit shown,

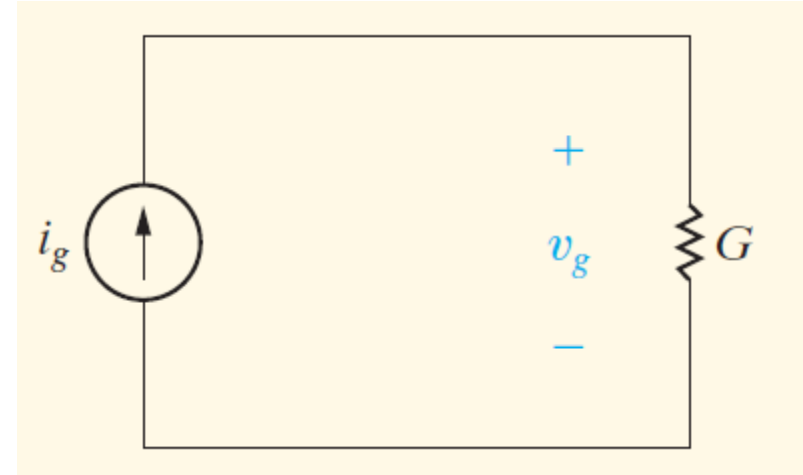- a) If  $i_g = 0.5$  A and  $G = 50$  mS, find  $v_g$  and the power delivered by the current source.
- b) If  $v_g = 15$  V and the power delivered to the conductor is 9 W, find the conductance  $G$  and the source current  $i_g$ .
- c) If  $G = 200$   $\mu$ S and the power delivered to the conductance is 8 W, find  $i_g$  and  $v_g$ .




**Answer:** (a) 10 V, 5 W;  
(b) 40 mS, 0.6 A;  
(c) 40 mA, 200 V.



**Class activity**
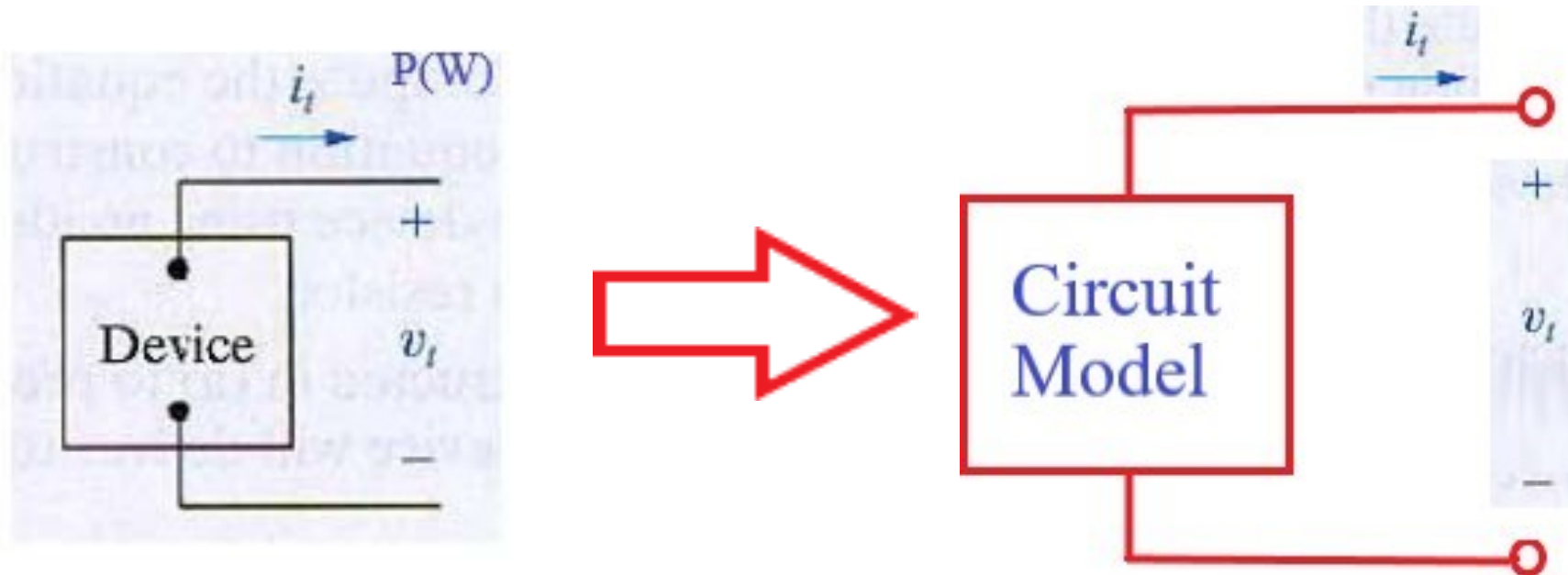
## 2-4 Construction of a circuit model

- One reason for an interest in the basic circuit elements is that they can be used to construct circuit models of practical systems.
- The construction of a circuit model based on a knowledge of the behavior of the system's components and how the components are interconnection



## 2-4 Construction of a circuit model

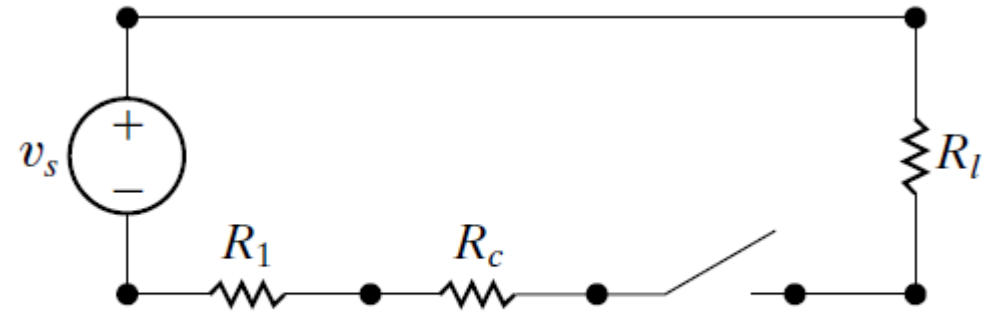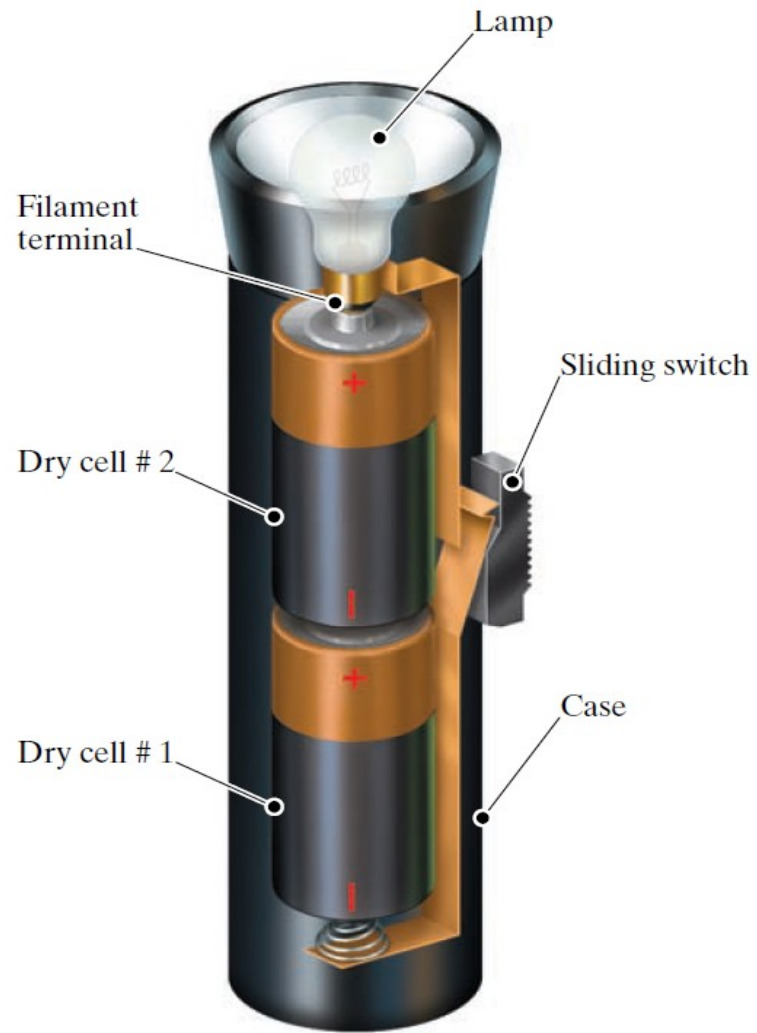


**Figure 2.12** ▲ A circuit model for a flashlight.

**Figure 2.11** ▲ The arrangement of flashlight components.

## 2-4 Construction of a circuit model
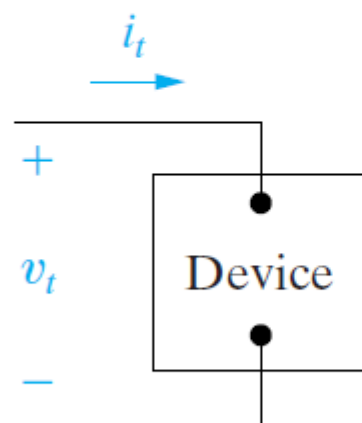
### Example 2.5 Constructing a Circuit Model Based on Terminal Measurements

The voltage and current are measured at the terminals of the device illustrated in Fig. 2.13(a), and the values of  $v_t$  and  $i_t$  are tabulated in Fig. 2.13(b). Construct a circuit model of the device inside the box.



(a)

| $v_t$ (V) | $i_t$ (A) |
|-----------|-----------|
| -40       | -10       |
| -20       | -5        |
| 0         | 0         |
| 20        | 5         |
| 40        | 10        |

(b)


**Figure 2.13** ▲ The (a) device and (b) data for Example 2.5.

## 2-4 Construction of a circuit model

### Example 2.5 Constructing a Circuit Model Based on Terminal Measurements

#### Solution

Plotting the voltage as a function of the current yields the graph shown in Fig. 2.14(a). The equation of the line in this figure illustrates that the terminal voltage is directly proportional to the terminal current,  $v_t = 4i_t$ . In terms of Ohm's law, the device inside the box behaves like a  $4\ \Omega$  resistor. Therefore, the circuit model for the device inside the box is a  $4\ \Omega$  resistor, as seen in Fig. 2.14(b).

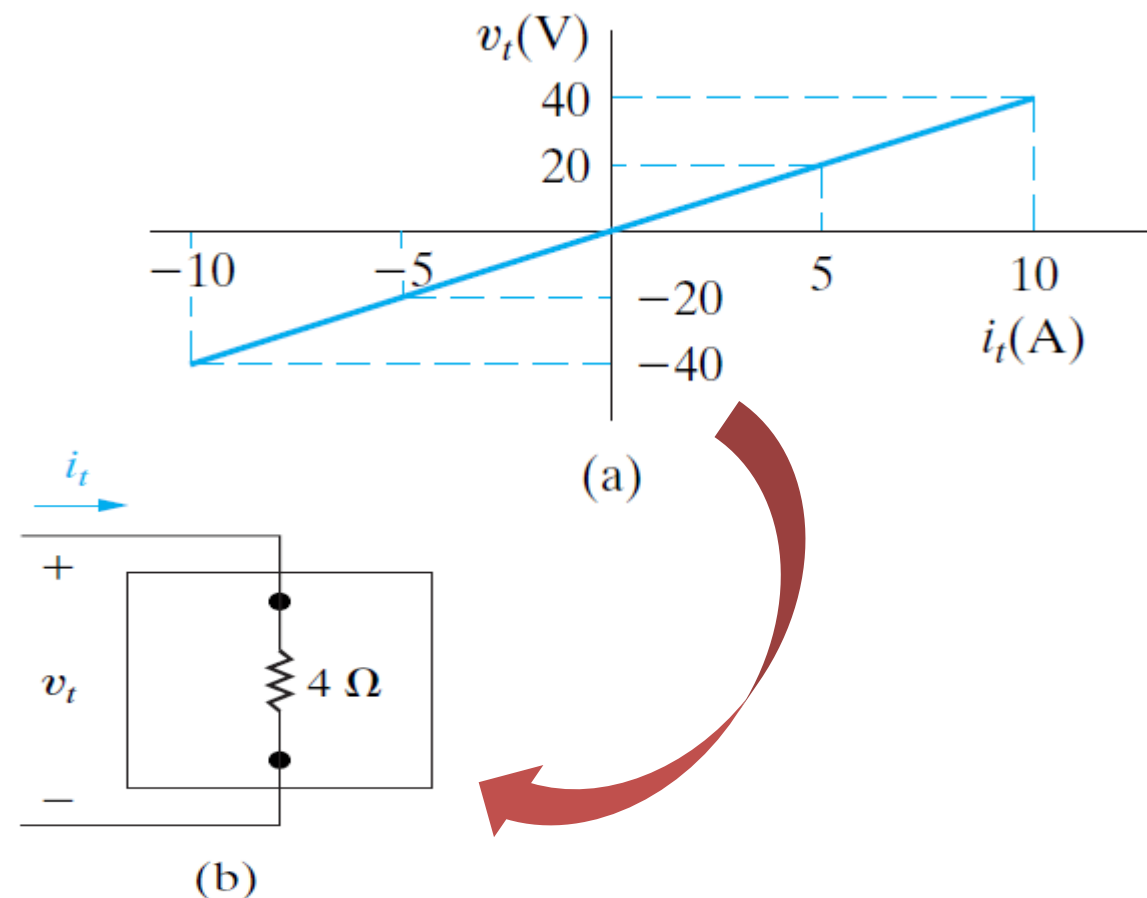


**Figure 2.14** ▲ (a) The values of  $v_t$  versus  $i_t$  for the device in Fig. 2.13. (b) The circuit model for the device in Fig. 2.13.

## 2-5 Kirchhoff's Laws

- **Node**

The node is a point where two or three or more circuit elements meet. It is necessary to identify nodes in order to use **Kirchhoff's Current Law (KCL)**.

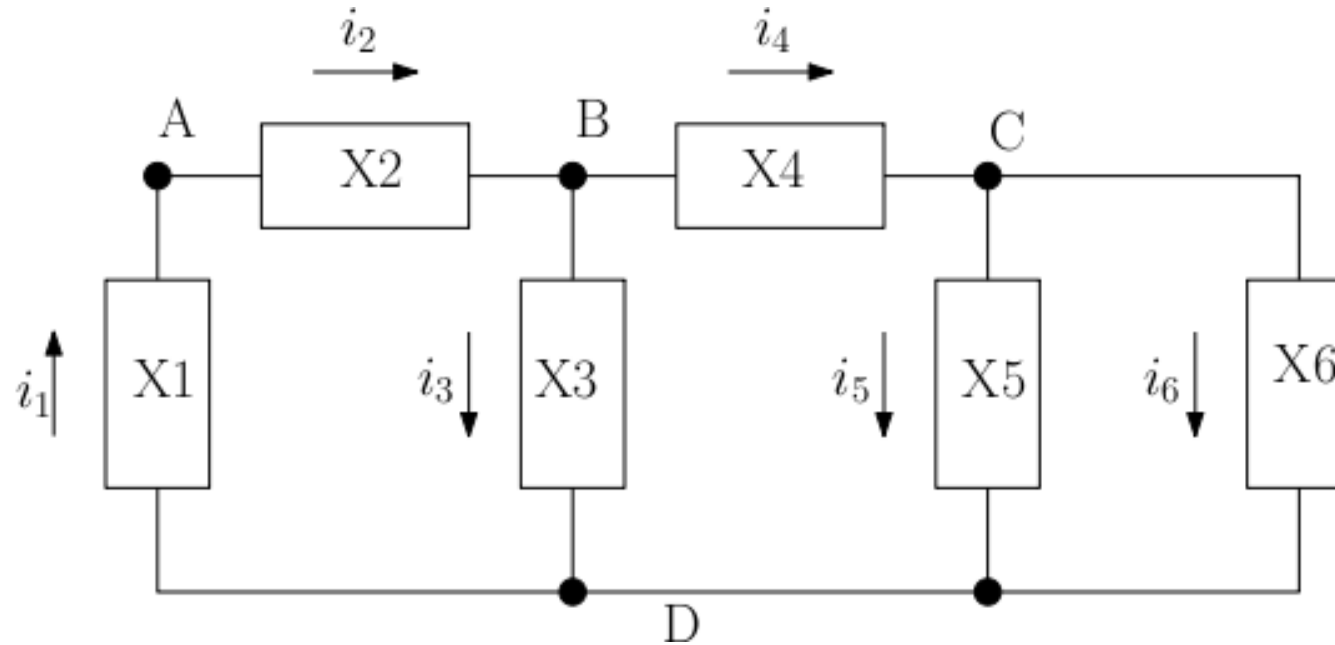In the circuit shown, the nodes are labeled : A, B, C, D




## 2-5 Kirchhoff's Laws

- Branches**

A circuit is visualized as a network in which each element constitute a **branch**.

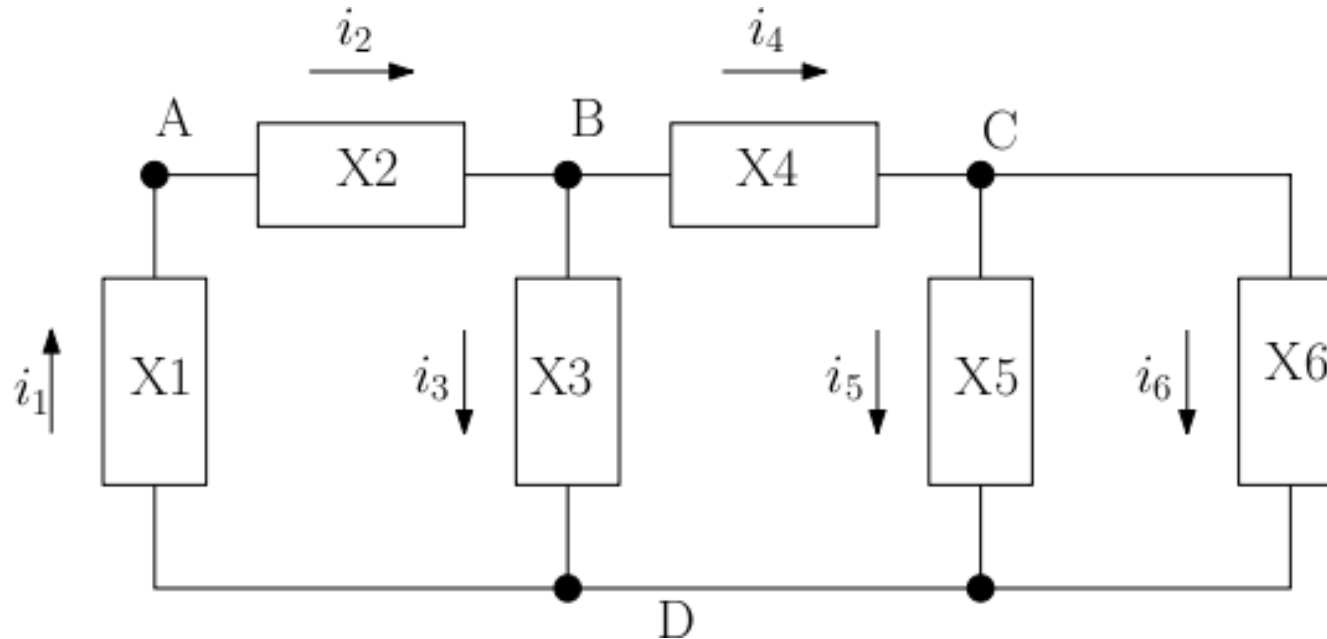The network shows in the figure has 6 branches labeled: X1, X2, X3, X4, X5, X6



## 2-5 Kirchhoff's Laws

- Loops**

we trace a closed path in a circuit through selected basic circuit elements and return to the original node without passing through any intermediate node more than once.

In the circuit shown in the figure, There are 6 Loops:

Loop (1): X1 X2 X3


Loop (2): X3 X4 X5

Loop (3): X5 X6

Loop (4): X1 X2 X4 X5

Loop (5): X1 X2 X4 X6

Loop (6): X3 X4 X6

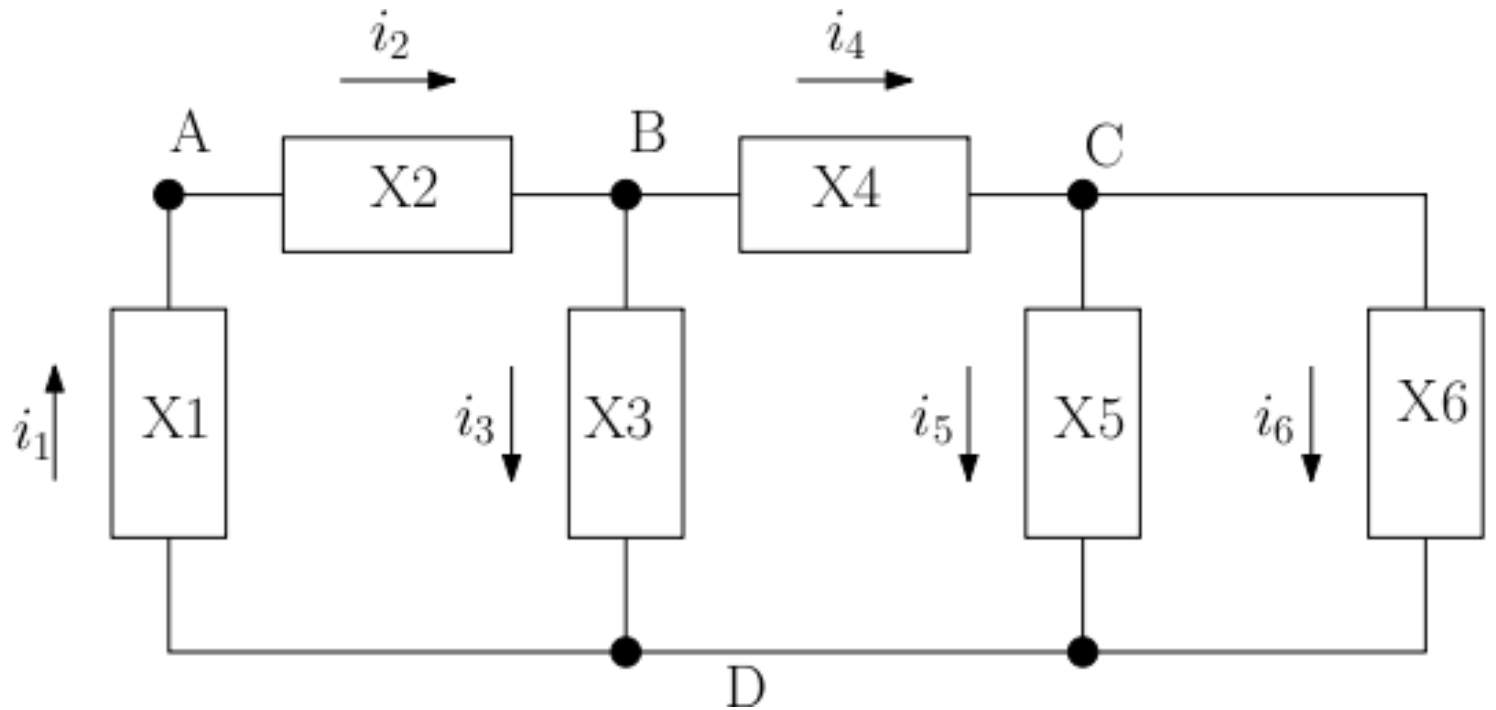

## 2-5 Kirchhoff's Laws

### a) KCL: Kirchhoff's Current Law


The algebraic sum of all the currents at any node in a circuit equals zero.

$$\sum i_{out} - \sum i_{in} = 0$$

Or

$$\sum i_{in} = \sum i_{out}$$

$$i_1 + i_2 = i_3 + i_4 + i_5$$

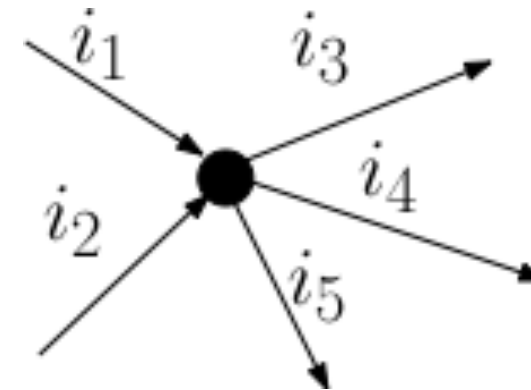

## 2-5 Kirchhoff's Laws

### Example 5:

Apply KCL to the circuit shown in the figure

At Node A :

$$i_1 = i_2$$

At Node B :


$$i_2 = i_3 + i_4$$

At Node C :

$$i_4 = i_5 + i_6$$

At Node D :

$$i_1 = i_3 + i_5 + i_6$$

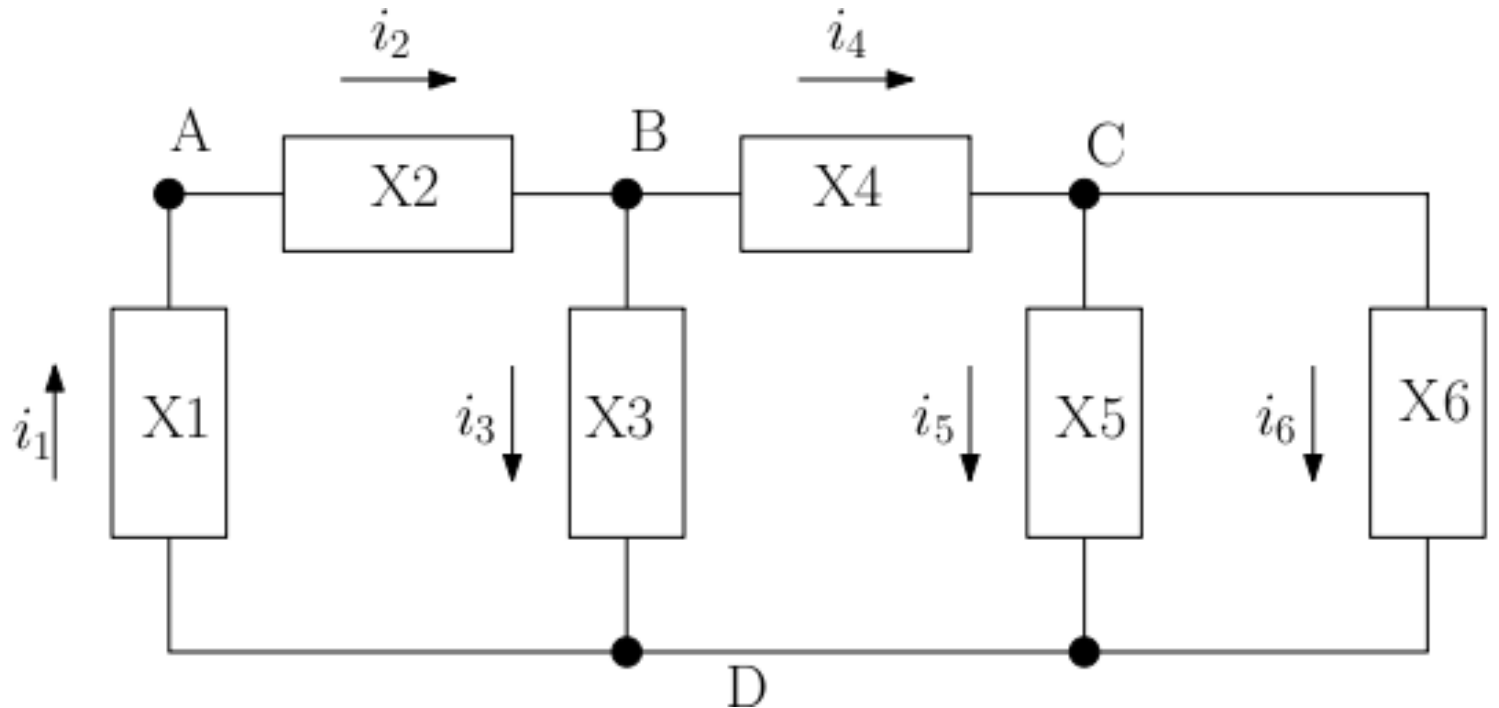

## 2-5 Kirchhoff's Laws

### b) KVL: Kirchhoff's Voltage Law

**The algebraic sum of all the voltages around any closed path in a circuit equals zero.**

$$\sum v_{rise} - \sum v_{drop} = 0$$

Or


$$\sum v_{rise} = \sum v_{drop}$$

**Closed path or Loop:** Starting at an arbitrary selected node, we trace a closed path in a circuit through selected basic circuit elements and return to the original node without passing through any intermediate node more than once.

## 2-5 Kirchhoff's Laws
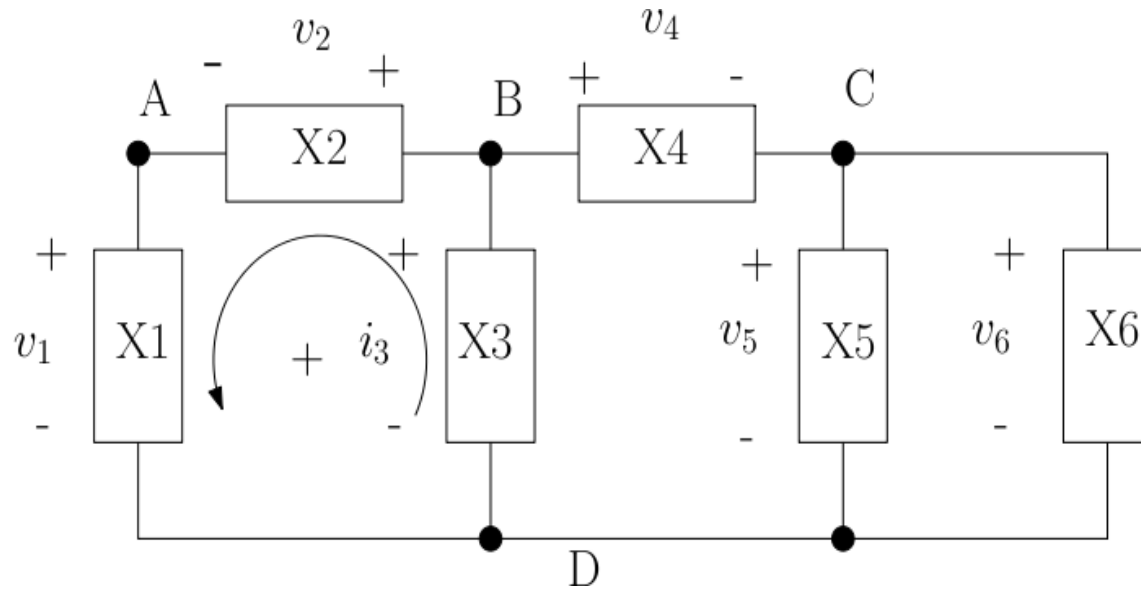
### Example 6:


Apply KVL to the circuit shown in the figure



## 2-5 Kirchhoff's Laws
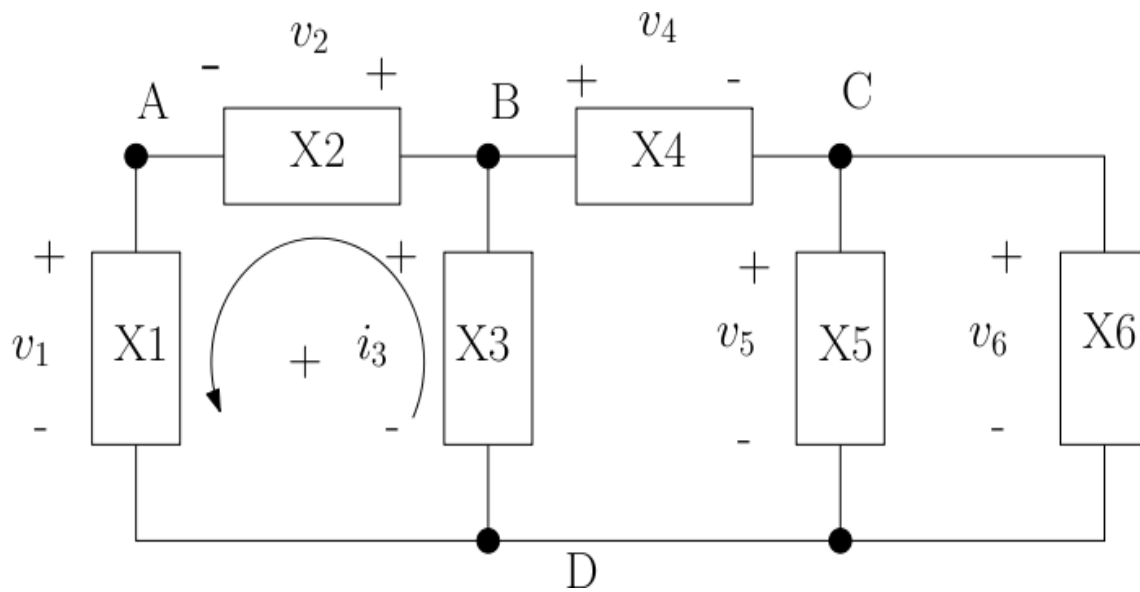
### Solution:

Apply KVL to the circuit shown in the figure



Loop (X1 X2 X3)

$$v_1 + v_2 - v_3 = 0$$

$$v_1 + v_2 = v_3$$

Loop (X3 X4 X5)

$$v_3 - v_4 - v_5 = 0$$

$$v_3 = v_4 + v_5$$

Loop (X5 X6)

$$v_5 - v_6 = 0 \rightarrow v_5 = v_6$$

Loop (X1 X2 X4 X5)

$$v_1 + v_2 - v_4 - v_5 = 0$$

$$v_1 + v_2 = v_4 + v_5$$

Loop (X1 X2 X4 X6)

$$v_1 + v_2 - v_4 - v_6 = 0$$

$$v_1 + v_2 = v_4 + v_6$$

Loop (X3 X4 X6)


$$v_3 - v_4 - v_6 = 0$$

$$v_3 = v_4 + v_6$$

## 2-5 Kirchhoff's Laws
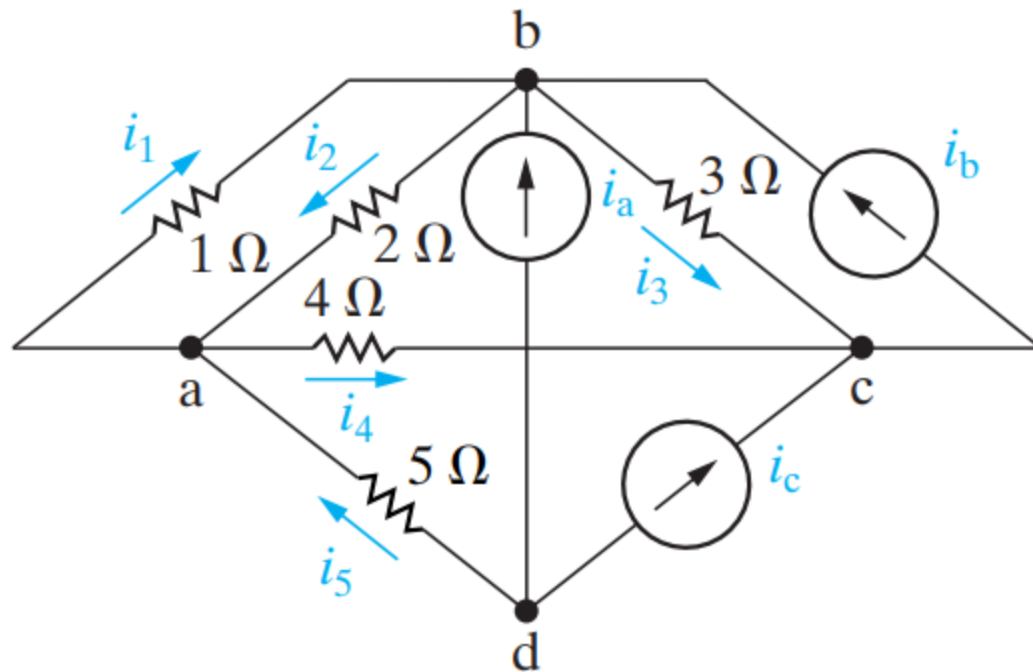
### Example 7:

Apply KCL to the circuit shown in the figure



### Solution

In writing the equations, we use a positive sign for a current leaving a node. The four equations are

$$\text{node a} \quad i_1 + i_4 - i_2 - i_5 = 0,$$

$$\text{node b} \quad i_2 + i_3 - i_1 - i_b - i_a = 0,$$


$$\text{node c} \quad i_b - i_3 - i_4 - i_c = 0,$$

$$\text{node d} \quad i_5 + i_a + i_c = 0.$$

## 2-5 Kirchhoff's Laws
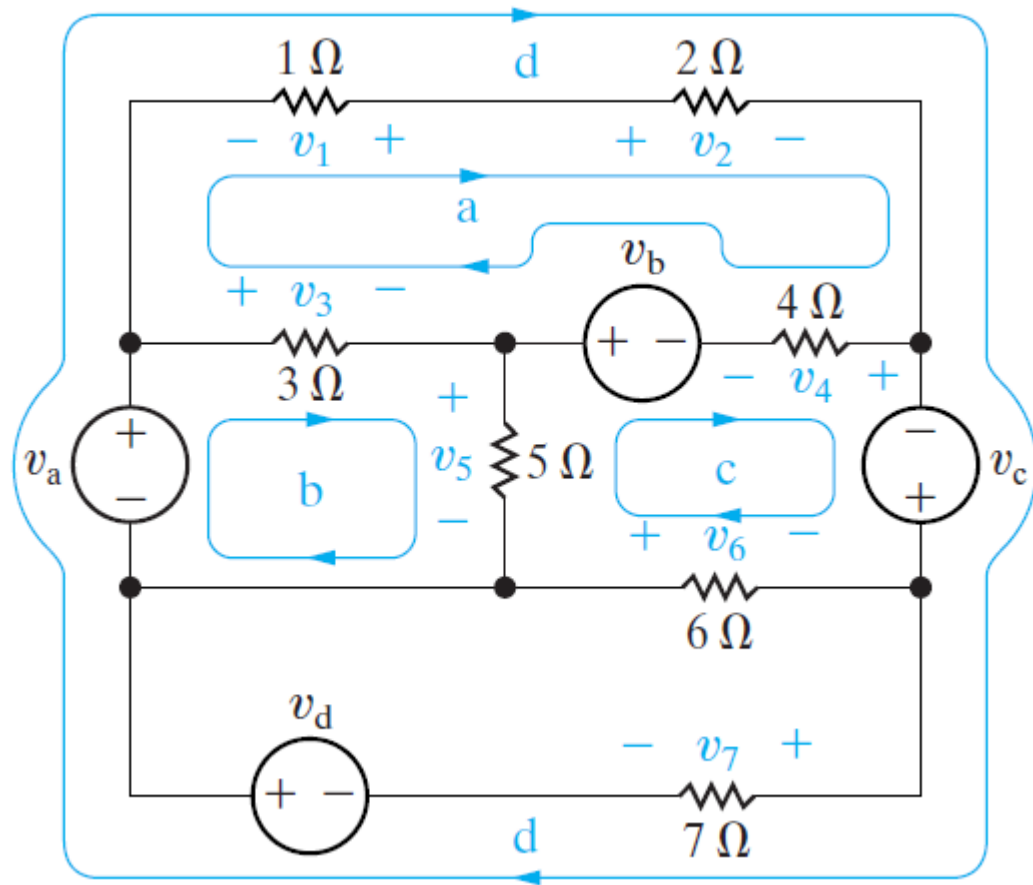
### Example 8:

Apply KVL to the circuit shown in the figure



### Solution

In writing the equations, we use a positive sign for a voltage drop. The four equations are

$$\text{path a} \quad -v_1 + v_2 + v_4 - v_b - v_3 = 0,$$

$$\text{path b} \quad -v_a + v_3 + v_5 = 0,$$

$$\text{path c} \quad v_b - v_4 - v_c - v_6 - v_5 = 0,$$

$$\text{path d} \quad -v_a - v_1 + v_2 - v_c + v_7 - v_d = 0.$$