

Topic 1

AC Networks Analysis

Dr. Ala A. Hussein

Part 2

Phasor Domain

- Phasor is a complex number representation in terms of amplitude & phase of a sinusoidal wave shape
- Engineers use phasors to simplify solution of circuitry involving sinusoidal voltages & currents.

* Time domain *

$$v(t) = \underline{\underline{5 \cos(30t + 60^\circ)}}$$

Dir-Lit, CIF

R $v_R = c'R$

C $i'_C = C \frac{\partial v}{\partial \underline{\underline{t}}} \rightarrow v_C = \frac{1}{C} \int \underline{\underline{i_C}}$

L $v_L = L \frac{\partial \underline{\underline{i'_L}}}{\partial t} \rightarrow i_L = \frac{1}{L} \int \underline{\underline{v_L}}$

* Complex number : *

①

$Z = a + j b$
Rectangular Form

Real Part
Imag Part

$$j = \sqrt{-1}$$

Real part

Im part

(3,3)

$j3$

$3 + j3$

Real part

$Z = 3 + j3$
Magnitude and Angle

$\sqrt{10}$

Angle

② polar form

$$z = \underline{|z|} \angle \theta$$

$$z = \textcircled{5} \angle \underline{+30} \checkmark$$



$$z = \underline{a} + j\underline{b} \rightarrow \text{rect}$$

$$z = \underline{|z|} \angle \underline{\theta} \rightarrow \text{polar}$$


کیف قبول $\rightarrow$ rect $\rightarrow$ polar

$$|z| = \sqrt{a^2 + b^2}, \quad \theta = \tan^{-1}\left(\frac{b}{a}\right)$$

کیف قبول $\rightarrow$ polar $\rightarrow$ rect

$$a = |z| \cos \theta, \quad b = |z| \sin \theta$$

Euler's identity

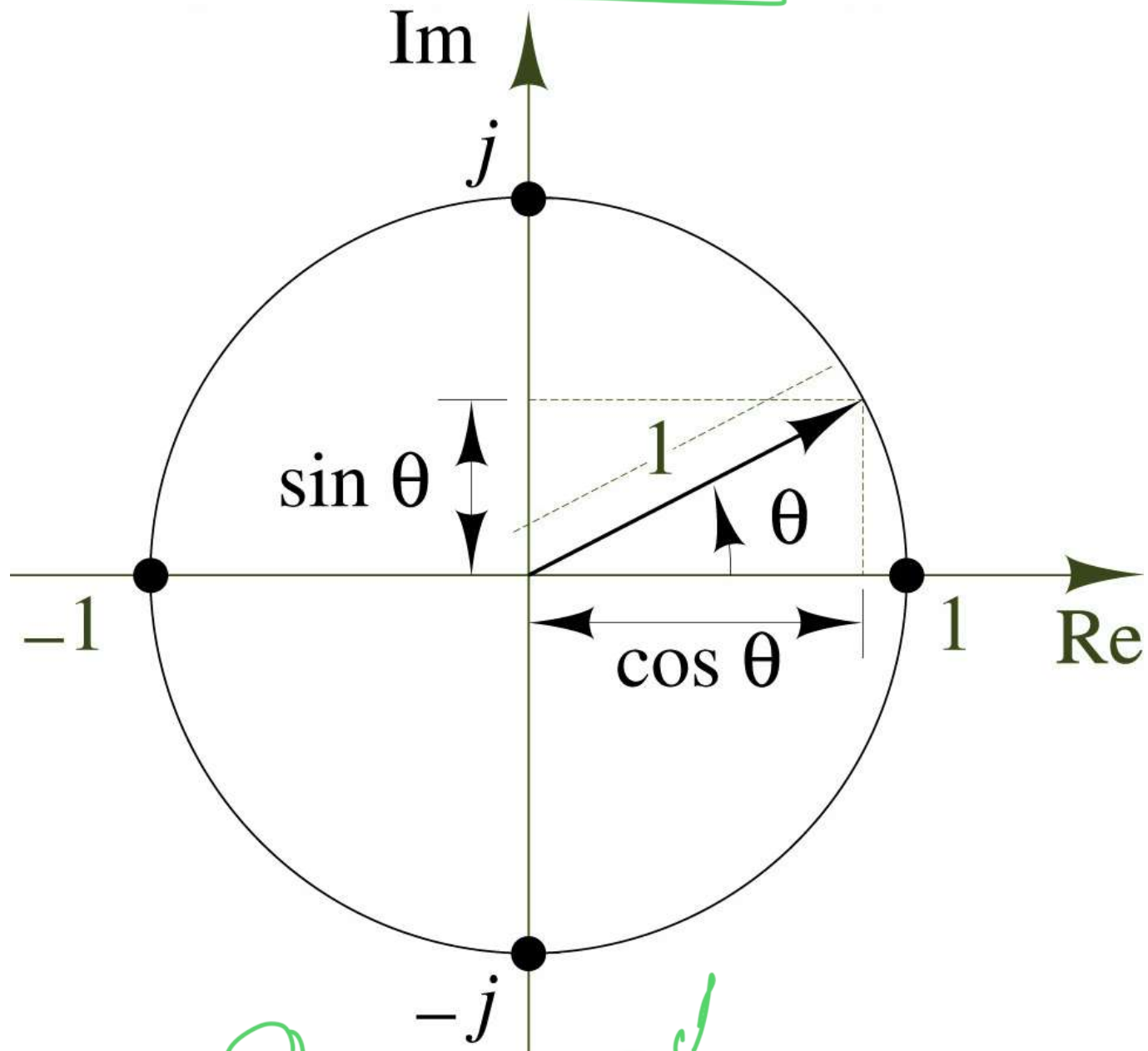

$$e^{j\theta} = \cos \theta + j \sin \theta \rightarrow \text{Imag}$$

Handwritten notes: $e^{j\theta}$ is circled in green with an arrow pointing to 'real'. $\cos \theta$ is underlined in green with an arrow pointing to 'real'. $j \sin \theta$ is circled in green with an arrow pointing to 'Imag'.

for Voltage $v(t)$

$$v(t) = V_M \cos(\omega t + \Theta)$$

Using Euler's formula

$$e^{jx} = \cos(x) + j \sin(x)$$

$$\Rightarrow V_M e^{j(\omega t + \Theta)} = V_M \cos(\omega t + \Theta) + j V_M \sin(\omega t + \Theta)$$

$$\Rightarrow v(t) = V_M \cos(\omega t + \Theta) = \text{Re}[V_M e^{j(\omega t + \Theta)}]$$

$$= \text{Re}[V_M e^{j\omega t} e^{j\Theta}]$$

$$= \text{Re}[V_M \angle \Theta e^{j\omega t}]$$

$$\Rightarrow v(t) = V e^{j\omega t}$$

where

$$\underbrace{V = V_M \angle \Theta}_{\text{Phasor form}}$$

Phasor form

← Dropping $e^{j\omega t}$ since it exists in all terms

X

Phasor representation :

Time domain $\leftrightarrow$ Phasor form

$$A \cos(\omega t \pm \Theta) \leftrightarrow A \angle \pm \Theta$$

$$+ A \sin(\omega t \pm \Theta) \leftrightarrow A \angle (\pm \Theta - 90^\circ)$$

Use Cosine as reference

$$\begin{aligned} + \sin(\omega t + \Theta) &\longrightarrow \cos(\omega t + \Theta - 90^\circ) \\ - \sin(\omega t + \Theta) &\longrightarrow \cos(\omega t + \Theta + 90^\circ) \end{aligned}$$


Current $\Rightarrow$ cos ✓
Voltage $\Rightarrow$ sin

Phasor form

تذکرہ

*

R

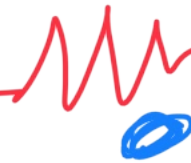

C




۱۱



L



۱۲

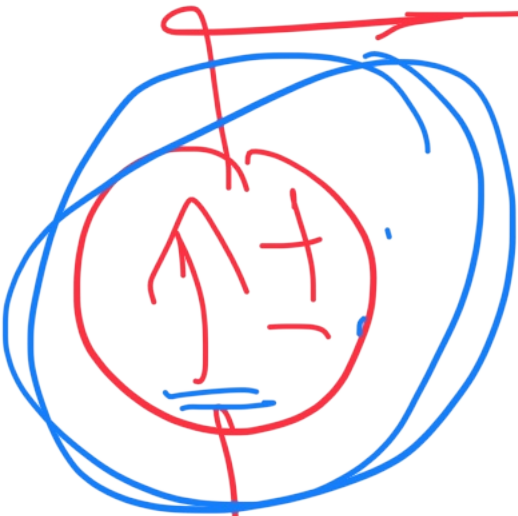

Example :

Convert from time domain to phasor form

$$v(t) = 24 \cos (337 t - 45^\circ)$$

$$i(t) = 12 \sin (337 t + 120^\circ)$$

$$V = 24 \angle (-45^\circ) \text{ V}$$

$$I = 12 \angle (120^\circ - 90^\circ) = 12 \angle 30^\circ \text{ A}$$

$$v(t) = \underline{24} \cos(\underline{337t} - \underline{45})$$

$$V = 24 \angle -45 \text{ V}$$

$$i'(t) = +12 \underline{\sin}(337t + 120)$$

$$= \underline{12} \cos(\cancel{337t} + 120 - 90)$$

$$I = 12 \angle 30 \text{ A}$$

$$\frac{d}{dt} \cos = -\sin$$

Example :

Convert from phasor form to time domain

$$V = 16 \angle 120^\circ \text{ V}$$

$$I = 10 \angle (-75^\circ)$$

if $f = 1 \text{ KHz}$

$$\omega = 2 \pi f = 2 \pi (1000) = 2000 \pi$$

$$v(t) = 16 \cos(2000 \pi t + 120^\circ)$$

$$i(t) = 10 \cos(2000 \pi t - 75^\circ)$$

Phasor
Time
V
v(t), i(t)

حرف کچھ
حرف کچھ

$$V = 16 \angle 120^\circ \text{ V}$$

$$v(t) = 16 \cos(\omega t + 120^\circ) \text{ V}$$

$$v(t) = 16 \cos(2000\pi t + 120^\circ) \text{ V}$$

$$I = 10 \angle -75^\circ \text{ A}$$

$$i(t) = 10 \cos(\omega t - 75^\circ) \text{ A}$$

$$i(t) = 10 \cos(2000\pi t - 75^\circ) \text{ A}$$

$$\omega = 2\pi f$$

$$\omega = 2\pi \times 1000$$

$$\omega = \underline{2000\pi} \text{ rad/s}$$

Phasor Domain Representation of Circuit Elements

For Resistors:

cos


$$i(t) = I_{max} \cos(\omega t + \phi)$$

$$v(t) = R * i(t)$$

Ohm


$$v(t) = R I_{max} \cos(\omega t + \phi)$$

$$v(t) = V_{max} \cos(\omega t + \phi)$$

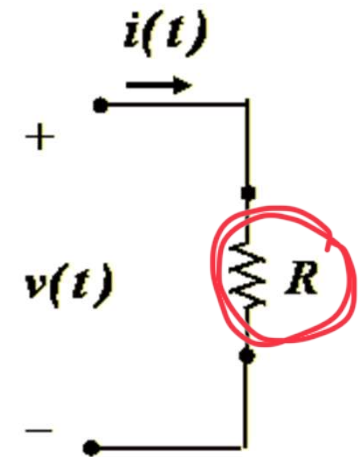

Time-domain

Phasor domain

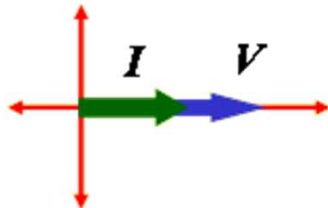


NOTE: The voltage and the current are in phase.

$$I = I_{max} \angle + \phi^o$$

$$V = V_{max} \angle \phi^o$$
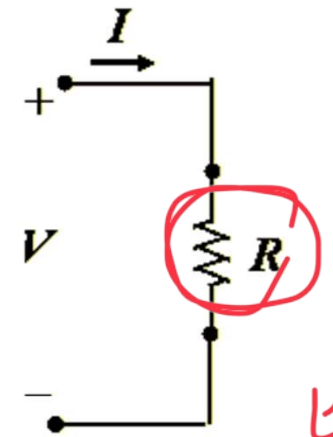
$$R = \frac{V_{max} \angle \phi^o}{I_{max} \angle \phi^o} = \frac{V_{max}}{I_{max}}$$



Phasor domain

$$Z_R = R$$

Impedance → phasor

15


me

$$e(k) \Rightarrow$$

$$R = Z \sim L$$

$$\Rightarrow v = C^T R \Rightarrow \text{size} \Rightarrow$$
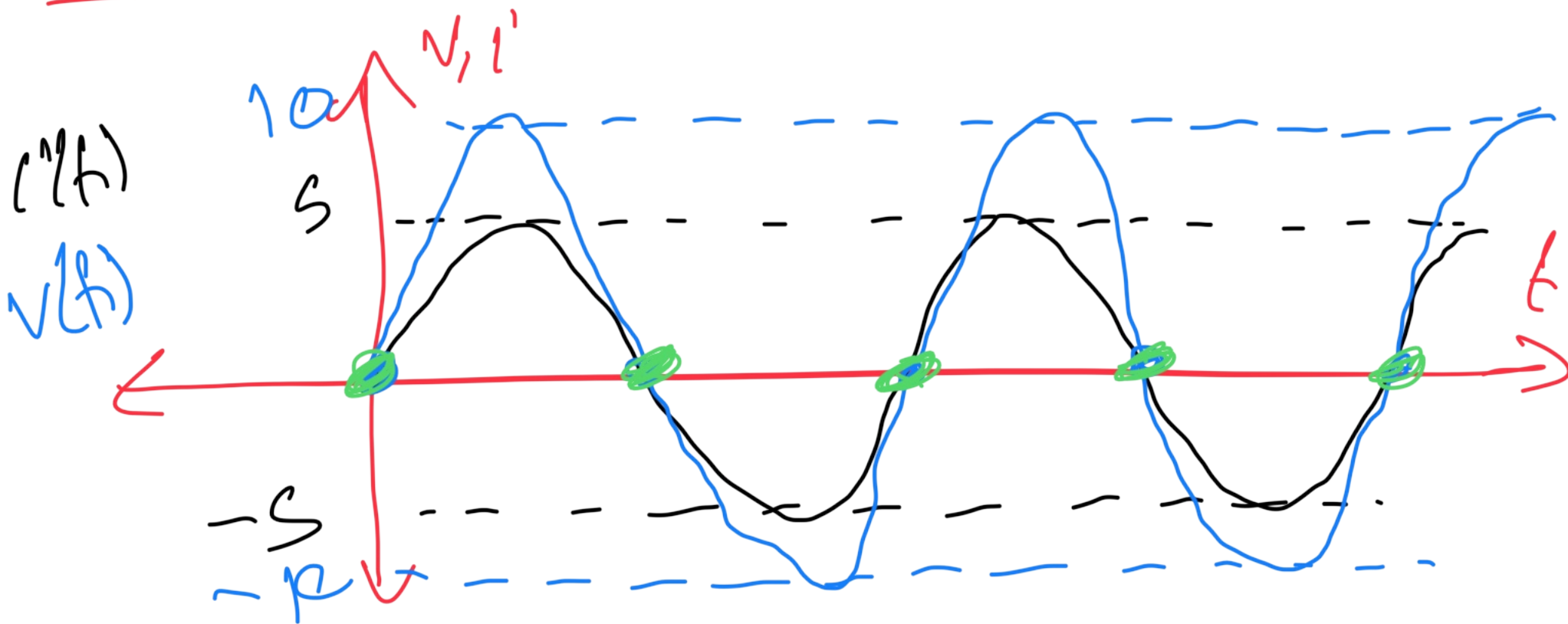
$$\underline{10 \cos(\omega t)} \cdot \checkmark$$



For Inductors:

$$Z_L = j\omega L$$




$$i(t) = I_{max} \cos(\omega t + \phi)$$

$$v(t) = L \frac{di(t)}{dt}$$


$$v(t) = -\omega L I_{max} \sin(\omega t + \phi)$$
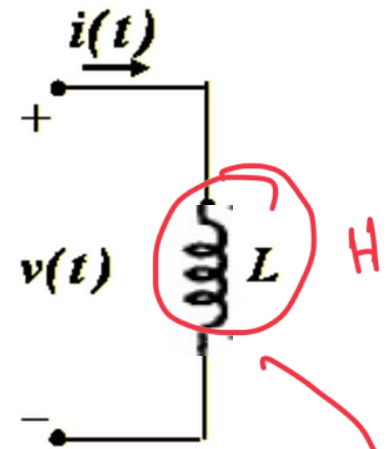
$$v(t) = +\omega L I_{max} \cos(\omega t + \phi + 90)$$



Time-domain

Phasor domain

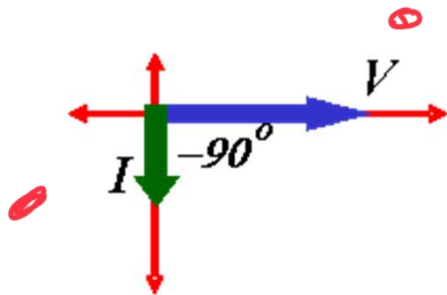

NOTE: The current lagging the voltage by 90°


$$I = I_{max} \angle +\phi^\circ$$

$$V = \omega L I_{max} \angle (\phi + 90)^\circ$$

$$V = (\omega L \angle 90^\circ)(I_{max} \angle \phi^\circ)$$

$$V = j\omega L I$$

$$Z_L = \frac{V}{I} = j\omega L$$

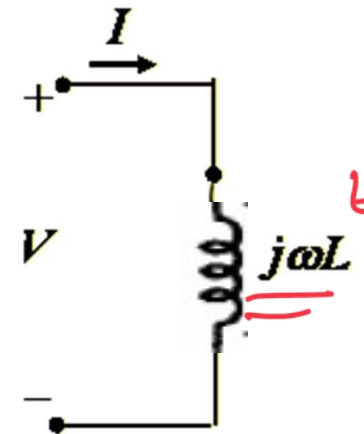

Phasor domain

$$Z_L = j\omega L$$

$$V_L = L \frac{di'}{dt}$$

$$\underline{i'(t)} \Rightarrow \underline{\text{Im}} \underline{\cos(\omega t + \theta)}$$

$$V_L = -L \cdot \text{Im} \omega \cdot \sin(\underline{\omega t} + \theta)$$

$$V_L = \ominus \text{Im} L \omega \underline{\sin(\omega t + \theta)}$$

$$V_L = + \text{Im} L \omega \cos(\omega t + \theta + 90)$$

$$\begin{aligned} \theta_V &= \theta + 90: \\ \theta_{i'} &= \theta \end{aligned} \quad \Rightarrow \quad \theta_V > \theta_{i'}$$

القائد / مركز الأول : lead

التابع / مركز الثاني : lag

مصدر سابق على ← مصدر : مركز الأول
على : مركز الثاني

على متأخر منه ← مصدر : مركز الأول
على : مركز الثاني

$$\theta_v > \theta_i$$


$\left\{ \begin{array}{l} \rightarrow \text{Voltage lead current by } \theta_v - \theta_i \\ \rightarrow \text{current lag voltage by } \theta_v - \theta_i \end{array} \right.$

For Capacitors:

$$Z_C = \frac{1}{j\omega C}$$


Phasor domain

$$\theta_i > \theta_v$$

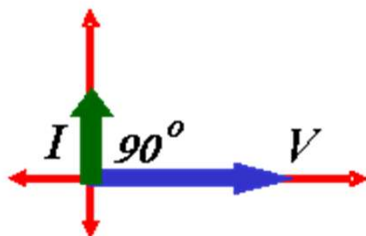


NOTE: The current leading the voltage by 90°

$$v(t) = V_{max} \cos(\omega t + \phi)$$


$$i(t) = C \frac{dv(t)}{dt}$$

$$i(t) = -\omega C V_{max} \sin(\omega t + \phi)$$
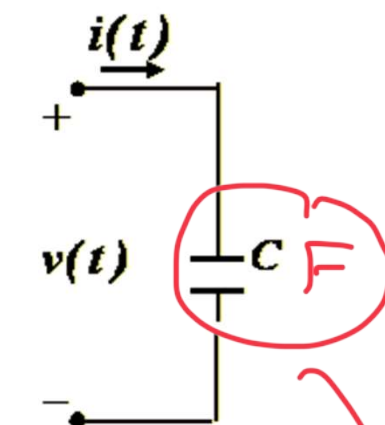
$$i(t) = +\omega C V_{max} \cos(\omega t + \phi + 90)$$



Time-domain

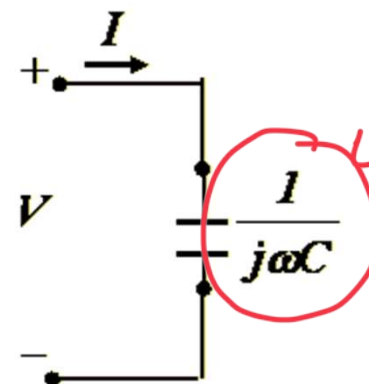

Phasor domain


$$Z_C = \frac{V}{I} = \frac{1}{j\omega C}$$

$$Z_C = \frac{1}{j\omega C}$$

Impedances of R , L , and C in the complex plane

needed

phasor domain

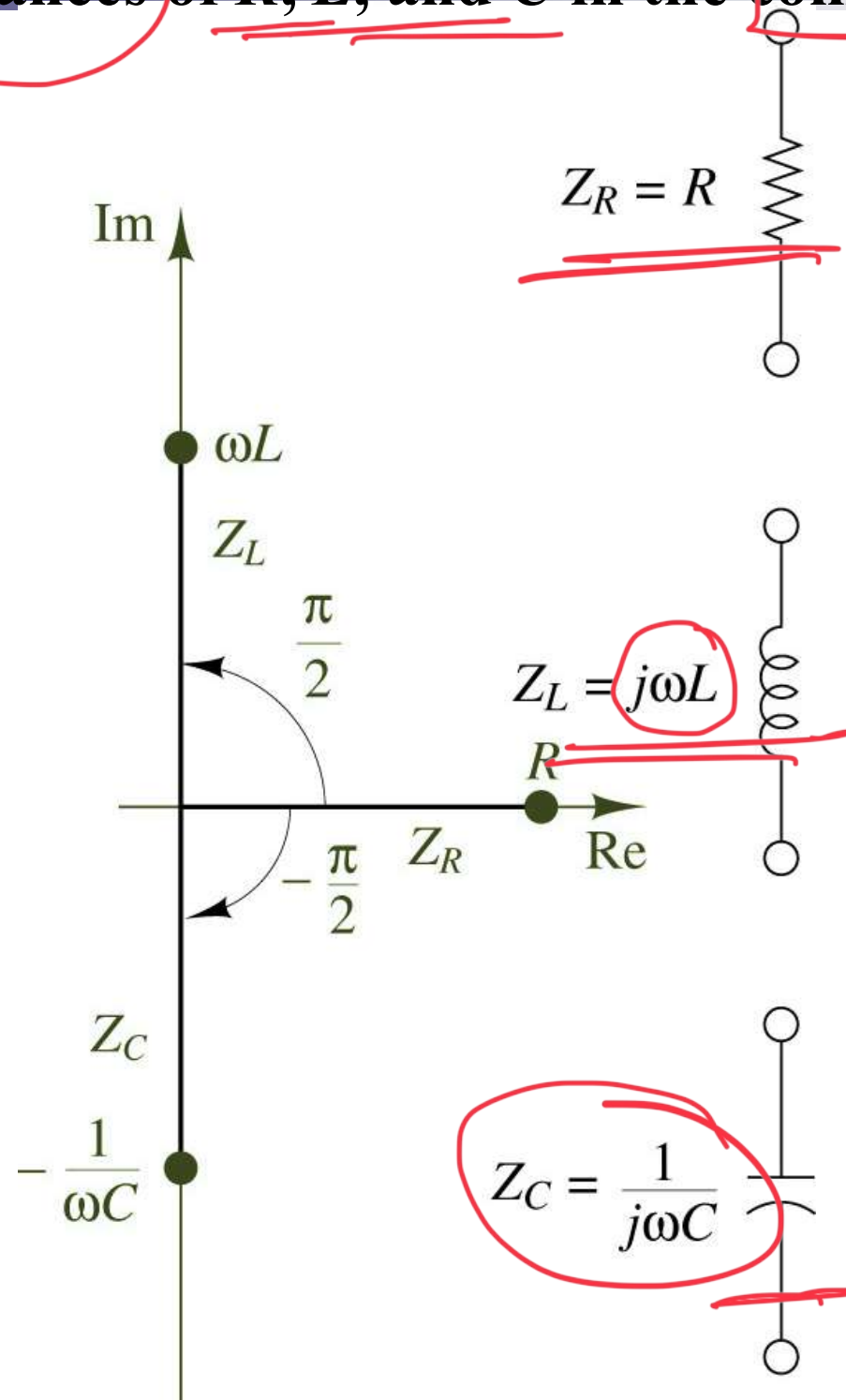

~~→ also $\vec{a}' \neq \vec{b}$~~

Impedance : $Z = \underline{R} + j \underline{X}$


"Rect / complex plane"

Real part : $R \Rightarrow$ Resistor or resistor


Imag part : $X \Rightarrow$ $+$ $\Rightarrow$ Inductor.
 $- \Rightarrow$ capacitor.

Rules for impedance reduction

Impedances in series add:

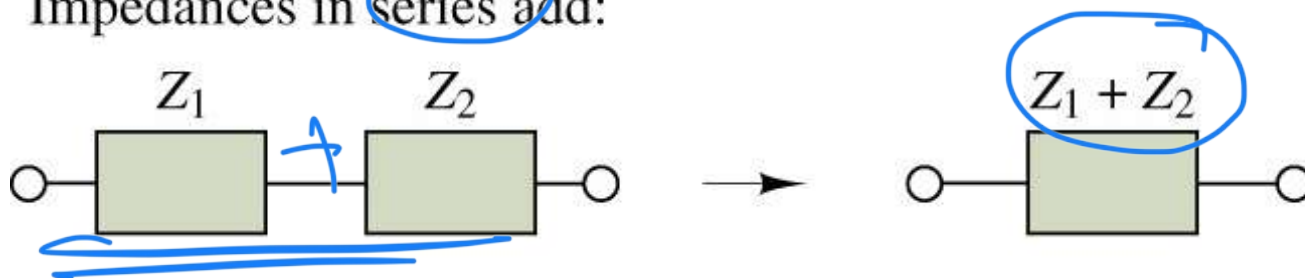

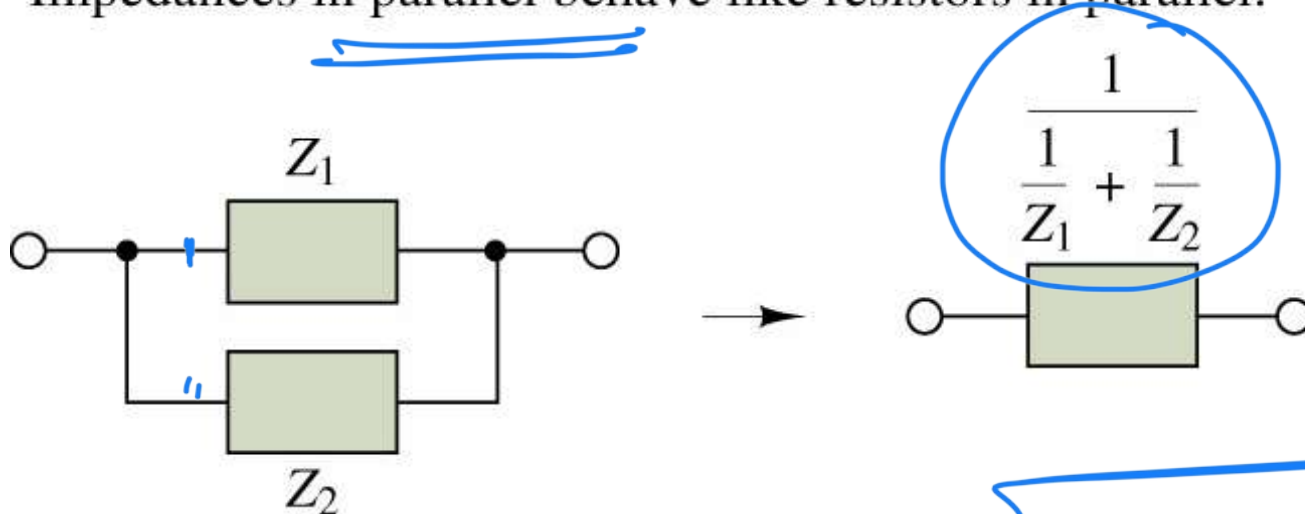Impedances in parallel behave like resistors in parallel:



Handwritten notes in blue ink:

Z_1

$$\frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$$

$||$

Handwritten notes in blue ink, enclosed in a box:

~~series~~

~~parallel~~

In summary :

phor
phasor form

$$Z = |Z| \angle \Theta_z$$

$$|Z| = \frac{V_m}{I_m}$$

$$\Theta_z = \Theta_v - \Theta_i$$

rect
complex form


$$Z = R + jX$$

$$|Z| = \sqrt{R^2 + X^2}$$

$$\Theta_z = \tan^{-1} \left(\frac{X}{R} \right)$$

Class Activity:

Find Z_{AB} as a function of frequency.

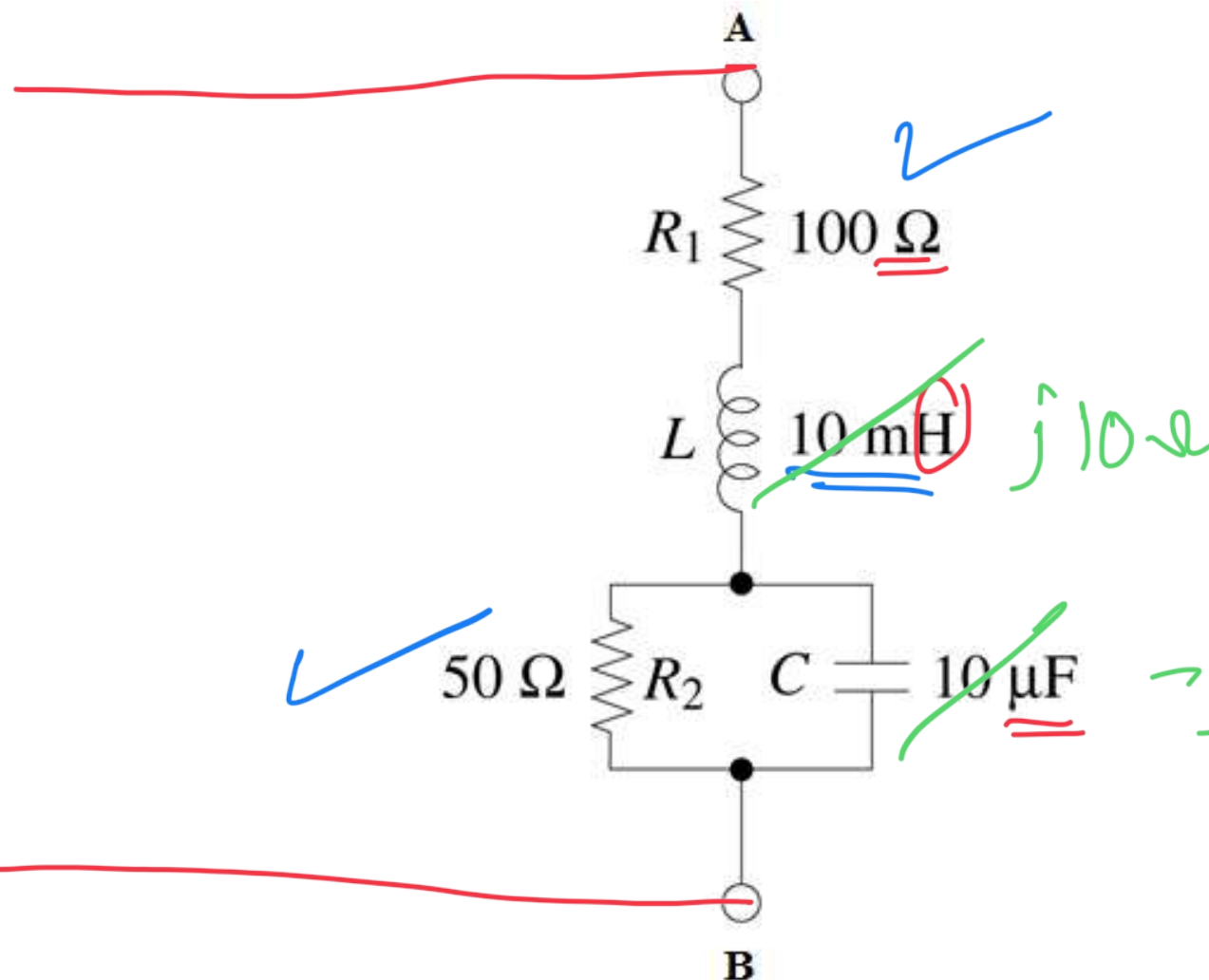

Time domain
 $\omega = 1000\text{ rad/s}$

Phasor domain

نقطة ١

$$Z_R = R$$


$$Z_L = j\omega L = j \times 1000 \times 10 \times 10^{-3} = +j10 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 1000 \times 10 \times 10^{-6}} = -j100 \Omega$$

$$Z_L \rightarrow +j$$

ملاحظة: j هو 90°


$$Z_C \rightarrow -j$$

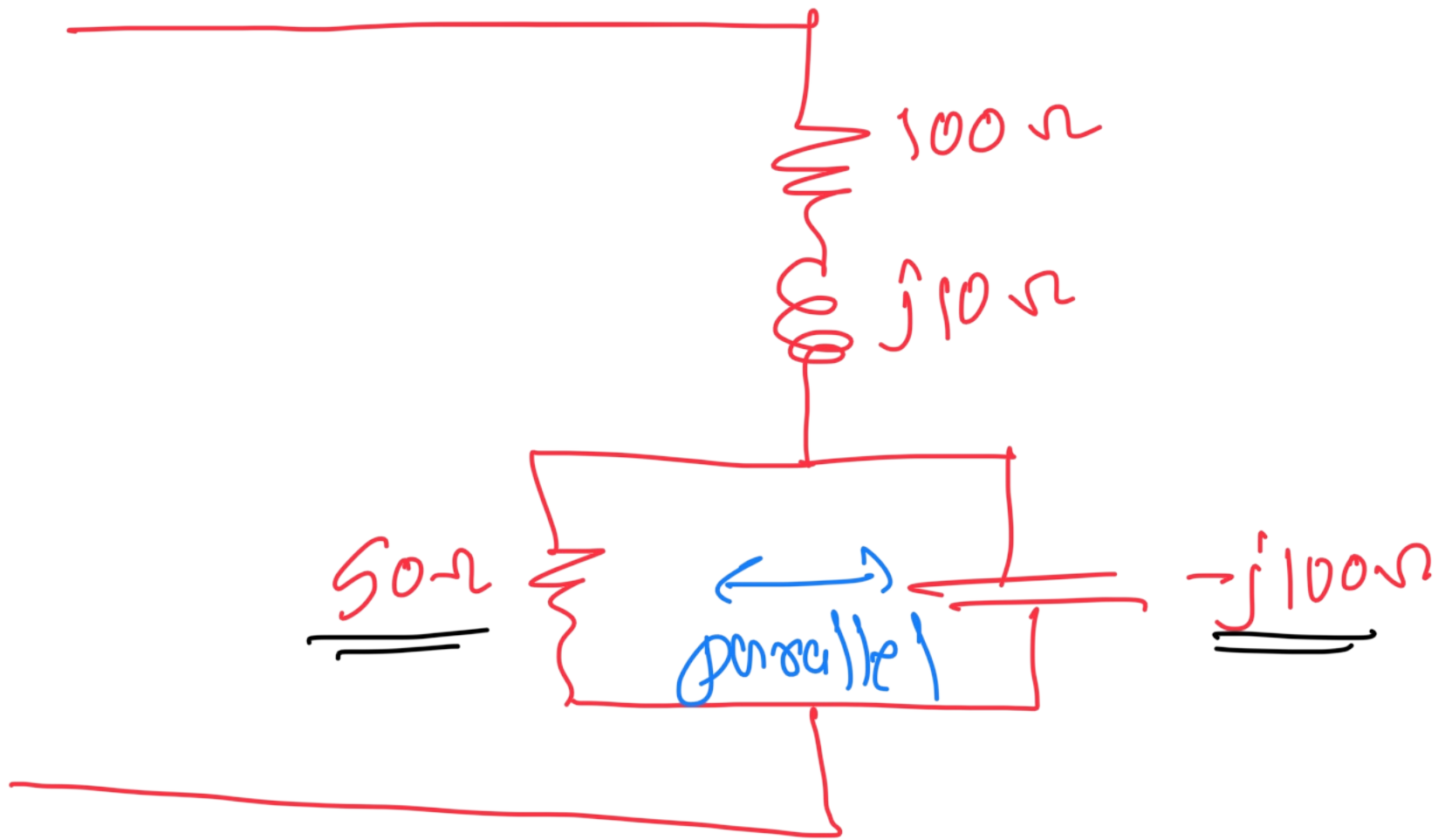

$$\frac{1}{\frac{1}{50} + \frac{1}{-j100}}$$

$$= \underline{\underline{40}} \ominus \underline{\underline{j20\ \Omega}}$$

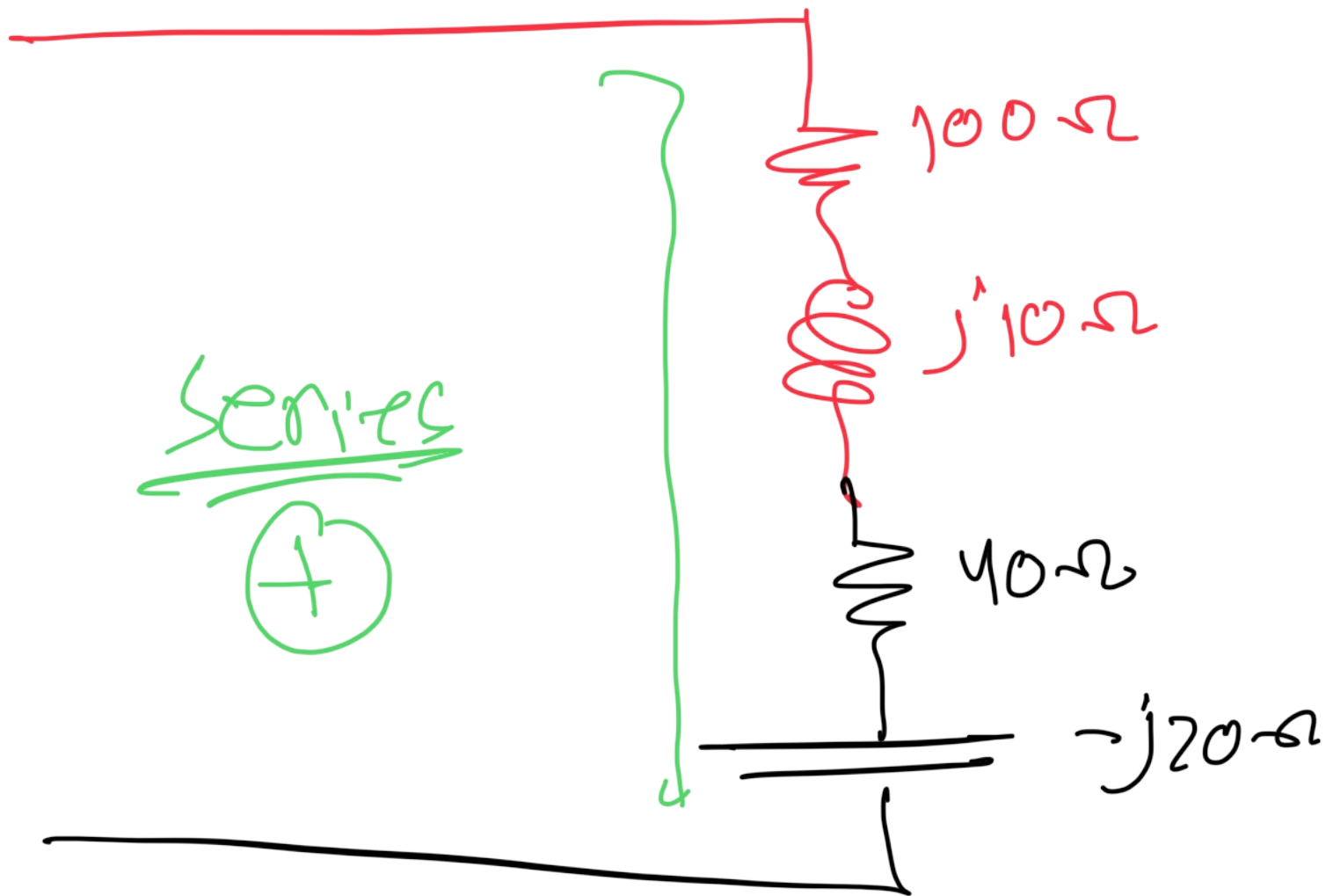$\underbrace{\hspace{1cm}}_R \qquad \underbrace{\hspace{1cm}}_C$



$$Z_{AB} = 100 + j10 + 40 - j20$$

$$Z_{AB} = 140 - j10\ \Omega$$



Example :

If the voltage across the 20 mH inductor is

$$v(t) = 12 \cos(377t + 20^\circ) \quad \text{find } i(t) ?$$


$$V = j \omega L I$$

$$12 \angle 20^\circ = j(377)(20 \text{ m}) I$$

$$I = \frac{12 \angle 20^\circ}{(377)(20 \text{ m}) \angle 90^\circ} = 1.59 \angle (-70^\circ)$$

$$i(t) = 1.59 \cos(377t - 70^\circ)$$

Time Domain

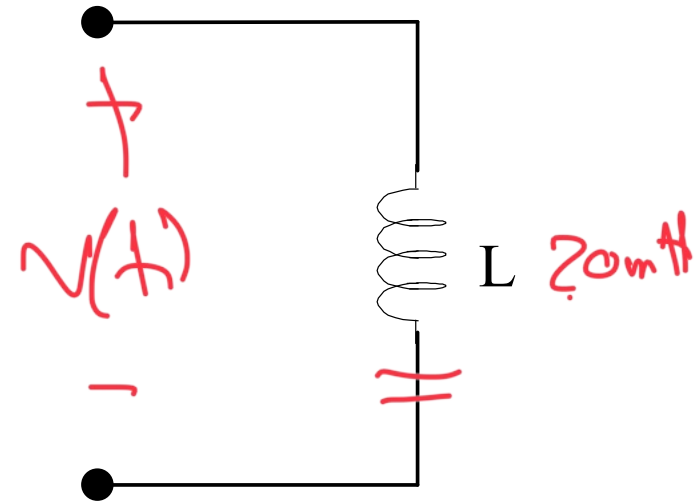

$$V(t) = 12 \cos(377t + 20^\circ) \text{ V}$$

$\mathcal{L} = \mathcal{L}_{\text{om}} + \mathcal{L}_{\text{A}}$

Time domain

Observer domain


لے فٹوں ای

$$V = 12 \text{ L @ } 20^\circ \text{C}$$

$\omega = \underline{\underline{377 \text{ rad/s}}}$

$$Z_L = j\omega L = j \times 377 \times 20 \times 10^{-3} = j 7.54 \Omega$$

ohm
↗

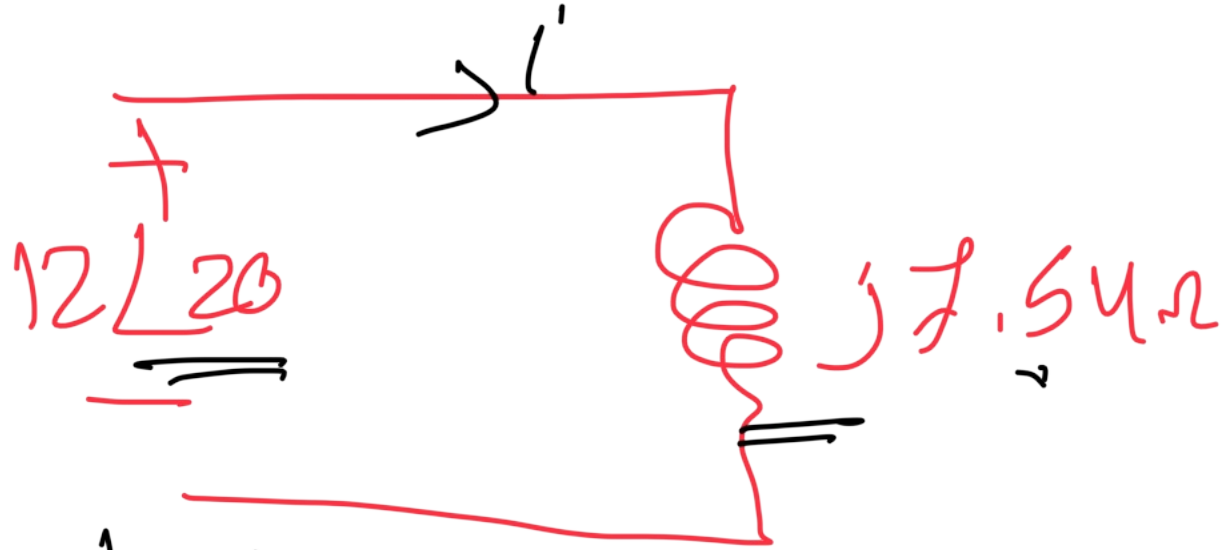

$$\underline{I} = \frac{V}{Z} \Rightarrow \frac{12\angle 20^\circ}{j7.54}$$

phasor
↗

$$\underline{I} = \underline{1.59\angle -70^\circ \text{ A}} = \frac{600}{377}\angle -70^\circ \text{ A}$$

$$i'(t) = 1.59 \cos(377t - 70^\circ) \text{ A}$$

عبر صيغة 2-1

$$V(t) = 12 \cos(377t + 20)$$

$$L = 20 \text{ mH}$$

$$V_L(t) = L \frac{di}{dt}$$

$$i_L(t) = \frac{1}{L} \int V_L(t) = \frac{1}{20 \times 10^{-3}} \int 12 \cos(377t + 20)$$

Example :

If the voltage across the capacitor is

$$v(t) = 100 \cos(314t + 15^\circ) \quad \text{find } \underline{i(t)} ??$$

$$C = 100 \mu\text{F}$$

$$I = j\omega CV$$

$$= j(314)(100)(100 \times 10^{-6}) \angle 15^\circ$$


$$I = (314)(10^4)(10^{-6}) \angle (15^\circ + 90^\circ) = 3.14 \angle 105^\circ$$

$$i(t) = 3.14 \cos(314t + 105^\circ)$$

or

$$i = C \frac{dv}{dt} = -(314)(100)(100 \times 10^{-6}) \sin(314t + 15^\circ)$$

$$i(t) = 3.14 \cos(314t + 105^\circ)$$

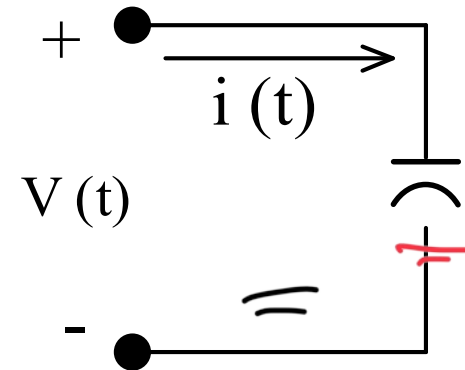

$$v(t) = 100 \cos(314t + \underline{15})$$

Example :

$$v(t)=10\sin(3t) \Leftrightarrow v=10\angle-90$$

Apply KVL to solve for the current

$$-V + RI + Z_L I = 0 \text{ where } Z_L = j\omega L$$

$$-10\angle-90 + 3I + j6I = 0$$

Solve for I


$$I = \frac{10\angle-90}{3+j6} = \frac{10\angle-90}{6.7\angle63.4} = 1.49\angle-153.4$$

in time domain reference is cosine

$$i(t) = 1.49\cos(3t - 153.43)$$

$$\sin(\phi) = \cos(\phi + 90)$$

$$i(t) = 1.49\sin(3t - 63.43)$$

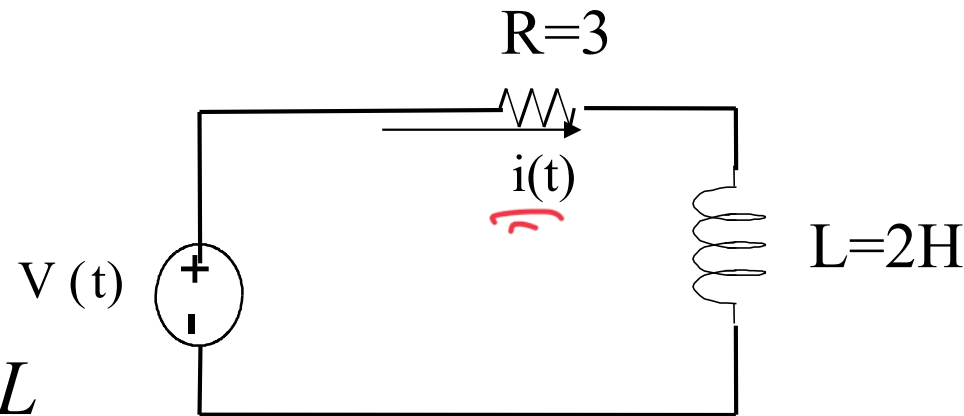

دالة الجهد
التيار

$$v(t) = 10 \sin(3t)$$

$$R = 3 \Omega$$

$$L = 2 \text{ H}$$

phasor $\rightarrow$

$$v(t) = 10 \cos(3t - 90^\circ)$$

$$V = 10 \angle -90^\circ \text{ V}$$

$$\omega = 3 \text{ rad/s}$$

$$Z_R = R = 3 \Omega$$

$$Z_L = j\omega L = j \times 3 \times 2 = j6 \Omega$$



Series

$$I = \frac{V}{Z} = \frac{10 \angle -90}{3 + j6}$$

$$I = \frac{2\sqrt{5}}{Z} \angle -153.43^\circ \text{ A}$$

$\hookrightarrow 1.4 \text{ A}$


Time $\int 1$ $\rightarrow$ $\int 1$

$$i(t) = 1.4 \cos(3t - 153.43^\circ) \text{ A}$$

Example:

Find the voltage across the capacitor.

$$v(t) = 10 \cos(4t)$$

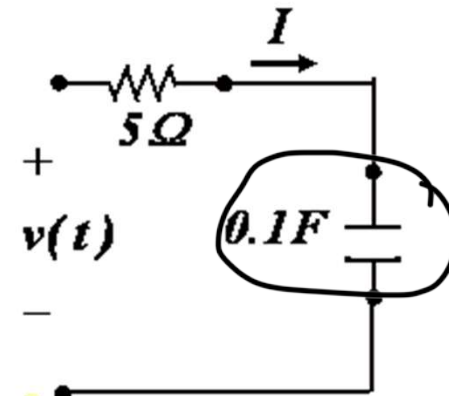

Solution:

Express circuit
In phasor domain

$$V = 10 \angle 0^\circ$$

$$Z_T = R + Z_C = R + \frac{1}{j\omega C} = 5 + \frac{1}{j(4)(0.1)}$$

$$Z_T = 5 - j2.5 \Omega$$

Solve for current

$$I = \frac{V}{Z_T} = \frac{10 \angle 0^\circ}{5 - j2.5}$$

$$I = 1.789 \angle 26.57^\circ \text{ A}$$

Solve for
capacitor voltage

$$V_C = IZ_C = (1.789 \angle 26.57^\circ) \left(\frac{1}{j(4)(0.1)} \right)$$

$$V_C = 4.47 \angle -63.43^\circ$$

Express voltage
In time domain

$$v_C(t) = 4.47 \cos(4t - 63.43^\circ)$$

$$v(t) = 10 \cos(4t) \quad R = 5\Omega \quad C = 0.1F$$

$$L, V = 10 \angle 0 = 10V$$

$$\omega = 4 \text{ rad/s}$$

$$Z_R = R = 5\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 4 \times 0.1} = -j2.5\Omega$$



Series

$$I = \frac{V}{Z} = \frac{10}{5 - j2.5}$$

①

$$I = 1.789 \angle 26.57^\circ \text{ A} \leftarrow$$

$$V_C = I Z_C = (1.789 \angle 26.57^\circ) \times (-j2.5)$$

$$V_C = 4.47 \angle -63.43^\circ \text{ V}$$

phasor

②

$$v_C(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

Series $\Rightarrow$ Voltage divider

$$V_C = \frac{-j2.5}{s - j2.5} \times 10 \quad \text{①}$$


$$V_C = 4.47 \angle -63.43^\circ \text{ V}$$

$$v_C(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

Example:

For the circuit shown in the Figure, determine:

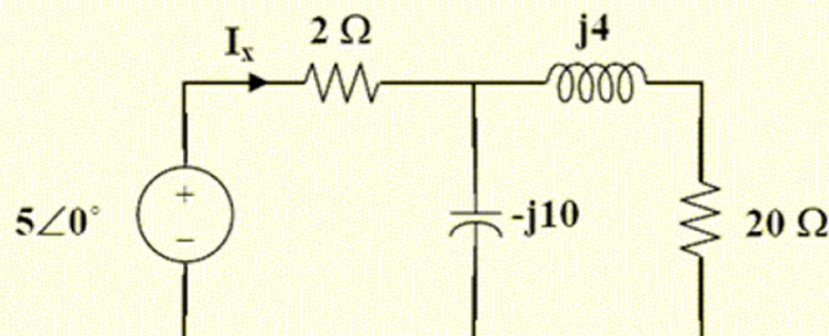1. The total impedance
2. The current I_X



Solution:

$$I_X = \frac{V}{Z_T}$$


$$Z_T = 2 + \left(\frac{(-j10)(20 + j4)}{(-j10) + (20 + j4)} \right) = 4.588 - j8.626\ \Omega$$

$$I_X = \frac{5}{2 + \frac{-j10(20 + j4)}{-j10 + 20 + j4}} = \frac{5}{2 + 4.588 - j8.626} = \frac{5}{10.854\angle -52.63^\circ} = 0.4607\angle 52.63^\circ$$

$$i_s(t) = \underline{\underline{0.4607\cos(2000t + 52.63^\circ)\text{ A}}}$$


Analysis of AC Circuits

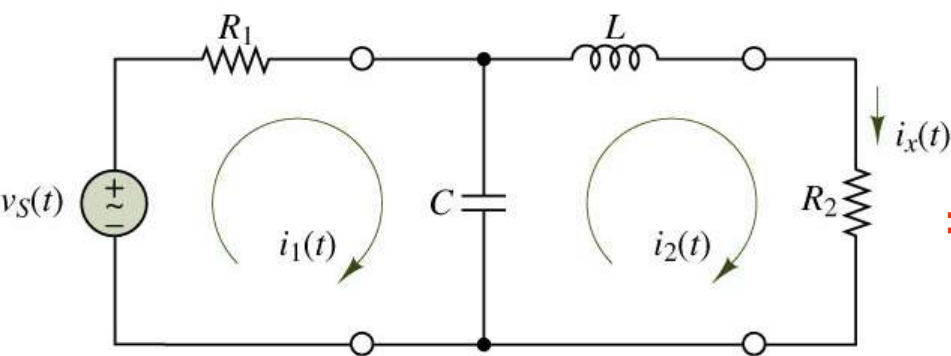- Substitute for every network with its impedance equivalent in phasor domain
- Express currents & voltages in phasor domain.
- Use same approach as DC network (Nodal analysis, Mesh Analysis or superposition) to solve for desired component



A sample circuit
for AC analysis

$\Rightarrow$

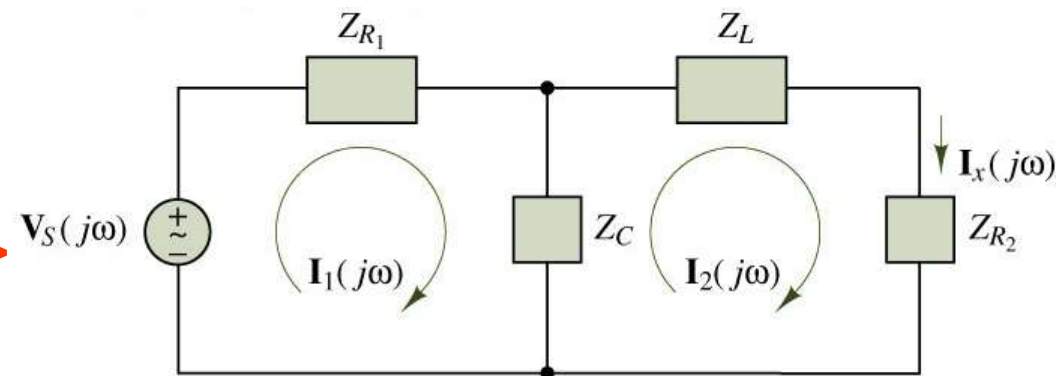

The same circuit
in phasor form