

Topic 1

AC Networks Analysis


Dr. Ala A. Hussein

part 3

⇒ **Example:**

For the circuit shown in the Figure, determine:

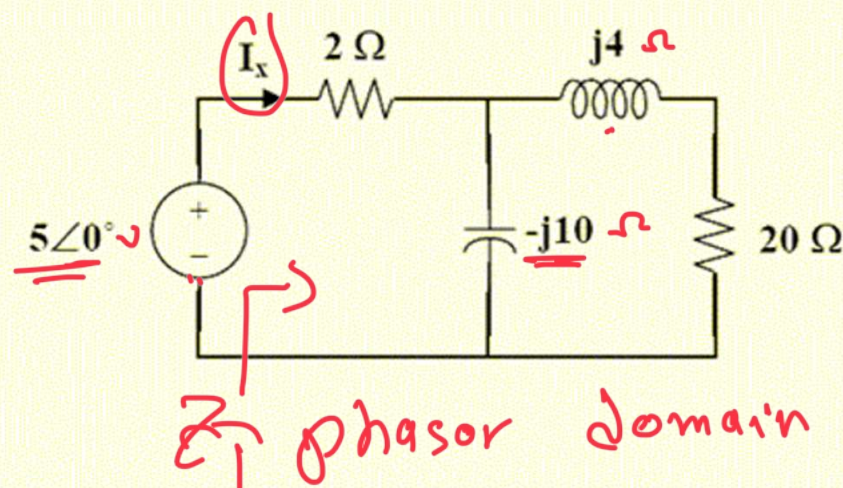1. The total impedance
2. The current I_x



Solution:


$$I_X = \frac{V}{Z_T}$$

$$Z_T = 2 + \frac{(-j10)(20 + j4)}{(-j10) + (20 + j4)} = 4.588 - j8.626 \, \Omega$$

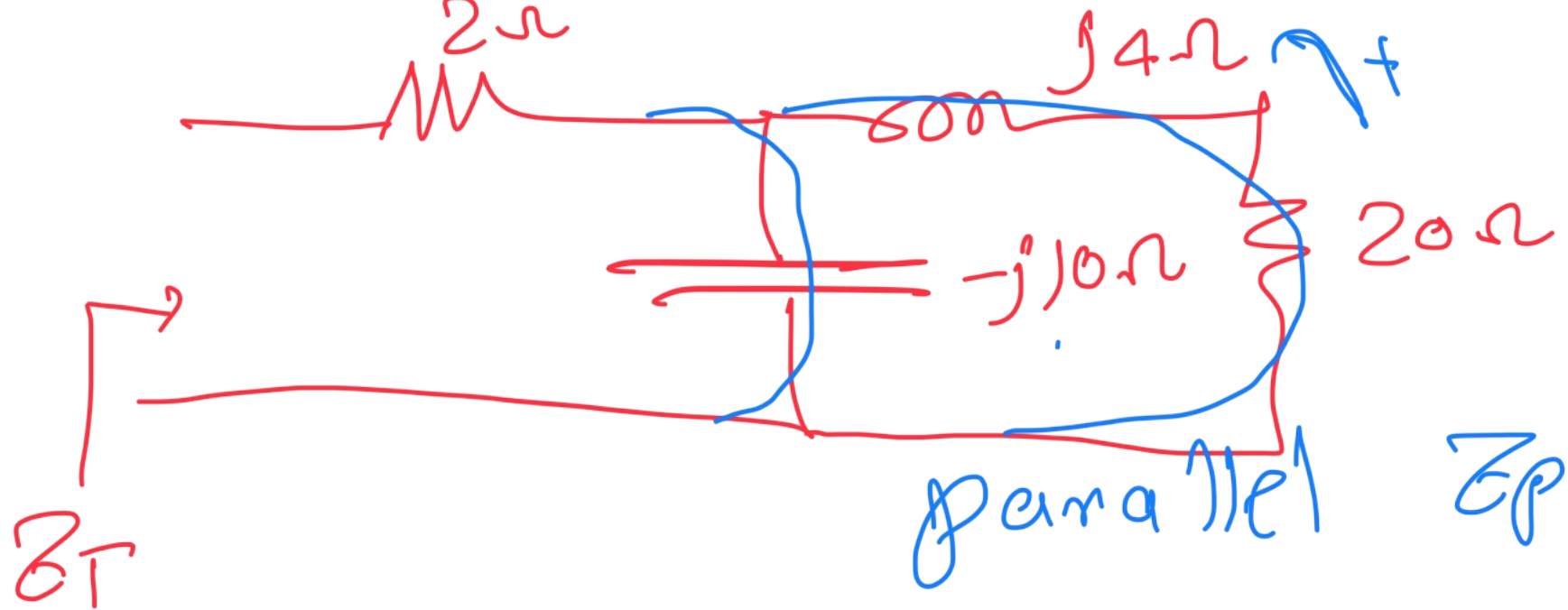6.587


$$I_x = \frac{5}{2 + \frac{-j10(20 + j4)}{-j10 + 20 + j4}} = \frac{5}{2 + 4.588 - j8.626} = \frac{5}{10.854 \angle -52.63^\circ} = 0.4607 \angle 52.63^\circ$$

$$i_s(t) = 0.4607 \cos(2000t + 52.63^\circ) \, \text{A}$$




$$Z_p = \frac{1}{\frac{1}{-j10} + \frac{1}{20 + j4}} = \frac{500}{100} - j \frac{940}{100} \Omega$$

$500/100 = 4.58 \Omega - j 8.62 \Omega$

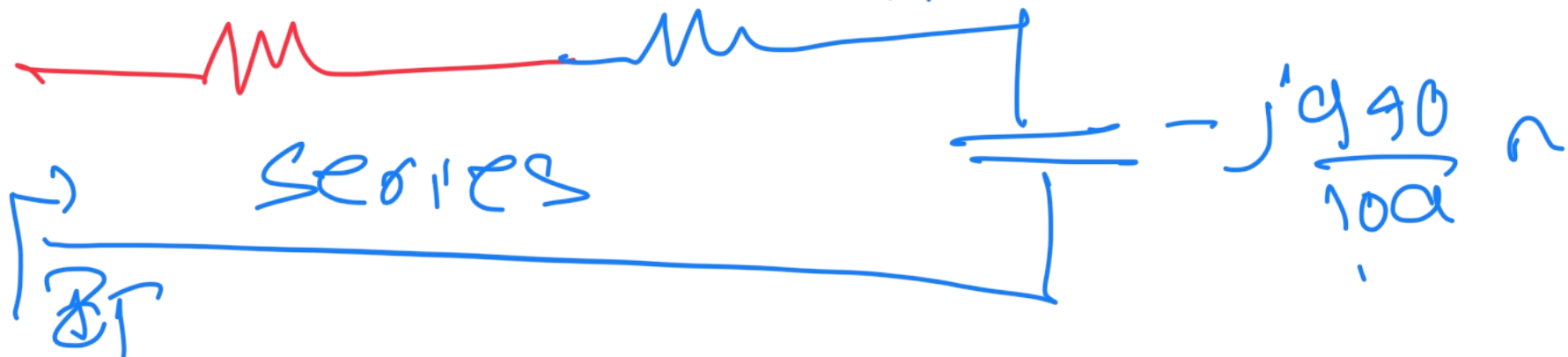

$$Z_T = Z + \frac{500}{100} - j \frac{940}{100}$$

$$Z_T = 6.587 - j8.624 \Omega$$

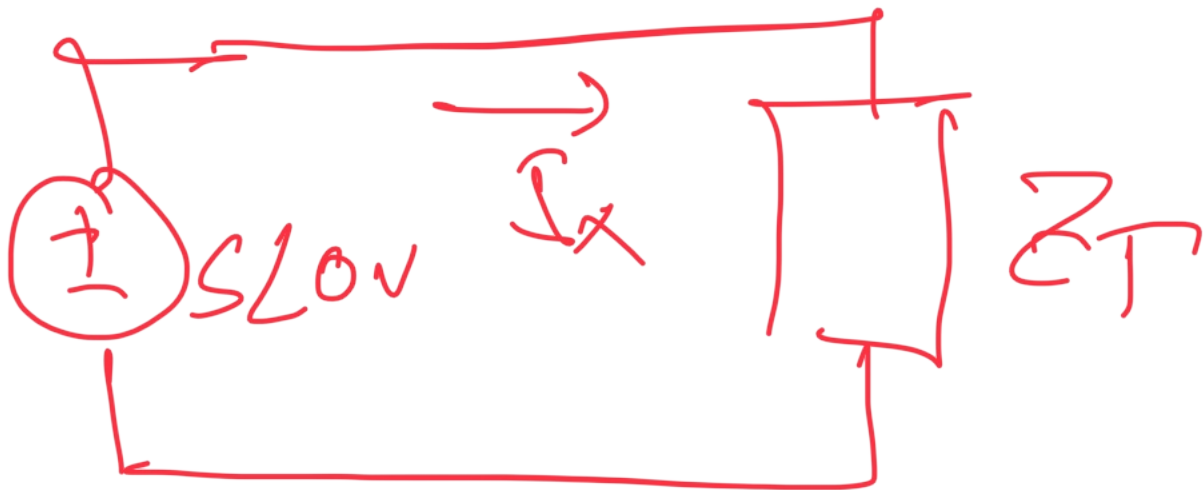

$$I_x = \frac{V}{Z_T} = \frac{520}{6.587 - j8.624}$$


$$I_X = \underline{0,4607} / \underline{52,63}^\circ \quad \text{amplitudă și fază}$$

$$\omega = \underline{\underline{2000}} \text{ rad/s}$$

$$i_X(t) = 0,4607 \cos(2000t + 52,63^\circ) \text{ A}$$


Analysis of AC Circuits

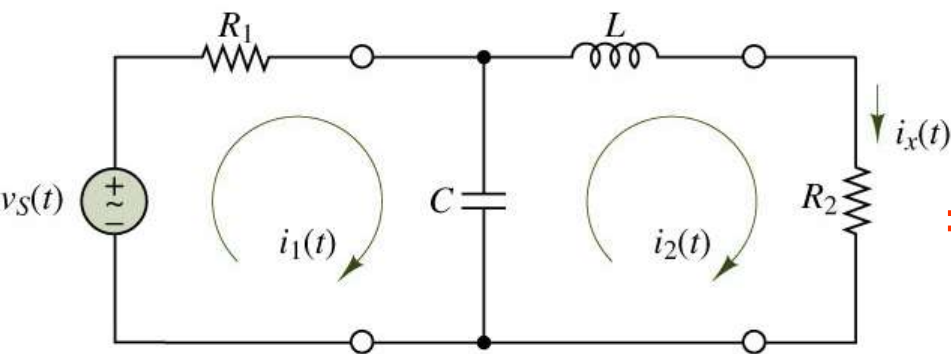- Substitute for every network with its impedance equivalent in phasor domain
- Express currents & voltages in phasor domain.
- Use same approach as DC network (Nodal analysis, Mesh Analysis or superposition) to solve for desired component



A sample circuit
for AC analysis

$\Rightarrow$

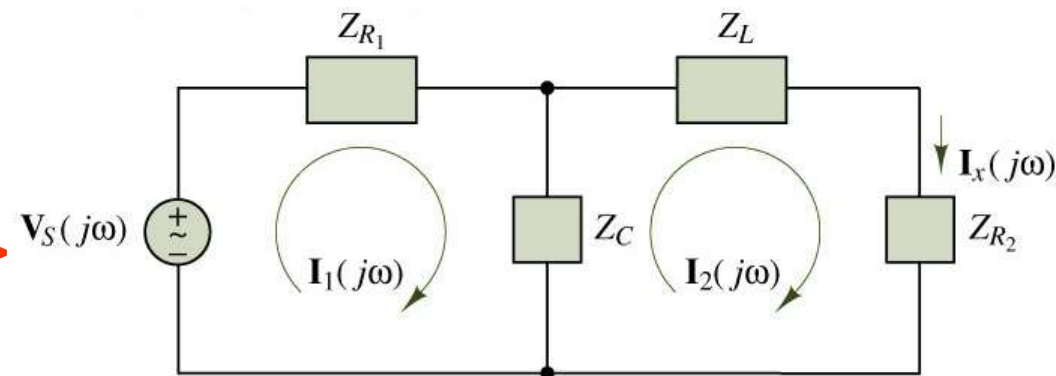


The same circuit
in phasor form

phasor $\Rightarrow$ ω $\Rightarrow$ $j\omega$

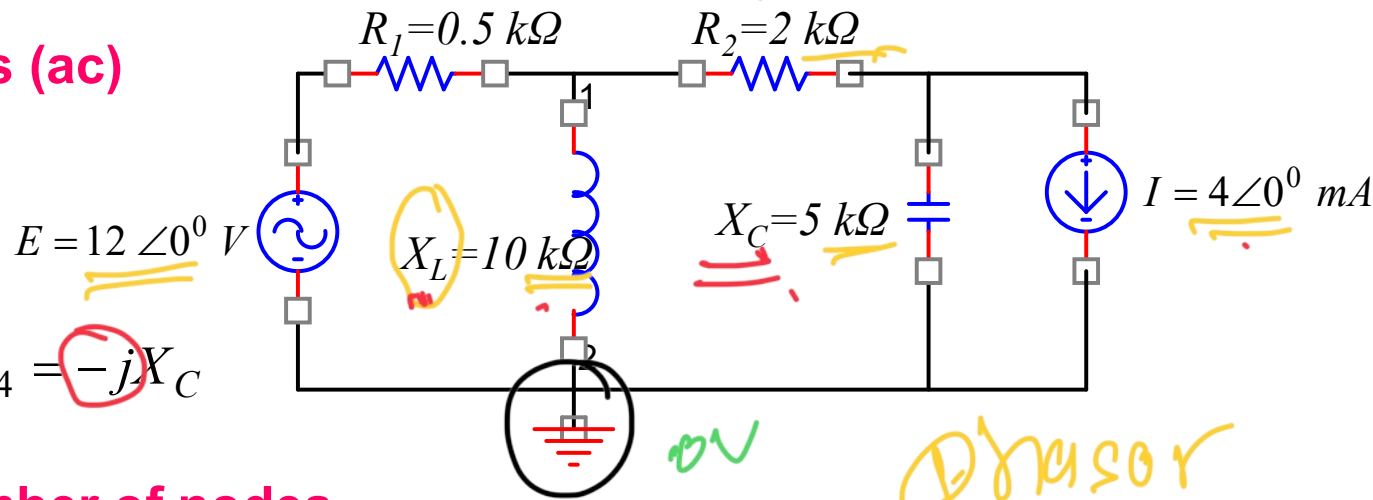Example: Nodal analysis (ac)

For simplification let

$$Z_1 = R_1, Z_2 = jX_L, Z_3 = R_2, Z_4 = -jX_C$$



Step 1: Determine the number of nodes

3 nodes in this circuit. Bottom node is the reference node


Step 2: Apply KCL at all nodes except reference node


Node V1:

$$0 = I_1 + I_2 + I_3$$

$$\frac{V_1 - E}{Z_1} + \frac{V_1}{Z_2} + \frac{V_1 - V_2}{Z_3} = 0$$
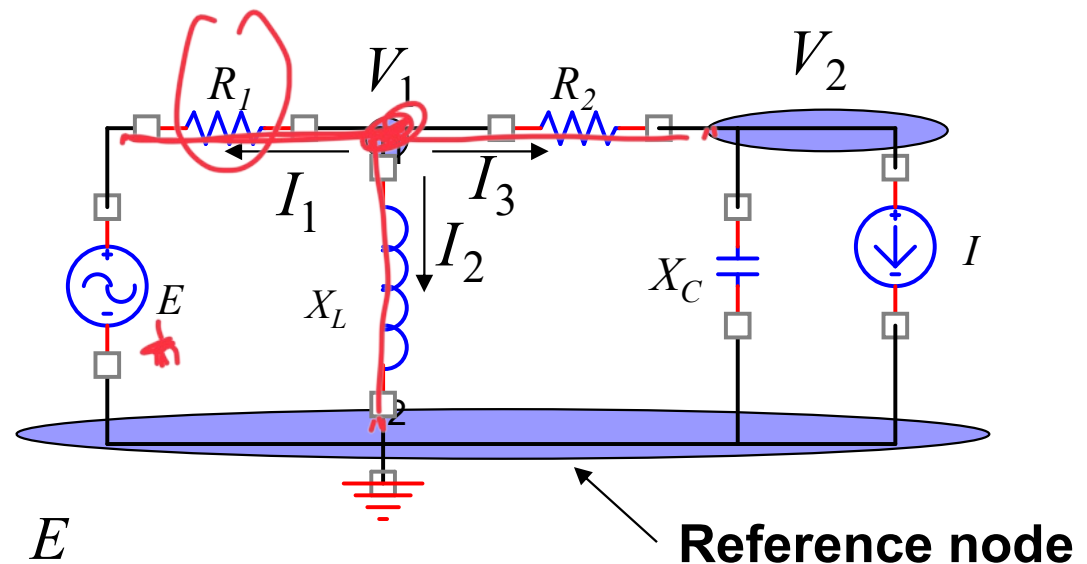
$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right] - V_2 \left[\frac{1}{Z_3} \right] = \frac{E}{Z_1} \quad (1)$$



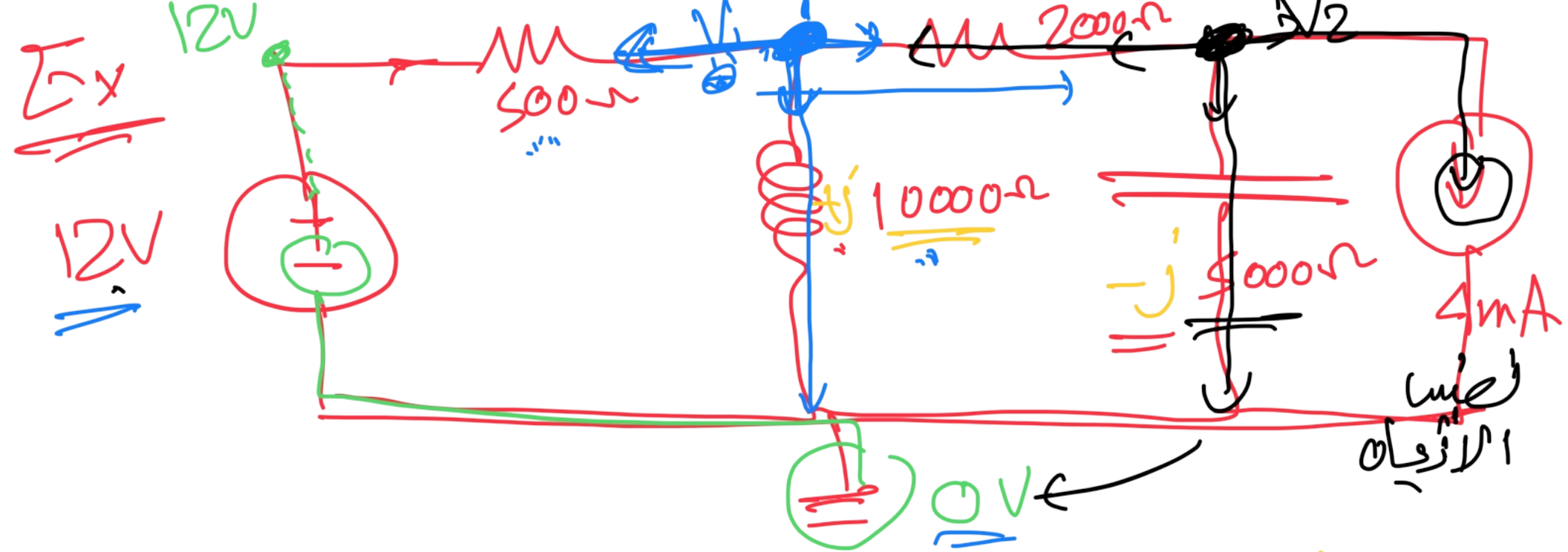

$$\underline{Z_L} = j\omega L = +jX_L \rightarrow X_L = \omega L$$

$$\underline{Z_C} = \frac{1}{j\omega C} = \frac{-j}{\omega C} = -jX_C \Rightarrow X_C = \frac{1}{\omega C}$$

Nodal Analysis

KCL

$$I = \frac{V}{Z}$$

↳

النسبة التي خالص من

node V_1

$$\frac{V_1 - 12}{500} + \frac{V_1 - 0}{10000} + \frac{V_1 - V_2}{2000} = 0$$

$$V_1 \left[\frac{1}{500} + \frac{1}{10000} + \frac{1}{2000} \right] + V_2 \left[\frac{-1}{2000} \right] = \frac{12}{500}$$

$$\boxed{V_1 \left[\frac{1}{400} \right] + V_2 \left[\frac{-1}{2000} \right] = \frac{12}{500}} \quad \text{①}$$

A B E

node V_2

$$\frac{V_2 - V_1}{2000} + \frac{V_2 - 0}{-j5000} + 4 \times 10^{-3} = 0$$


$$V_1 \left[\frac{-1}{2000} \right] + V_2 \left[\frac{1}{2000} + \frac{1}{-j5000} \right] = -4 \times 10^{-3}$$

$$V_1 \left[\frac{-1}{2000} \right] + V_2 \left[\frac{1}{2000} + j \frac{1}{5000} \right] = -4 \times 10^{-3}$$

1 2

$$V_1 = \frac{ED - BF}{AD - BC} = 9.95 \angle 11.835^\circ \text{ V}$$
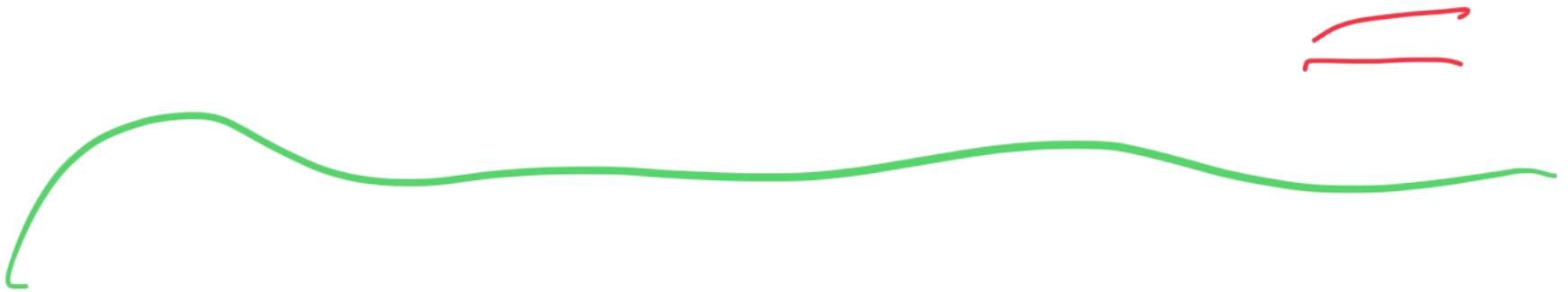
$$V_2 = \frac{AF - EC}{AD - BC} = 1.83 \angle -12.496^\circ \text{ V}$$




Applying KCL at node 2 (note the direction of currents in node 2)

$$0 = I_3 + I_4 + I$$

$$\frac{V_2 - V_1}{Z_3} + \frac{V_2}{Z_4} + I = 0$$

$$V_2 \left[\frac{1}{Z_3} + \frac{1}{Z_4} \right] - V_1 \left[\frac{1}{Z_3} \right] = -I \quad (2)$$

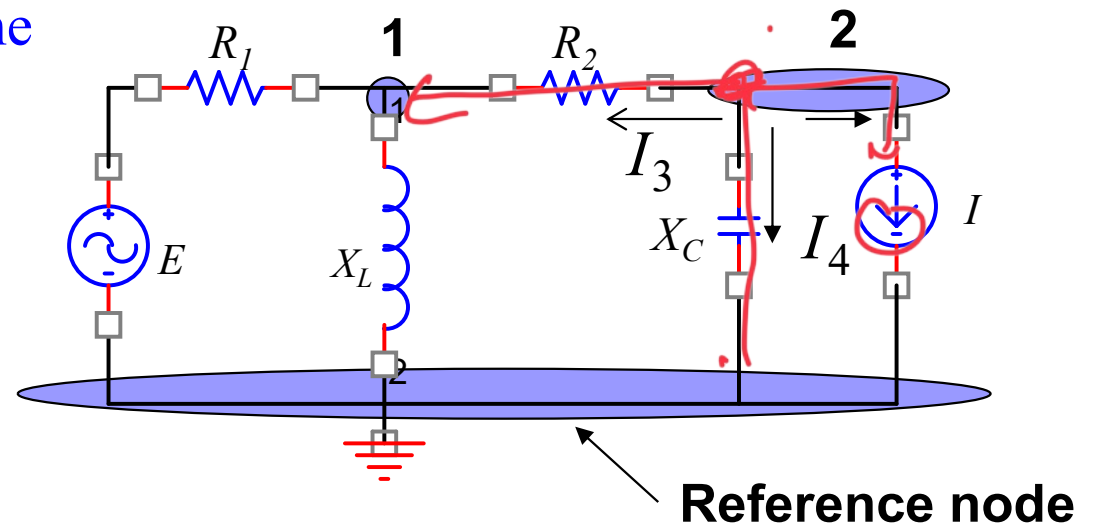Solve equation (1) and (2) and find V_1 and V_2 , and then find the node currents



Example: Loop analysis (ac) *→ mesh*

Using loop analysis find the current I_1

$$Z_1 = jX_L, \quad Z_2 = R = 4\Omega, \quad Z_3 = -jX_C$$

Apply KVL around each closed loop



$$\text{Loop 1: } +E_1 - I_1 Z_1 - Z_2(I_1 - I_2) = 0$$


$$\text{Loop 2: } -Z_2(I_2 - I_1) - I_2 Z_3 - E_2 = 0$$

Solve above equations to find I_1 and I_2

$$I_1 = 3.61 \angle -236.30^\circ$$

$$3.61 \angle 123.7^\circ$$

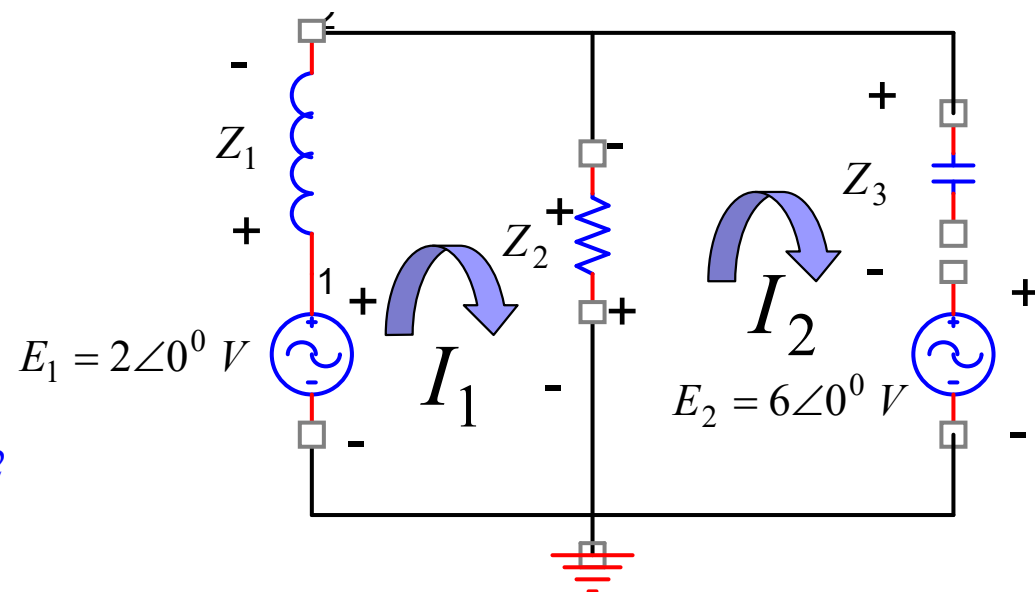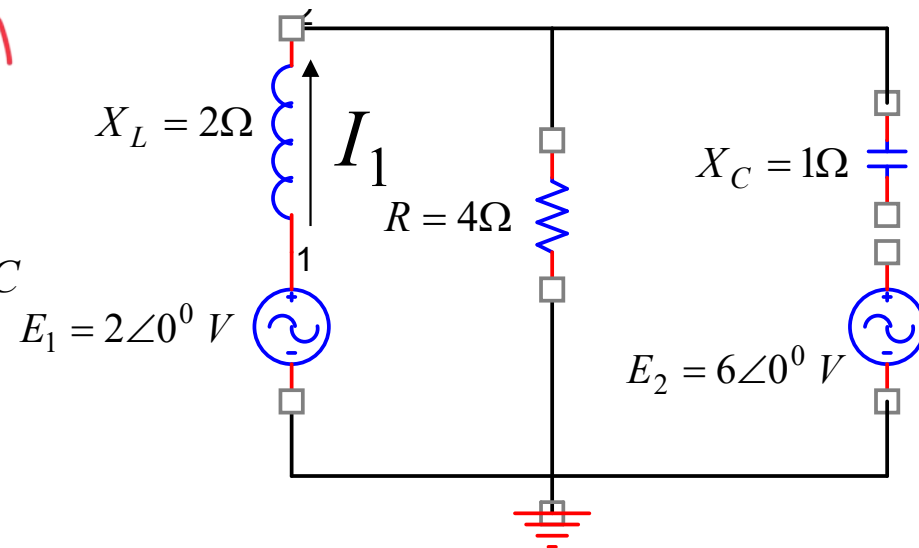

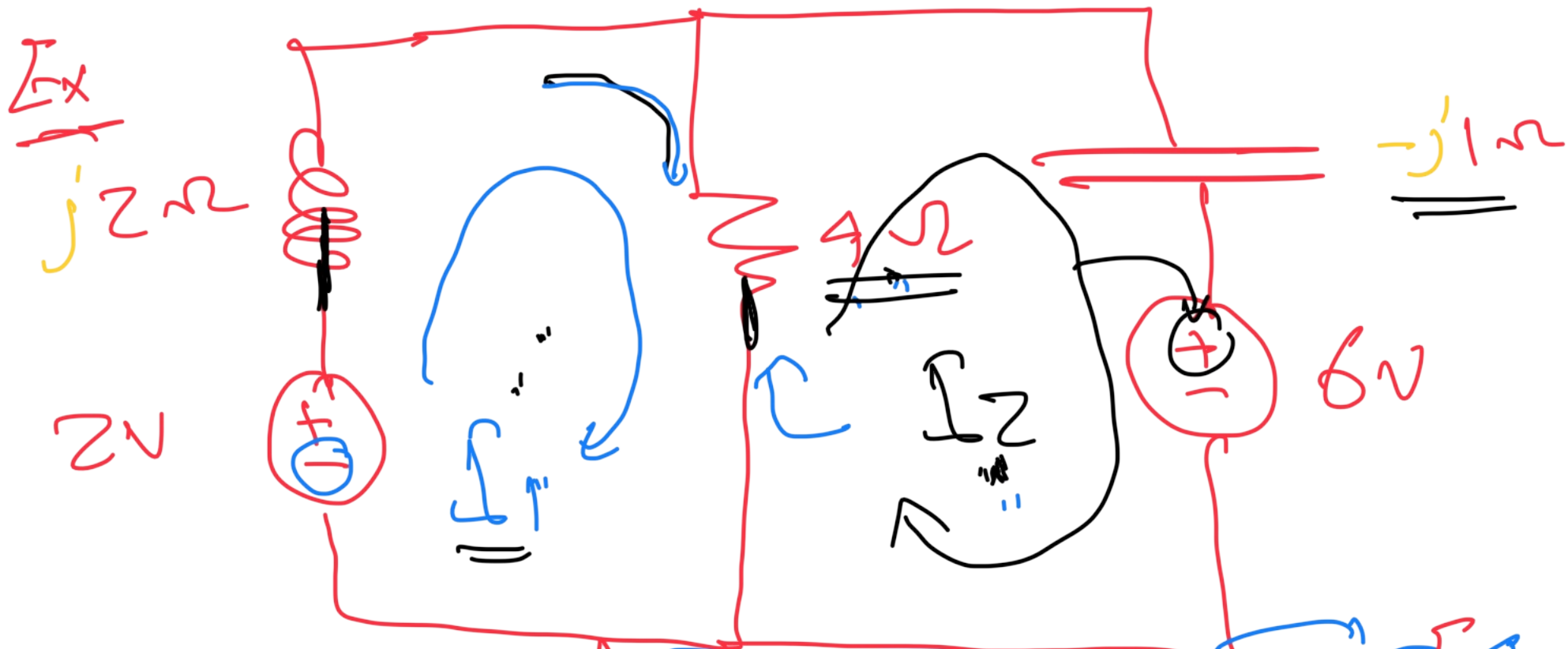

mesh C_1 :

$$(4 + j2) \hat{I}_1 + \hat{I}_2 (-4) = 2 \quad (1)$$

mesh C_2 :

$$\hat{I}_1 (-4) + (4 - j) \hat{I}_2 = -6 \quad (2)$$

$$\vec{L}_1 = \frac{ED - BF}{AD - BC} = \underline{\underline{3.6056 \angle 123.69^\circ \text{ A}}}$$

$$\vec{L}_2 = \frac{AF - EC}{AD - BC} = 4.4721 \angle 153.43^\circ \text{ A}$$


$-180 \leq \theta \leq 180$ complex عدد

Example (ac): Find the current I through the $4\text{-}\Omega$ reactance (X_{L2}) for the network below using superposition theorem.

$$Z_1 = jX_{L1} = j4\Omega$$

$$Z_2 + jX_{L2} = j4\Omega$$

$$Z_3 = -jX_C = -j3\Omega$$

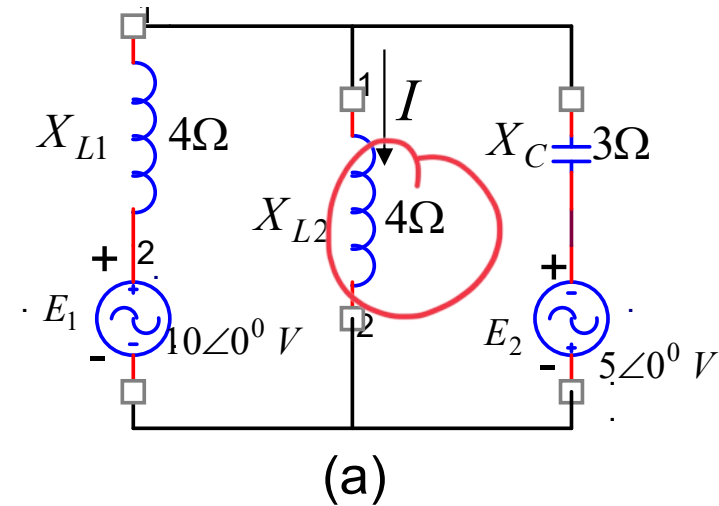


Considering the effect of voltage source E_1 (fig. b)


$$Z_2 \parallel Z_3 = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(j4)(-j3)}{j4 - j3} = \frac{12}{j} = \frac{12}{j} \times \frac{j}{j} = -j12 \Omega$$

$$I_{s1} = \frac{E_1}{Z_2 \parallel Z_3 + Z_1} = \frac{10\angle 0^\circ}{-j12 + j4} = \frac{10\angle 0^\circ}{-j8} = \frac{10\angle 0^\circ}{8\angle -90^\circ}$$

$$= 1.25\angle 0 - (-90^\circ) = 1.25\angle 90^\circ = j1.25$$
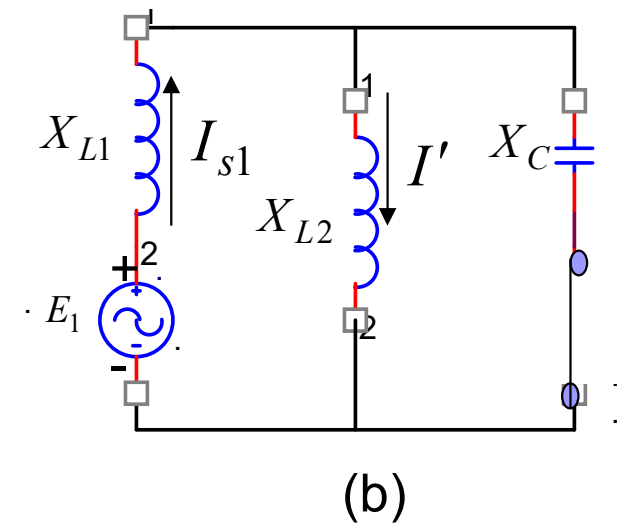
$$I' = I_{s1} \times \frac{Z_3}{Z_2 + Z_3} = \frac{(-j3)(j1.25)}{j4 - j3} = \frac{3.75}{j1} = \frac{3.75\angle 0^\circ}{1\angle 90^\circ} = 3.75\angle -90^\circ \text{ A}$$




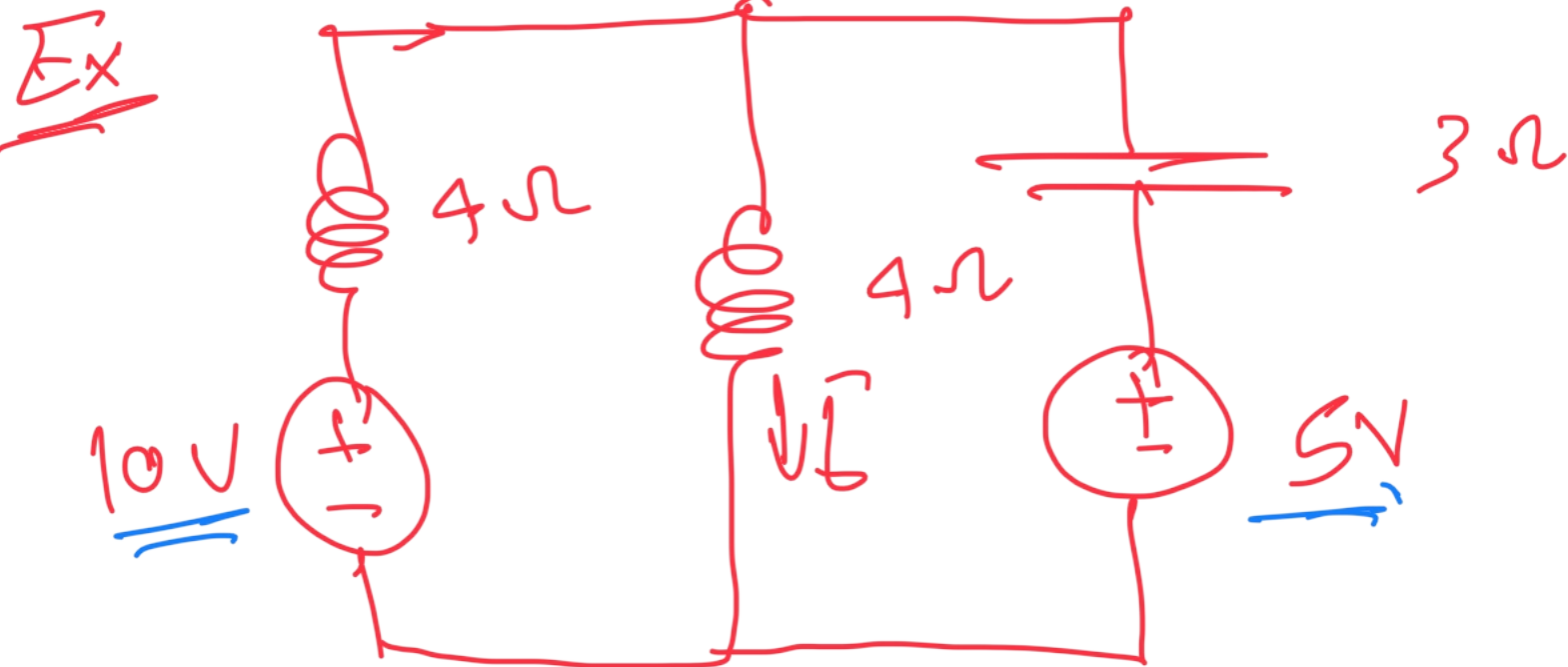

Super position :


8Mw

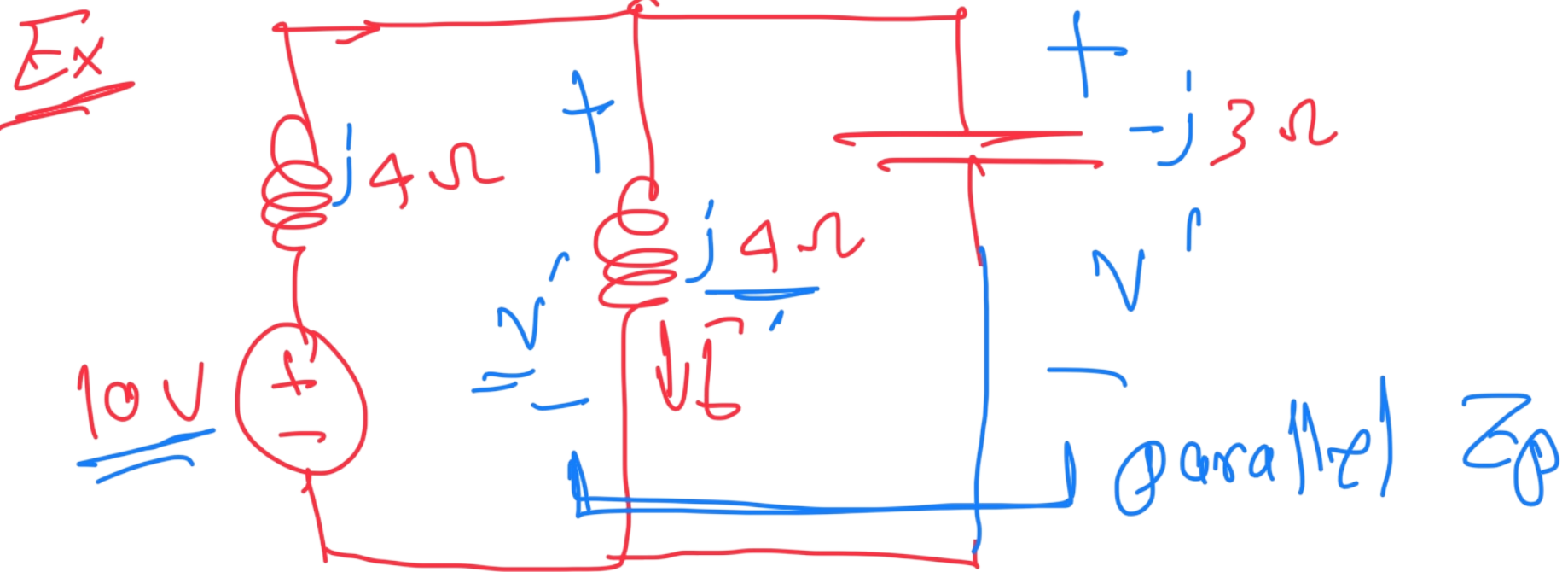- ↳ Turn off voltage $\Rightarrow 0V \Rightarrow$ short circuit
- ↳ Turn off current $\Rightarrow 0A \Rightarrow$ open circuit




Turn off 5V and keep 10V
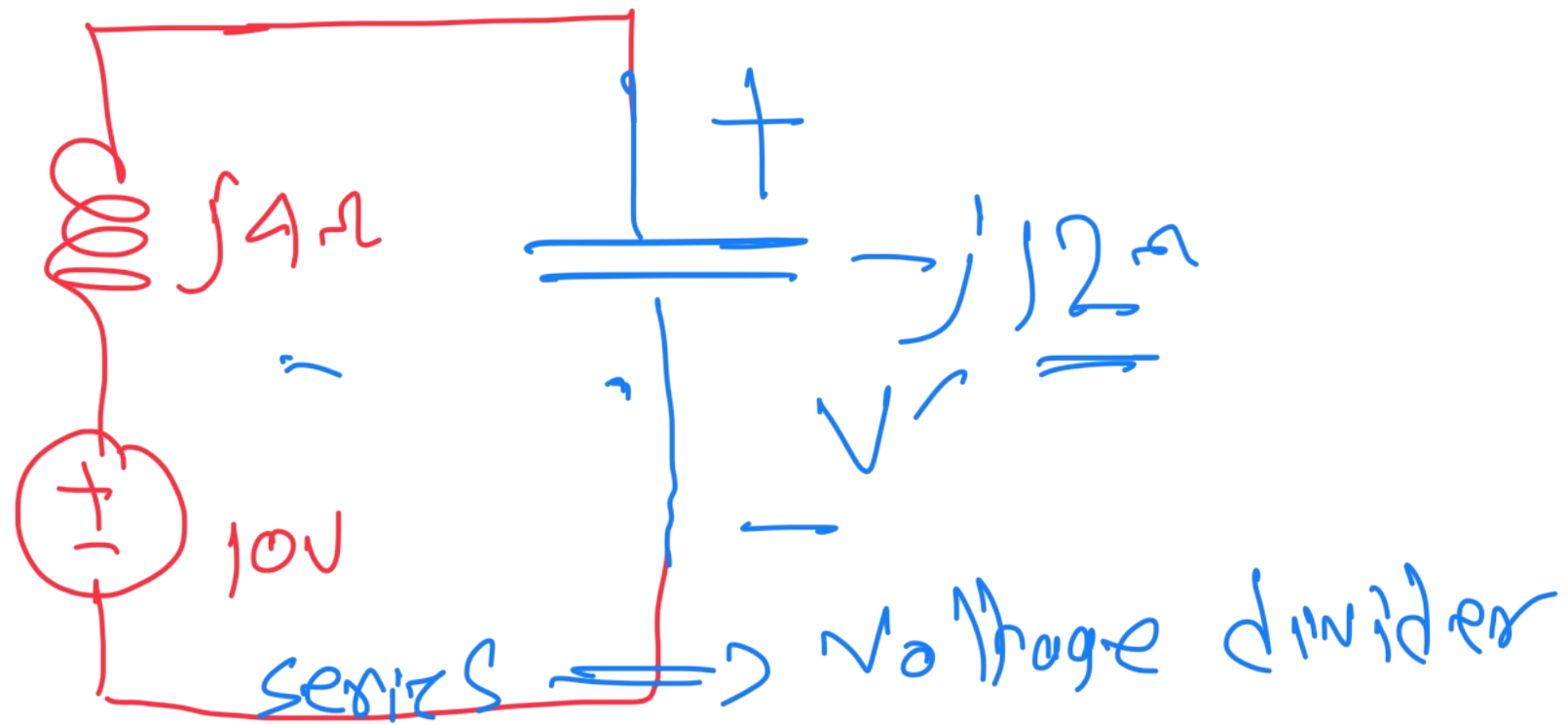
$$Z_p = \frac{1}{\frac{1}{j4} + \frac{1}{-j3}} = -j12\Omega$$




$$\Rightarrow V' = \frac{-j12}{-j12 + j4} \times 10 = 15V$$
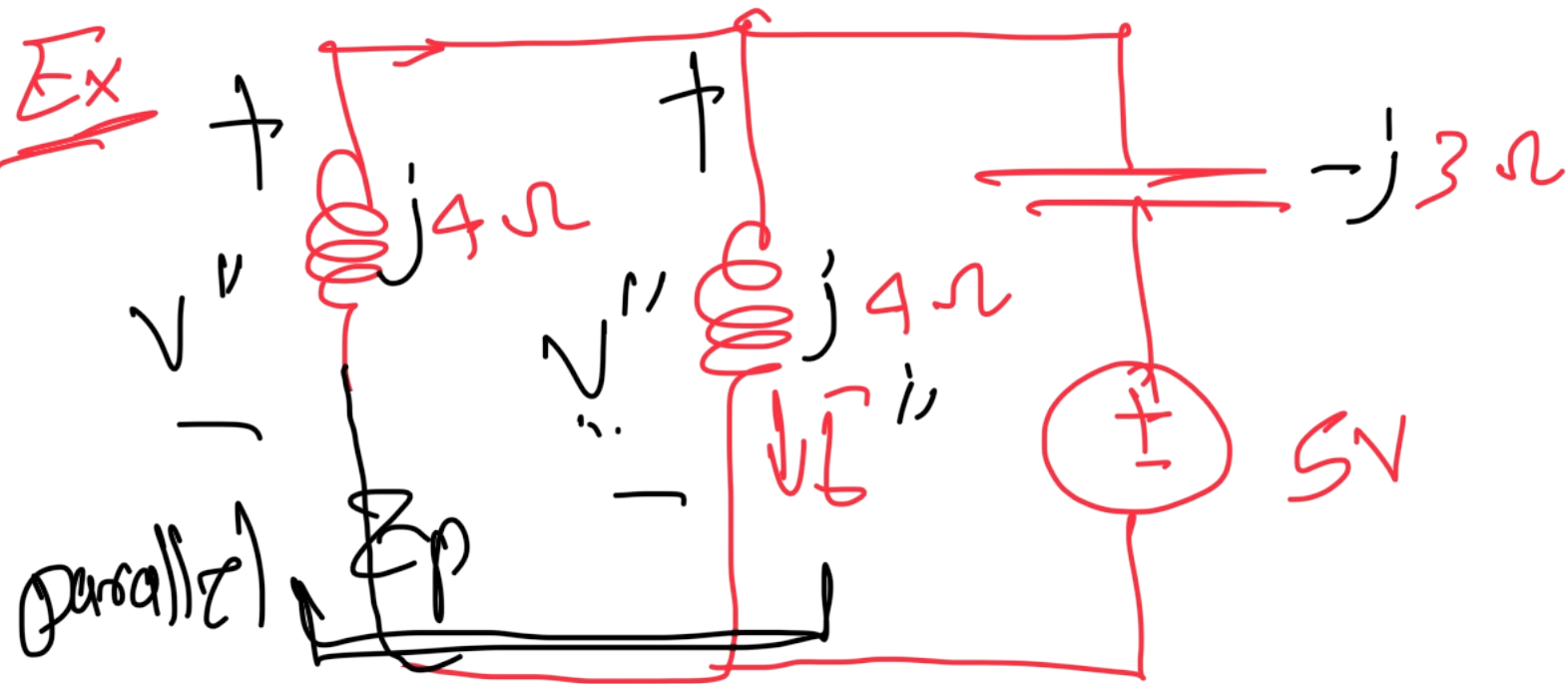
$$I' = \frac{V'}{Z} = \frac{15}{j4} = \boxed{-j3.75 = 3.75 \angle -90^\circ \text{ A}}$$



Turn off 10V and keep 5V
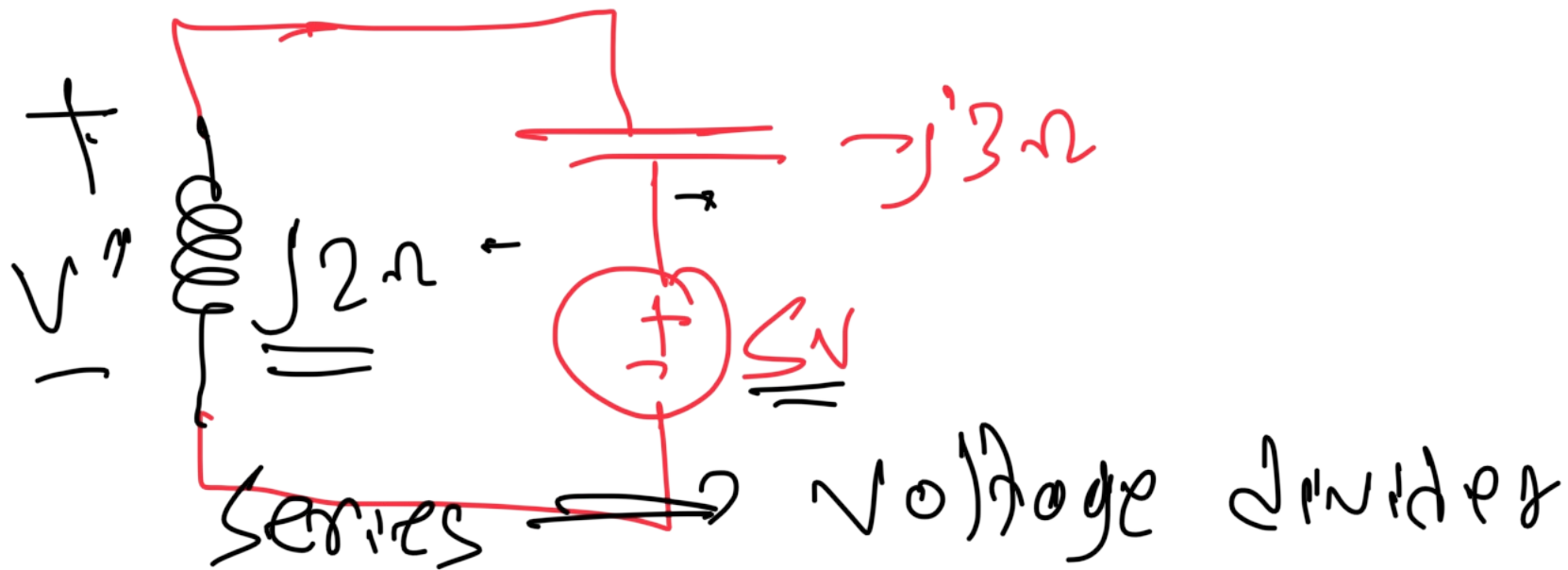
$$Z_p = \frac{1}{\frac{1}{j4} + \frac{1}{j4}} = j2\Omega$$



$$V'' = \frac{j2}{j2 - j3} \times 5 = -10V$$

$$I'' = \frac{V''}{Z} = \frac{-10}{j4} = 2.5A = 2.5 \angle 90^\circ A$$

$$\underline{I}_{\text{Total}} = \underline{I}' + \underline{I}''$$

$$\underline{I} = -j3.75 + j2.5$$


$$\underline{I} = -j1.25 = 1.25 \angle -90^\circ$$

Considering the effect of voltage source E_2 (fig. c)

$$Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(j4)(j4)}{j4 + j4} = \frac{j^2 16}{j8} = j2 \Omega$$

$$I_{s2} = \frac{E_2}{Z_1 \parallel Z_2 + Z_3} = \frac{5 \angle 0^\circ}{j2 - j3} = \frac{5 \angle 0^\circ}{1 \angle -90^\circ} = 5 \angle 90^\circ$$
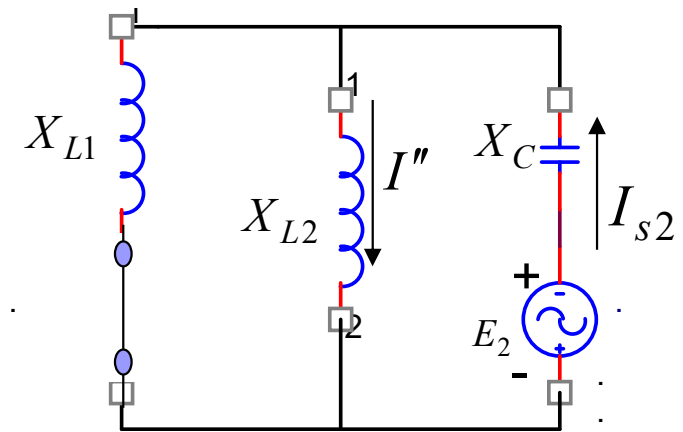
$$I'' = I_{s2} \times \frac{Z_1}{Z_1 + Z_2} = 2.5 \angle 90^\circ$$



(c)

The resultant current through the 4-Ω reactance.

$$I = I' + I'' = 3.75 \angle -90^\circ + 2.5 \angle 90^\circ = -j3.75 + j2.5 = -j1.25 = 1.25 \angle -90^\circ$$

8.12 Find the impedance, Z , shown in Fig. P8.12 at a frequency of 60 Hz.


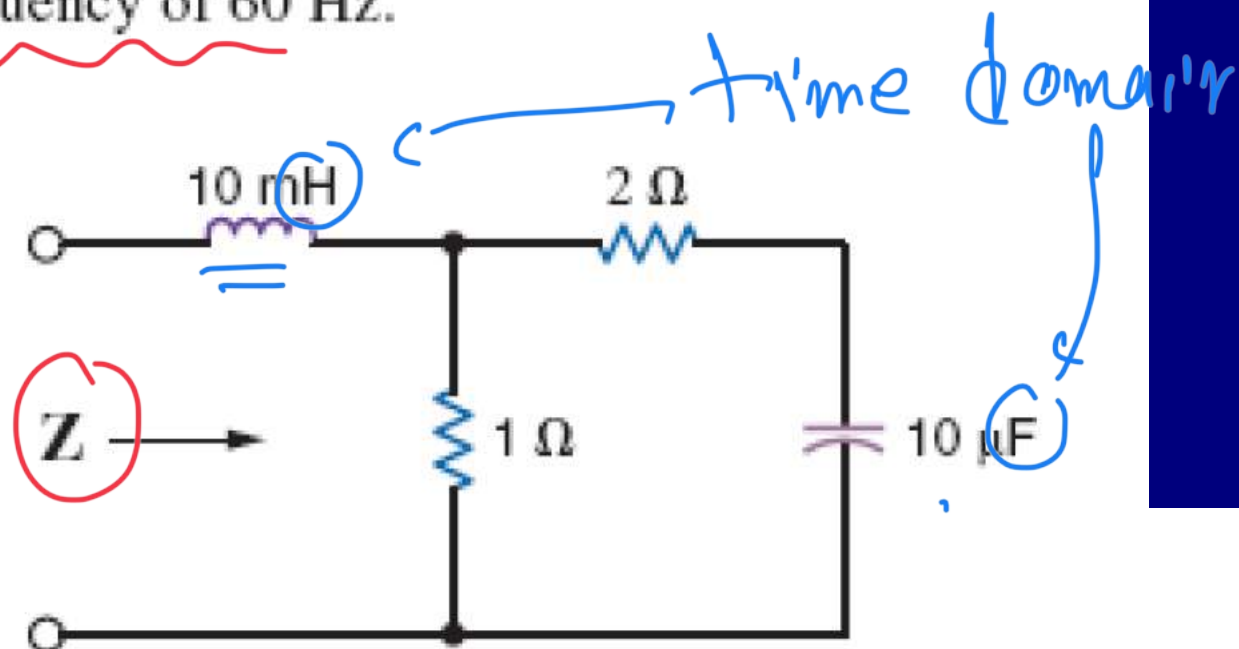


Figure P8.12

$$\omega = 2\pi f = 2\pi \times 60 \approx 120\pi \approx 377 \text{ rad/s}$$


$$Z_L = j\omega L = j \times 377 \times 10 \times 10^{-3} = j3.77 \Omega$$
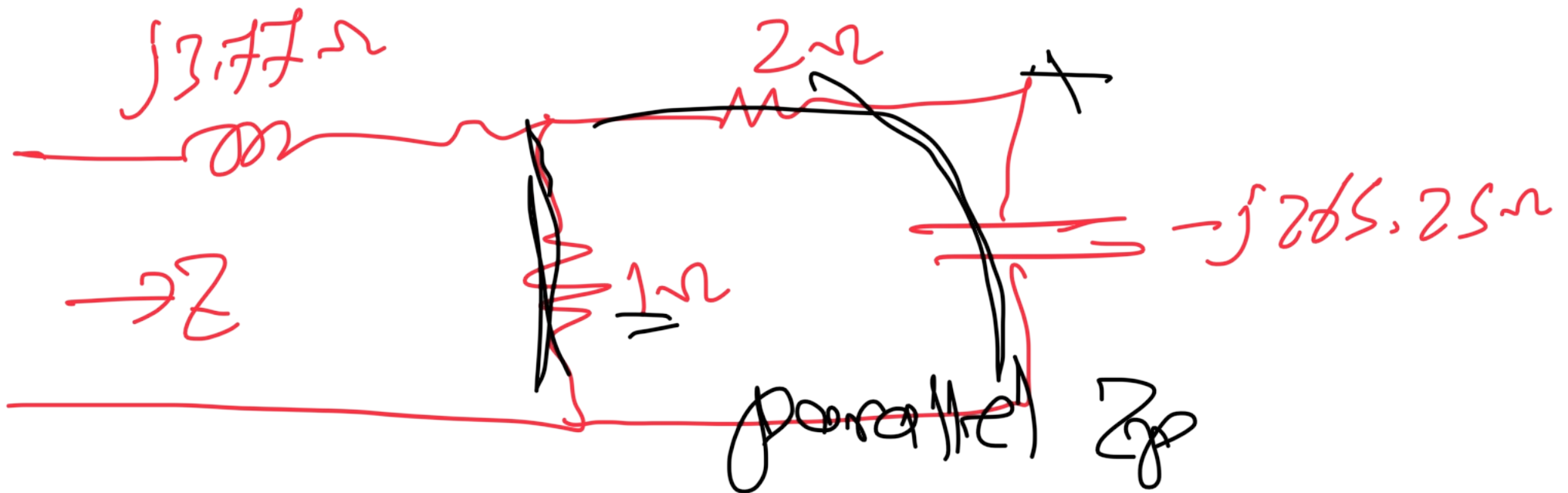
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 377 \times 10 \times 10^{-6}} = -j265.25 \Omega$$



$$Z_p = \frac{1}{\frac{1}{1} + \frac{1}{2 - j26525}} \quad \checkmark \Rightarrow 1 - j3.769 \times 10^{-3} \Omega$$


$$j3.77 \Omega$$

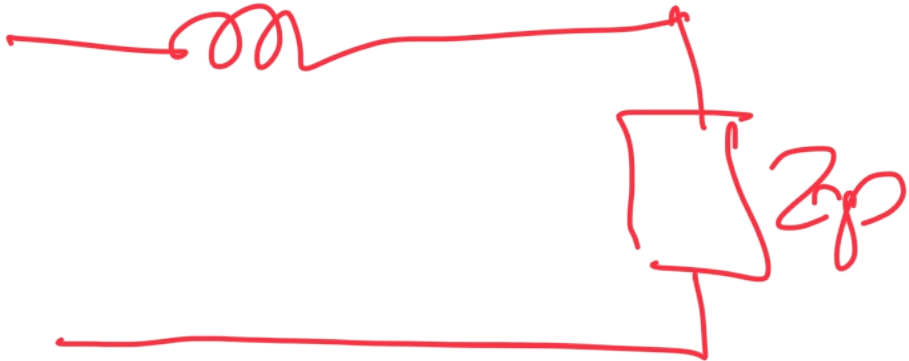

$$Z_T = j3.77 + Z_p =$$

$$Z_T = 1 + j3.7662 \Omega$$

SOLUTION:

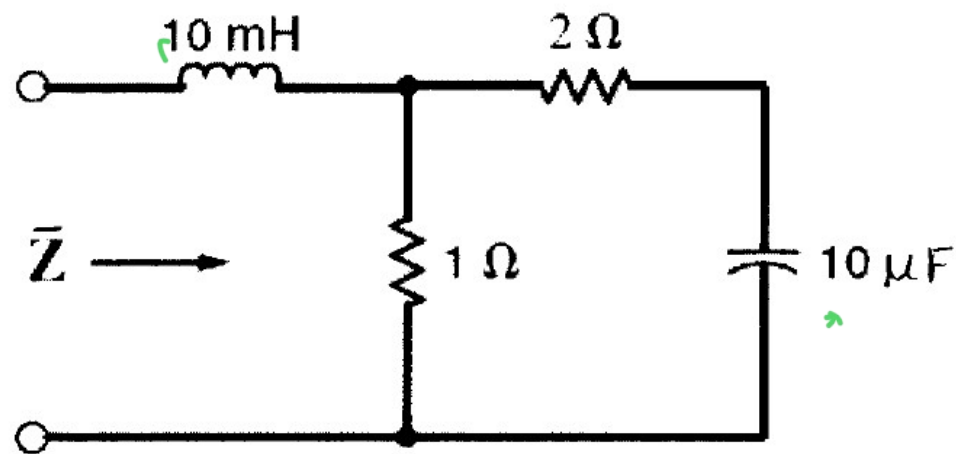


$$\bar{Z}_L = j(377)(10\text{m}) = \underline{j 3.77\ \Omega}$$

$$\bar{Z}_C = \frac{1}{j(377)(10\mu)} = -j 265.25\ \Omega$$



// $\rightarrow$ parallel

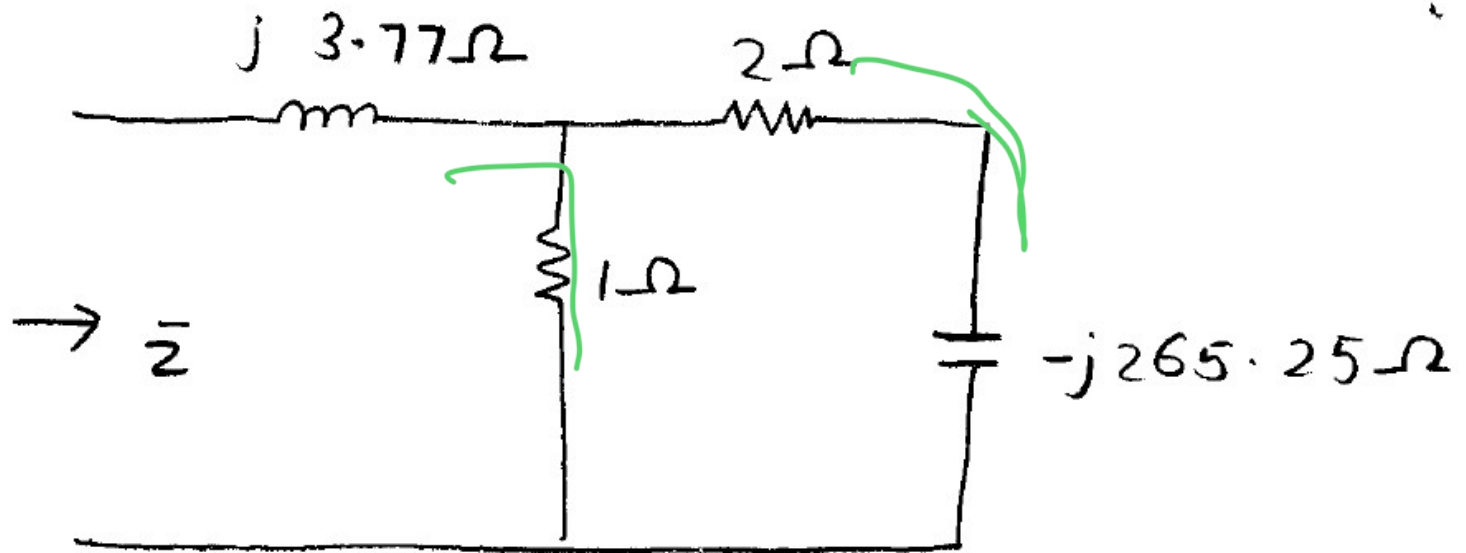

$$\bar{Z} = \left[1 \parallel [2 - j 265.25] \right] + j 3.77$$

8.36 Find $v_x(t)$ in the circuit in Fig. P8.36.

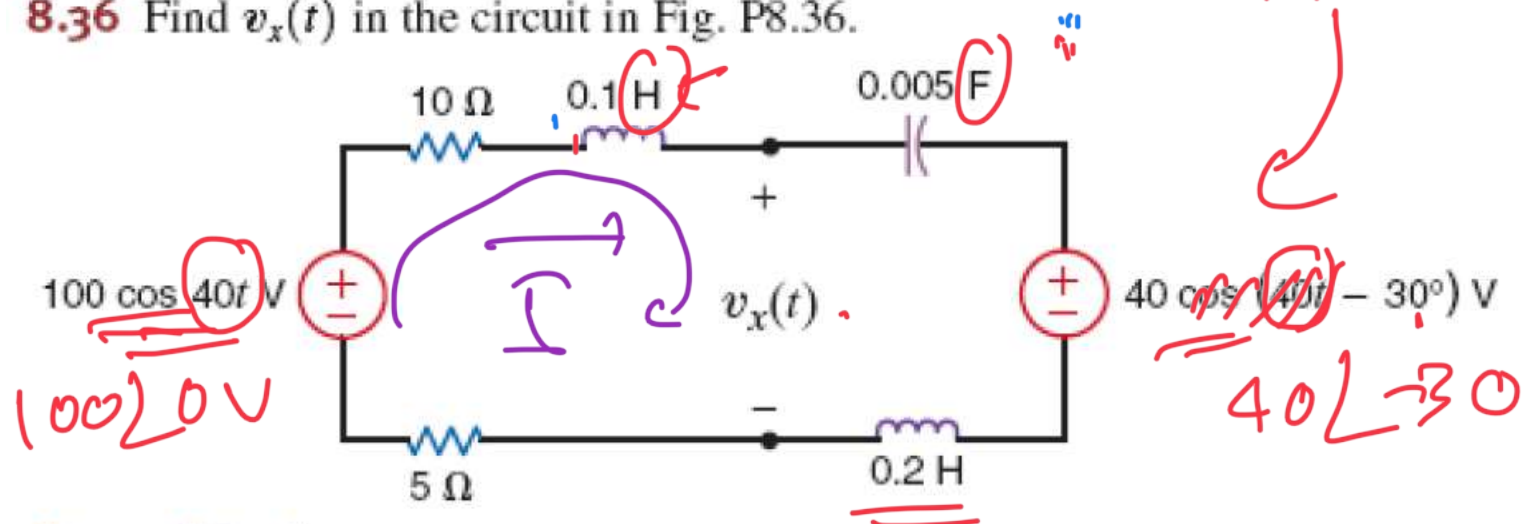


Figure P8.36

series

SOLUTION:

$$\bar{Z}_{L_1} = j(40)(0.1) = j4 \Omega$$


$$\bar{Z}_{L_2} = j(40)(0.2) = j8 \Omega$$

$$\omega = 40 \text{ rad/s} \leftarrow$$

$$Z_{L1} = j\omega L_1 = j \times 40 \times 0.1 = j4 \Omega$$

$$Z_{L2} = j\omega L_2 = j \times 40 \times 0.2 = j8 \Omega$$
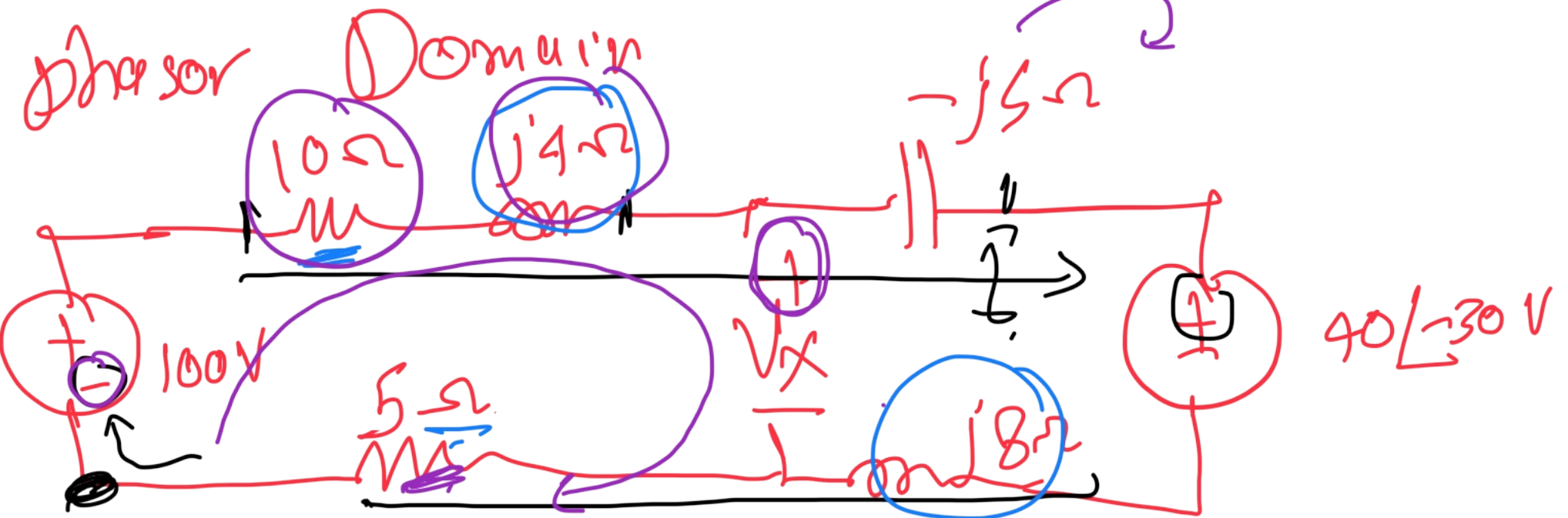
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 40 \times 0.005} = -j5 \Omega$$



To find current $\vec{I}$ using KVL

$$\sum V = 0$$

$$\underbrace{-100}_{\text{KVL}} + 10\vec{I} + j4\vec{I} - j5\vec{I} + \underbrace{40\angle -30^\circ}_{\text{KVL}} + j8\vec{I} + 5\vec{I} = 0$$

$$\frac{(15 + j7)\vec{I}}{15 + j7} = \frac{100 - 40\angle -30^\circ}{15 + j7}$$

$$\vec{I} = \frac{100 - 40\angle -30^\circ}{15 + j7}$$

$$I = 4.13 \angle -8^\circ \text{ A}$$

To find V_x using Also KVL

$$\underline{\rightarrow 100 + 10I + j4I + \underline{V_x} + \underline{5I} = 0}$$

$$V_x = 100 + (-15 - j4)I$$



$$V_x = 100 + (-15 - j4)(4.13 \angle -8^\circ)$$

$$\boxed{V_x = 37.18 \angle -12^\circ \text{ V}}$$

$$V_x(t) = 37.18 \cos(40t - 12^\circ) \text{ V}$$


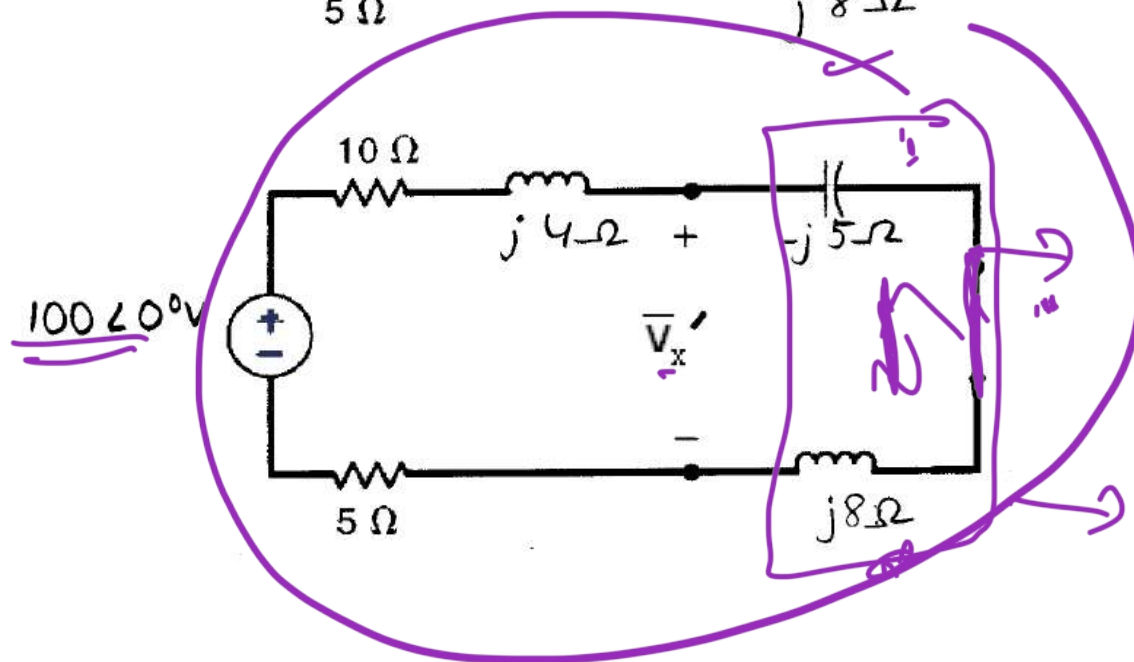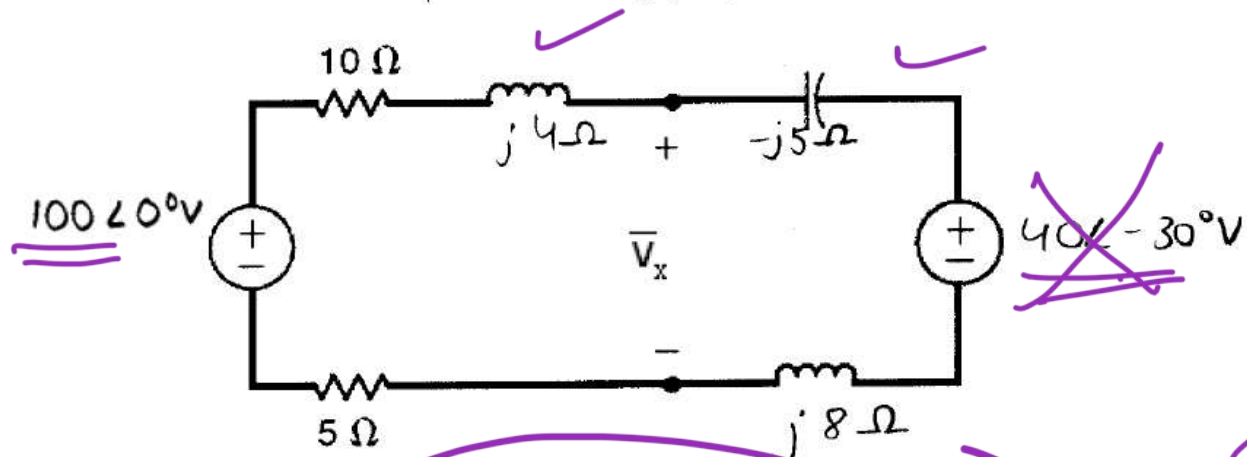
$$\bar{Z}_c = \frac{1}{j(40)(0.005)} = -j5\Omega$$




super
position

voltage
divider

$$\bar{V}_x' = \left(\frac{j8 - j5}{j8 - j5 + 10 + j4 + 5} \right) (100 \angle 0^\circ)$$
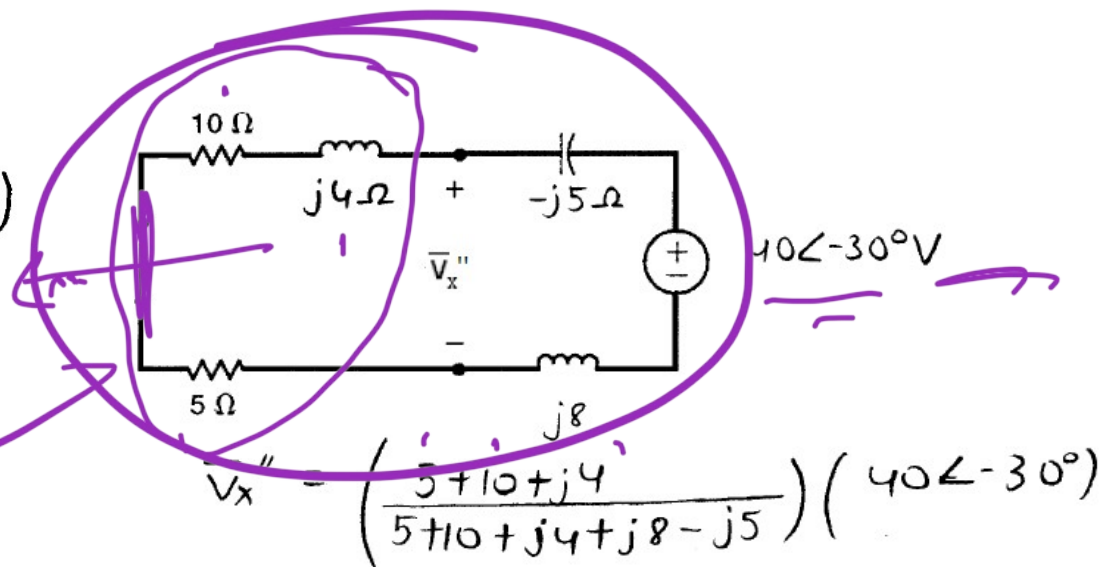
$$\bar{V}_x' = 18.12 \angle 64.98^\circ \text{ V}$$




$$\bar{V}_x'' = 37.51 \angle -40.1^\circ \text{ V}$$

$$\bar{V}_x = \bar{V}_x' + \bar{V}_x'' = 18.12 \angle 64.98^\circ + 37.51 \angle -40.1^\circ$$

$$\bar{V}_x = 37.17 \angle -12.02^\circ \text{ V}$$

$$v_x(t) = 37.17 \cos(40t - 12.02^\circ) \text{ V}$$

Voltage divider

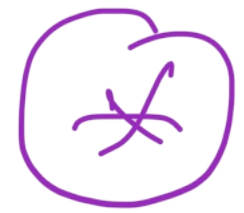

8.68 Find V_o in the network in Fig. P8.68 using nodal analysis.

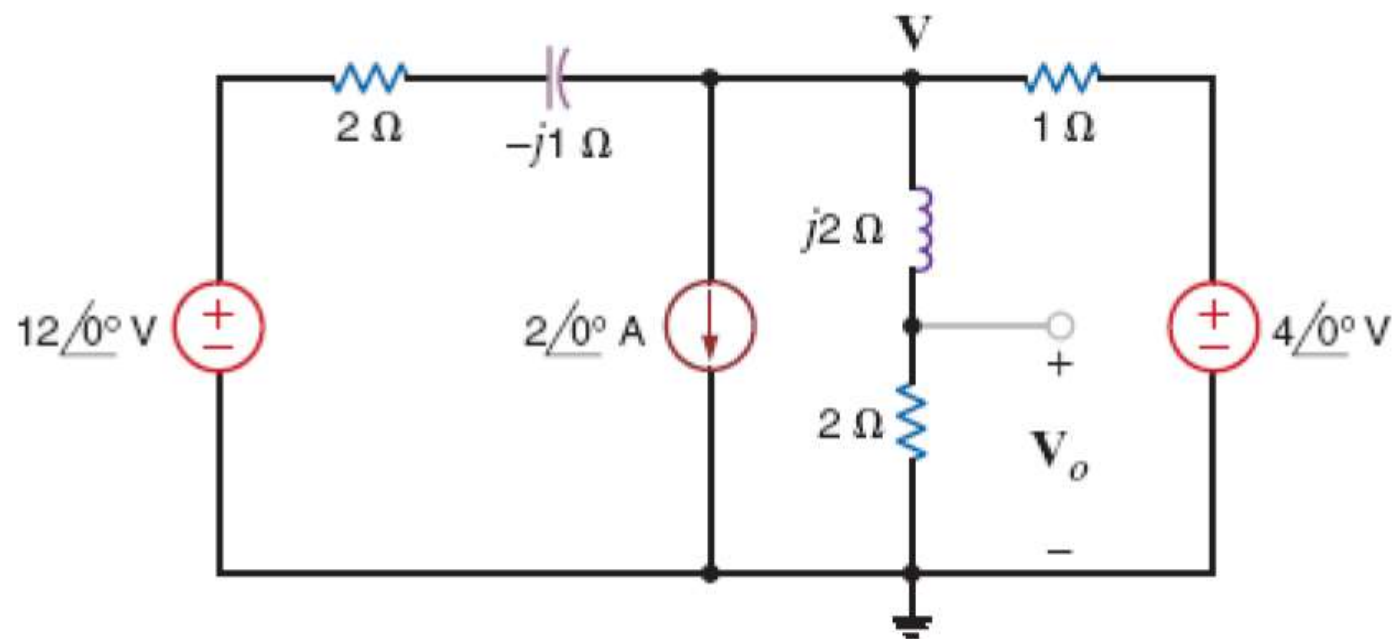


Figure P8.68