

~~Topic 1~~

AC Networks Analysis

Dr. Ala A. Hussein

part 4 last

نقطة تيار، في عنصر أو أكثر
 node →

8.68 Find V_o in the network in Fig. P8.68 using nodal analysis.

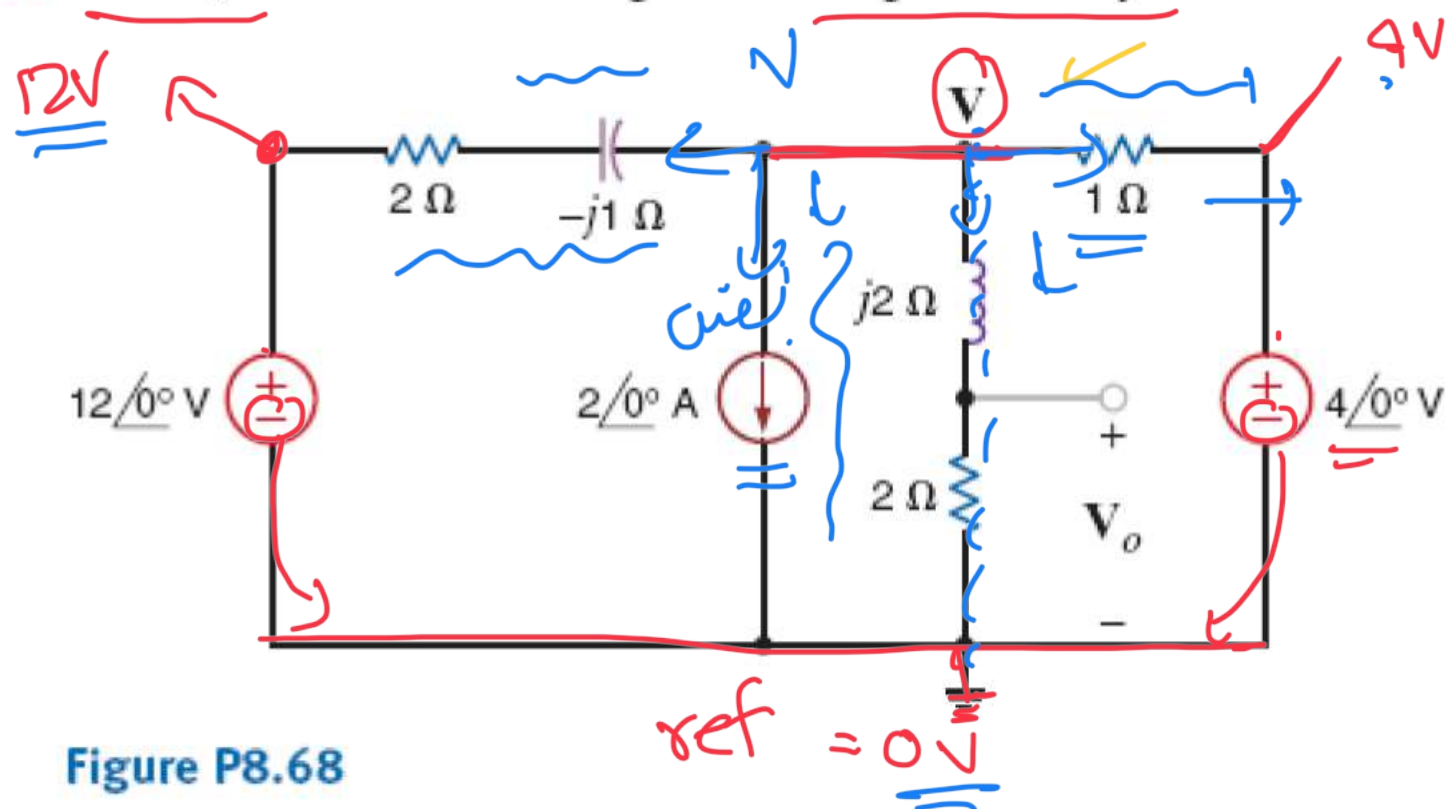


Figure P8.68

node v

$$\frac{1V - 12}{2 - j} + \frac{1}{2} + \frac{1V - 0}{2 + 2j} + \frac{1V - 4}{1} = 0$$

$$v \left[\frac{1}{2 - j} + \frac{1}{2 + 2j} + \frac{1}{1} \right] = -2 + \frac{4}{1} + \frac{12}{2 - j}$$

$$v \left[\frac{33}{20} - j \frac{1}{20} \right] = \frac{34}{5} + j \frac{12}{5}$$
$$\frac{33}{20} - j \frac{1}{20} \quad \frac{34}{20} - j \frac{1}{20}$$

نقطة تيار، في عناصر أو الكثر
node $\rightarrow$

8.68 Find V_o in the network in Fig. P8.68 using nodal analysis.

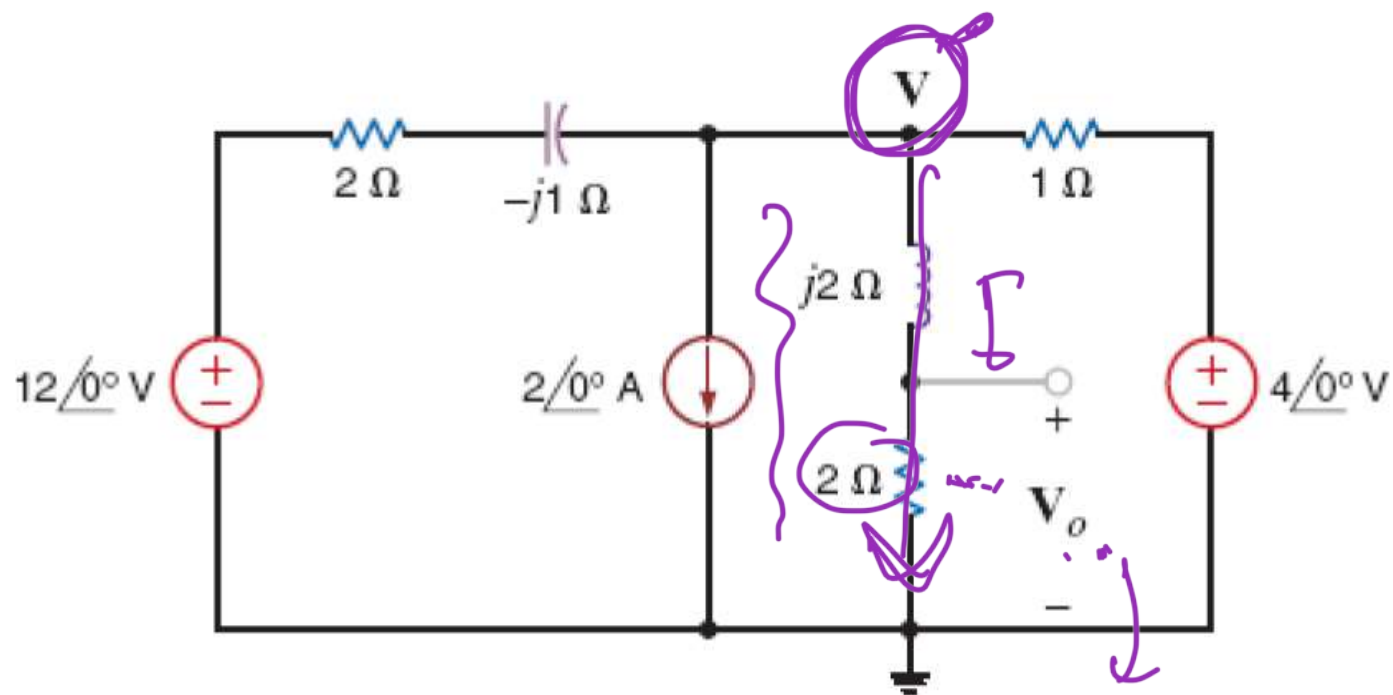


Figure P8.68

$$V_o = \underline{\underline{I \times R}}$$

$$V = 4.3684 \angle 21.176^\circ \text{ V}$$

$$I = \frac{V - 0}{2 + j2} = \frac{4.3684 \angle 21.176^\circ}{2 + j2}$$

$$I = 1.544 \angle -23.824^\circ \text{ A}$$

$$V_0 = 2 \times 1.544 \angle -23.824^\circ$$

$$V_0 = 3.1 \angle -23.8^\circ \text{ V}$$

نقطة تيارية أو الجهد $\rightarrow$ node

8.68 Find V_o in the network in Fig. P8.68 using nodal analysis.

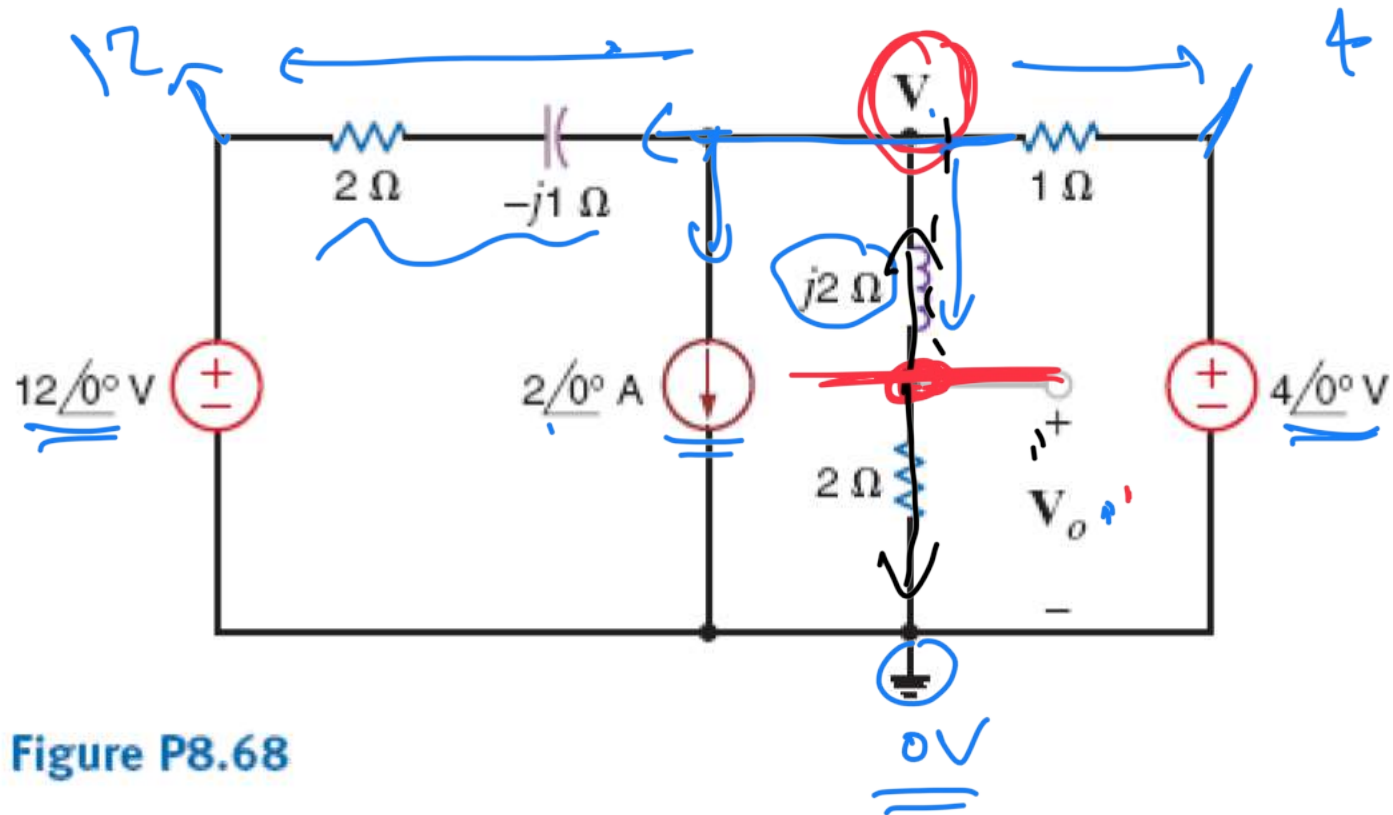


Figure P8.68

node V

$$\frac{1}{j2} = \underline{\underline{j\frac{1}{2}}}$$

$$\frac{1V - 12}{2} + \frac{1V - V_0}{j2} + \frac{1V - 4}{1} = 0$$

$$V \left[\frac{7}{5} - j\frac{3}{10} \right] + V_0 \left[j\frac{1}{2} \right] = 6.8 + j2.4$$

A B E

↑↑

node V_0

$$\frac{V_0 - V}{j2} + \frac{V_0 - 0}{2} = 0$$


$$\Rightarrow V \left[j\frac{1}{2} \right] + V_0 \left[\frac{1}{2} - j\frac{1}{2} \right] = 0$$

C D F

$$V = \frac{ED - BF}{AD - BC} = 4.368 \underline{21.176} \text{ V}$$

$$V_0 = \frac{AF - EC}{AD - BC} = 3.1 \underline{-23.8} \text{ V}$$

SOLUTION:

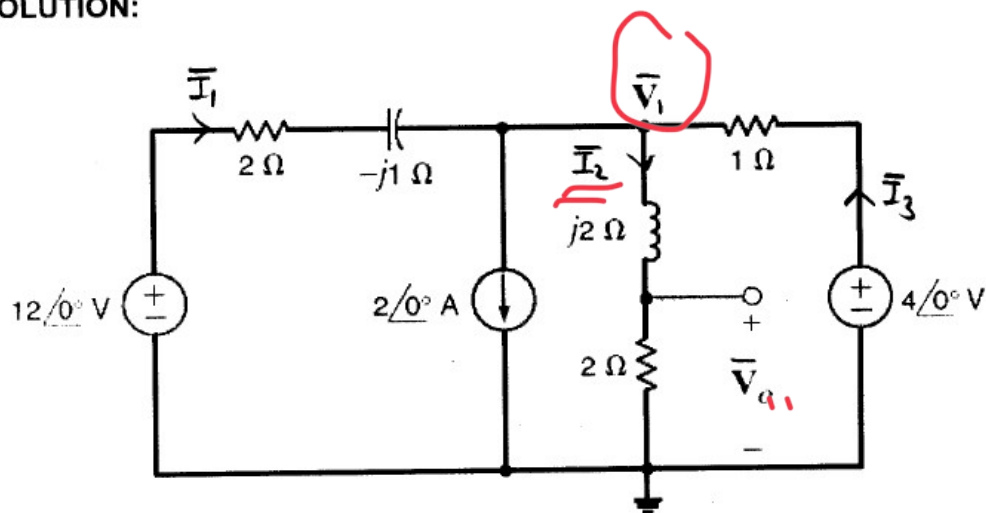

$$\text{KCL at } \textcircled{1}: \bar{I}_1 + \bar{I}_3 = 2\angle 0^\circ + \bar{I}_2$$

$$\frac{12\angle 0^\circ - \bar{V}_1}{2-j1} + \frac{4\angle 0^\circ - \bar{V}_1}{1} = 2\angle 0^\circ + \frac{\bar{V}_1}{2+j2}$$

$$\frac{\bar{V}_1}{2+j2} + \frac{\bar{V}_1}{2-j1} + \bar{V}_1 = \frac{12\angle 0^\circ + 4\angle 0^\circ - 2\angle 0^\circ}{2-j1}$$

$$\bar{V}_1 = \frac{7.21 \angle 19.44^\circ}{1.65 \angle -1.74^\circ}$$

✓

$$\bar{V}_1 = 4.37 \angle 21.2^\circ \text{ V}$$

$$\bar{I}_2 = \frac{\bar{V}_1}{2+j2} = \frac{4.37 \angle 21.2^\circ}{2+j2}$$

$$\bar{I}_2 = 1.55 \angle -23.8^\circ \text{ A}$$

$$\bar{V}_0 = 2(1.55 \angle -23.8^\circ)$$

$$\bar{V}_0 = 3.1 \angle -23.8^\circ \text{ V}$$

8.39 Find $v_o(t)$ and $i_o(t)$ in the network in Fig. P8.39.

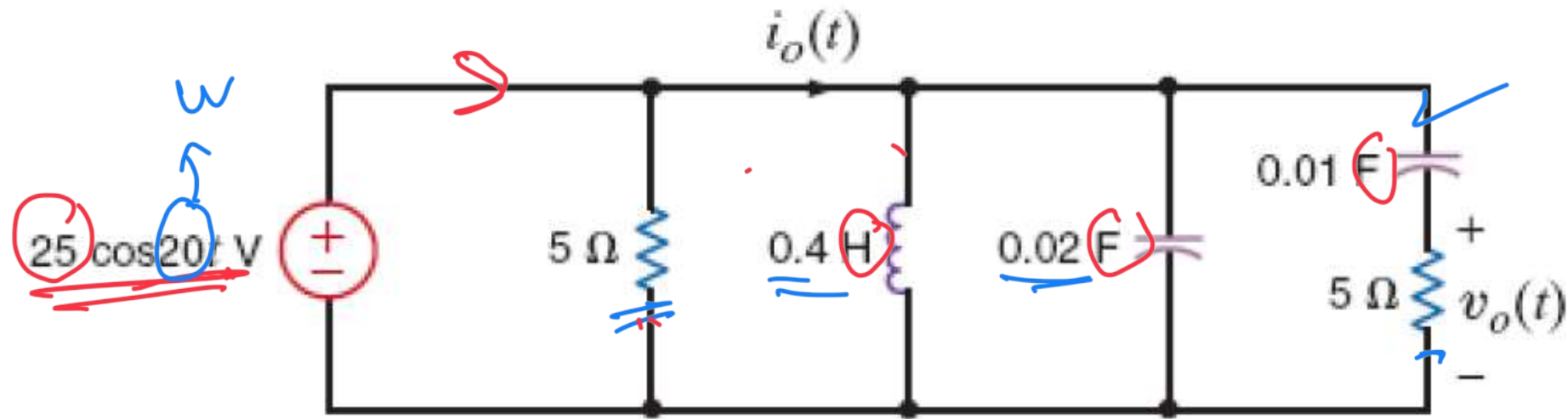


Figure P8.39

Time
domain

سوال کوئی


$$\omega = 20 \text{ rad/s}$$

$$Z_R = R = 5 \Omega$$

$$Z_L = j\omega L = j \times 20 \times 0.4 = j8 \Omega$$

$$Z_{C1} = \frac{1}{j\omega C} = \frac{1}{j \times 20 \times 0.01} = -j5 \Omega$$
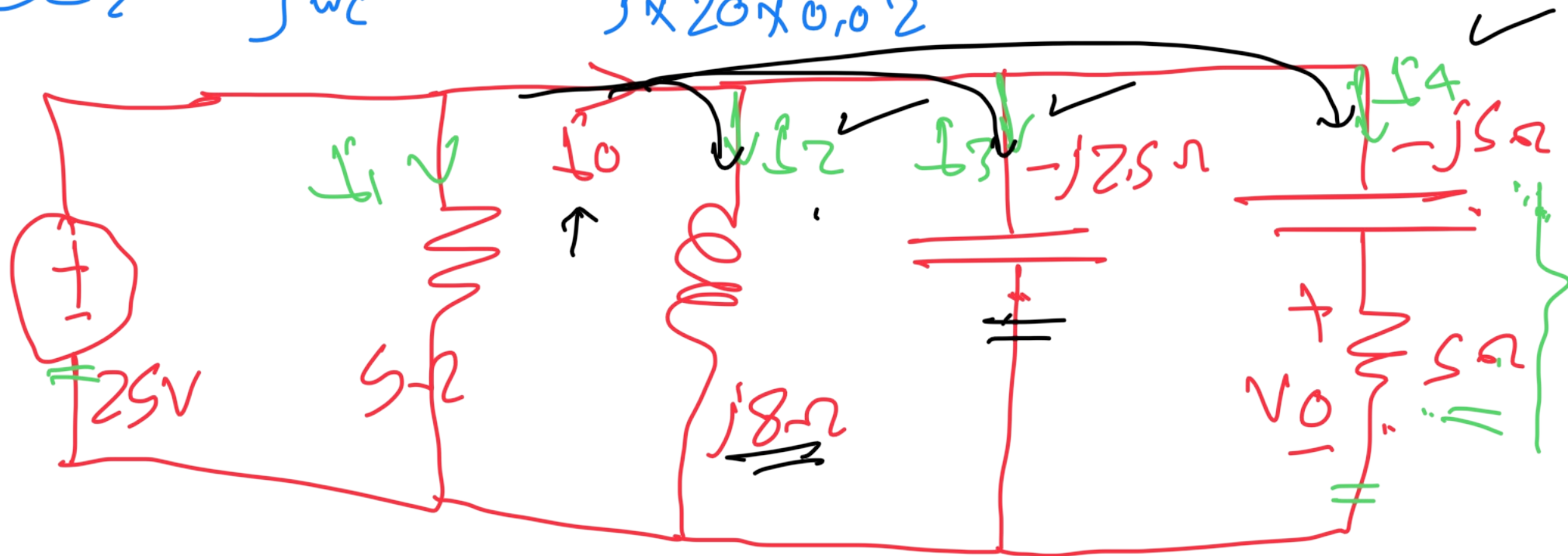
$$Z_{C2} = \frac{1}{j\omega C} = \frac{1}{j \times 20 \times 0.02} = -j \underline{\underline{2.5 \Omega}}$$



parallel

$$V_0 = 14 \times \underline{\underline{R}}$$

$$I_4 = \frac{V}{Z} = \frac{25}{5-j5} = 2.5 + j2.5 \text{ A} \checkmark$$

$$V_0 = (2.5 + j2.5) \times 5 = 12.5 + j12.5 \text{ V}$$

$$V_0 = 17.678 \angle \underline{45}^\circ \text{ V} \textcircled{P}$$

$$I_0 = I_2 + I_3 + I_4$$

$$I_3 = \frac{V}{Z} = \frac{25}{-j2.5} = \underline{\underline{j10 \text{ A}}}$$

$$I_2 = \frac{V}{Z} = \frac{25}{j8} = -j3.125 \text{ A}$$

$$I_0 = -j3.125 + j10 + 2.5 + j2.5 \text{ A}$$

$$I_0 = 2.5 + j9.375 \text{ A} = \underline{9.703} \angle \underline{75.1^\circ} \text{ A}$$

$$v_0(t) = 17.678 \cos(20t + 45^\circ) \text{ V}$$

$$i_0(t) = 9.703 \cos(20t + 75.1^\circ) \text{ A}$$

8.39 Find $v_o(t)$ and $i_o(t)$ in the network in Fig. P8.39.

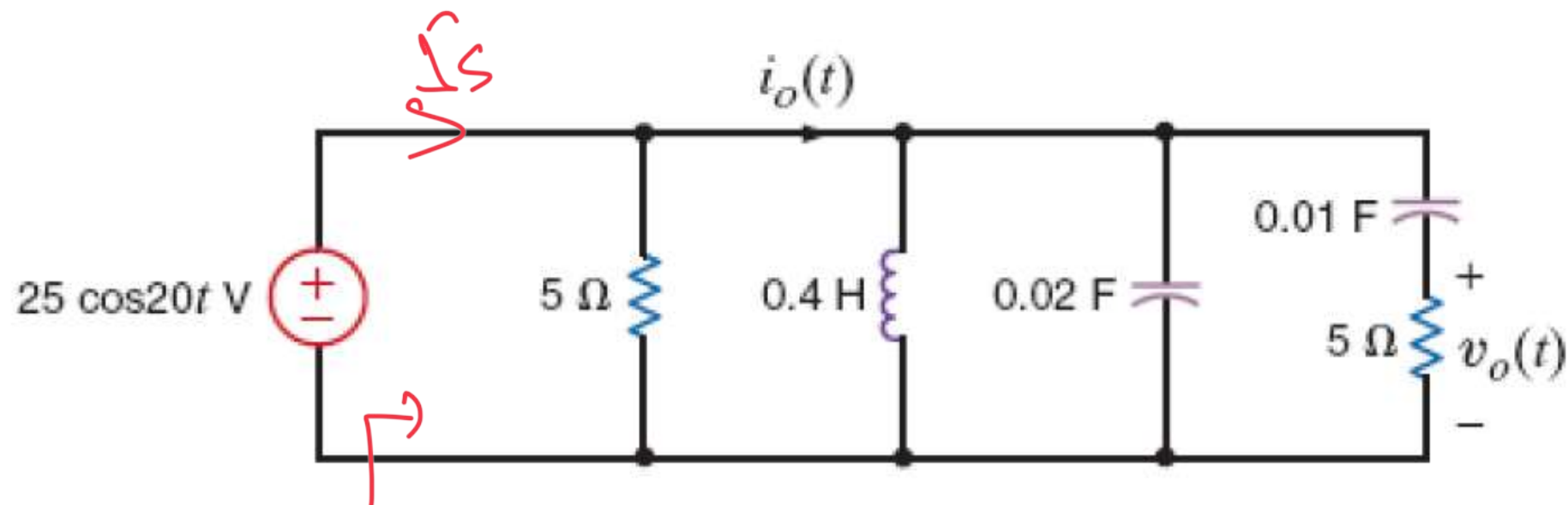


Figure P8.39

سؤال الكويز


$$\omega = 20 \text{ rad/s}$$

$$Z_R = R = 5 \Omega$$

$$Z_L = j\omega L = j \times 20 \times 0.4 = j8 \Omega$$

$$Z_{C1} = \frac{1}{j\omega C} = \frac{1}{j \times 20 \times 0.01} = -j5 \Omega$$

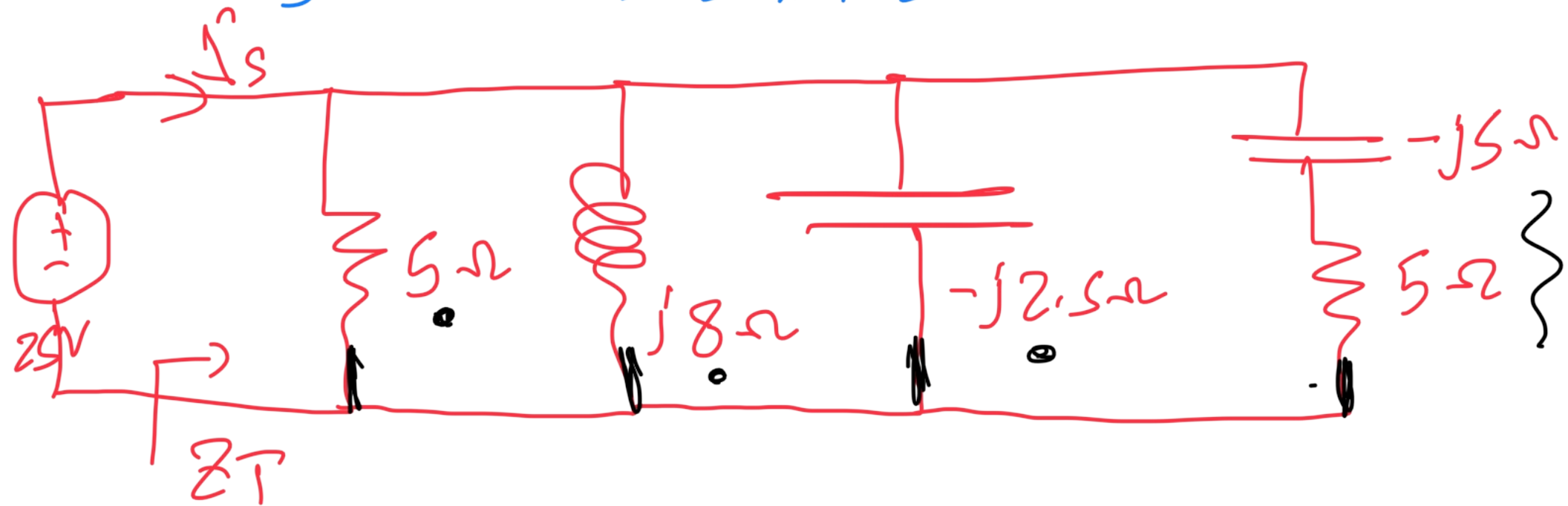
$$Z_{C2} = \frac{1}{j\omega C} = \frac{1}{j \times 20 \times 0.02} = -j\underline{\underline{2.5}} \Omega$$



Parallel

$$Z_T = \frac{1}{\frac{1}{5} + \frac{1}{j8} + \frac{1}{-j2.5} + \frac{1}{5-j5}}$$
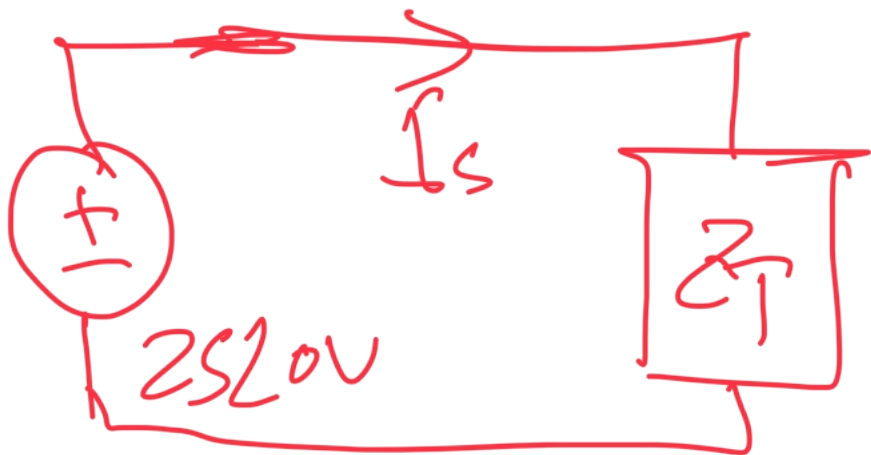
$$Z_T = \underline{2.082 \angle -51.34^\circ} \Omega$$



$$I_s = \frac{V}{Z_T} = \frac{25}{2.082 \angle -51.34}$$

$$I_s = 7.5 + j 9.375 \text{ A}$$

$$I_s = 12.01 \angle 51.34 \text{ A}$$


$$i_s(t) = 12.01 \cos(20t + 51.34) \text{ A}$$

SOLUTION:

$$\bar{Z}_L = j(20)(0.4) = j8\Omega$$

$$\bar{Z}_{c1} = \frac{1}{j(20)(0.02)} = -j2.5\Omega$$
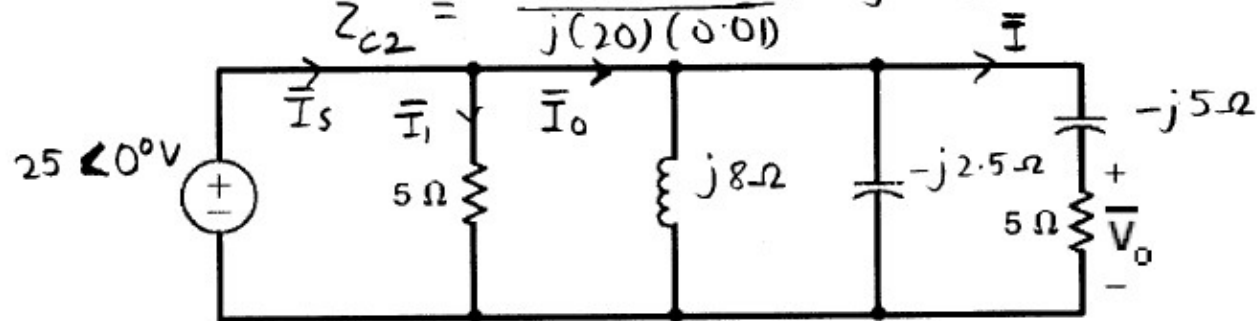
$$\bar{Z}_{c2} = \frac{1}{j(20)(0.01)} = -j5\Omega$$



$$\bar{I} = \frac{25\angle 0^\circ}{5-j5} = 3.54\angle 45^\circ \text{ A}$$

$$\bar{V}_0 = (3.54\angle 45^\circ)(5)$$

$$\bar{V}_0 = 17.68\angle 45^\circ \text{ V}$$

$$v_0(t) = 17.68 \cos(20t + 45^\circ) \text{ V}$$

$$\bar{I}_1 = \frac{25\angle 0^\circ}{5} = 5\angle 0^\circ \text{ A}$$

$$\bar{Z}_{eq} = [(5-j5) \parallel -j2.5] \parallel j8 \parallel 5$$

$$\bar{Z}_{eq} = \left[\frac{(5-j5)(-j2.5)}{5-j5-j2.5} \right] \parallel j8 \parallel 5$$

$$\bar{Z}_{eq} = (1.96 \angle -78.7^\circ \parallel j8) \parallel 5$$

$$\bar{Z}_{eq} = 2.57 \angle -75.08^\circ \parallel 5$$

$$\bar{Z}_{eq} = 2.08 \angle -51.4^\circ \Omega$$

$$\bar{I}_s = \frac{25 \angle 0^\circ}{2.08 \angle -51.4^\circ} = 12.02 \angle 51.4^\circ \text{ A}$$

$$\text{KCL: } \bar{I}_s = \bar{I}_1 + \bar{I}_0$$

$$\bar{I}_0 = \bar{I}_s - \bar{I}_1$$

$$\bar{I}_0 = 12.02 \angle 51.4^\circ - 5 \angle 0^\circ$$

$$\bar{I}_0 = 9.72 \angle 75.1^\circ \text{ A}$$

$$i_0(t) = 9.72 \cos(20t + 75.1^\circ) \text{ A}$$

8.79 Using loop analysis and MATLAB, find I_o in the network in Fig. P8.79.

mesh analysis

phasor Domain

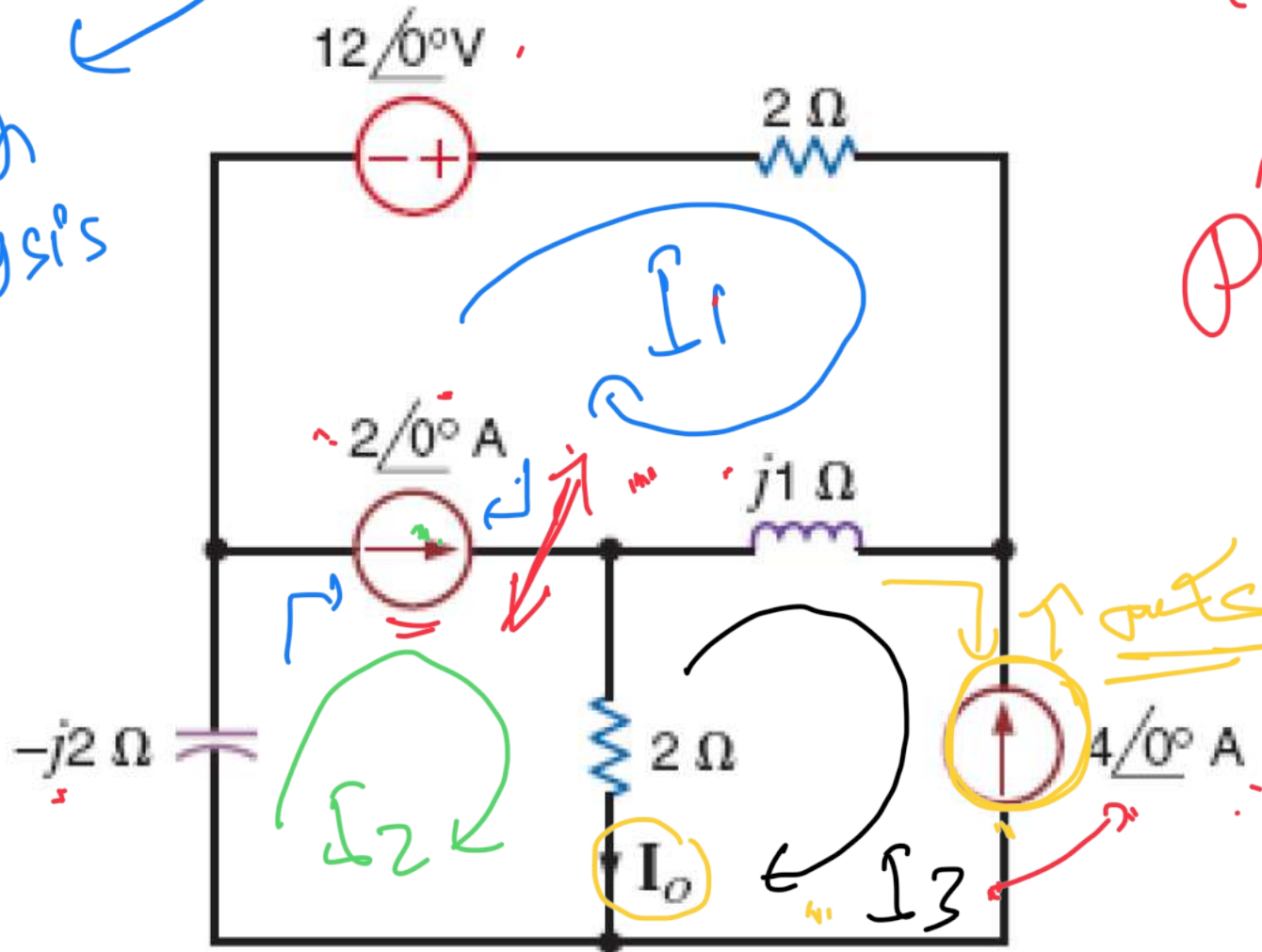


Figure. P8.79



Note

$$I_0 = I_2 - I_3 \rightarrow \textcircled{1}$$

$$I_3 = \underline{\underline{-4A}} \rightarrow \textcircled{2} \checkmark$$

③ $\Rightarrow$ super mesh / super loop $\Rightarrow \underline{\underline{2 \text{ eq}}}$

$$L, \quad I_2 - I_1 = \underline{\underline{2}} \rightarrow \textcircled{1}$$



loop 1+2

$$\underline{-j2 I_2 - 12} + \underline{2 I_1} + \underline{j1(I_1 - I_3)} + \underline{2(I_2 - I_3)} = 0$$

$$I_3 = -4$$

$$I_1(2+j) + I_2(2-j2) = 12 + jI_3 + 2I_3$$

$$12 + jx - 4 + 2x - 4$$

$$\begin{aligned} \xrightarrow{A} & \boxed{I_1(2+j) + I_2(2-j2) = 4 - j4} \xrightarrow{E} \textcircled{1} \\ \xrightarrow{C} & \boxed{I_1(-1) + I_2(1) = 2} \xrightarrow{F} \textcircled{2} \end{aligned}$$

$$I_1 = \frac{ED - BF}{AD - BC}$$

$$I_1 = 0 \quad A$$




$$I_2 = \frac{AF - EC}{AD - BC} = \underline{\underline{2A}} = 20A$$

$$I_0 = I_2 - I_3 = 2 \text{ (} \textcircled{2-4} \text{)}$$

$$I_0 = 2 + 4 = 6A$$

$$\boxed{I_0 = 60A}$$

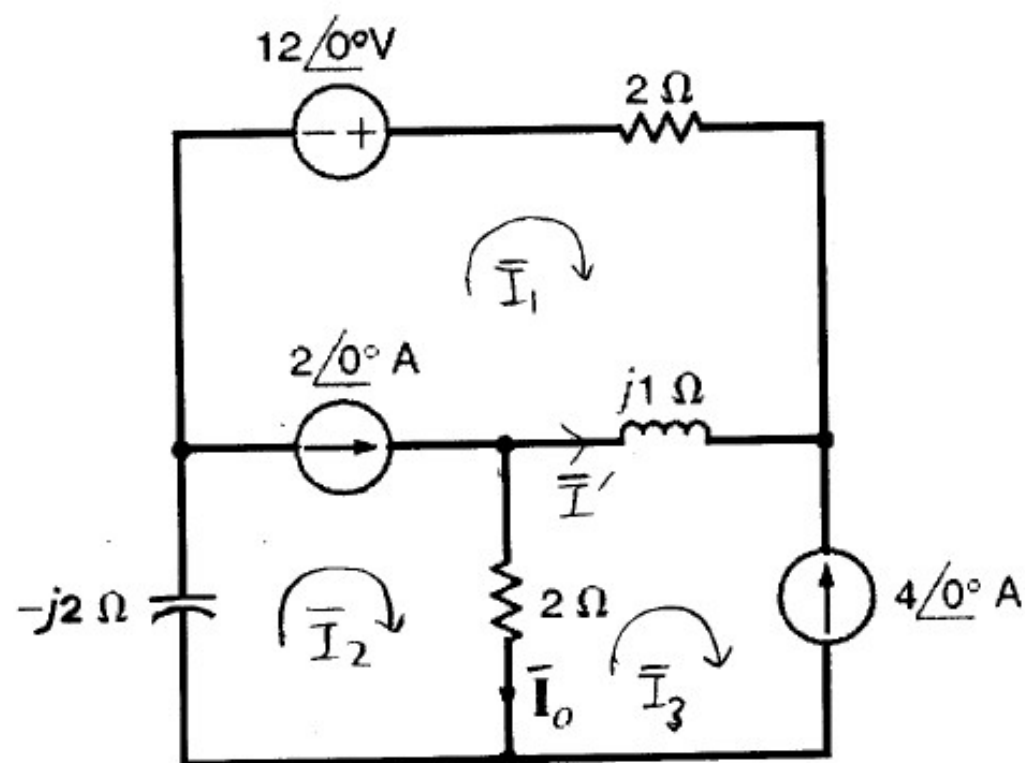SOLUTION:

$$\text{KCL : } \bar{I}_0 + \bar{I}_3 = \bar{I}_2$$
$$\bar{I}_0 = \bar{I}_2 - \bar{I}_3$$

$$\text{KCL : } \bar{I}' + \bar{I}_0 = 2\angle 0^\circ$$
$$\bar{I}' = 2\angle 0^\circ - \bar{I}_0$$

$$\text{KVL : } 2\bar{I}_1 + j1(-\bar{I}') + 2\bar{I}_0 - j2\bar{I}_2 = 12\angle 0^\circ$$

$$2\bar{I}_1 - j1(2\angle 0^\circ - \bar{I}_0) + 2(\bar{I}_2 - \bar{I}_3) - j2\bar{I}_2 = 12\angle 0^\circ$$

$$2\bar{I}_1 + (2 - j2)\bar{I}_2 - 2\bar{I}_3 + j1(\bar{I}_2 - \bar{I}_3) = 12\angle 0^\circ + j1(2\angle 0^\circ)$$

$$2\bar{I}_1 + (2 - j1)\bar{I}_2 + (-2 - j1)\bar{I}_3 = 12\angle 0^\circ + j1(2\angle 0^\circ)$$

$$\bar{I}_3 = -4\angle 0^\circ = 4\angle 180^\circ \text{ A}$$

$$2\bar{I}_1 + (2 - j1)\bar{I}_2 + (-2 - j1)(4\angle 180^\circ) = 12.17\angle 9.46^\circ$$

$$2\bar{I}_1 + (2 - j1)\bar{I}_2 = 4.48\angle -26.54^\circ$$

$$\text{KCL: } \bar{I}_1 + 2\angle 0^\circ = \bar{I}_2$$

$$\bar{I}_1 - \bar{I}_2 = 2\angle 180^\circ$$

$$2\bar{I}_1 + (2-j1)\bar{I}_2 = 4.48 \angle -26.54^\circ$$

$$\bar{I}_1 - \bar{I}_2 = 2 \angle 180^\circ$$

$$\bar{I}_1 = 0 \text{ A}$$

$$\bar{I}_2 = 2 \angle 1.43^\circ \text{ A}$$

$$\bar{I}_3 = 4 \angle 180^\circ \text{ A}$$

$$\bar{I}_0 = \bar{I}_2 - \bar{I}_3$$

$$\bar{I}_0 = 2 \angle 1.4^\circ - 4 \angle 180^\circ$$

$$\bar{I}_0 = 6 \angle 0^\circ \text{ A}$$

MATLAB Solution:

$$Z = \begin{bmatrix} 2 & 2-i & 1 & -1 \end{bmatrix}$$

$$V = \begin{bmatrix} 4-2i & -2 \end{bmatrix}$$

$$I = \text{inv}(Z) * V$$

$$I_2 = I(2)$$

$$I_3 = -4$$

$$I_0 = I_2 - I_3$$

Answer:

$$Z =$$

$$\begin{bmatrix} 2.0000 & 2.0000-1.0000i \\ 1.0000 & -1.0000 \end{bmatrix}$$

$$V =$$

$$\begin{bmatrix} 4.0000 & -2.0000i \\ -2.0000 \end{bmatrix}$$

$$I =$$

$$\begin{bmatrix} -0.0000 \\ 2.0000 \end{bmatrix}$$

$$I_2 =$$

$$2$$

$$I_3 =$$

$$-4$$

$$I_0 =$$

$$6$$

8.91 Using superposition, find V_o in the circuit in Fig. P8.91.


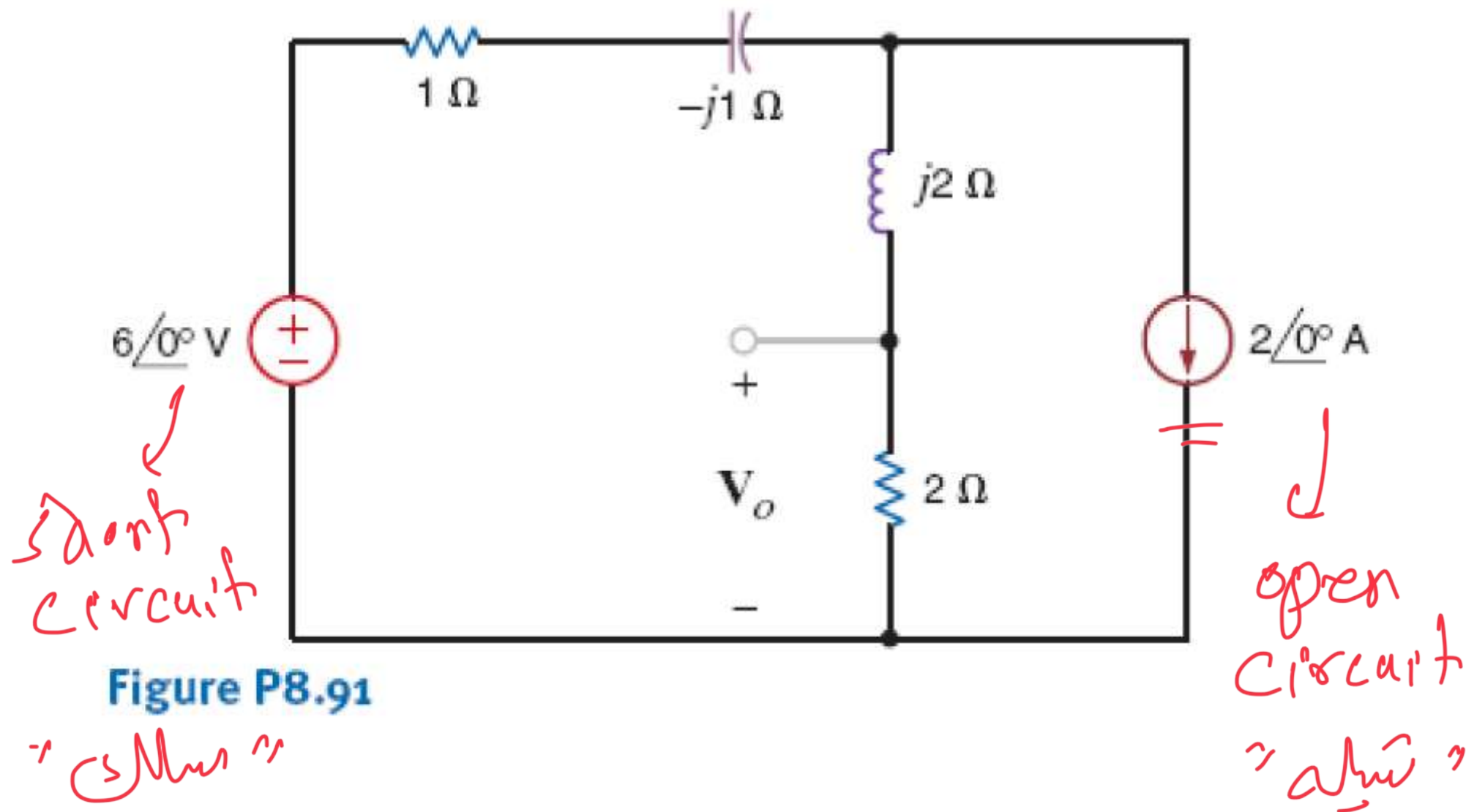


Figure P8.91


1) Turn off 2A and keep 6V

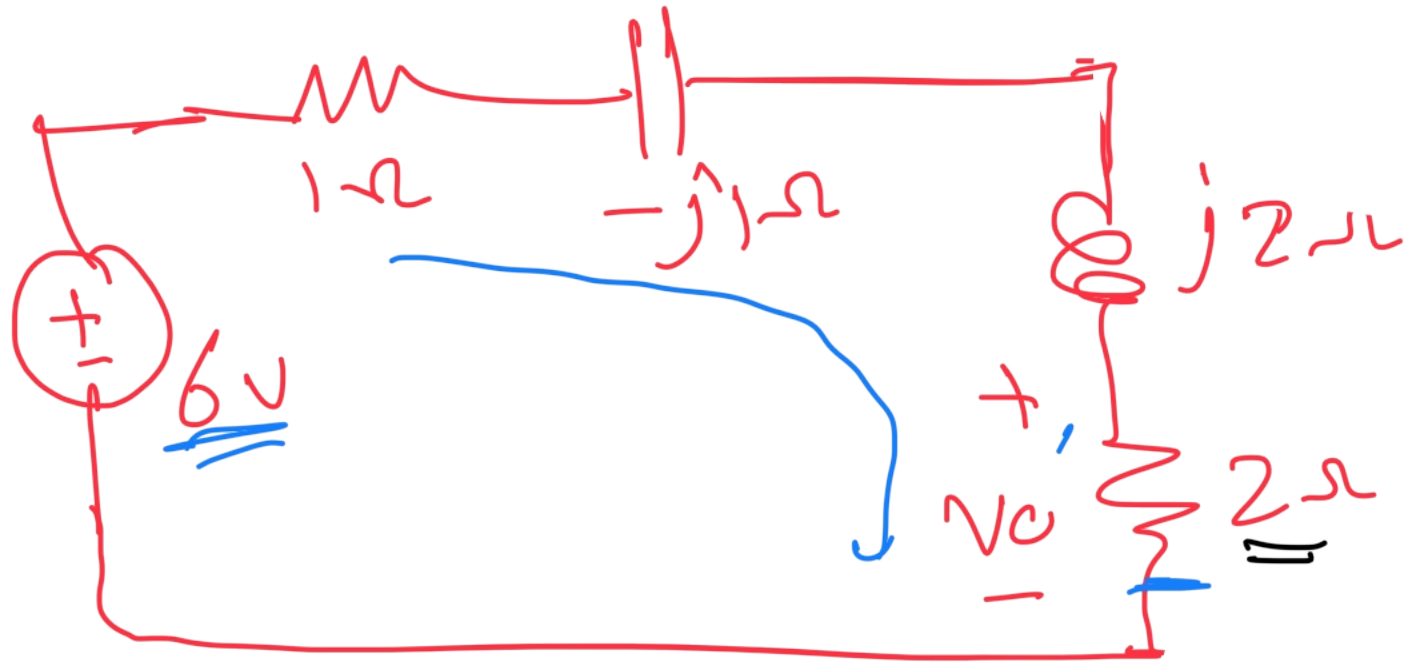

Series
$$V_o' = \frac{2}{1 - j1 + j2 + 2} * 6$$

$$V_o' = \underline{3.6 - j1.2 \text{ V}} = 3.79 \angle -18.43^\circ \text{ V}$$

12) Turn off 6V and keep 2A

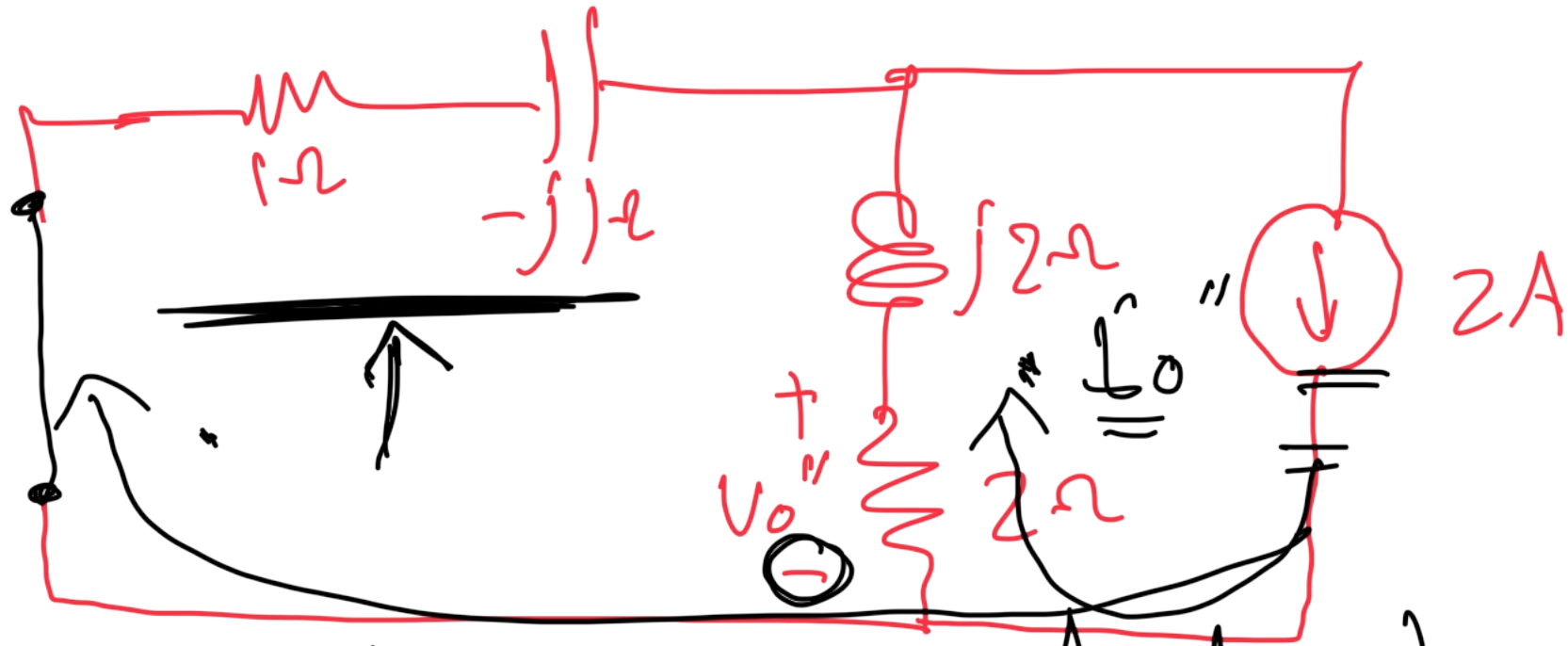

parallel $\Rightarrow$ current divider

$$I_{o''} = \frac{1 - j1}{1 - j + j^2 2 + 2} * 2$$

$$\hat{I}_0'' = 0,4 - j0,8 \text{ A}$$


$$V_0'' = -\hat{I}_0'' \times R = -(0,4 - j0,8) \times 2$$

$$V_0'' = \underline{-0,8 + j1,6 \text{ V}} = \underline{1,79 \angle 116,365^\circ \text{ V}}$$

$$V_0 = V_0' + V_0'' = 3,6 - j1,2 + -0,8 + j1,6$$

$$V_0 = \underline{2,8 + j0,4} = 2,828 \angle 8,13^\circ \text{ V}$$


SOLUTION:

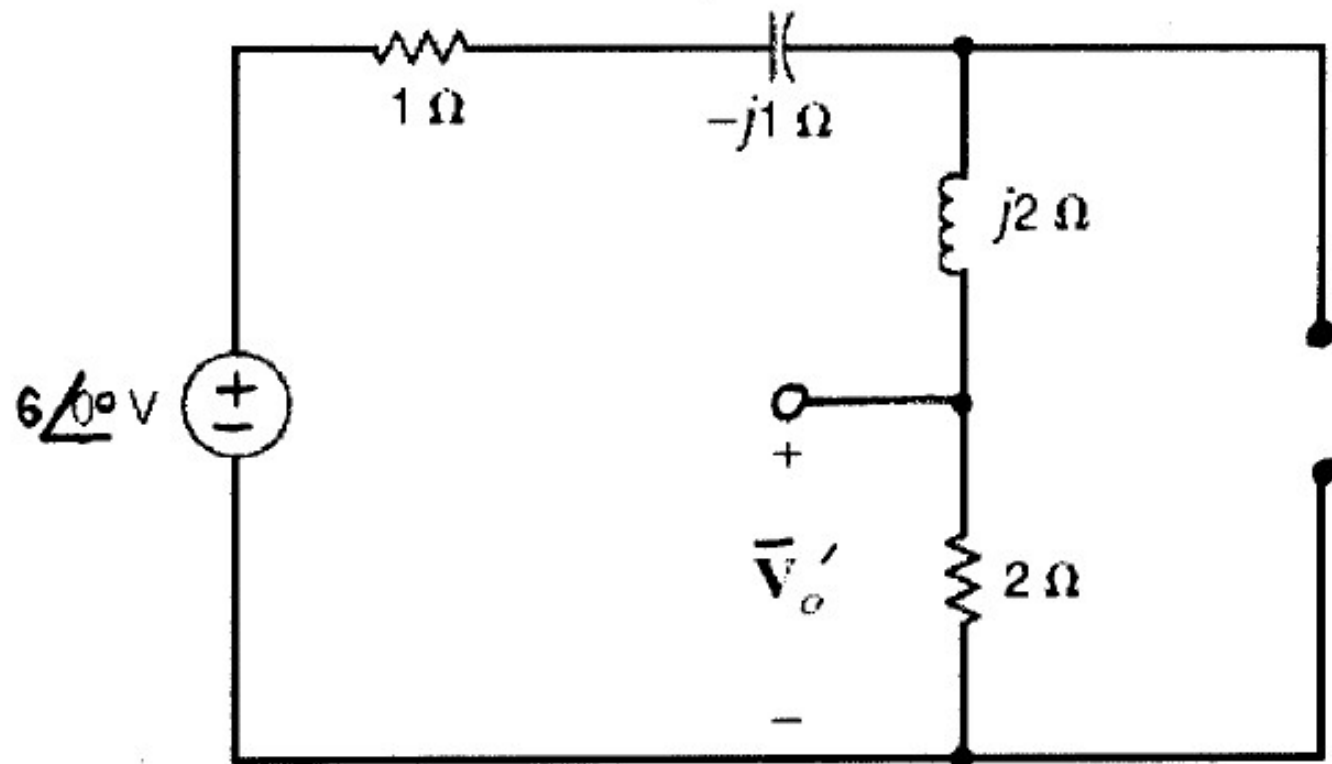

$$\bar{V}_o' = \left(\frac{2}{2 + j2 + 1 - j1} \right) (6\angle 0^\circ)$$
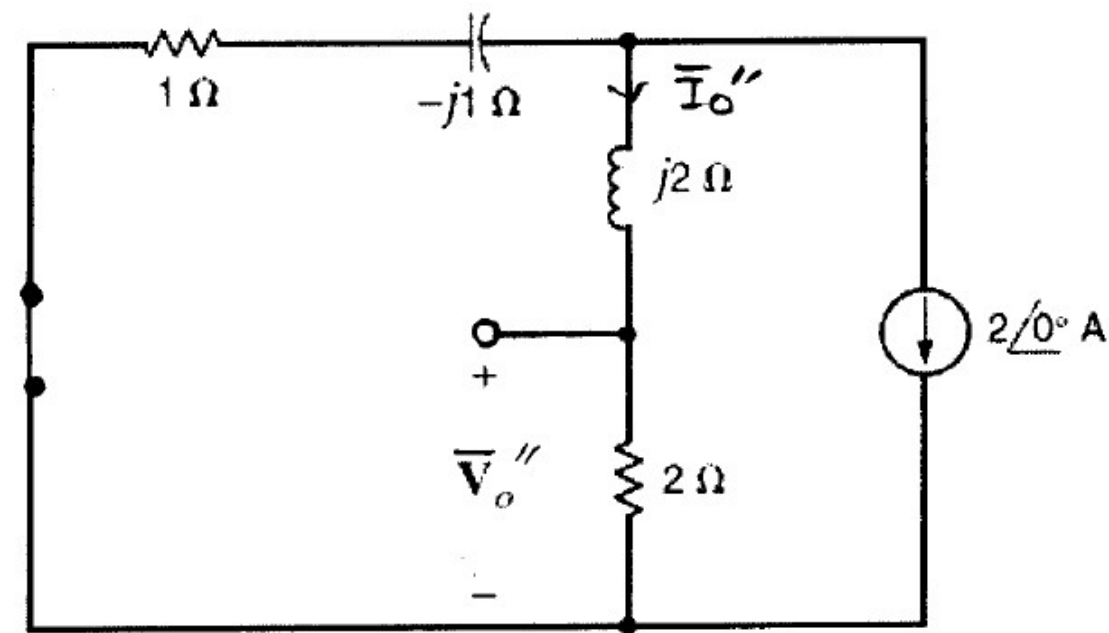
$$\bar{V}_o' = 3.79 \angle -18.43^\circ \text{ V}$$





$$\bar{I}_o'' = \left(\frac{1-j1}{1-j1+2+j2} \right) (-2 \angle 0^\circ)$$

$$\bar{I}_o'' = 0.89 \angle 116.57^\circ \text{ A}$$


$$\bar{V}_o'' = 2(0.89 \angle 116.57^\circ \text{ A})$$

$$\bar{V}_o'' = 1.79 \angle 116.57^\circ \text{ V}$$



$$\bar{V}_o = \bar{V}_o' + \bar{V}_o'' = 3.79 \angle -18.43^\circ + 1.79 \angle 116.57^\circ$$

$$\bar{V}_o = 2.82 \angle 8.2^\circ \text{ V}$$

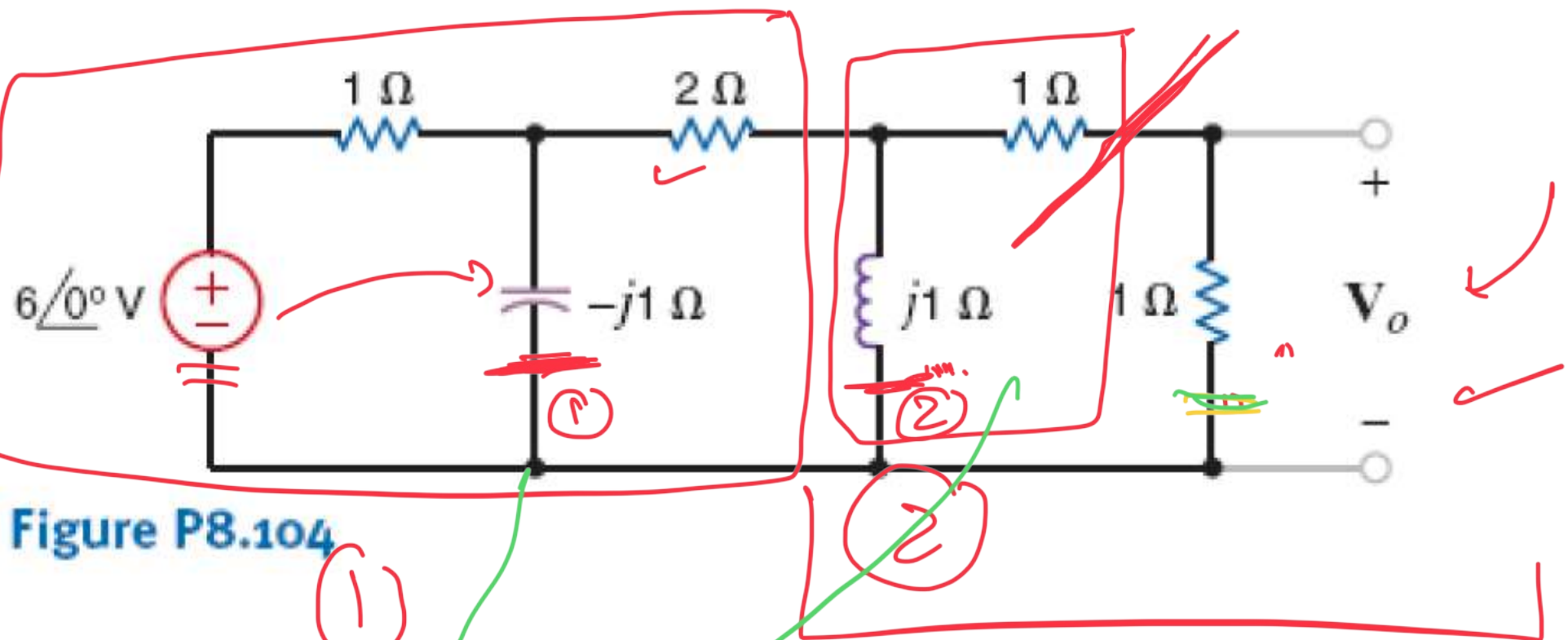8.104 Apply Thévenin's theorem twice to find V_o in the circuit in Fig. P8.104.




$V_{o,c}$ →
 Z_{th} → Thév

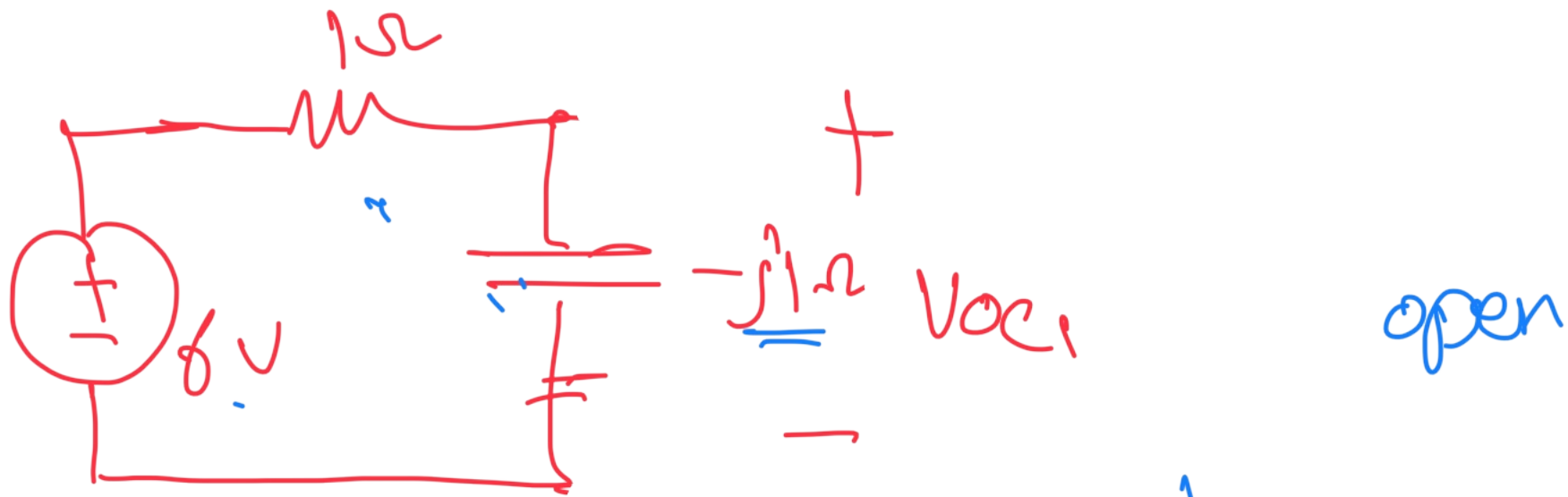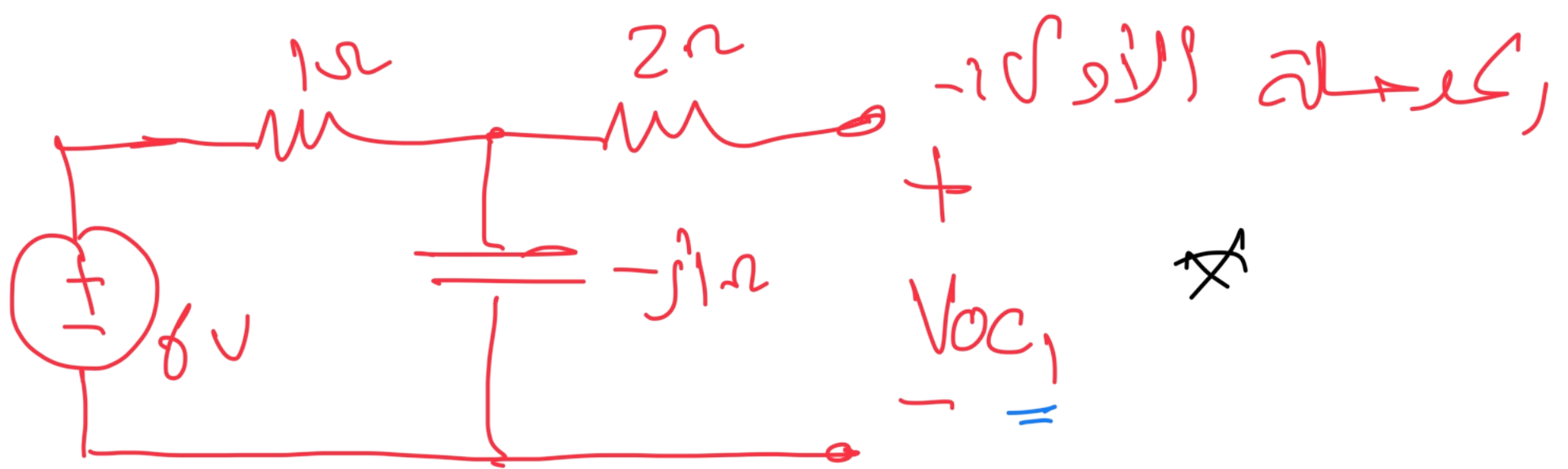

Series $\Rightarrow$ Voltage divider

$$V_{oc1} = \frac{-j1}{1-j1} \times 6 = 3-j3 = 3\sqrt{2} \angle -45^\circ \text{ V}$$

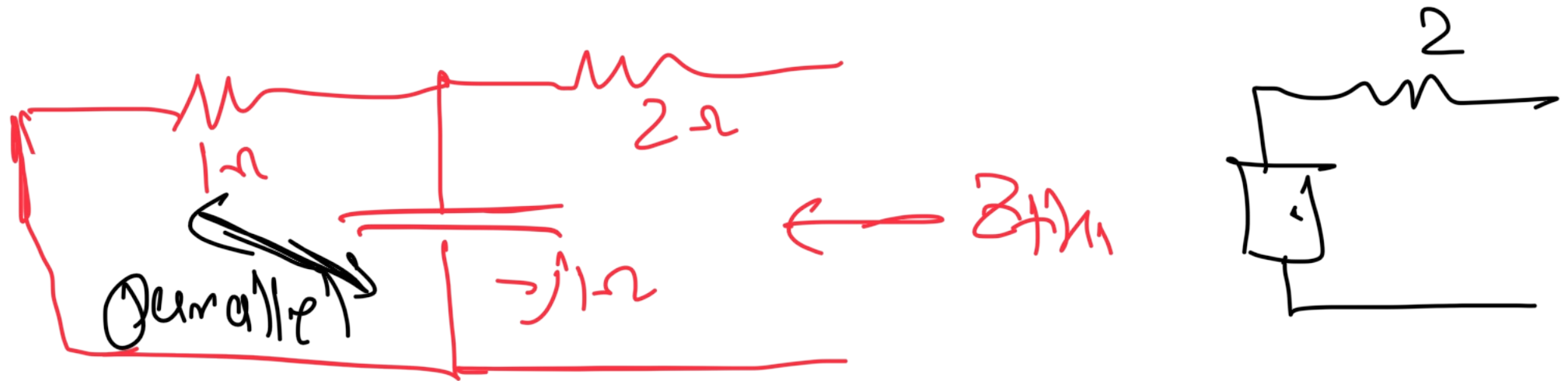
To find Z_{th} : Turn off all ind sources



$$Z_{th} = \frac{1}{\frac{1}{1} + \frac{1}{-j1}} + 2$$

$$Z_{th} = 2.5 - j0.5 = 2.55 \angle -11.31^\circ \Omega$$

المرحلة الثانية :-

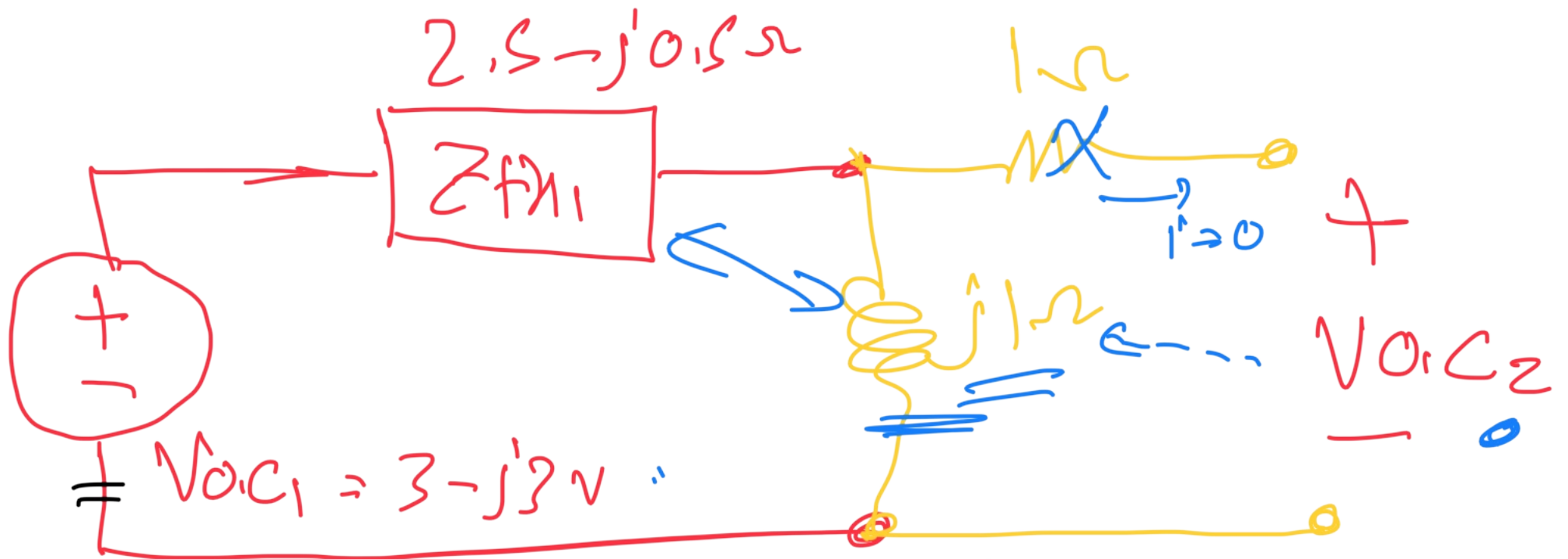


series $\Rightarrow$ voltage divider

$$V_{OC2} = \frac{j1}{2.5 - j0.5 + j1} \times (3 - j3)$$


$$V_{O.C} Z = \frac{18}{13} + j\frac{12}{13} \text{ V} = 1.66 \angle 33.7^\circ \text{ V}$$

$Z_{th} Z$

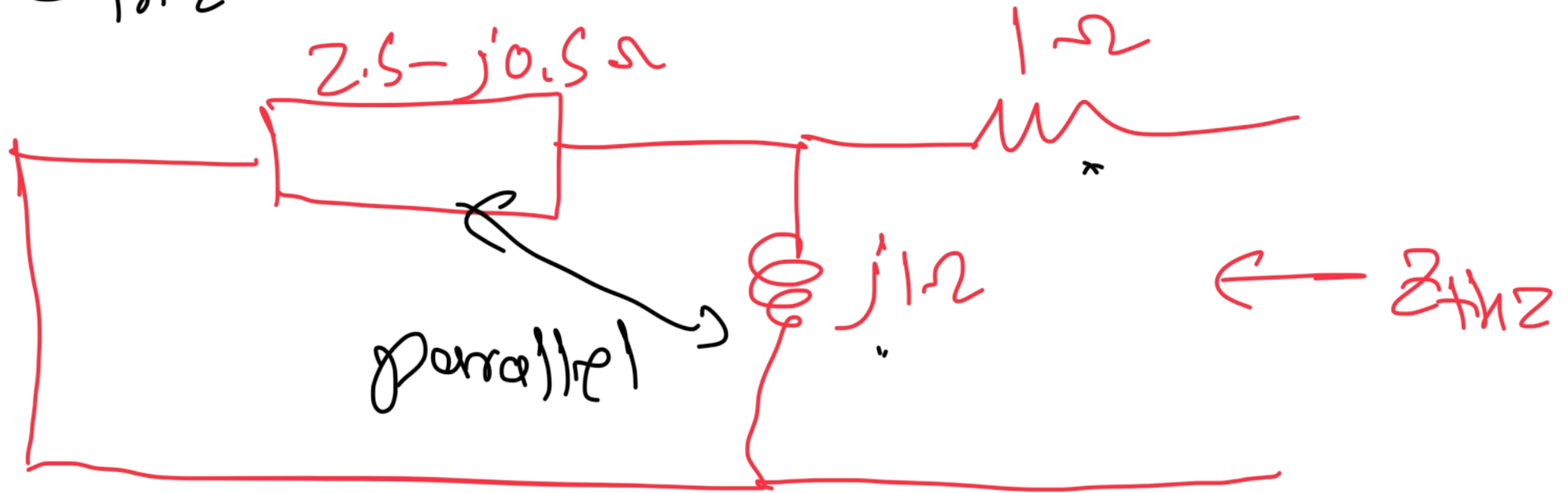

$$Z_{th} Z = 1 + \frac{1}{\frac{1}{j1} + \frac{1}{2.5 - j0.5}}$$
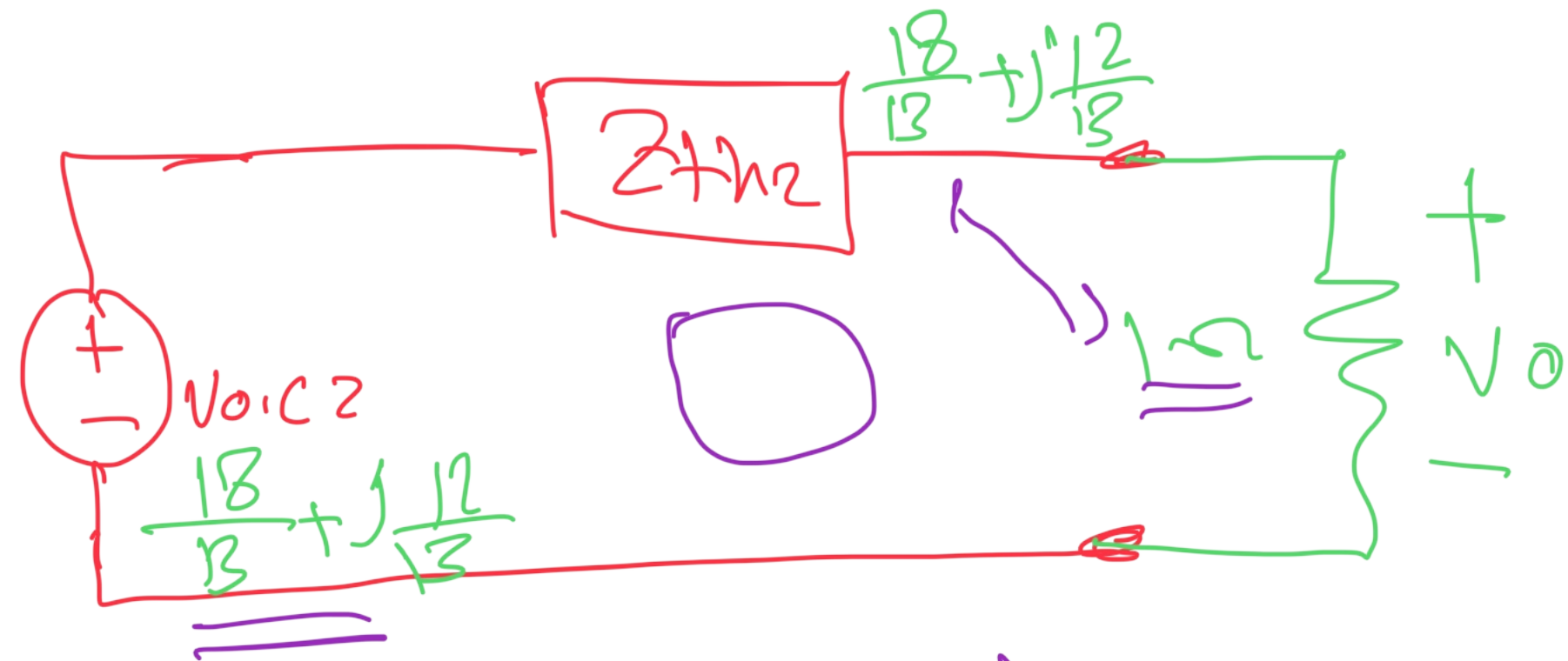
$$Z_{th2} = \frac{18}{13} + j\frac{12}{13} \Omega = 1.66 \angle 33.7^\circ \Omega$$




Series $\Rightarrow$ Voltage divider

$$V_0 = \frac{1}{1 + \frac{18}{13} + j \frac{12}{13}} \times \left(\frac{18}{13} + j \frac{12}{13} \right)$$

$$\Rightarrow V_0 = \frac{54}{85} + j \frac{12}{85} \text{ V}$$


$$V_0 = 0,635294 \angle 10,7288^\circ \text{ V}$$

SOLUTION:

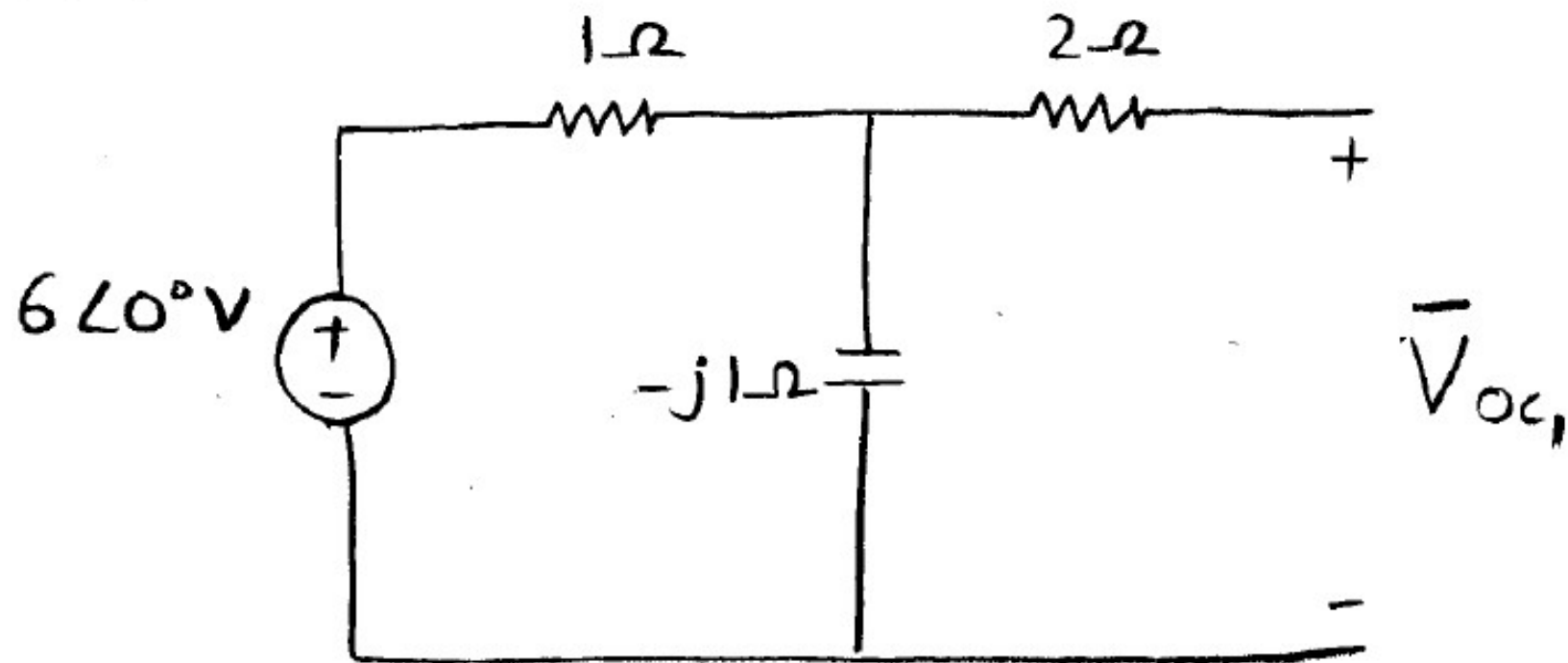

$$\bar{V}_{oc} = \left(\frac{-j1}{1-j1} \right) (6\angle 0^\circ)$$


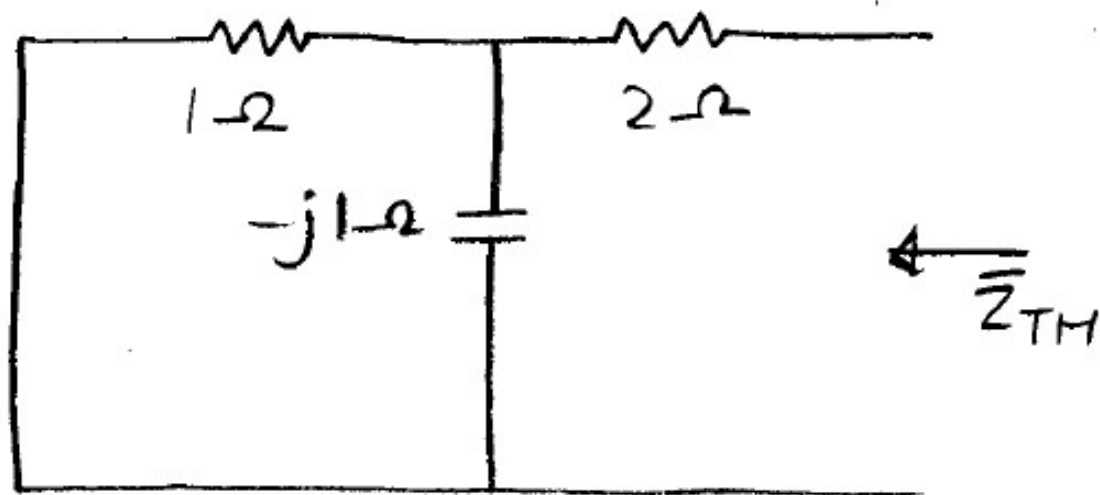
$$\bar{V}_{oc} = 4.24\angle -45^\circ \text{ V}$$



$$\bar{Z}_{TH} = 2 + (1 \parallel -j1) = 2 + \frac{1(-j1)}{1-j1}$$

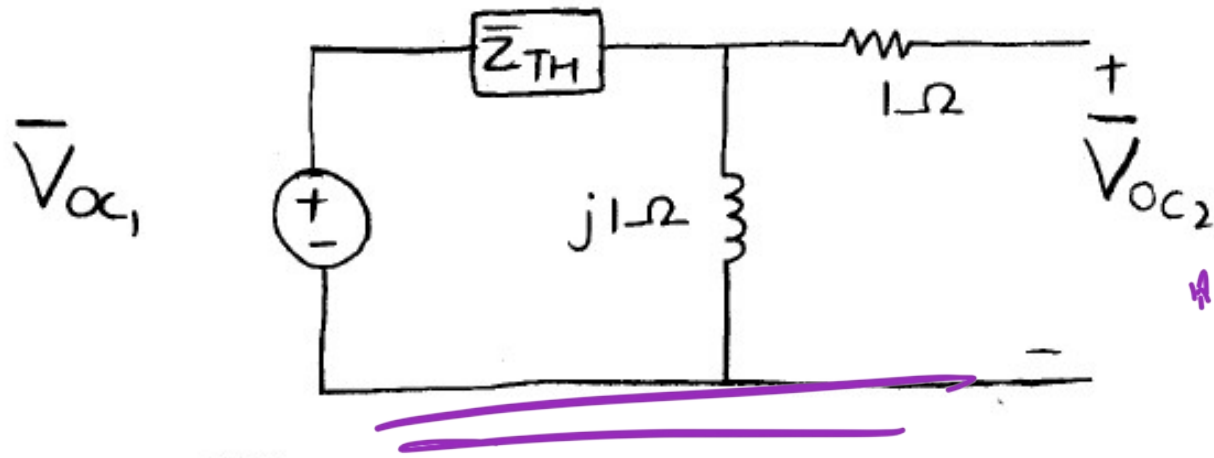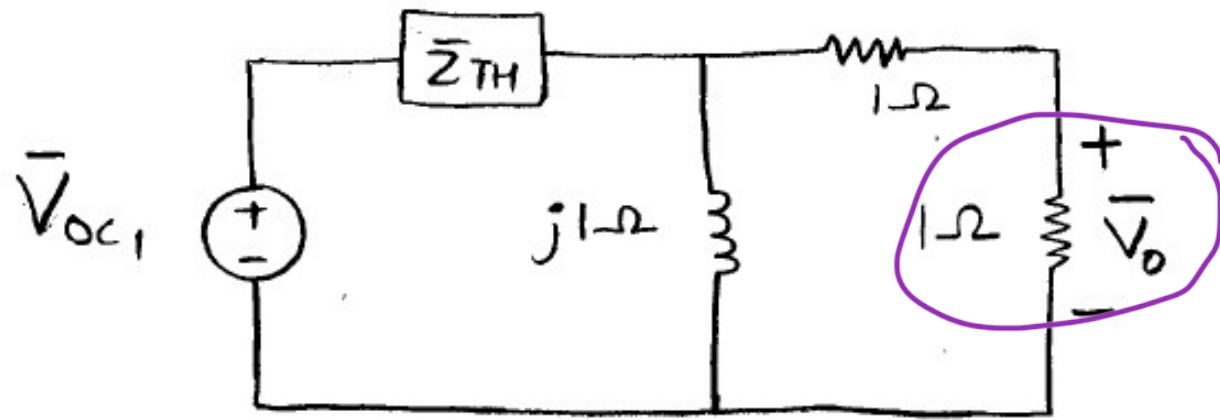
$$\bar{Z}_{TH} = 2.55 \angle -11.31^\circ \text{ }\Omega$$






$$\bar{V}_{OC2} = \left(\frac{j1}{j1 + 2.55 \angle -11.31^\circ} \right) (4.24 \angle -45^\circ)$$
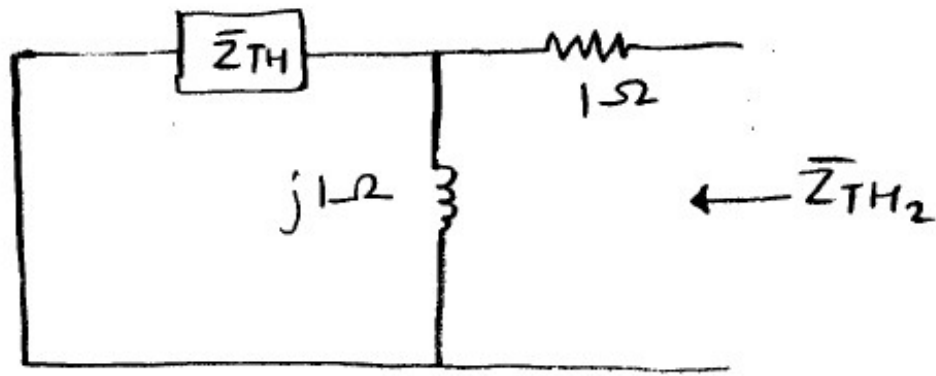
$$\bar{V}_{OC2} = 1.66 \angle 33.7^\circ$$



$$\bar{Z}_{TH2} = 1 + (\bar{Z}_{TH1} \parallel j1)$$
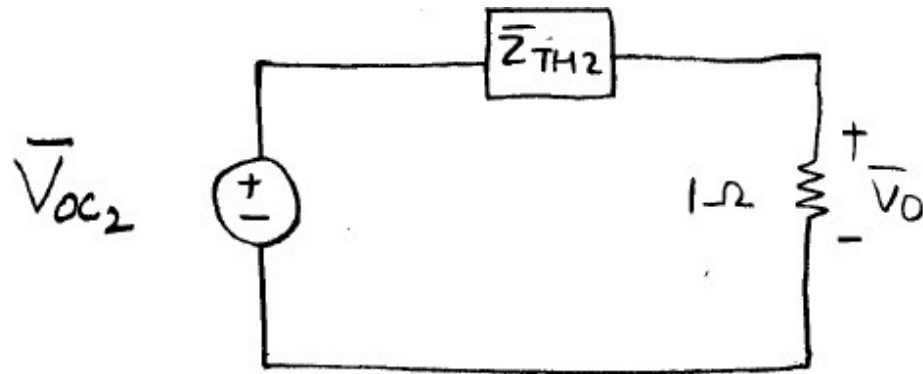
$$\bar{Z}_{TH2} = 1 + \frac{(2.55 \angle -11.31^\circ)(j1)}{2.55 \angle -11.31^\circ + j1} = \underline{\underline{1.66 \angle 33.67^\circ \Omega}}$$



$$\bar{V}_o = \left(\frac{1}{1 + 1.66 \angle 33.67^\circ} \right) (1.66 \angle 33.67^\circ)$$

$$\bar{V}_o = 0.65 \angle 12.54^\circ \text{ V}$$

