



EEN 313 : Power Electronics Circuits

ZUHER ALNASIR, PhD.
Dept. of Electrical Engineering, JIC.
Naser_z@rcjy.edu.sa

Lecture 2

Uncontrolled Rectifiers



AC → DC

•Outline

- Part 01 : Half-Wave Rectifiers
- Part 02: Full-Wave Rectifiers

Part 01

Half-Wave Uncontrolled Rectifiers




•Outline

- Half-Wave Diode Rectifier with ***R*** Load
- Half-Wave Diode Rectifier with ***RL*** Load
- Half-Wave Diode Rectifier with **freewheeling Diode**
- Half-Wave **Battery Charger**



Half-Wave Diode Rectifier with R Load-1

- Half-Wave Diode Rectifier is the simplest PEC circuit.
- It is not normally used in industrial applications. However, it is very useful in understanding the basic of rectification process.
- A basic half-wave diode rectifier with a resistive load is shown below. It delivers a half-cycle of dc output for every full cycle of the applied ac voltage.

Diode Conduction angle is π

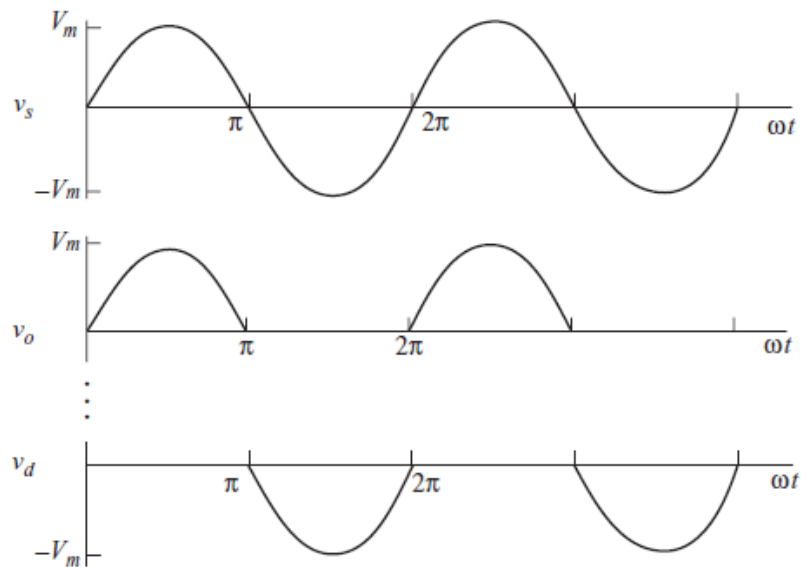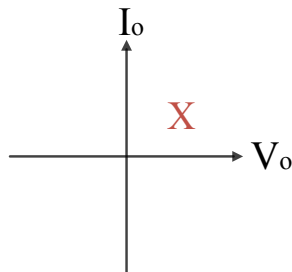
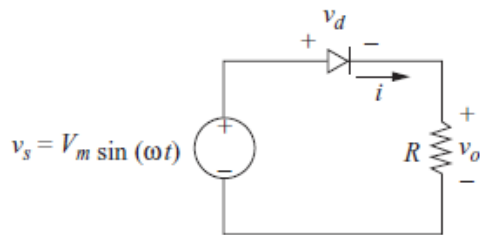


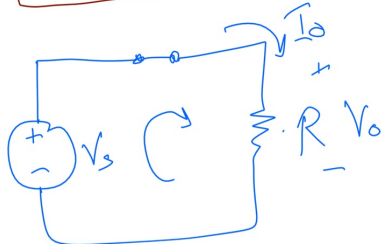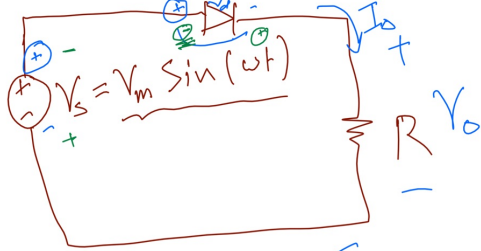The output ripple frequency is same as the source frequency.



$$-V_s + V_o = 0$$

$$V_s = V_o$$

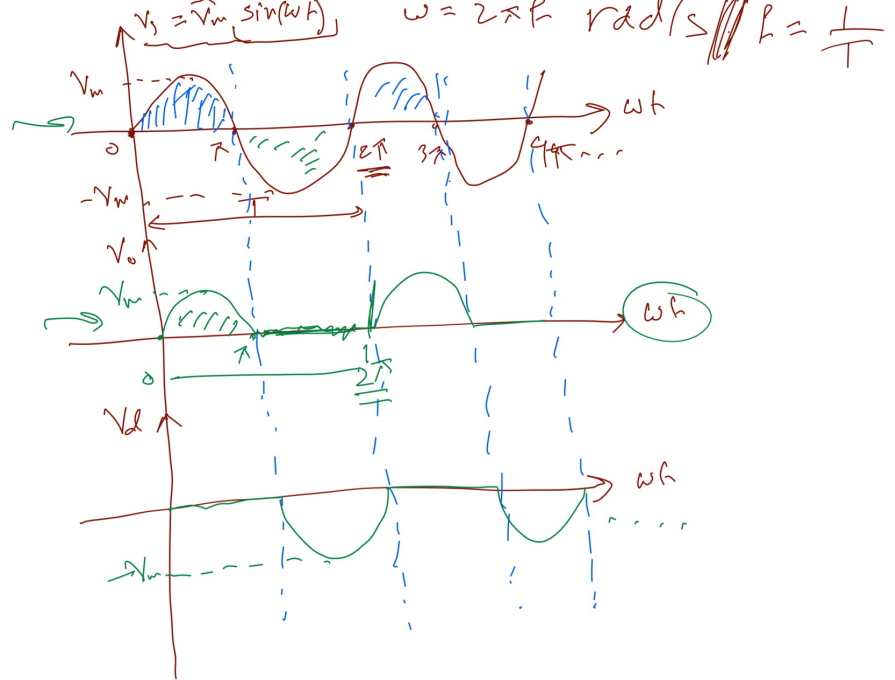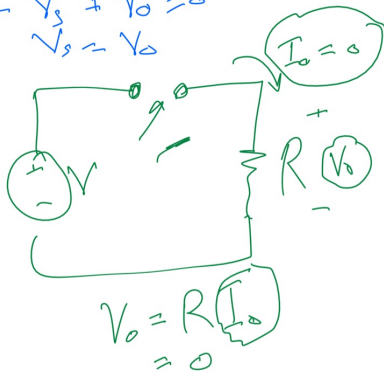

$$V_o = V_{avg} = V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} (V_m) \sin(\omega t) d\omega t = \frac{V_m}{2\pi} \int_0^{2\pi} \sin \omega t d\omega t$$

$$= \frac{V_m}{2\pi} [\cos(\omega t)]_0^{2\pi}$$

$$= \frac{V_m}{2\pi} [1 - 1]$$

$$I_{\text{avg}} = I_{\text{dc}} = \frac{V_{\text{avg}}}{R} = \frac{V_m}{\pi R}$$

$$P_{\text{avg}} = P_{\text{dc}} = V_{\text{avg}} I_{\text{avg}} = \frac{V_m}{\pi} \cdot \frac{V_m}{\pi R} = \frac{V_m^2}{\pi^2 R}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin(\omega t))^2 d\omega t}$$

$$= \frac{V_m}{2}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{V_m}{2R}$$

$$P_{\text{ac}} = V_{\text{orms}} I_{\text{orms}} = \frac{(V_{\text{orms}})^2}{R} = (I_{\text{orms}})^2 R$$

$$\eta \approx \frac{P_k}{P_{al}}$$

Half-Wave Diode Rectifier with R Load-2


- The output voltage is composed of two components: **dc** component and **ac** component.
- The **dc** component or average value of the output is

$$\underline{V_{dc} = V_{o,avg} = \frac{\text{Peak of sinusoidal input voltage}}{\pi} = \frac{V_m}{\pi}}$$

- The **dc** component of the current through the resistive load is

$$I_{dc} = I_{o,avg} = \frac{V_m}{\pi R}$$

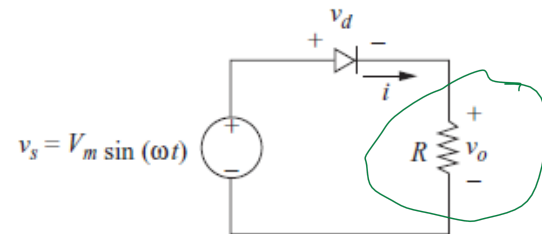- The output **dc** power is $\underline{P_{dc} = P_{o,avg} = V_{dc} I_{dc}}$



Half-Wave Diode Rectifier with R Load-3

- The **rms** value of the output voltage is $V_{o,rms} = \frac{V_m}{2}$
- The **rms** value of the current through the resistive load is

$$I_{o,rms} = \frac{V_m}{2 R}$$

- The output **ac** power is $P_{ac} = V_{o,rms} I_{o,rms} = \frac{V_{o,rms}^2}{R} = I_{o,rms}^2 R$
- The rectification ratio is $\eta = \frac{P_{dc}}{P_{ac}}$
- In summary:

DC components	AC components
$V_{dc} = \frac{V_m}{\pi}$	$V_{o,rms} = \frac{V_m}{2}$
$I_{dc} = \frac{V_m}{\pi R}$	$I_{o,rms} = \frac{V_m}{2 R}$
$P_{dc} = V_{dc} I_{dc}$	$P_{ac} = V_{o,rms} I_{o,rms}$

Half-Wave Diode Rectifier with R Load-4

$$f = 60 \text{ Hz}$$

$$W = Z \angle \phi \\ = 2 \angle 60 = 3.72$$

Example


→ A 120V rms, 60Hz power source supplies a 5Ω resistive load through a half-wave diode rectifier. Draw the circuit of the question and determine

- (a) The average of the output voltage.
- (b) The average load current.
- (c) The dc power delivered to the load.
- (d) The rms value of the output voltage.
- (e) The rms value of the load current.
- (f) The ac power delivered to the load.
- (g) The rectification ratio of the rectifier.
- (h) The power factor of the circuit.

$$V_{rms} = \underline{120}$$


$$\rightarrow V_m = 120\sqrt{2} \\ = 169.7$$

$$R = 5 \Omega$$

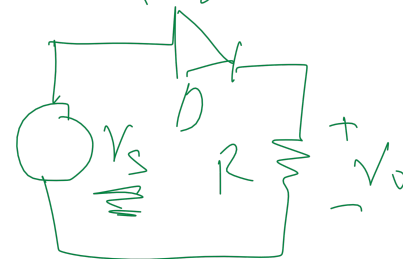

$$V_s = V_m \sin(\omega t)$$

Solution

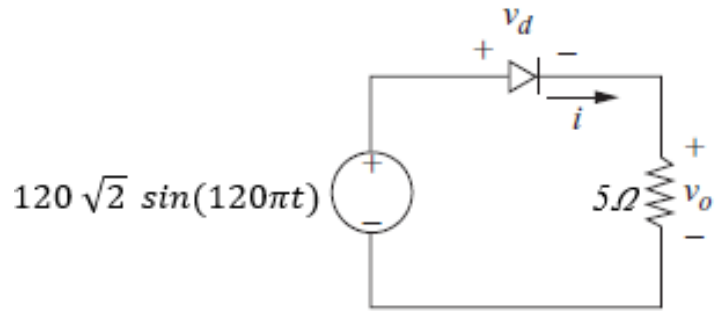

$(a) V_{dc} = \frac{V_m}{\pi} = \frac{120\sqrt{2}}{\pi} = 54 \text{ V}$

$(b) I_{dc} = \frac{V_m}{\pi R} = \frac{120\sqrt{2}}{\pi (5)} = 10.8 \text{ A}$

$(c) P_{dc} = V_{dc} I_{dc} = 583.4 \text{ W} \approx 54 \times 10.8$

$(d) V_{o,rms} = \frac{V_m}{2} = \frac{120\sqrt{2}}{2} = 84.9 \text{ V}$

$(e) I_{o,rms} = \frac{V_m}{2R} = \frac{120\sqrt{2}}{2(5)} = 17 \text{ A}$

$(f) P_{ac} = V_{o,rms} I_{o,rms} = 1443 \text{ W}$

$(g) \% \eta = \frac{P_{dc}}{P_{ac}} = \frac{583.4}{1443} \times 100\% = 40\%$

$(h) PF = \frac{P_{ac}}{|S|} = \frac{1443}{V_{s,rms} I_{s,rms}} = \frac{1443}{(120)(17)} = 0.707$

$= \frac{1443}{120 \times 17} = 0.707$

$V_m = V_{rms} \sqrt{2}$

$P.f = \frac{P_{ac}}{S}$







$S = V_{s,rms} \times I_{s,rms}$

Half-Wave Diode Rectifier with ***RL*** Load

- The conduction period of the diode will extend beyond π (180°) until the current becomes zero at $\omega t = \pi + \beta$. **Explain why?**
- Would you expect average output voltage to increase or decrease ?**





$$V_{dc} = V_{o,avg} = \frac{V_m}{2\pi} [1 - \cos(\pi + \beta)]$$

$$I_{dc} = \frac{V_{dc}}{R}$$

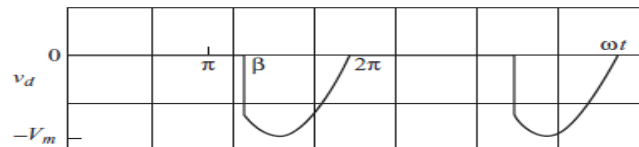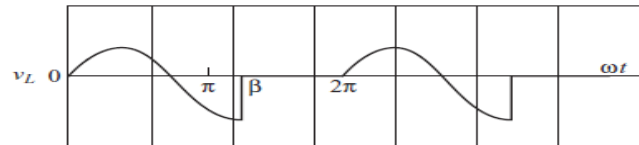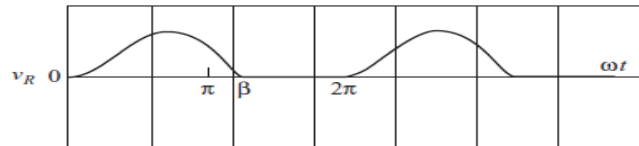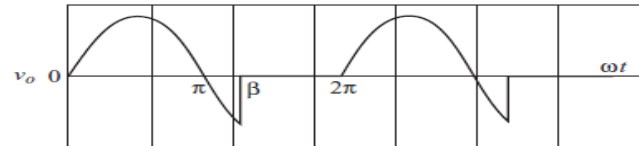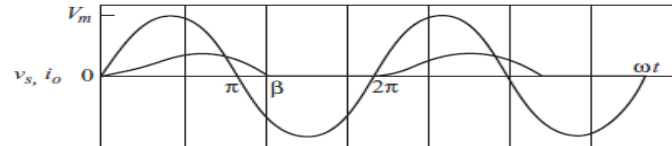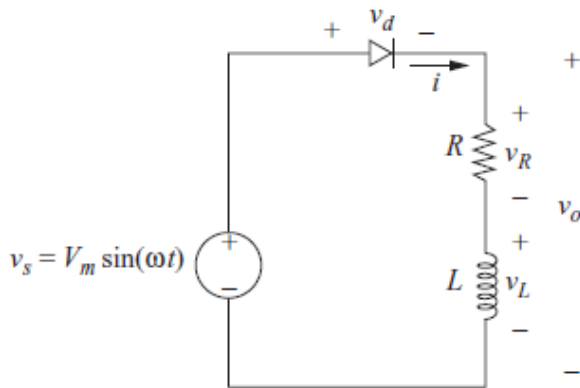

Half-Wave Diode Rectifier with ***RL*** Load and Freewheeling Diode

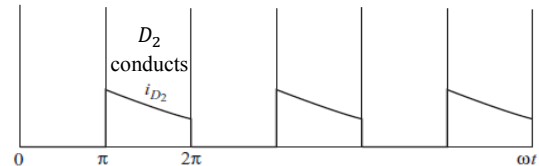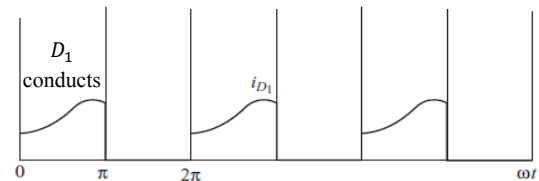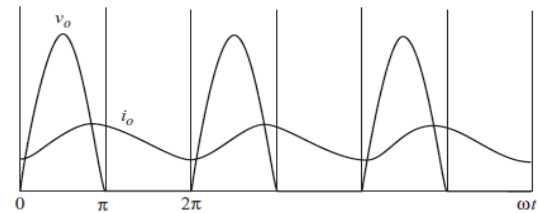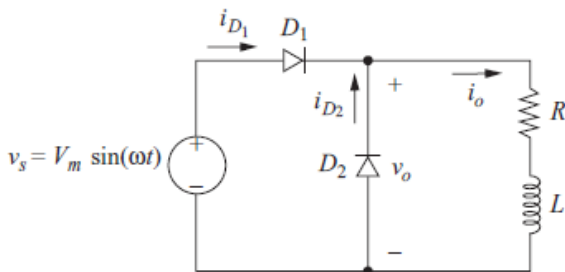- To prevent the output voltage from going negative, a freewheeling diode (D_2) can be placed in parallel with the RL load. This will make $\beta = 0$.
- D_1 and D_2 can never conduct at the same time. Why?
- i_o can be continuous or discontinuous depending on $\tau = L/R$.



Steady-state load voltage and current waveforms with freewheeling diode.

